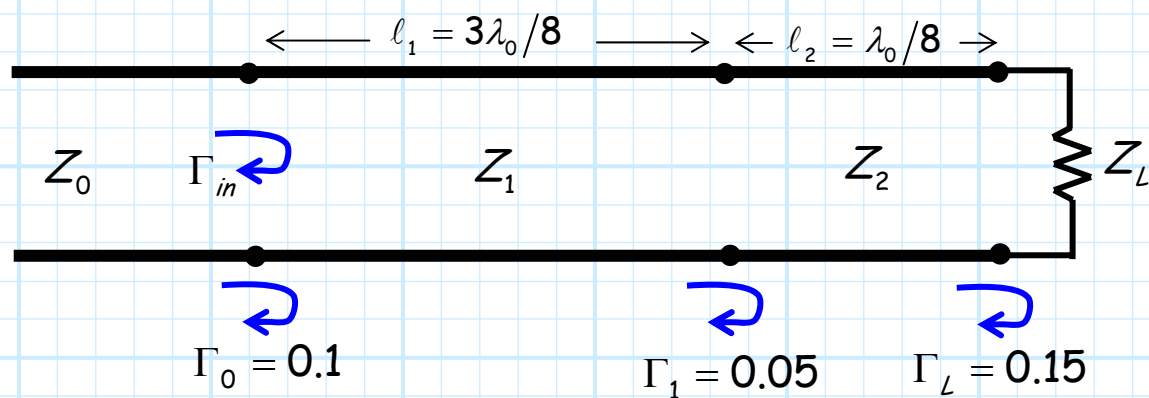


Example: The Theory of Small Reflections


Use the **theory of small reflections** to determine a **numeric** value for the **input reflection coefficient** Γ_{in} , at the design frequency ω_0 .



Note that the transmission line sections have **different lengths!**

Solution

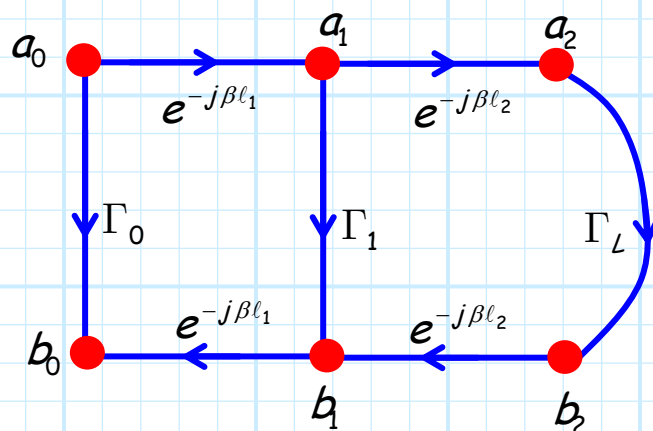Applying the theory of small reflections, the **approximate signal flow graph** of the structure becomes:




$$e^{-j\beta l_1} = e^{-j\left(\frac{2\pi}{\lambda} \frac{3\lambda}{8}\right)} = e^{-j\left(\frac{3\pi}{4}\right)}$$


$$e^{-j\beta l_2} = e^{-j\left(\frac{2\pi}{\lambda} \frac{\lambda}{8}\right)} = e^{-j\left(\frac{\pi}{4}\right)}$$

Note there are three **direct** propagation paths:

Path 1

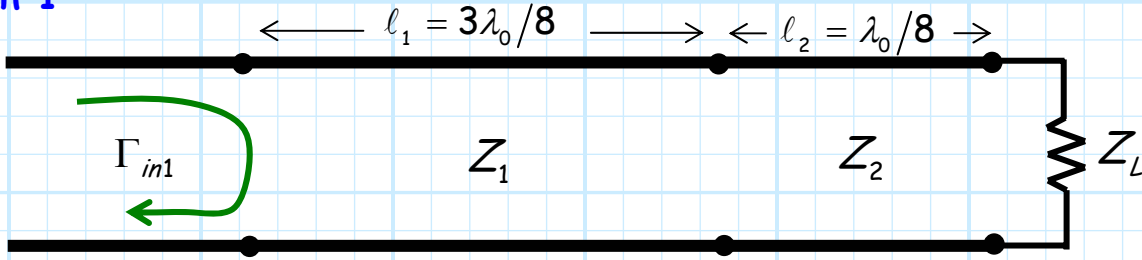


$\therefore \rho_1 = \Gamma_0 = 0.1$

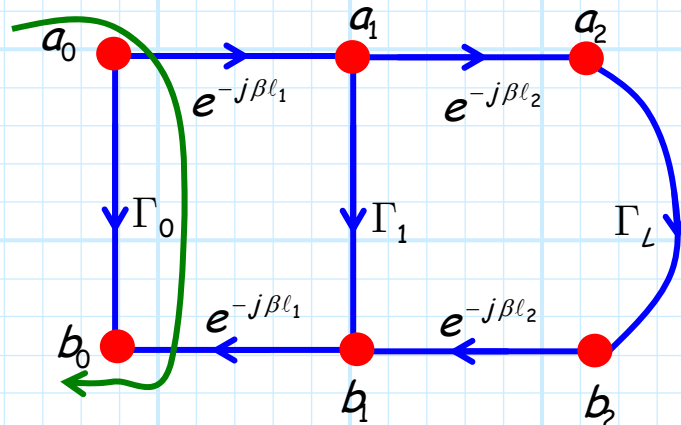


Path 2

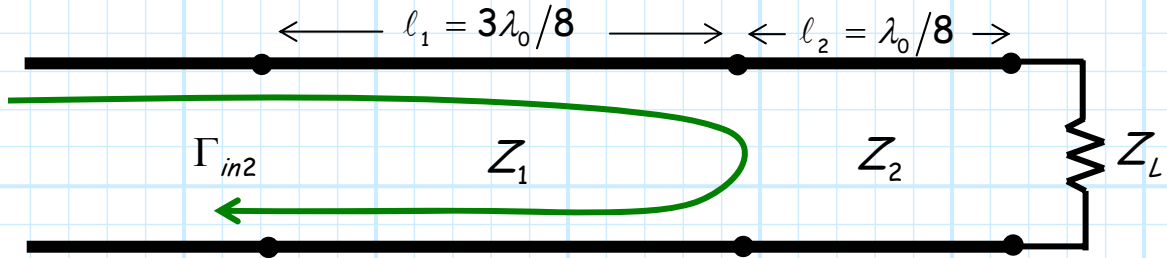This path includes propagation **down** and **back** a transmission line length l_1 !




$$\begin{aligned} \rho_2 &= e^{-j\beta l_1} \Gamma_1 e^{-j\beta l_1} \\ &= e^{-j^{3\pi/4}} 0.05 e^{-j^{3\pi/4}} \\ &= e^{-j^{3\pi/2}} 0.05 \\ &= +j0.05 \end{aligned}$$

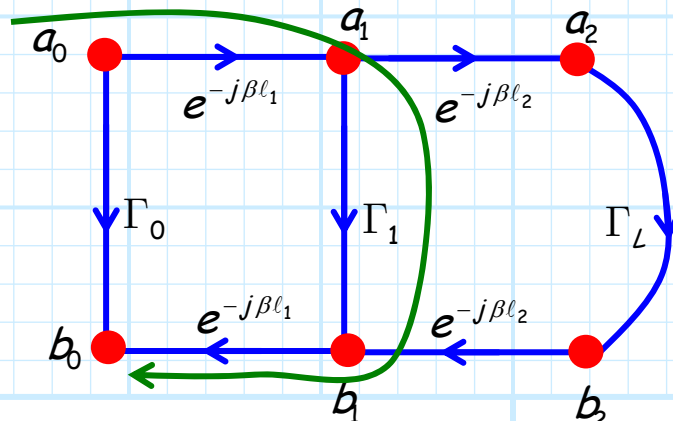


Path 3

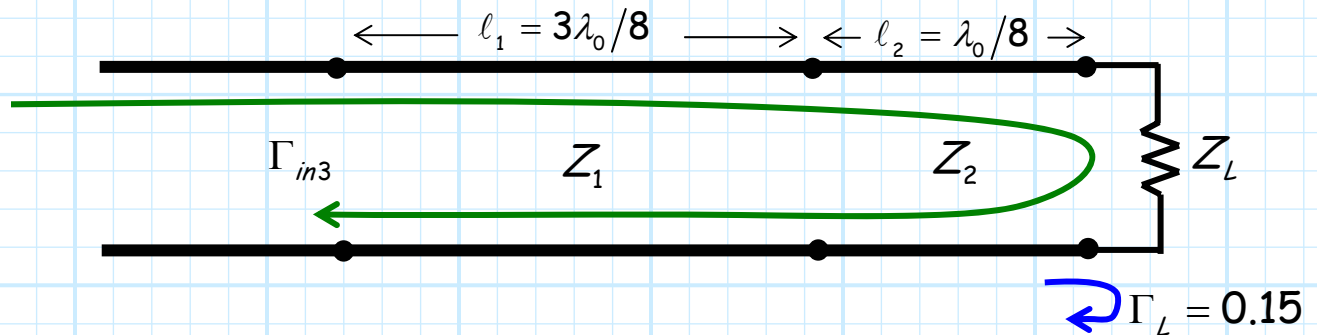This path includes propagation **down** and **back** transmission line lengths of $l_1 + l_2$!


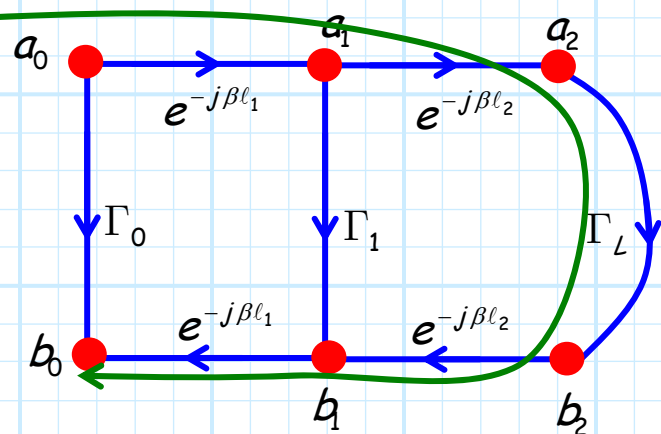
$$\begin{aligned} p_3 &= e^{-j\beta(l_1+l_2)} \Gamma_L e^{-j\beta(l_1+l_2)} \\ &= e^{-j\pi} 0.15 e^{-j\pi} \\ &= e^{-j2\pi} 0.15 \\ &= 0.15 \end{aligned}$$



Thus, using the **theory of small reflections** we can determine approximately the input reflection coefficient:

$$\begin{aligned} \Gamma_{in} &= \frac{b_0}{a_0} \\ &= p_1 + p_2 + p_3 \\ &= 0.1 + j0.05 + 0.15 \\ &= \underline{\underline{0.25 + j0.05}} \end{aligned}$$