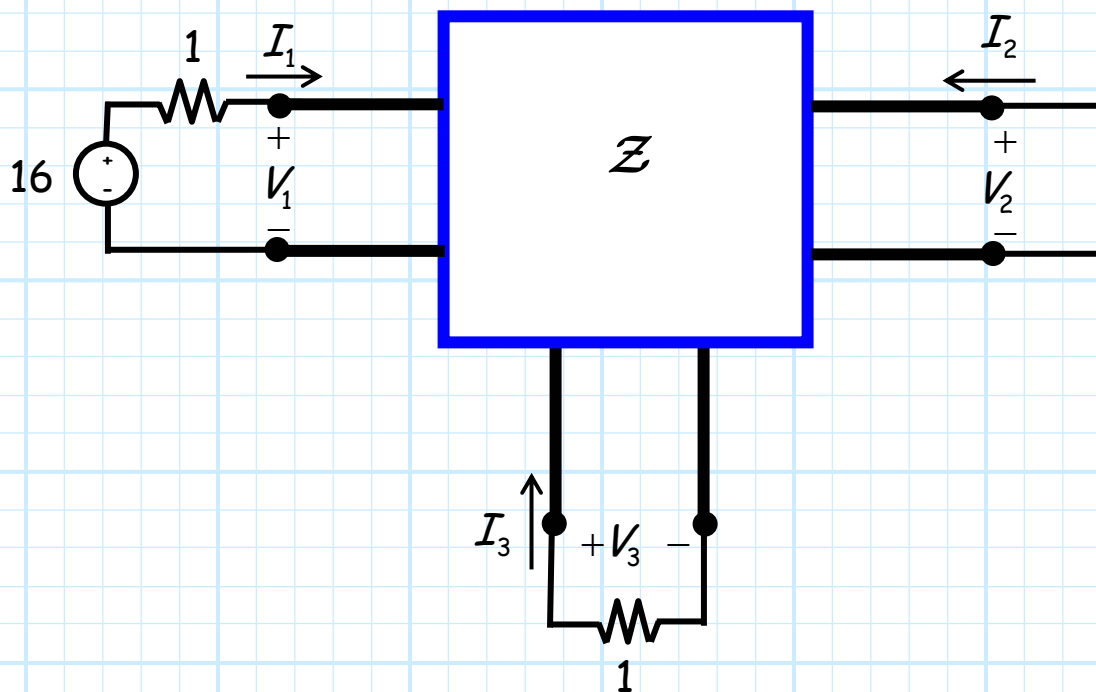


Example: Using the Impedance Matrix

Consider the following circuit:



Where the 3-port **device** is characterized by the **impedance matrix**:

$$\mathbf{Z} = \begin{bmatrix} 2 & 1 & 2 \\ 1 & 1 & 4 \\ 2 & 4 & 1 \end{bmatrix}$$

Let's now determine all port **voltages** V_1, V_2, V_3 and all **currents** I_1, I_2, I_3 .



Q: *How can we do that—we **don't** know what the device is made of! What's inside that box?*

A: We **don't** need to know what's inside that box! We know its impedance matrix, and that **completely** characterizes the device (or, at least, characterizes it at **one** frequency).

Thus, we have enough information to solve this problem. From the impedance matrix we know:

$$V_1 = 2 I_1 + I_2 + 2 I_3$$

$$V_2 = I_1 + I_2 + 4 I_3$$

$$V_3 = 2 I_1 + 4 I_2 + I_3$$



Q: *Wait! There are only **3** equations here, yet there are **6** unknowns!?*

A: True! The impedance matrix describes the device in the box, but it does **not** describe the devices **attached** to it. We require **more** equations to describe them.

1. The **source** at port 1 is described by the equation:

$$V_1 = 16.0 - (1)I_1$$

2. The **short** circuit on port 2 means that:

$$V_2 = 0$$

3. While the **load** on port 3 leads to:

$$V_3 = -(1)I_3 \quad (\text{note the minus sign!})$$

Now we have **6** equations and **6** unknowns! Combining equations, we find:

$$\begin{aligned} V_1 &= 16 - I_1 = 2I_1 + I_2 + 2I_3 \\ \therefore 16 &= 3I_1 + I_2 + 2I_3 \end{aligned}$$

$$\begin{aligned} V_2 &= 0 = I_1 + I_2 + 4I_3 \\ \therefore 0 &= I_1 + I_2 + 4I_3 \end{aligned}$$

$$\begin{aligned} V_3 &= -I_3 = 2I_1 + 4I_2 + I_3 \\ \therefore 0 &= 2I_1 + 4I_2 + 2I_3 \end{aligned}$$

Solving, we find (I'll let you do the algebraic details!):

$$I_1 = 7.0 \qquad I_2 = -3.0 \qquad I_3 = -1.0$$

$$V_1 = 9.0 \qquad V_2 = 0.0 \qquad V_3 = 1.0$$