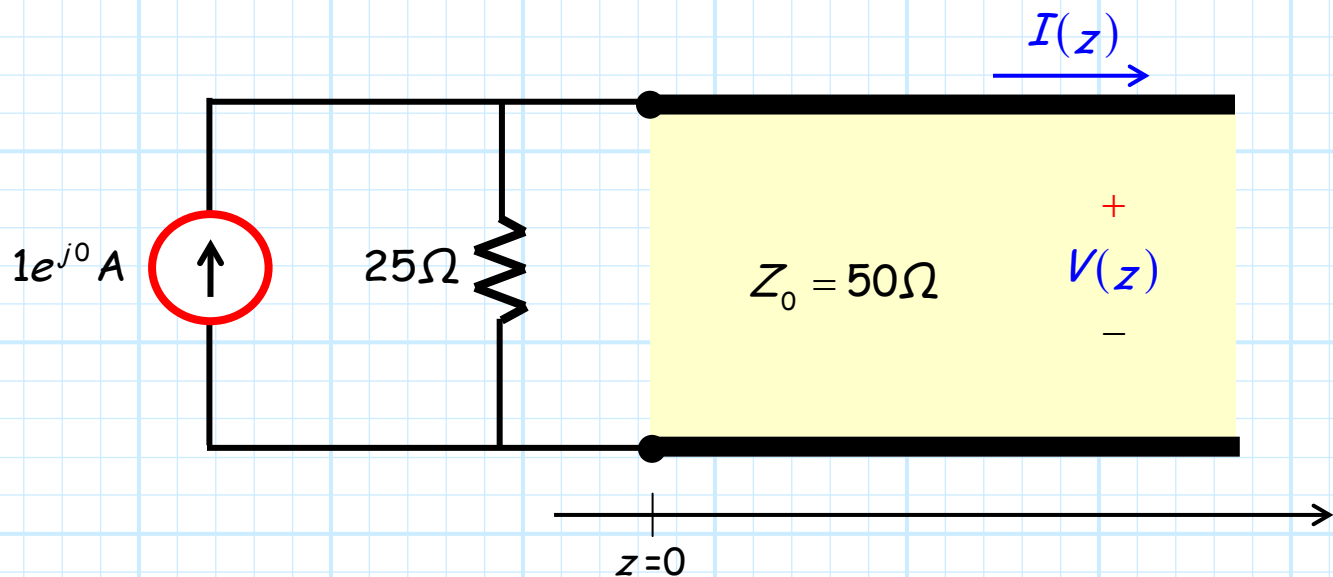


Example: Boundary Conditions and Sources

Consider the circuit below:



It is known that the **current** along the transmission line is:

$$I(z) = 0.4 e^{-j\beta z} - B e^{+j\beta z} \quad \text{A for } z > 0$$

where B is some unknown **complex** value.

Determine the value of B .

Hint: $B \neq -0.6$

Solution

Since the line current is:

$$I(z) = 0.4 e^{-j\beta z} - B e^{+j\beta z} = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z}$$

we conclude from inspection that:

$$I_0^+ = 0.4 \quad \text{and} \quad I_0^- = -B$$

and since:


$$V_0^+ = Z_0 I_0^+ \quad \text{and} \quad V_0^- = -Z_0 I_0^-$$

we conclude:

$$V_0^+ = Z_0 I_0^+ = 50(0.4) = 20.0 \quad \text{and} \quad V_0^- = -Z_0 I_0^- = -50(-B) = 50B$$

Therefore, the voltage along this transmission line is:
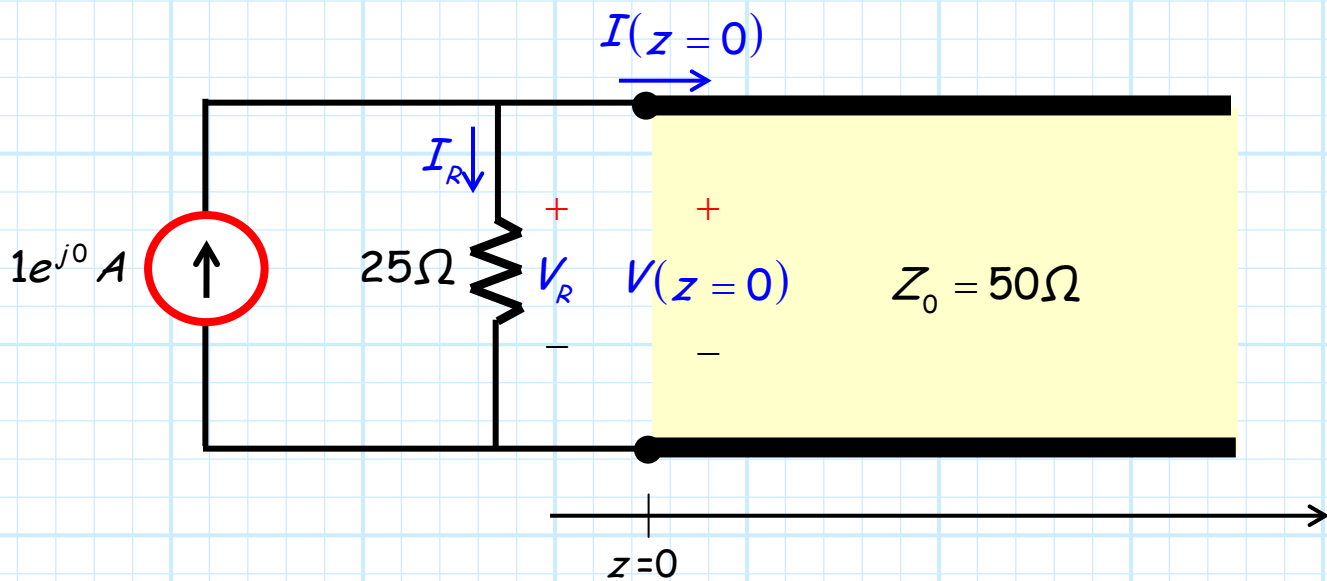
$$\begin{aligned} V(z) &= V^+(z) + V^-(z) \\ &= V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z} \\ &= 20 e^{-j\beta z} + 50B e^{+j\beta z} \end{aligned}$$



Now, from **KCL** we find the **boundary condition** imposed by the source:

$$1.0 - I_R = I(z = 0)$$

And from **KVL**:

$$V_R = V(z = 0)$$

Thus from Ohm's Law we find:

$$25 = \frac{V_R}{I_R} = \frac{V(z = 0)}{e^{j0} - I(z = 0)}$$

Therefore:

$$V(z = 0) = 25(e^{j0} - I(z = 0))$$

where:

$$\begin{aligned} I(z = 0) &= 0.4 e^{-j\beta(0)} - B e^{+j\beta(0)} \\ &= 0.4 - B \end{aligned}$$

and:

$$\begin{aligned}V(z = 0) &= 20 e^{-j\beta(0)} + 50B e^{+j\beta(0)} \\ &= 20 + 50B\end{aligned}$$

Inserting this into the previous equation:

$$\begin{aligned}(20 + 50B) &= 25(e^{j0} - (0.4 - B)) \\ &= 25 - 0.4(25) + 25B \\ &= 15 + 25B\end{aligned}$$

One equation and one unknown! Solving for B :

$$\underline{\underline{B = -0.2}}$$