


# Filter Transformations

**Q:** *OK, so we now know how to design a lumped-element lowpass filter—how do we design say, a **bandpass** or **highpass** filter??*

**A:** If we have **already** designed a **lowpass** filter, we are **almost** done!

We can use the concept of **filter transformations** to determine the **new** filter designs from a lowpass design. As a result, we can construct a 3<sup>rd</sup>-order Butterworth **high-pass** filter or a 5<sup>th</sup>-order Chebychev **bandpass** filter!

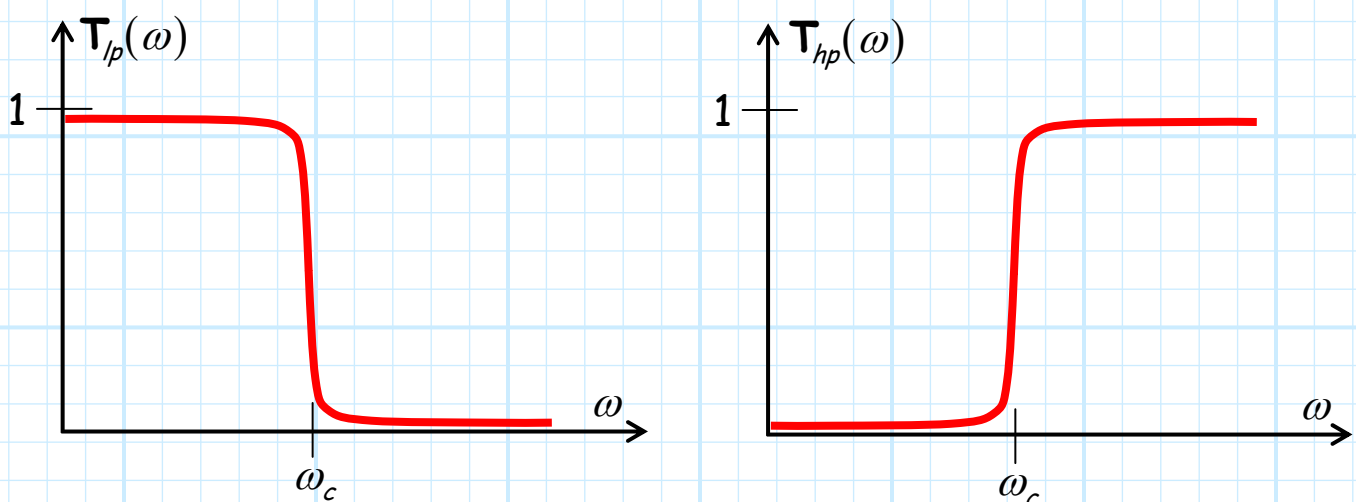We will find that the mathematics for each filter design will be very **similar**. For example, the difference between a lowpass and highpass filter is essentially an **inverse**—the frequencies below  $\omega_c$  are mapped into frequencies above  $\omega_c$ —and vice versa.



For example, we find that:

$$\mathbf{T}_{lp}(\omega = 0) = \mathbf{T}_{hp}(\omega = \infty) = 1$$

likewise:

$$\mathbf{T}_{lp}(\omega = \infty) = \mathbf{T}_{hp}(\omega = 0) = 0$$

but:

$$\mathbf{T}_{lp}(\omega = \omega_c) = \mathbf{T}_{hp}(\omega = \omega_c) = 0.5$$

Thus, in general we find:

$$\mathbf{T}_{lp}(\omega = \alpha \omega_c) = \mathbf{T}_{hp}\left(\omega = \frac{1}{\alpha} \omega_c\right)$$

where  $\alpha$  is some positive, real value (i.e.,  $0 \leq \alpha < \infty$ ).

For example, if  $\alpha = 0.5$ , then

$$\mathbf{T}_{lp}(\omega = 0.5 \omega_c) = \mathbf{T}_{hp}(\omega = 2.0 \omega_c)$$

In other words, the transmission through a low-pass filter at one half the cutoff frequency will be equal to the transmission through a (mathematically similar) high-pass filter at twice the cutoff frequency.

Now, recall the loss-ratio functions for Butterworth and Chebychev low-pass filters:

$$P_{LR}^{lp}(\omega) = 1 + \left(\frac{\omega}{\omega_c}\right)^{2N} \qquad P_{LR}^{lp}(\omega) = 1 + k^2 T_N^2\left(\frac{\omega}{\omega_c}\right)$$

Note in each case that the argument of the function has the form:

$$\frac{\omega}{\omega_c}$$

In other words, the frequency is **normalized** by the cutoff frequency.

Consider now **this** mapping:

$$\frac{\omega}{\omega_c} \Rightarrow -\frac{\omega_c}{\omega}$$

This mapping **transforms** our lowpass filter response into a corresponding high pass filter response! I.E.:

$$\begin{aligned} P_{LR}^{hp}(\omega) &= 1 + \left(-\frac{\omega_c}{\omega}\right)^{2N} & P_{LR}^{hp}(\omega) &= 1 + k^2 T_N^2 \left(-\frac{\omega_c}{\omega}\right) \\ &= 1 + \left(\frac{\omega_c}{\omega}\right)^{2N} & &= 1 + k^2 T_N^2 \left(\frac{\omega_c}{\omega}\right) \end{aligned}$$

**Q:** *Yikes! Where did this mapping come from? Are sure this works?*

Consider the again the case where  $\omega = \alpha \omega_c$ ; the low pass responses are:

$$\begin{aligned} P_{LR}^{lp}(\omega) &= 1 + \left(\frac{\alpha \omega_c}{\omega_c}\right)^{2N} & P_{LR}^{lp}(\omega) &= 1 + k^2 T_N^2 \left(\frac{\alpha \omega_c}{\omega_c}\right) \\ &= 1 + (\alpha)^{2N} & &= 1 + k^2 T_N^2 (\alpha) \end{aligned}$$

Now consider the high-pass responses where  $\omega = \omega_c / \alpha$ :

$$\begin{aligned} P_{LR}^{hp}(\omega) &= 1 + \left( \frac{\omega_c}{\omega_c / \alpha} \right)^{2N} & P_{LR}^{hp}(\omega) &= 1 + k^2 T_N^2 \left( \frac{\omega_c}{\omega_c / \alpha} \right) \\ &= 1 + (\alpha)^{2N} & &= 1 + k^2 T_N^2(\alpha) \end{aligned}$$

Thus, we can conclude from this mapping that:

$$P_{LR}^p(\omega = \alpha \omega_c) = P_{LR}^{hp} \left( \omega = \frac{1}{\alpha} \omega_c \right)$$

And since  $\mathbf{T} = P_{LR}^{-1}$ :

$$\mathbf{T}_{lp}(\omega = \alpha \omega_c) = \mathbf{T}_{hp} \left( \omega = \frac{1}{\alpha} \omega_c \right)$$

Exactly the result that we expected! Our mapping provides a method for transforming a low-pass filter into a high-pass filter!

**Q:** *OK Poindexter, you have succeeded in providing another one of your "fascinating" mathematical insights, but does this "mapping" provide anything useful for us engineers?*

**A:** Absolutely! We can apply this mapping one component element (capacitor or inductor) at a time to our low-pass schematic design, and the result will be a direct transformation into a high-pass filter schematic.

Recall the reactance of an inductor element in a low-pass filter design is:

$$jX_n^{lp} = j\omega L_n^{lp} = j\omega g_n \left( \frac{R_s}{\omega_c} \right) = j g_n R_s \left( \frac{\omega}{\omega_c} \right)$$

while that of a capacitor is:

$$jX_n^{lp} = \frac{1}{j\omega C_n^{lp}} = \frac{1}{j\omega \left( \frac{g_n}{R_s \omega_c} \right)^{-1}} = -j \frac{R_s}{g_n} \left( \frac{\omega_c}{\omega} \right)$$

Now applying the mapping:

$$\frac{\omega}{\omega_c} \Rightarrow -\frac{\omega_c}{\omega}$$

we find for the inductor:

$$jX_n^{hp} = j g_n R_s \left( -\frac{\omega_c}{\omega} \right) = -j \frac{g_n R_s \omega_c}{\omega} = \frac{1}{j (g_n R_s \omega_c)^{-1} \omega}$$

and the capacitor:

$$jX_n^{hp} = -j \frac{R_s}{g_n} \left( -\frac{\omega}{\omega_c} \right) = j\omega \left( \frac{R_s}{g_n \omega_c} \right)$$

It is clear (do **you** see why?) that the transformation has converted a positive (i.e., inductive) reactance into a negative (i.e., capacitive) reactance—and vice versa.

As a result, to transform a low-pass filter schematic into a high-pass filter schematic, we:


1. Replace each inductor with a capacitor of value:

$$C_n^{hp} = \frac{1}{g_n R_s \omega_c} = \frac{1}{\omega_c^2 L_n^{lp}}$$

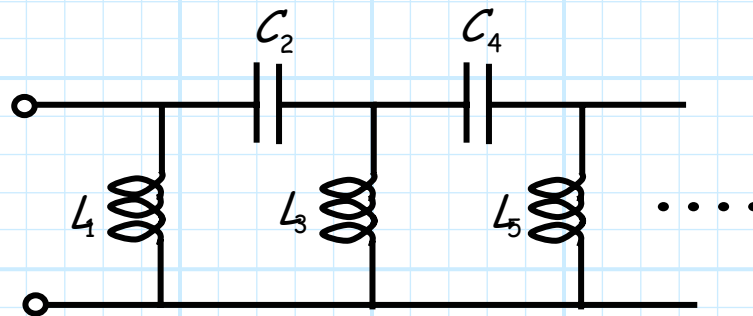2. Replace each capacitor with an inductor of value:

$$L_n^{hp} = \frac{R_s}{g_n \omega_c} = \frac{1}{\omega_c^2 C_n^{lp}}$$

Thus, a **high-pass ladder circuit** consists of **series capacitors** and **shunt inductors** (compare this to the low-pass) ladder circuit!).



**Q:** *What about band-pass filters?*

**A:** The difference between a lowpass and bandpass filter is simply a **shift** in the "center" frequency of the filter, where the center frequency of a lowpass filter is essentially  $\omega = 0$ .

For this case, we find that the **mapping**:

$$\frac{\omega}{\omega_c} \Rightarrow \frac{1}{\Delta} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)$$

transforms a low-pass function into a **band-pass function**, where  $\Delta$  is the **normalized bandwidth**:

$$\Delta = \frac{\omega_2 - \omega_1}{\omega_0}$$

and  $\omega_1$  and  $\omega_2$  define the two **3dB frequencies** of the bandpass filter.

For example, the Butterworth **low-pass** function:

$$P_{LR}(\omega) = 1 + \left( \frac{\omega}{\omega_c} \right)^{2N}$$

becomes a Butterworth **band-pass** function:

$$P_{LR}(\omega) = 1 + \frac{1}{\Delta^{2N}} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^{2N}$$

Applying this transform to the reactance of a low-pass inductive element:

$$jX_n^{bp} = j g_n R_s \frac{1}{\Delta} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = j\omega \left( \frac{g_n R_s}{\omega_0 \Delta} \right) + \frac{1}{j\omega (\Delta / g_n \omega_0 R_s)}$$

Look what happened! The transformation turned the inductive reactance into an inductive reactance in series with a capacitive reactance.

As similar analysis of the transformation of the low-pass capacitive reactance shows that it is transformed into an inductive reactance in parallel with an capacitive reactance.

As a result, to transform a low-pass filter schematic into a band-pass filter schematic, we:

1. Replace each series inductor with a capacitor and inductor in series, with values:

$$L_n^{bp} = g_n \frac{R_s}{\omega_0 \Delta} \qquad C_n^{bp} = \frac{1}{g_n} \frac{\Delta}{\omega_0 R_s}$$

2. Replace each shunt capacitor with an inductor and capacitor in parallel, with values:

$$L_n^{bp} = \frac{1}{g_n} \frac{\Delta R_s}{\omega_0} \qquad C_n^{bp} = g_n \frac{1}{\omega_0 \Delta R_s}$$

Thus, the ladder circuit for **band-pass circuit** is simply a ladder network of  $LC$  resonators, both series and parallel:

