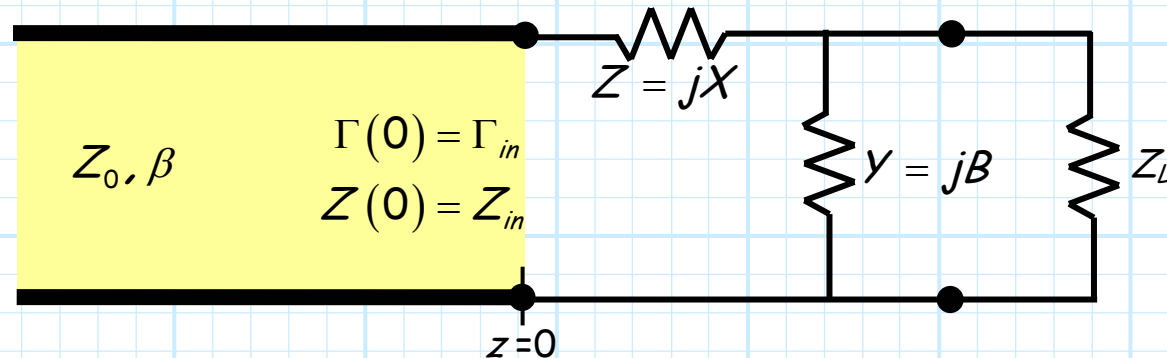


# L-Network Analysis

Consider the **first** matching L-network, which we shall denote as matching **network (A)**:



Note that this matching network consists of just **two** lumped elements, which must be **purely reactive**—in other words, a **capacitor** and an **inductor**!

To make  $\Gamma_{in} = 0$ , the **input impedance** of the network must be:

$$Z_{in} = Z_0$$

Note that using **basic** circuit analysis we find that this input impedance is:

$$Z_{in} = jX + \frac{\left(\frac{1}{jB}\right)Z_L}{\frac{1}{jB} + Z_L} = jX + \frac{Z_L}{1 + jBZ_L}$$

Note that a **matched** network, with  $Z_{in} = Z_0$ , means that:

$$\operatorname{Re}\{Z_{in}\} = Z_0 \quad \text{AND} \quad \operatorname{Im}\{Z_{in}\} = 0$$

Note that there are **two** equations.

This works out well, since we have **two** unknowns ( $B$  and  $X$ )!

Essentially, the L-network matching network can be viewed as consisting of **two distinct parts**, each attempting to satisfy a specific requirement.


### Part 1: Selecting $Y = jB$

Since the shunt element  $Y$  and  $Z_L$  are in **parallel**, we can combine them into one element that we shall call  $Y_1$ :

$$Y_1 \doteq Y + \frac{1}{Z_L} = jB + Y_L$$

The impedance of this element is therefore:

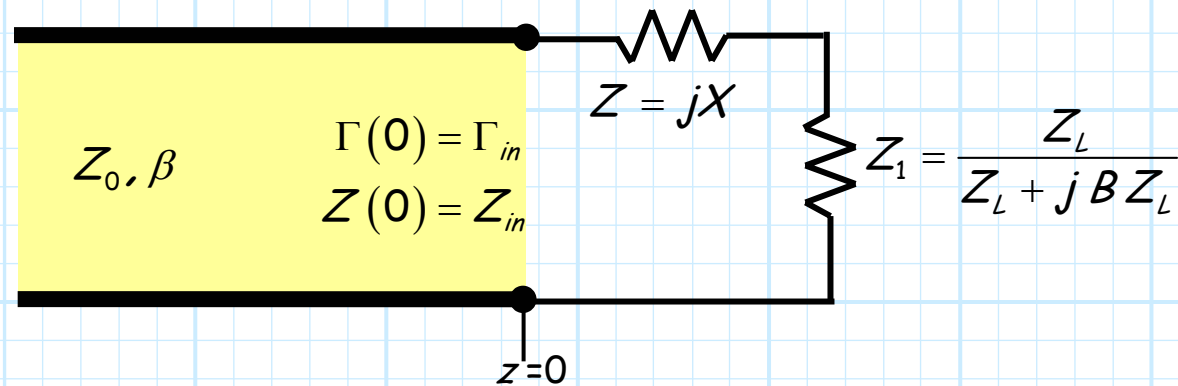
$$Z_1 = \frac{1}{Y_1} = \frac{1}{jB + Y_L} = \frac{Z_L}{Z_L + jB Z_L}$$



To achieve a perfect match, we must set the value of susceptance  $B$  such that:

$$\text{Re}\{Z_1\} = \text{Re}\left\{\frac{Z_L}{Z_L + jB Z_L}\right\} = Z_0$$

Thus, if  $B$  is properly selected:

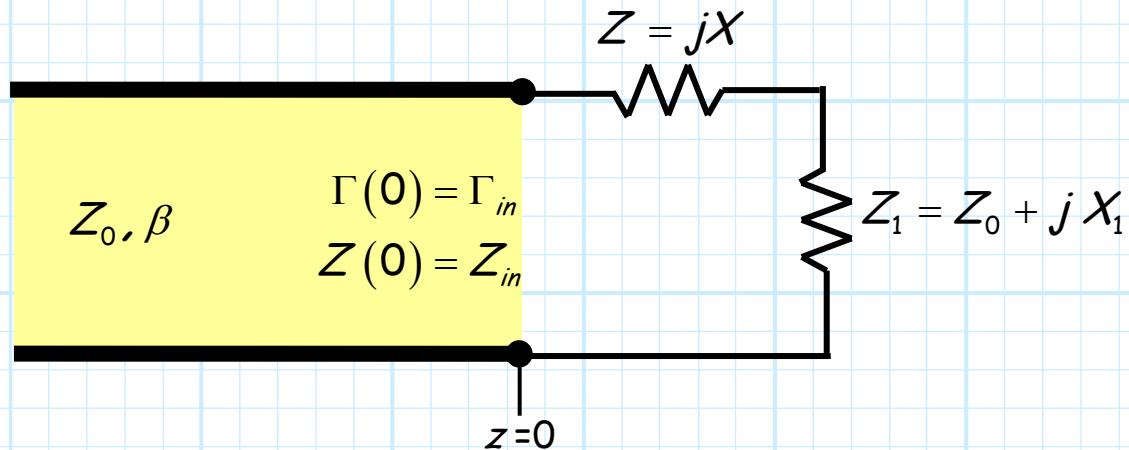

Hopefully, the second part of the matching is now very obvious to **you!**


## Part 2: Selecting $Z = jX$

Note that the impedance  $Z_1 = Z_L \parallel 1/jB$  has the ideal real value of  $Z_0$ . However, it likewise possesses an **annoying** imaginary part of:

$$X_1 = \text{Im}\{Z_1\} = \text{Im}\left\{\frac{Z_L}{Z_L + jBZ_L}\right\}$$

However, this imaginary component is easily removed by setting the **series** element  $Z = jX$  to its equal but **opposite** value! I.E.,:
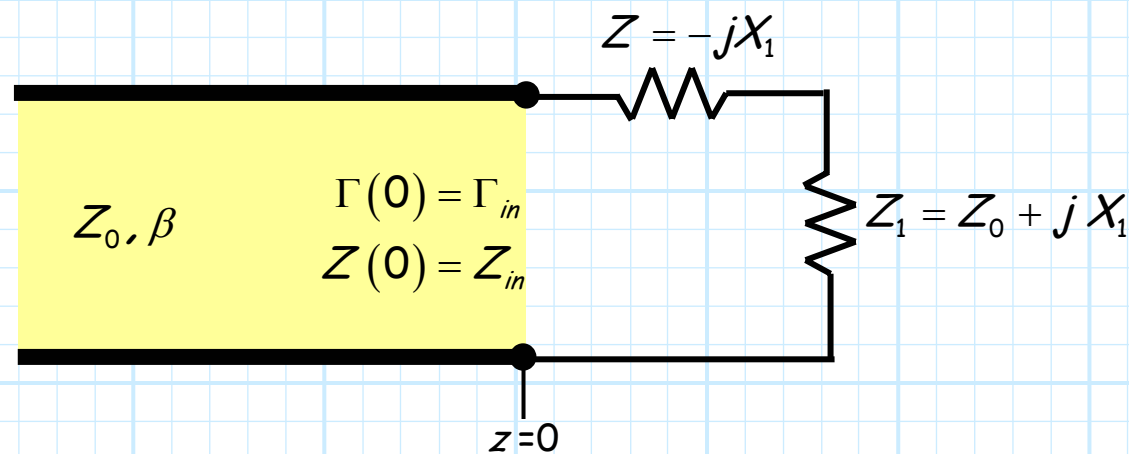
$$X = -X_1 = -\text{Im}\left\{\frac{Z_L}{Z_L + jBZ_L}\right\}$$



Thus, we find that:

$$\begin{aligned} Z_{in} &= Z + Z_1 \\ &= -jX_1 + Z_0 + jX_1 \\ &= Z_0 \end{aligned}$$



We have created a **perfect match!**

Going through this complex algebra, we can solve for the **required** values  $X$  and  $B$  to **satisfy** these two equations—to create a **matched** network!

$$B = \frac{X_L \pm \sqrt{R_L/Z_0} \sqrt{R_L^2 + X_L^2 - Z_0 R_L}}{R_L^2 + X_L^2}$$

and,

$$X = \frac{1}{B} + \frac{X_L Z_0}{R_L} - \frac{Z_0}{B R_L}$$

where  $Z_L = R_L + jX_L$ .


**Note:**

- 1) Because of the  $\pm$ , there are **two** solutions for  $B$  (and thus  $X$ ).
- 2) For  $jB$  to be purely imaginary (i.e., reactive),  $B$  must be **real**. From the term:


$$\sqrt{R_L^2 + X_L^2 - Z_0 R_L}$$

in the expression for  $B$ , we note that  $R_L$  **must** be greater than  $Z_0$  ( $R_L > Z_0$ ) to insure that  $B$  and thus  $X$  is real.

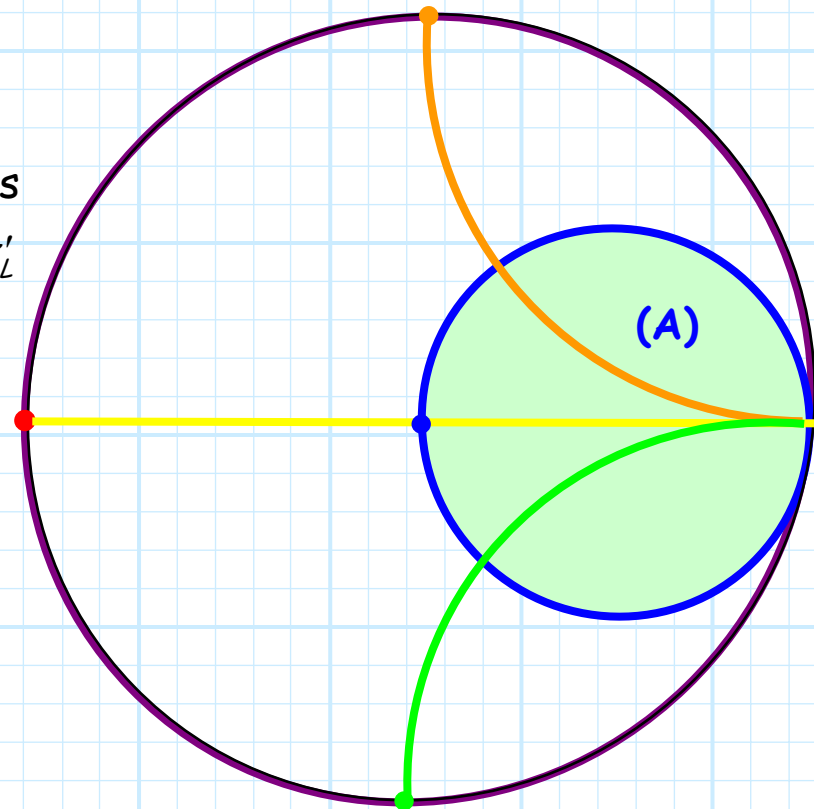In other words, this matching network can only be used when  $R_L > Z_0$ . Notice that this condition means that the normalized load  $z'_L$  lies **inside** the  $r=1$  circle on the Smith Chart!



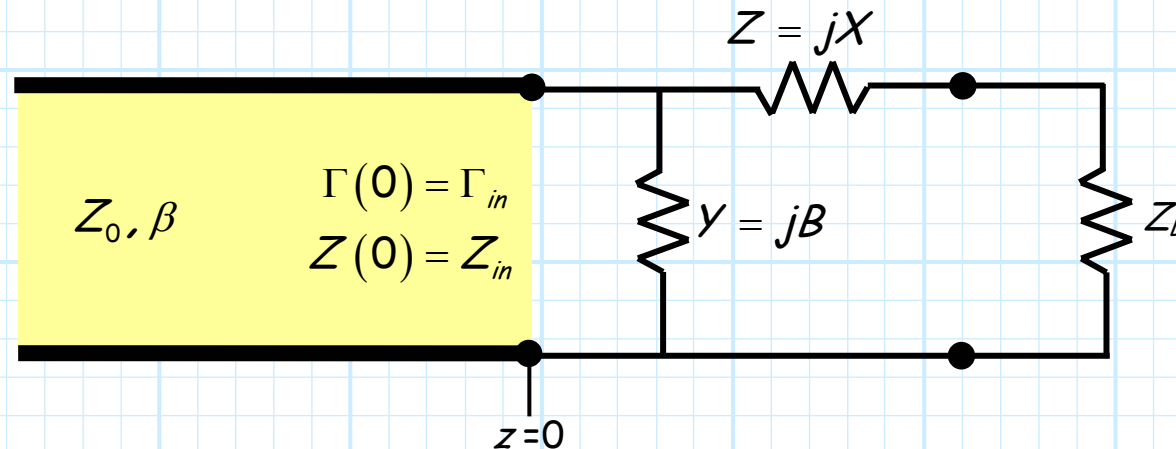Now let's consider the **second** of the two L-networks, which we shall call **network (B)**. Note it **also** is formed with just two lumped elements.



To make  $\Gamma_{in} = 0$ , the **input admittance** of the network must be:

$$Y_{in} = Y_0$$

Note from circuit theory that the input **admittance** for this network is:

$$Y_{in} = jB + \frac{1}{jX + Z_L}$$

Therefore a **matched** network, with  $Y_{in} = Y_0$ , is described as:


$$\text{Re}\{Y_{in}\} = Y_0 \quad \text{AND} \quad \text{Im}\{Y_{in}\} = 0$$

For this design, we set the value of  $Z = jX$  such that the admittance  $Y_1$ :

$$Y_1 \doteq \frac{1}{Z + Z_L} = \frac{1}{jX + Z_L}$$

has a real part equal to  $Y_0$ :
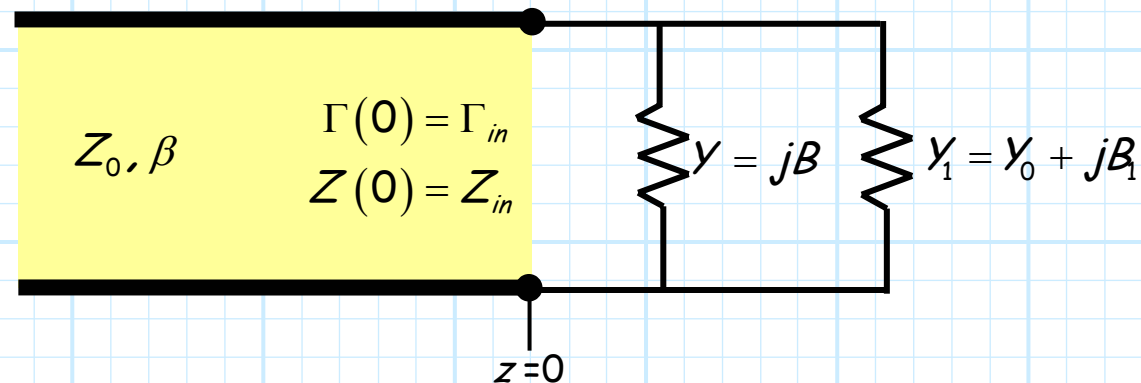
$$Y_0 = \text{Re}\{Y\}_1 = \text{Re}\left\{\frac{1}{jX + Z_L}\right\}$$



Now, it is evident that a perfect match will occur if the shunt element  $Y = jB$  is set to "cancel" the reactive component of  $Y_1$ :



$$B = -\text{Im}\{Y\}_1 = -\text{Im}\left\{\frac{1}{jX + Z_L}\right\}$$



So that we find:

$$Y_{in} = Y + Y_1 = -jB_1 + (Y_0 + jB_1) = Y_0$$

A perfect match!

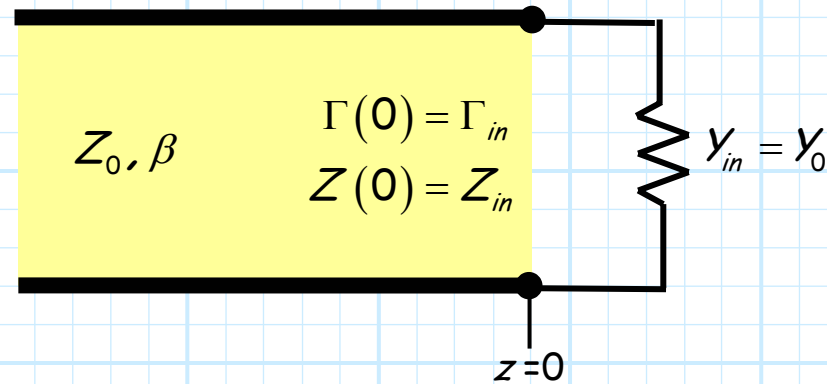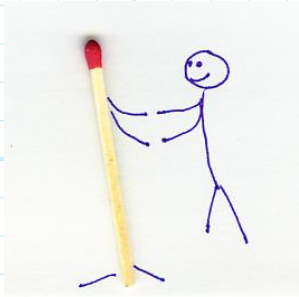

With these two equations, we can directly solve for the **required** values  $X$  and  $B$  for a **matched** network:

$$X = \pm \sqrt{R_L (Z_0 - R_L)} - X_L$$

and,

$$B = \pm \frac{\sqrt{(Z_0 - R_L)/R_L}}{Z_0}$$

where  $Z_L = R_L + jX_L$ .


## Note:

- 1) Because of the  $\pm$ , there are **two** solutions for  $B$  (and thus  $X$ ).
- 2) For  $jB$  and  $jX$  to be purely imaginary (i.e., reactive),  $B$  and  $X$  must be **real**. We note from the term:

$$(Z_0 - R_L)$$

that  $R_L$  must be **less** than  $Z_0$  ( $R_L < Z_0$ ) to insure that  $B$  and thus  $X$  are real.

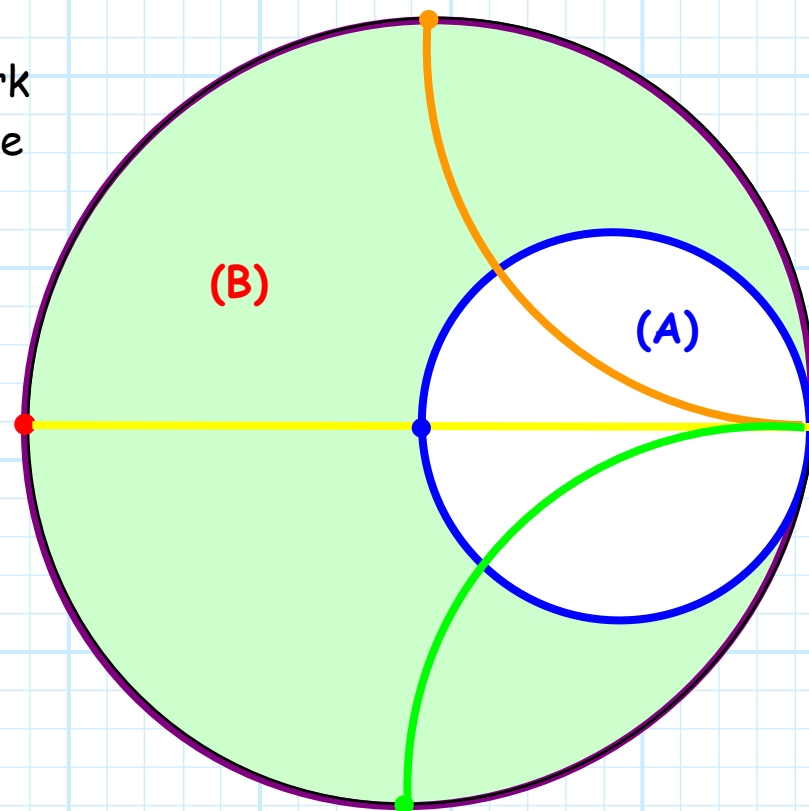In other words, this matching network can **only** be used when  $R_L < Z_0$ . Notice that this condition means that the normalized load  $z'_L$  lies **outside** the  $r = 1$  circle on the Smith Chart!



Once the values of  $X$  and  $B$  are found, we can determine the required values of inductance  $L$  and/or capacitance  $C$ , for the signal frequency  $\omega_0$ !

Recall that:

$$X = \begin{cases} \omega_0 L & \text{if } X > 0 \\ \frac{-1}{\omega_0 C} & \text{if } X < 0 \end{cases}$$

and that:

$$B = \begin{cases} \omega_0 C & \text{if } B > 0 \\ \frac{-1}{\omega_0 L} & \text{if } B < 0 \end{cases}$$



Make sure that **you** see and know why these equations are true.

As a result, we see that the reactance or susceptance of the elements of our L-network will have the proper values for matching at precisely **one** and **only** one frequency!

→ And this frequency **better** be the signal frequency  $\omega_0$ !

If the signal frequency **changes** from this design frequency, the reactance and susceptance of the matching network inductors and capacitors will likewise change. The circuit will **no longer** be matched.

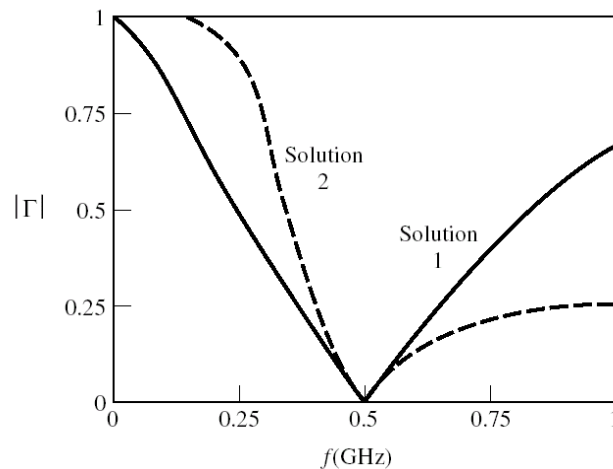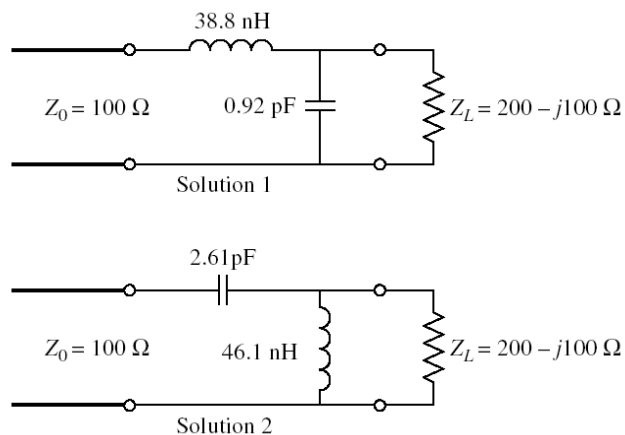→ This matching network has a **narrow bandwidth!**



### An L-Network Design Example

One other problem; it becomes **very** difficult to build quality **lumped** elements with useful values past 1 or 2 GHz. Thus, L-Network solutions are generally applicable only in the **RF region** (i.e., < 2GHz).

