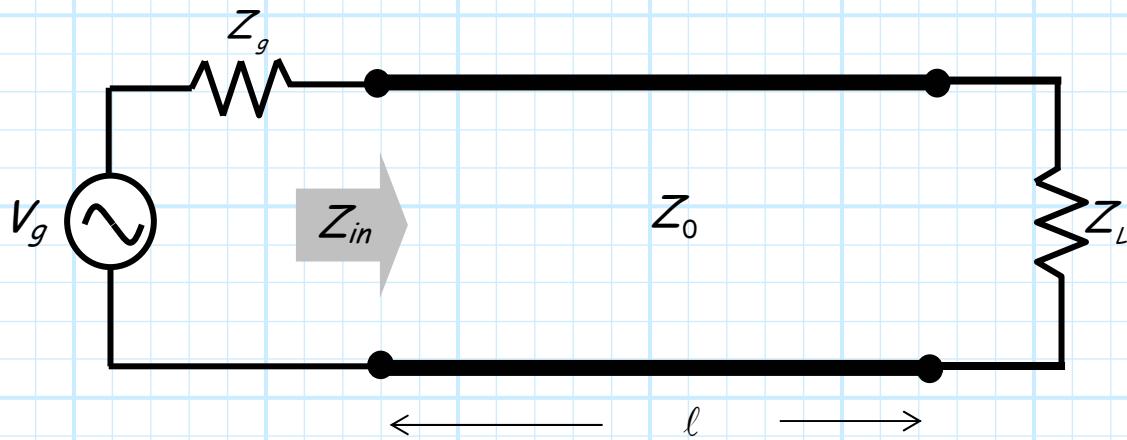


Matching Networks and Transmission Lines

Recall that a primary purpose of a transmission line is to allow the transfer of power from a source to a load.



Q: So, say we directly connect an arbitrary source to an arbitrary load via a length of transmission line. Will the power delivered to the load be equal to the available power of the source?

A: Not likely! Remember we determined earlier that the efficacy of power transfer depends on:

1. the source impedance Z_g .
2. load impedance Z_L .
3. the transmission line characteristic impedance Z_0 .

4. the transmission line length ℓ .


Recall that maximum power transfer occurred only when these four parameters resulted in the input impedance of the transmission line being equal to the complex conjugate of the source impedance (i.e., $Z_{in}^* = Z_g$).

It is of course unlikely that the very specific conditions of a conjugate match will occur if we simply connect a length of transmission line between an arbitrary source and load, and thus the power delivered to the load will generally be less than the available power of the source.

Q: Is there any way to use a matching network to fix this problem? Can the power delivered to the load be increased to equal the available power of the source if there is a transmission line connecting them?


A: There sure is! We can likewise construct a matching network for the case where the source and load are connected by a transmission line.

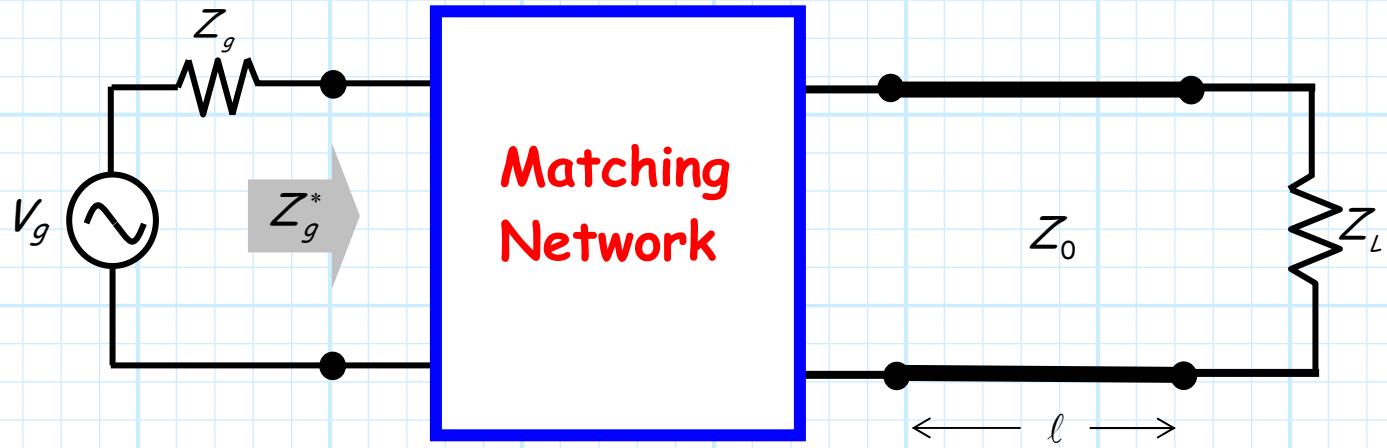For example, we can construct a network to transform the input impedance of the transmission line into the complex conjugate of the source impedance:




Q: But, do we **have** to place the matching network between the source and the transmission line?

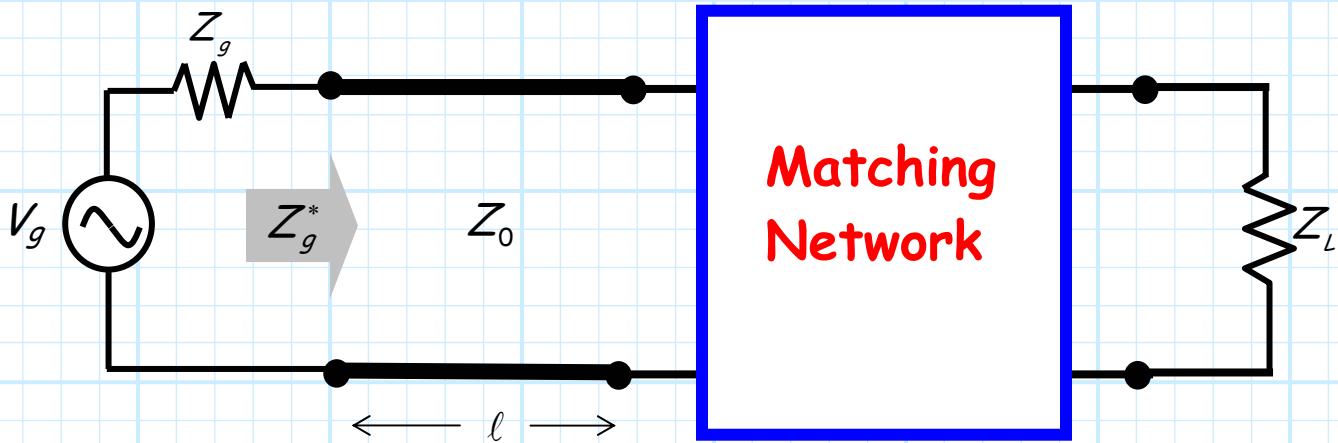A: Nope! We could **also** place a (different) matching network between the transmission line and the load.



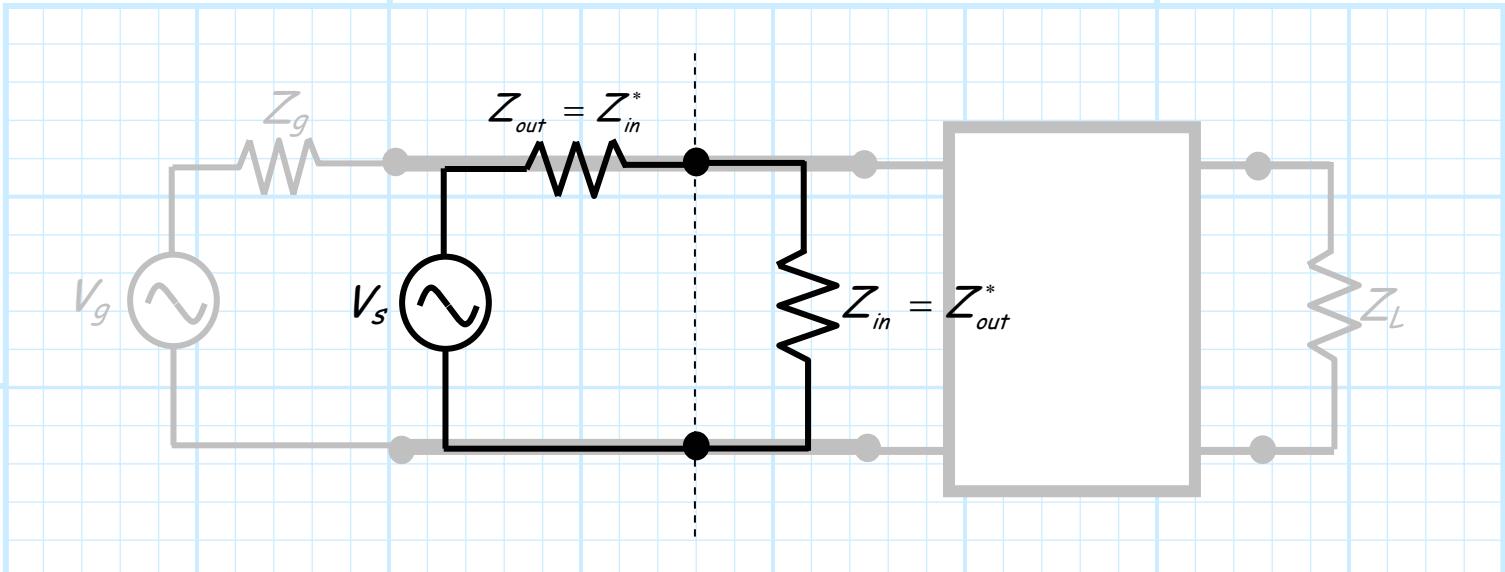
In either case, we find that at **any** and **all** points along this matched circuit, the output impedance of the equivalent source (i.e., looking left) will be equal to the **complex conjugate** of the input impedance (i.e., looking right).




Q: So which method should we chose? Do engineers typically place the matching network between the source and the transmission line, or place it between the transmission line and the load?

A: Actually, the typical solution is to do both!

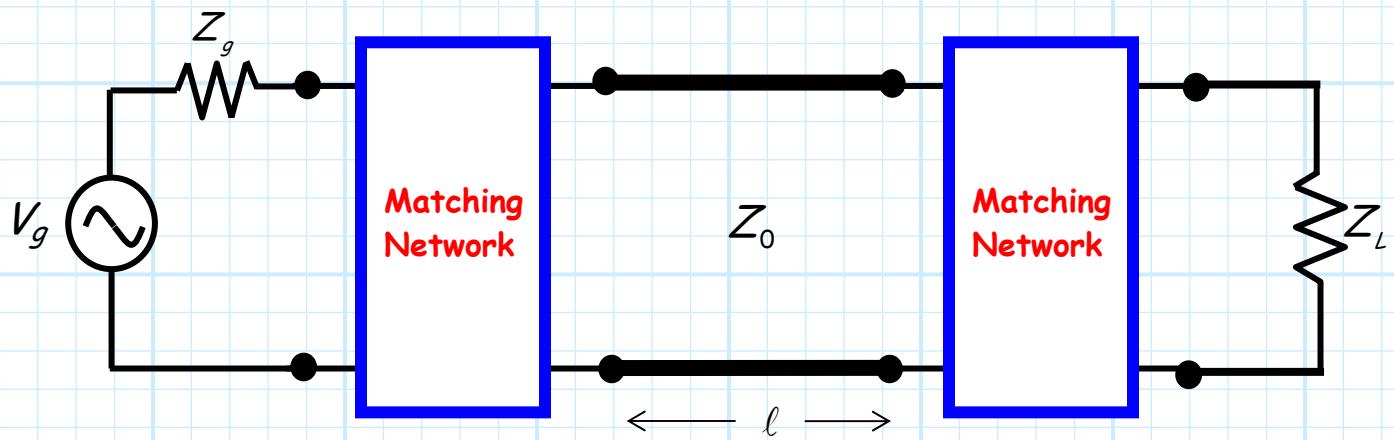
We find that often there is a matching network between the source and the transmission line, and between the line and the load.



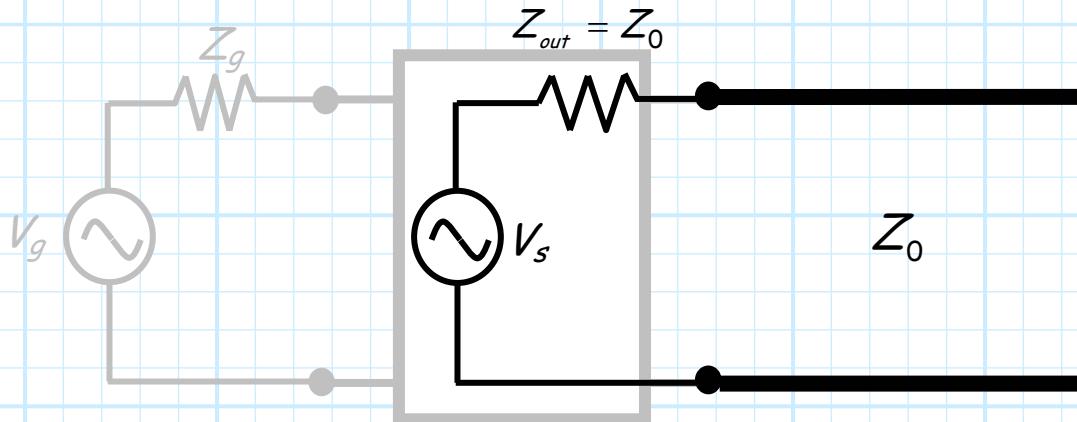The first network matches the **source** to the transmission line—in other words, it transforms the **output impedance** of the equivalent source to a value numerically equal to **characteristic impedance** Z_0 :



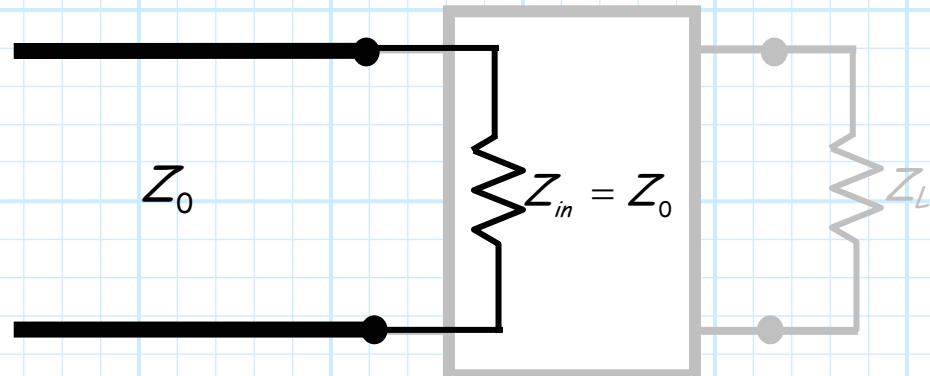The second network matches the **load** to the transmission line—in other words it transforms the **load impedance** to a value numerically equal to **characteristic impedance** Z_0 :



Q: Yikes! Why would we want to build **two separate matching networks**, instead of just one?

A: By using two separate matching networks, we can **decouple** the design problem. Recall again that the design of a **single** matching network solution would depend on four separate parameters:

1. the source impedance Z_s .
2. load impedance Z_L .
3. the transmission line characteristic impedance Z_0 .
4. the transmission line length ℓ .

Alternatively, the design of the network matching the **source** and **transmission line** depends on **only**:

1. the source impedance Z_s .
2. the transmission line characteristic impedance Z_0 .

Whereas, the design of the network matching the **load** and **transmission line** depends on **only**:

1. the source impedance Z_L .
2. the transmission line characteristic impedance Z_0 .

Note that **neither** design depends on the transmission line **length** ℓ !

Q: How is that possible?

A: Remember the case where $Z_g = Z_0 = Z_L$. For that **special** case, we found that a conjugate match was the result—**regardless** of the transmission line length.

Thus, by matching the source to line impedance Z_0 and likewise matching the load to the line impedance, a conjugate match is **assured**—but the **length** of the transmission line does **not matter!**

In fact, the typically problem for microwave engineers is to match a load (e.g., device input impedance) to a **standard** transmission line impedance (typically $Z_0 = 50\Omega$); or to independently match a source (e.g., device output impedance) to a **standard** line impedance.

A **conjugate match** is thus obtained by connecting the two with a transmission line of **any length!**

