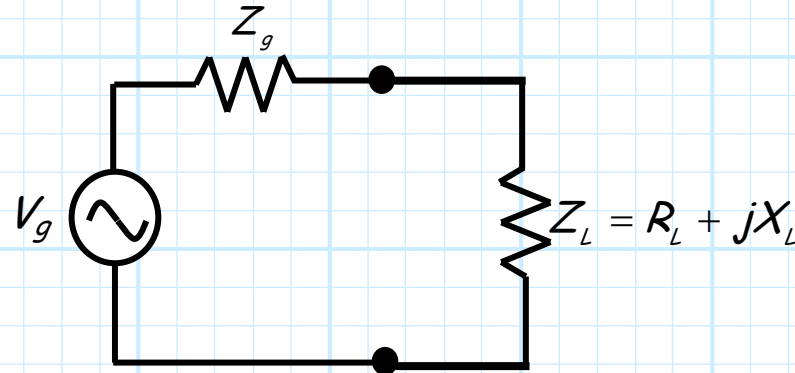


# Matching Networks

Consider again the problem where a **passive load** is attached to an **active source**:



The load will **absorb power**—power that is **delivered** to it by the **source**.

$$P_L = \frac{1}{2} |V_g|^2 \frac{R_L}{|Z_g + Z_L|^2}$$

Recall that the power delivered to the load will be **maximized** (for a given  $V_g$  and  $Z_g$ ) if the load impedance is equal to the **complex conjugate** of the source impedance ( $Z_L = Z_g^*$ ). We call this maximum power the **available power**  $P_{avl}$  of the **source**—it is, after all, the **largest** amount of power that the source can **ever** deliver!

$$P_L^{max} \doteq P_{avl} = \frac{1}{2} |V_g|^2 \frac{R_g}{|Z_g + Z_g^*|^2} = \frac{1}{2} |V_g|^2 \frac{R_g}{|2R_g|^2} = \frac{|V_g|^2}{8R_g}$$

- \* Note the available power of the **source** is dependent on **source** parameters **only** (i.e.,  $V_g$  and  $R_g$ ). This makes sense! Do **you** see why?
- \* Thus, we can say that to "take full advantage" of all the available power of the source, we must to make the load impedance the complex conjugate of the source impedance.
- \* Otherwise, the power delivered to the load will be less than power made available by the source! In other "words":


$$P_L \leq P_{avl}$$

**Q:** *But, you said that the load impedance typically models the input impedance of some useful device. We **don't** typically get to "select" or adjust this impedance—it is what it is. Must we then simply **accept** the fact that the delivered power will be less than the available power?*




**A:** NO! We can in fact modify our circuit such that all available source power is delivered to the load—**without** in any way **altering** the impedance value of that load!

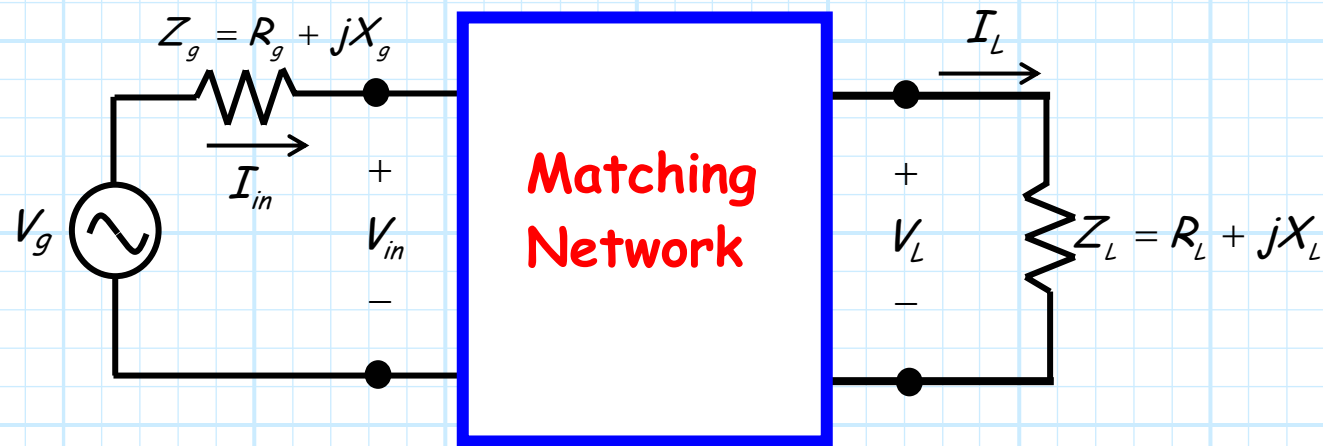To accomplish this, we must insert a **matching network** between the source and the load:




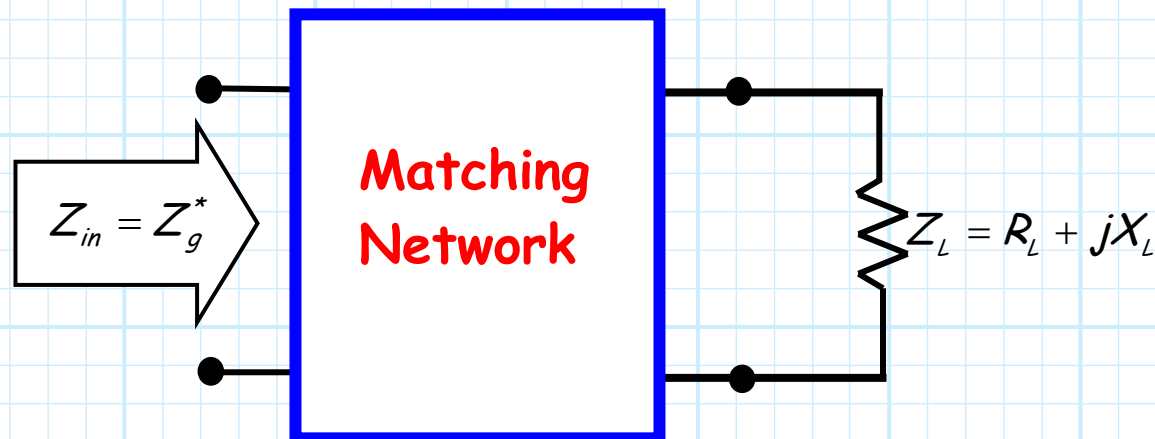The sole purpose of this matching network is to "transform" the load impedance into an input impedance that is **conjugate matched** to the source! I.E.:




Because of this, **all** available source power is delivered to the input of the matching network (i.e., delivered to  $Z_{in}$ ):

$$P_{in} = P_{avl}$$

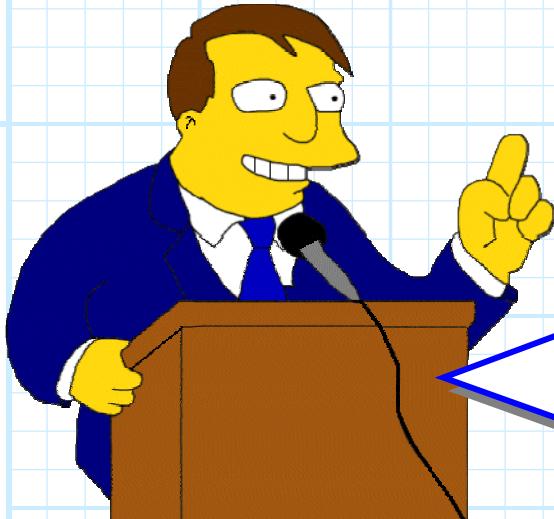

**Q:** *Wait just one second! The matching network ensures that **all** available power is delivered to the **input** of the matching network, but that does **not** mean (necessarily) that this power will be delivered to the **load**  $Z_L$ . The power delivered to the load **could still be much less** than the available power!*

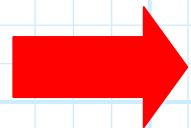**A:** True! To ensure that the **available power** delivered to the input of the matching network is **entirely** delivered to the **load**, we must construct our matching network such that it **cannot absorb any power**—the matching network must be **lossless**!



We must construct our matching network entirely with **reactive elements**!


Examples of reactive elements include inductors, capacitors, transformers, as well as lengths of **lossless transmission lines**.

Thus, constructing a proper lossless matching network will lead to the **happy** condition where:


$$P_L = P_{in} = P_{avl}$$

- \* Note that the design and construction of this lossless network will depend on **both** the value of source impedance  $Z_g$  and load impedance  $Z_L$ .
- \* However, the matching network does **not physically alter** the values of either of these two quantities—the source and load are left physically unchanged!

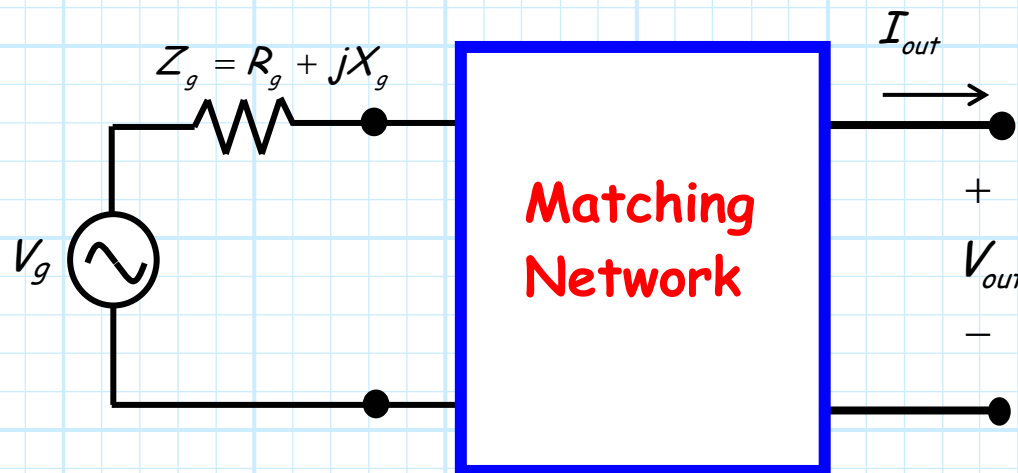Now, let's consider the matching network from a **different perspective**. Instead of defining it in terms of its **input impedance** when attached the load, let's describe it in terms of its **output impedance** when attached to the source:



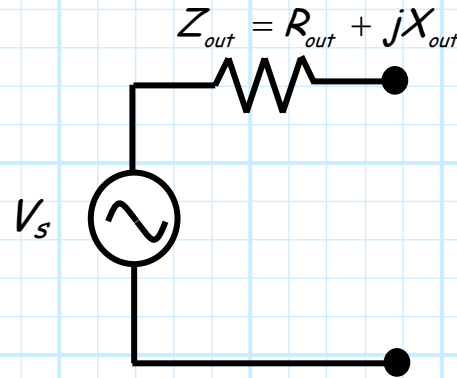This "new" source (i.e., the original source with the matching network attached) can be expressed in terms of its **Thevenin's equivalent circuit**:



Note that in general that  $V_s \neq V_g$  and  $Z_{out} \neq Z_g$ —the matching network "transforms" **both** the values of both the impedance **and** the voltage source.




**Q:** *Arrrrgg! Doesn't that mean that the available power of this "transformed" source will be different from the original?*


**A:** Nope. If the matching network is **lossless**, the available power of this equivalent source is **identical** to the available power of the original source—the lossless matching network does **not** alter the available power!

Now, for a **properly** designed, **lossless** matching network, it turns out that (as you might have expected!) the output impedance  $Z_{out}$  is equal to the **complex conjugate** of the load impedance. I.E.:


$$Z_{out} = Z_L^*$$

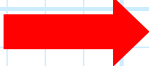 The source and load are again matched!

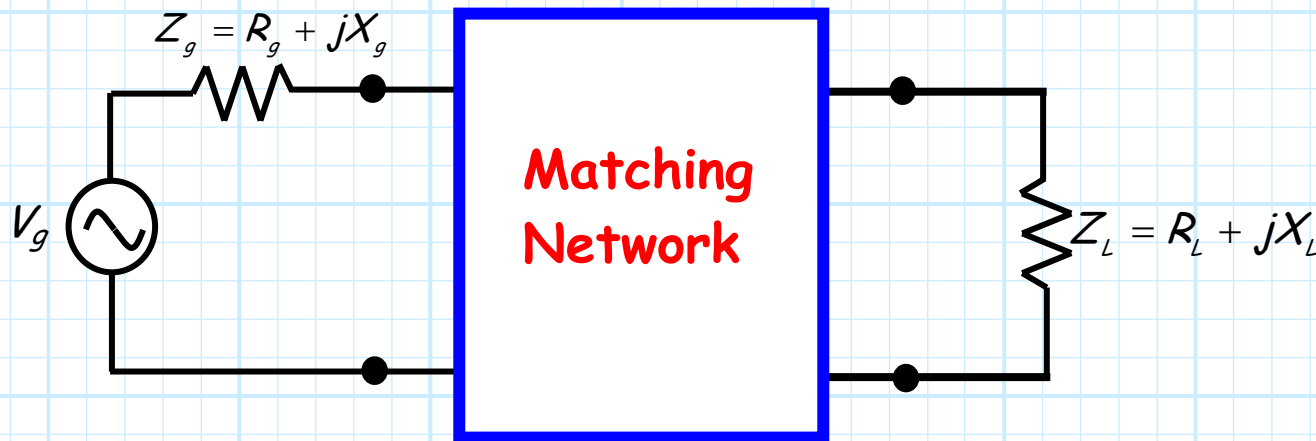
Thus, we can look at the matching network in two equivalent ways:



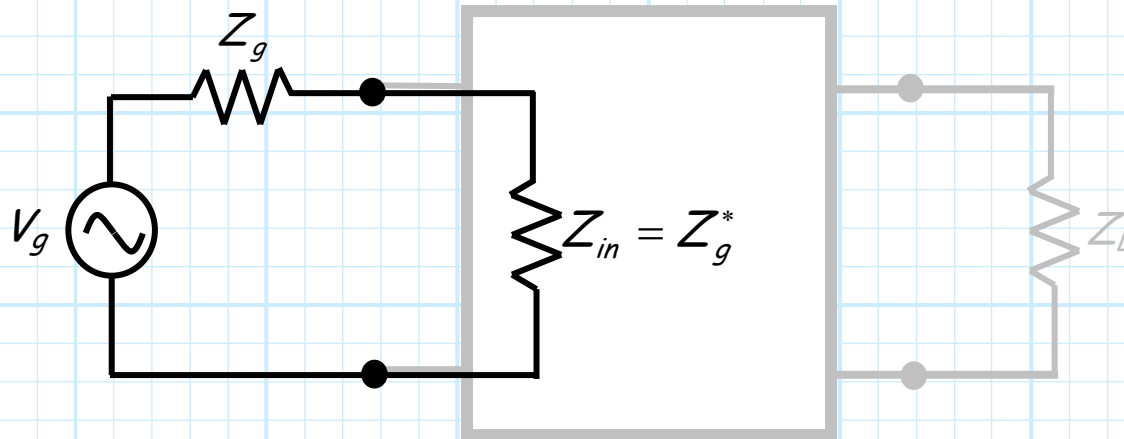1. As a network attached to a load, one that "transforms" its impedance to  $Z_{in}$ —a value matched to the source impedance  $Z_g$ :



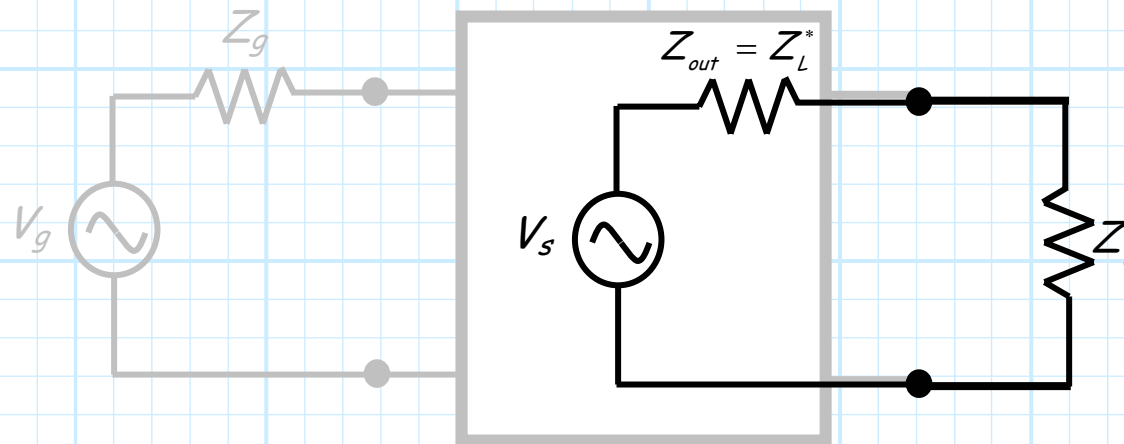2. Or, as network attached to a source, one that "transforms" its impedance to  $Z_{out}$ —a value matched to the load impedance  $Z_L$ :



Either way, the source and load impedance are conjugate matched—**all** the available power is delivered to the load!