
Multi-Section Coupled Line Couplers

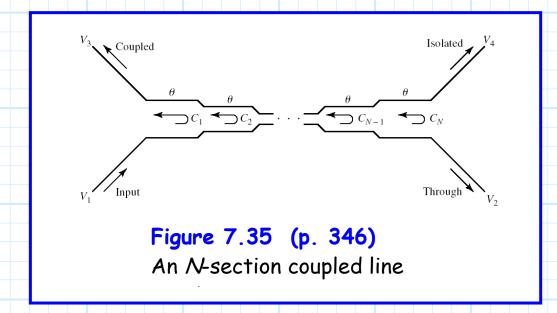We can add **multiple** coupled lines in series to increase coupler bandwidth.



We typically design the coupler such that it is symmetric, i.e.:

$$c_1 = c_N$$
, $c_2 = c_{N-1}$, $c_3 = c_{N-2}$, etc.

where Nis odd.

Q: What is the coupling of this device as a function of frequency?

A: To analyze this structure, we make an approximation similar to that of the theory of small reflections.

First, if c is **small** (i.e., less than 0.3), then we can make the approximation:

$$S_{31}(\theta) = \frac{jc \tan \theta}{\sqrt{1 - c^2} + j \tan \theta}$$

$$\approx \frac{jc \tan \theta}{1 + j \tan \theta}$$

$$= jc \sin \theta e^{-j\theta}$$

Likewise:


$$S_{21}(\theta) = \frac{\sqrt{1-c^2}}{\sqrt{1-c^2}\cos\theta + j\sin\theta}$$

$$\approx \frac{1}{\cos\theta + j\sin\theta}$$


$$= e^{-j\theta}$$

where of course $\theta=\beta\ell=\omega\mathcal{T}$, and $\mathcal{T}=\ell/v_p$.

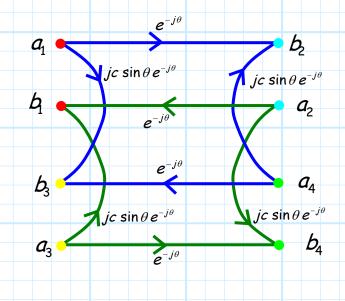
We can use these approximations to construct a signal flow graph of a single-section coupler:



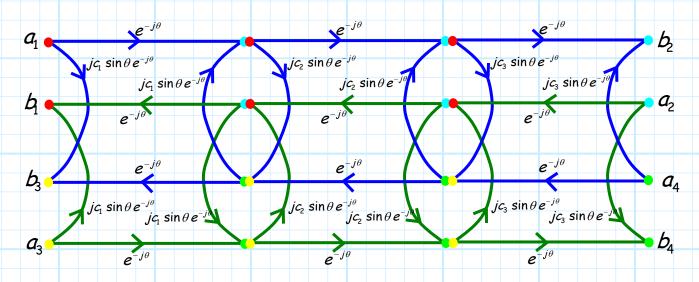Now, say we cascade three coupled line pairs, to form a three section coupled line coupler. The signal flow graph would thus be:



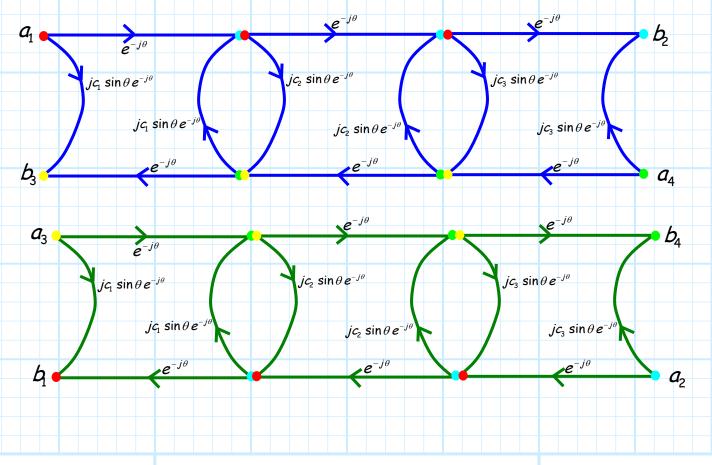
Note that this signal flow graph decouples into two separate and graphs (i.e., the blue graph and the green graph).



Jim Stiles The Univ. of Kansas Dept. of EECS

Note also that these two graphs are essentially identical, and emphasize the symmetric structure of the coupled-line coupler.

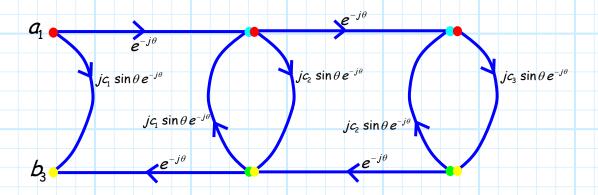Now, we are interested in describing the **coupled output** (i.e., b_3) in terms of the incident wave (i.e., a_1). Assuming ports 2, 3 and 4 are **matched** (i.e., $a_2 = a_3 = a_4 = 0$), we can reduce the graph to simply:




Now, we **could** reduce this signal flow graph even further—**or** we could truncate a **propagation series** by considering only the **direct paths!**

We of course used this idea to analyze multi-section matching networks, an approach dubbed the "theory of small reflections".

Essentially we are now applying a "theory of small couplings". In other words, we consider only the propagation paths where one coupling is involved—the signal propagates across a coupled-line pair only once!

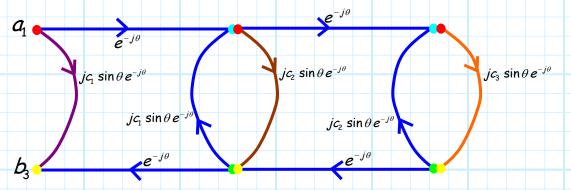Note from the signal flow graph that there are **three** such mechanisms, corresponding to the coupling across each of the **three** separate coupled line pairs:



$$b_{3} \approx \left(jc_{1} \sin \theta e^{-j\theta} + e^{-j\theta} jc_{2} \sin \theta e^{-j\theta} e^{-j\theta} + e^{-j2\theta} jc_{3} \sin \theta e^{-j\theta} e^{-j2\theta} \right) a_{1}$$

$$= \left(jc_{1} \sin \theta e^{-j\theta} + jc_{2} \sin \theta e^{-j3\theta} + jc_{3} \sin \theta e^{-j5\theta} \right) a_{1}$$

Note that all other terms of the infinite series would involve at least three couplings (i.e., three crossings), and thus these terms would be exceeding small (i.e., $c^3 \approx 0$).

Therefore, according to this approximation:

$$S_{31}(\theta) = \frac{V_3^-}{V_1^+}(\theta) = \frac{b_3}{a_1}(\theta) = jc_1 \sin\theta e^{-j\theta} + jc_2 \sin\theta e^{-j3\theta} + jc_3 \sin\theta e^{-j5\theta}$$

Moreover, for a multi-section coupler with N sections, we find:

$$S_{31}(\theta) = \int c_1 \sin \theta \ e^{-j\theta} + \int c_2 \sin \theta \ e^{-j3\theta} + \int c_3 \sin \theta e^{-j5\theta} + \cdots + \int c_N \sin \theta \ e^{-j(2N-1)\theta}$$

And for symmetric couplers with an odd value N, we find:

$$S_{31}(\theta) = j2\sin\theta \ e^{-jN\theta} \left[c_1 \cos(N-1)\theta + c_2 \cos(N-3)\theta + c_3 \cos(N-5)\theta + \cdots + \frac{1}{2}c_M \right]$$

where M = (N+1)/2.

Thus, we find the coupling **magnitude** as a function of frequency is:

$$\begin{aligned} \left| c(\theta) \right| &= \left| \mathcal{S}_{31}(\theta) \right| \\ &= c_1 2 \sin \theta \cos \left(\mathcal{N} - 1 \right) \theta + c_2 2 \sin \theta \cos \left(\mathcal{N} - 3 \right) \theta \\ &+ c_3 2 \sin \theta \cos \left(\mathcal{N} - 5 \right) \theta + \dots + c_M \sin \theta \end{aligned}$$

And thus the coupling in dB is:

$$C(\theta) = -10\log_{10}|c(\theta)|^2$$

Now, our design goals are to **select** the coupling values $c_1, c_2, \cdots c_N$ such that:

- 1. The coupling value $C(\theta)$ is a specific, **desired** value at our design frequency.
- 2. The coupling bandwidth is as large as possible.

For the first condition, recall that the at the design frequency:

$$\theta = \beta \ell = \pi/2$$

I.E., the section lengths are a quarter-wavelength at our design frequency.

Thus, we find our first design equation:

$$|c(\theta)|_{\theta=\frac{\pi}{2}} = c_1 2\cos(N-1)\pi/2 + c_2 2\cos(N-3)\pi/2 + c_3 2\cos(N-5)\pi/2 + \cdots + c_M$$

where we have used the fact that $\sin(\pi/2) = 1$.

Note the value $|c(\theta)|_{\theta=\frac{\pi}{2}}$ is set to the value necessary to achieve the **desired** coupling value. This equation thus provides **one** design constraint—we have **M-1** degrees of design freedom left to accomplish our **second** goal!

To maximize bandwidth, we typically impose the maximally flat condition:

$$\frac{d^{m}|c(\theta)|}{d\theta^{m}}\bigg|_{\theta=\frac{\pi}{2}}=0 \qquad m=1,2,3\cdots$$

Be careful! Remember to perform the derivative **first**, and **then** evaluate the result at $\theta = \pi/2$.



You will find for a **symmetric** coupler, the **odd**-ordered derivatives (e.g., $d|c(\theta)|/d\theta$, $d^3|c(\theta)|/d\theta^3$,

 $d^5|c(\theta)|/d\theta^5$)are uniquely **zero**. In other words, they are zero-valued at $\theta = \pi/2$ **regardless** of the values of coupling coefficients c_1, c_2, c_3, \cdots !

As a result, these odd-order derivatives do not impose a maximally flat design equation—only the even-ordered derivatives do. Keep taking these derivatives until your design is fully constrained (i.e., the number of design equations equals the number of unknown coefficients c_1, c_2, c_3, \cdots).

One final note, you may find that this **trig** expression is helpful in **simplifying** your derivatives:

$$\sin\phi\cos\psi = \frac{1}{2}\sin(\phi + \psi) + \frac{1}{2}\sin(\phi - \psi)$$

For example, we find that:

$$2 \sin \theta \cos 2\theta = \sin(\theta + 2\theta) + \sin(\theta - 2\theta)$$
$$= \sin(3\theta) + \sin(-\theta)$$
$$= \sin(3\theta) - \sin(\theta)$$