


Odd/Even Mode Analysis

Q: Although symmetric *circuits* appear to be plentiful in microwave engineering, it seems unlikely that we would often encounter symmetric *sources*. Do virtual shorts and opens typically ever occur?



A: One word—superposition!

If the elements of our circuit are independent and linear, we can apply superposition to analyze symmetric circuits when non-symmetric sources are attached.

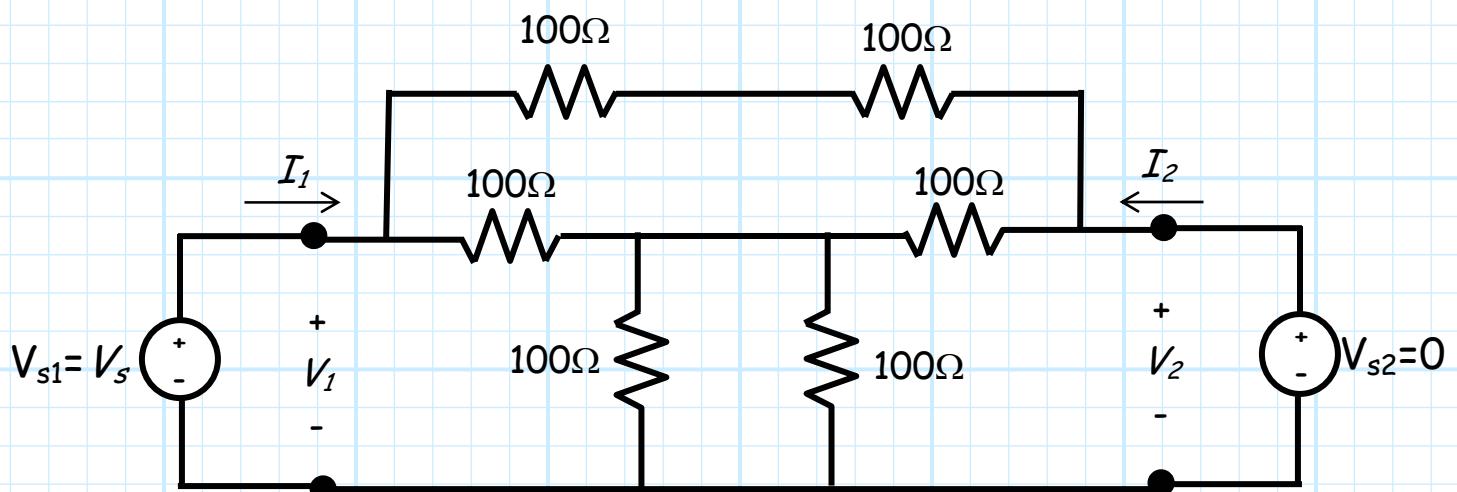
For example, say we wish to determine the admittance matrix of this circuit. We would place a **voltage source** at port 1, and a **short circuit** at port 2—a set of **asymmetric sources** if there ever was one!



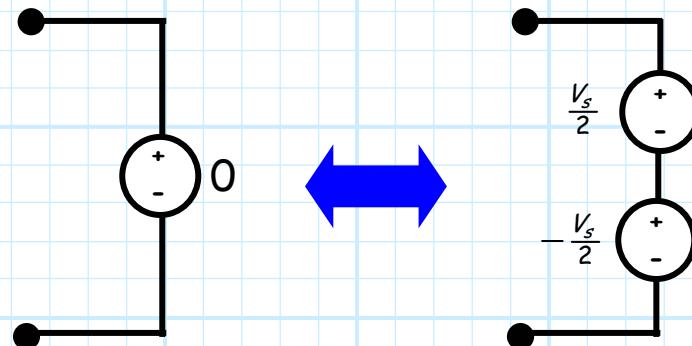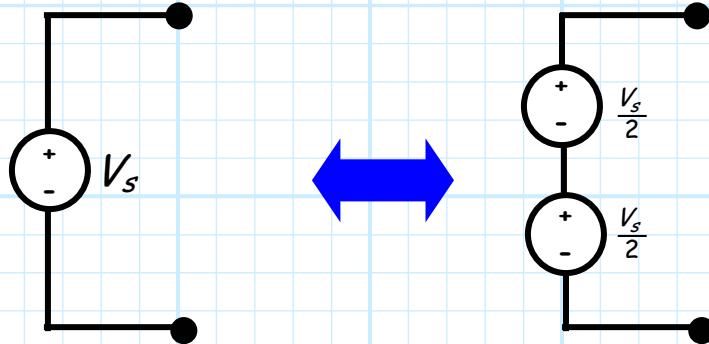
Here's the really **neat** part. We find that the source on port 1 can be modeled as **two equal** voltage sources in series, whereas the source at port 2 can be modeled as **two equal but opposite** sources in series.



Therefore an **equivalent circuit** is:

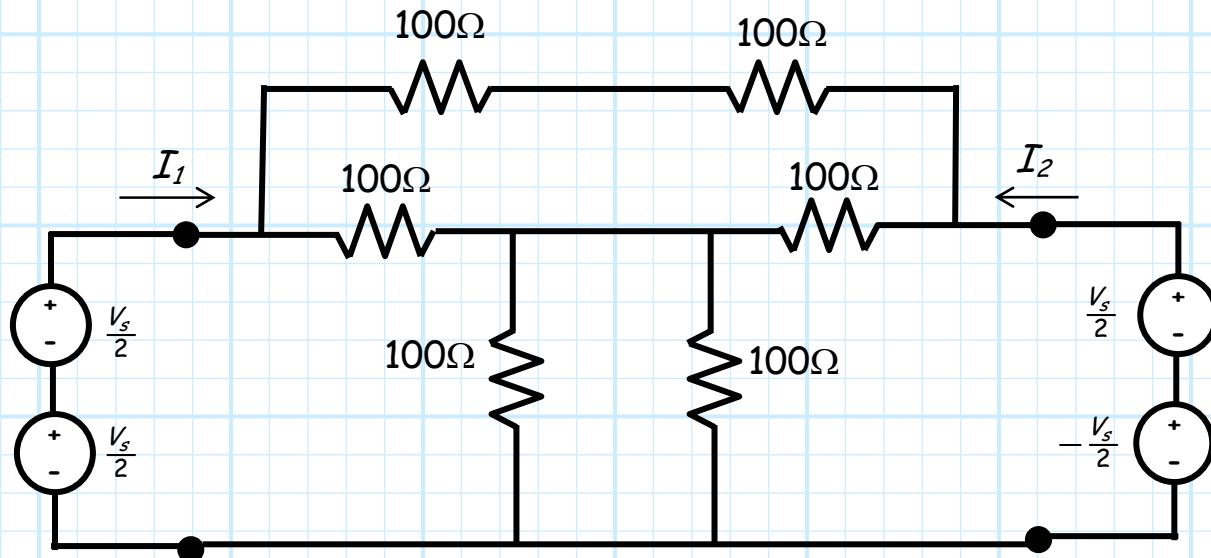

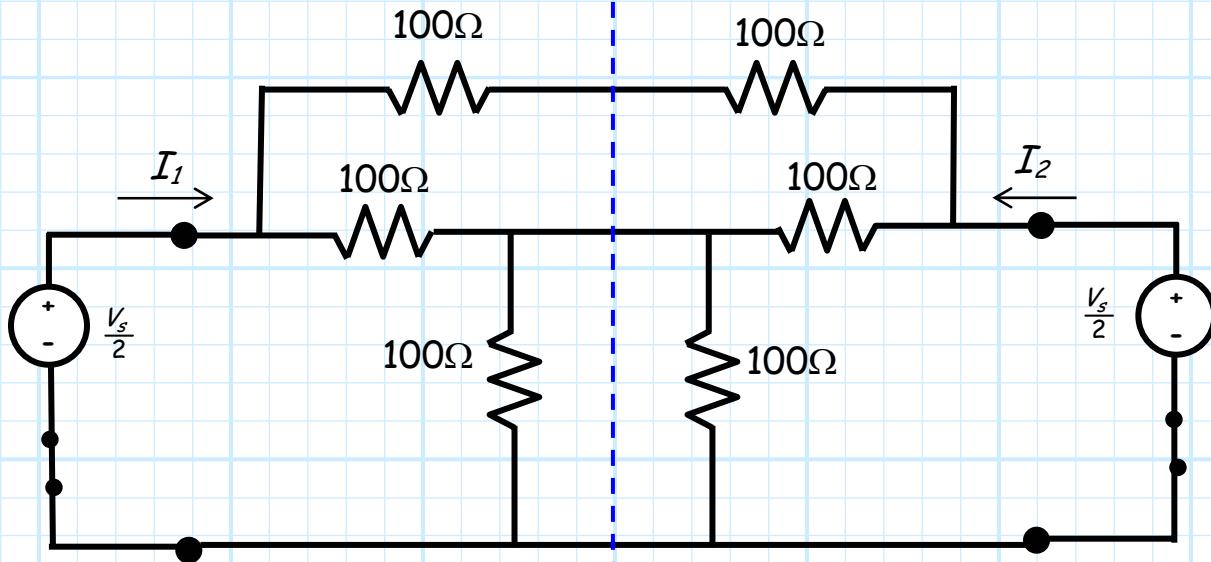
Now, the above circuit (due to the sources) is obviously **asymmetric**—no virtual ground, nor virtual short is present. But, let's say we turn off (i.e., set to $V=0$) the bottom source on each side of the circuit:



Our symmetry has been restored! The symmetry plane is a virtual open.


This circuit is referred to as its **even mode**, and analysis of it is known as the **even mode analysis**. The solutions are known as the **even mode currents and voltages**!

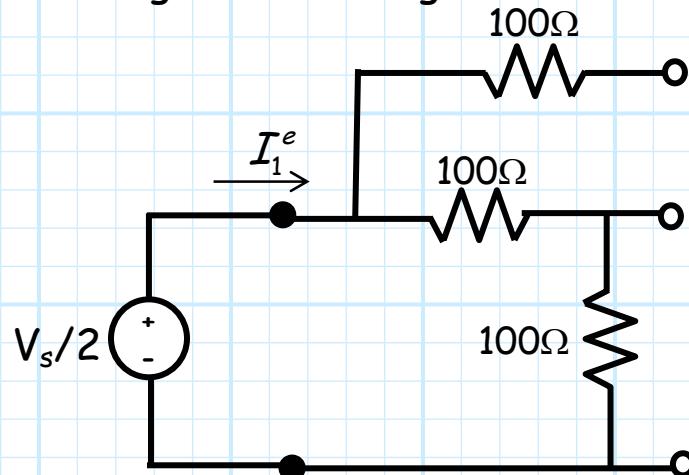Evaluating the resulting **even mode** half circuit we find:



$$I_1^e = \frac{V_s}{2} \cdot \frac{1}{200} = \frac{V_s}{400} = I_2^e$$

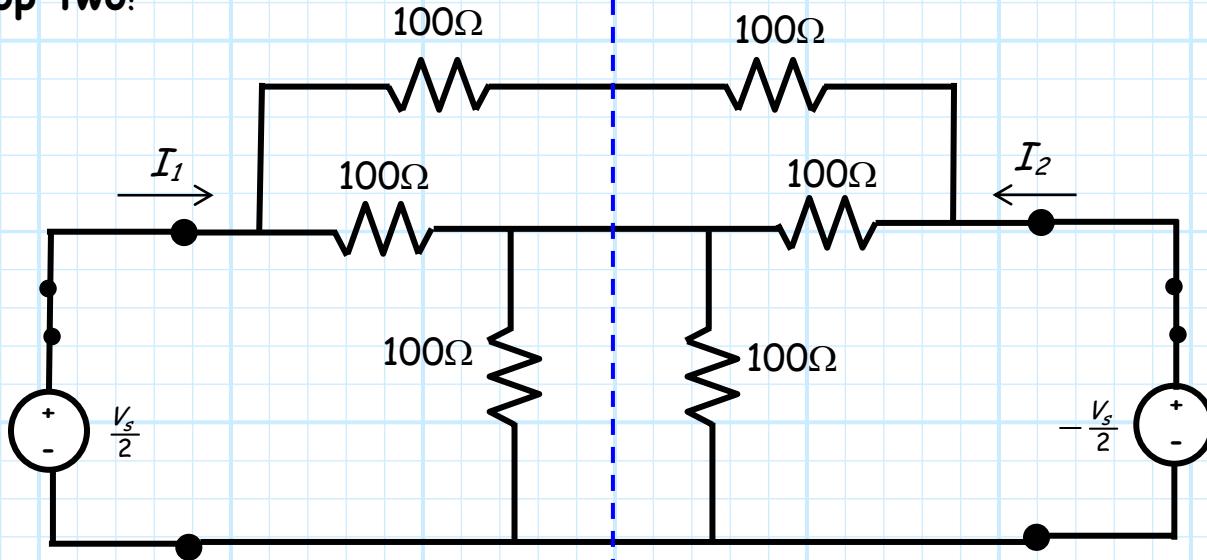
Now, let's turn the bottom sources back on—but turn off the top two!



We now have a circuit with **odd symmetry**—the symmetry plane is a **virtual short**!

This circuit is referred to as its **odd mode**, and analysis of it is known as the **odd mode analysis**. The solutions are known as the **odd mode currents and voltages**!

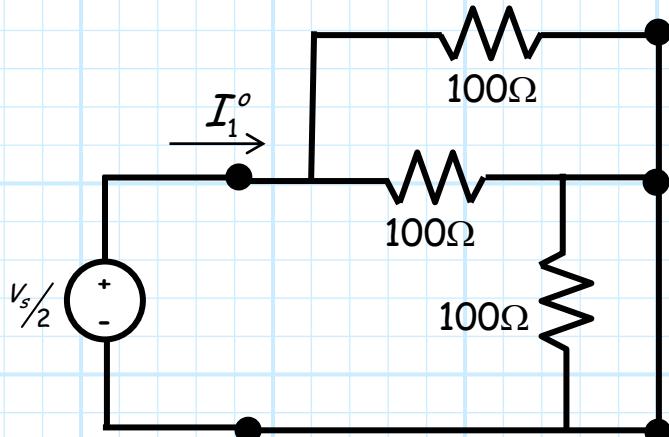Evaluating the resulting odd mode half circuit we find:



$$I_1^o = \frac{V_s}{2} \cdot \frac{1}{50} = \frac{V_s}{100} = -I_2^o$$

Q: But what good is this "even mode" and "odd mode" analysis? After all, the source on port 1 is $V_{s1} = V_s$, and the source on port 2 is $V_{s2} = 0$. What are the currents I_1 and I_2 for these sources?


A: Recall that these sources are the sum of the even and odd mode sources:

$$V_{s1} = V_s = \frac{V_s}{2} + \frac{V_s}{2}$$

$$V_{s2} = 0 = \frac{V_s}{2} - \frac{V_s}{2}$$

and thus—since all the devices in the circuit are linear—we know from superposition that the currents I_1 and I_2 are simply the sum of the odd and even mode currents!
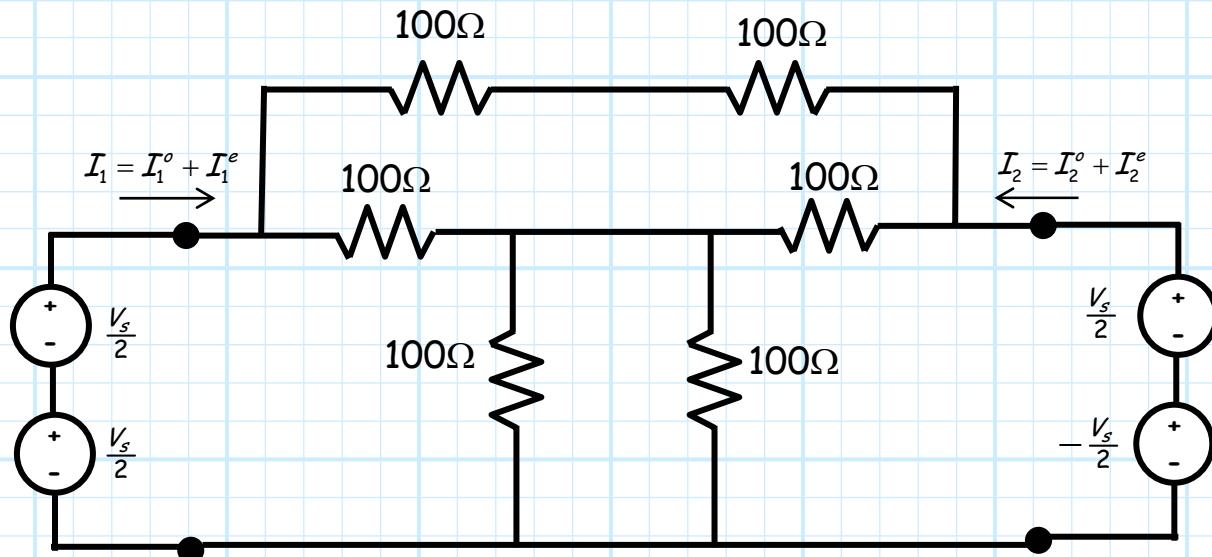
$$I_1 = I_1^e + I_1^o \quad I_2 = I_2^e + I_2^o$$



Thus, adding the odd and even mode analysis results together:

$$\begin{aligned} I_1 &= I_1^e + I_1^o \\ &= \frac{V_s}{400} + \frac{V_s}{100} \\ &= \frac{V_s}{80} \end{aligned}$$

$$\begin{aligned} I_2 &= I_2^e + I_2^o \\ &= \frac{V_s}{400} - \frac{V_s}{100} \\ &= -\frac{3V_s}{400} \end{aligned}$$

And then the **admittance parameters** for this two port network is:

$$Y_{11} = \left. \frac{I_1}{V_{s1}} \right|_{V_{s2}=0} = \frac{V_s}{80} \frac{1}{V_s} = \frac{1}{80}$$

$$Y_{21} = \left. \frac{I_2}{V_{s1}} \right|_{V_{s2}=0} = -\frac{3V_s}{400} \frac{1}{V_s} = -\frac{3}{400}$$

And from the **symmetry** of the device we know:

$$Y_{22} = Y_{11} = \frac{1}{80}$$


$$Y_{12} = Y_{21} = -\frac{3}{400}$$

Thus, the full **admittance matrix** is:

$$Y = \begin{bmatrix} \frac{1}{80} & -\frac{3}{400} \\ -\frac{3}{400} & \frac{1}{80} \end{bmatrix}$$



Q: What happens if both sources are non-zero? Can we use symmetry then?

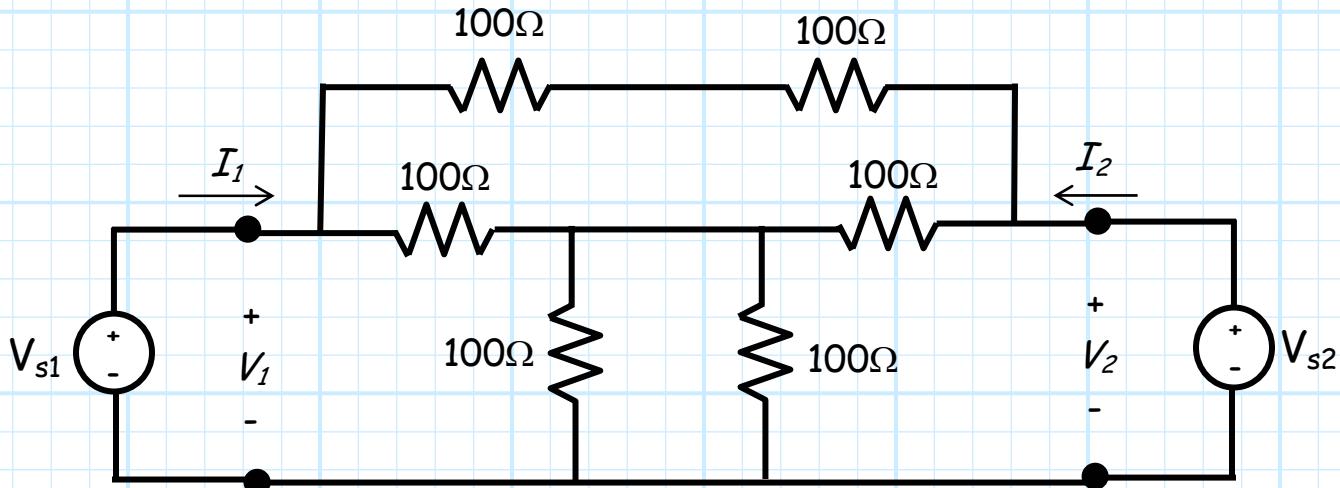A: Absolutely! Consider the problem below, where neither source is equal to zero:





In this case we can define an even mode and an odd mode source as:
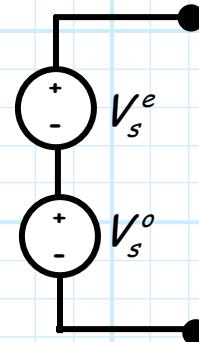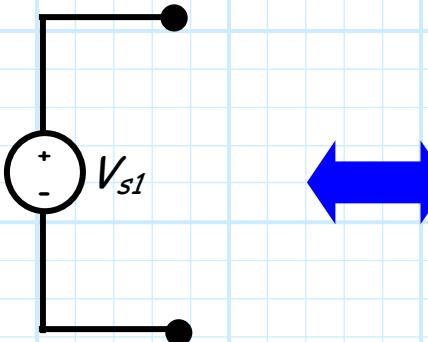
$$V_s^e = \frac{V_{s1} + V_{s2}}{2} \quad V_s^o = \frac{V_{s1} - V_{s2}}{2}$$




$$V_{s1} = V_s^e + V_s^o$$

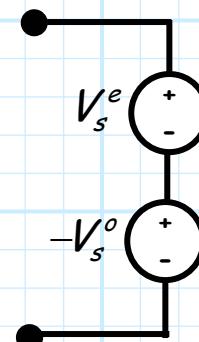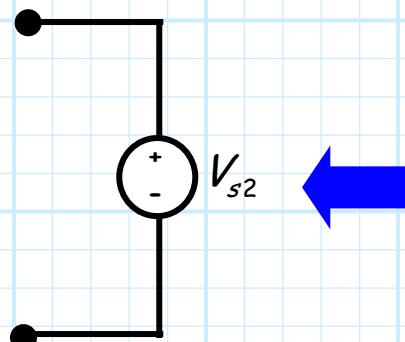


$$V_{s2} = V_s^e - V_s^o$$

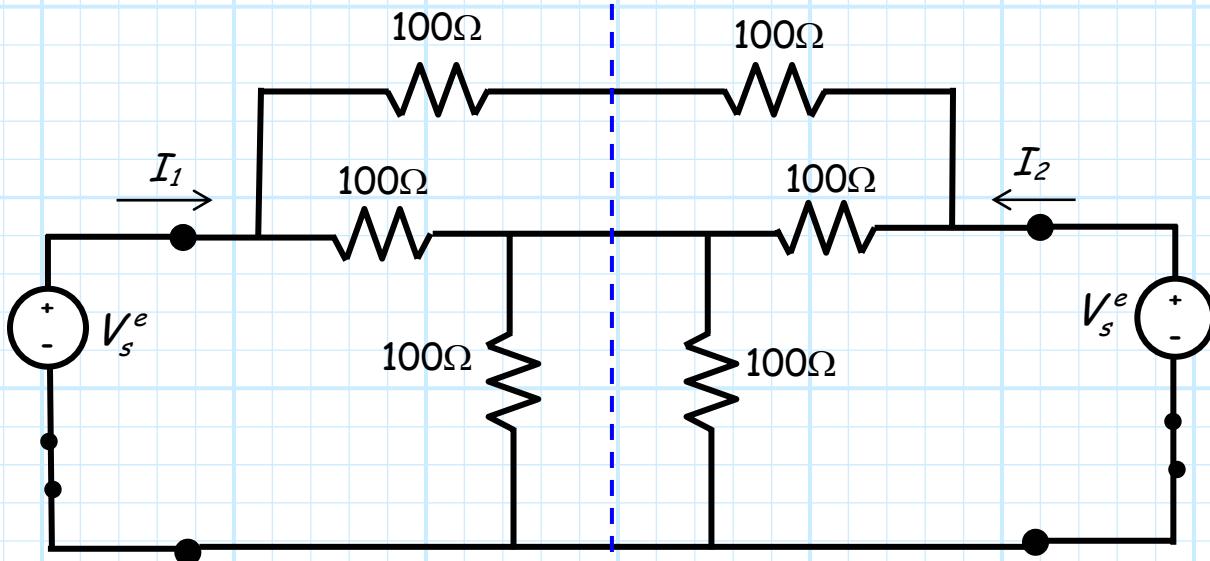We then can analyze the **even mode** circuit:



And then the **odd mode** circuit:

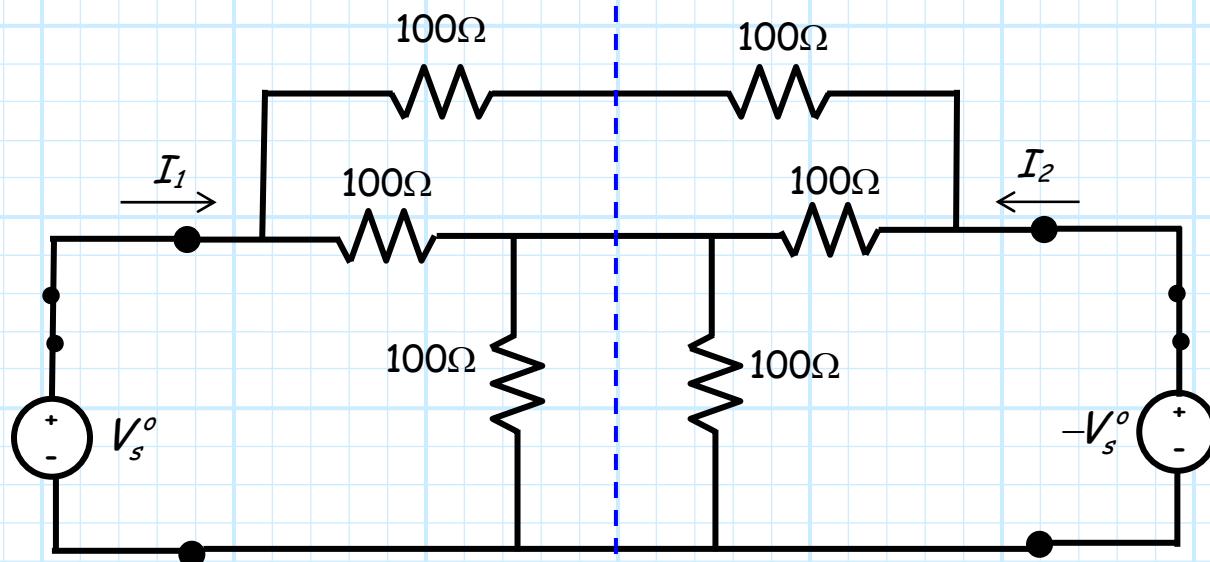

And then combine these results in a **linear superposition**!

One final word (I promise!) about circuit symmetry and even/odd mode analysis: precisely the same concept exists in electronic circuit design!

Specifically, the differential (odd) and common (even) mode analysis of bilaterally symmetric electronic circuits, such as differential amplifiers!



Hi! You might remember differential and common mode analysis from such classes as "EECS 412- Electronics II", or handouts such as "Differential Mode Small-Signal Analysis of BJT Differential Pairs"

