
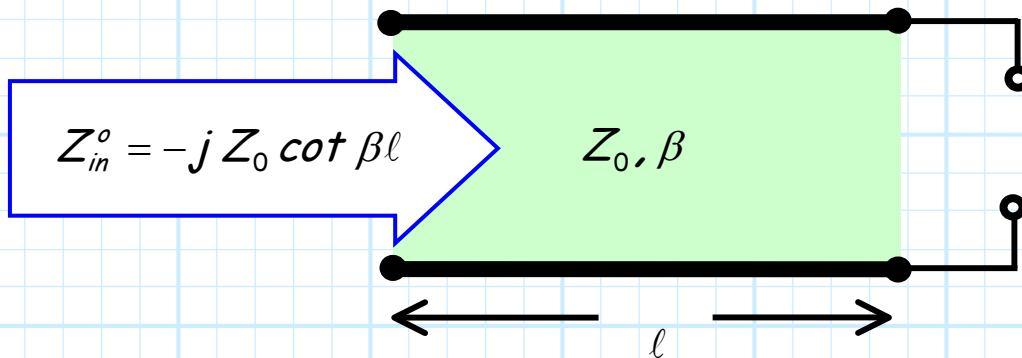

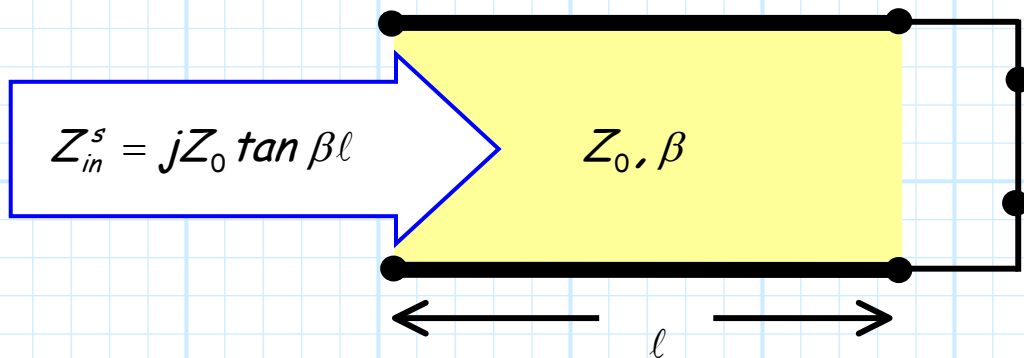
# Richard's Transformations

Recall the input impedances of short-circuited and open-circuited transmission line **stubs**.



Note that the input impedances are purely **reactive**—just like **lumped** elements!

However, the reactance of lumped inductors and capacitors have a **different** mathematical form to that of transmission line stubs:

$$Z_L = j\omega L$$

$$Z_C = \frac{-j}{\omega C}$$

In other words, the impedance of transmission line stubs and lumped elements (capacitors and inductors) are different functions with respect to **frequency**. Therefore, we can say in general that, for example:

$$Z_{in}^s \neq Z_L \qquad Z_{in}^o \neq Z_C$$

However, for a given lumped element ( $L$  or  $C$ ) and a given stub (with a given  $Z_0$  and length  $l$ ) the functions **will** be equal at precisely **one frequency**!

For example, there is one frequency—let's call it  $\omega_c$ —that satisfies **this** equation for a given  $L, Z_0$ , and  $l$ :

$$\begin{aligned} j\omega_c L &= j Z_0 \tan \beta_c l \\ &= j Z_0 \tan \left[ \frac{\omega_c}{v_p} l \right] \end{aligned}$$

or similarly satisfies **this** equation:

$$\begin{aligned} \frac{-j}{\omega_c C} &= -j Z_0 \cot \beta_c l \\ &= -j Z_0 \cot \left[ \frac{\omega_c}{v_p} l \right] \end{aligned}$$

To make things easier, let's set the **length** of our transmission line stub to  $\lambda_c/8$ , where:

$$\lambda_c = \frac{v_p}{\omega_c} = \frac{2\pi}{\beta_c}$$


**Q:** Why  $\ell = \lambda_c/8$  ?

**A:** Well, for **one** reason,  $\beta_c \ell = \pi/4$  and therefore  $\tan(\pi/4) = 1.0!$


This of course greatly **simplifies** our earlier results:

$$\begin{aligned} j\omega_c L &= j Z_0 \tan\left(\frac{\pi}{4}\right) & \frac{-j}{\omega_c C} &= -j Z_0 \cot\left(\frac{\pi}{4}\right) \\ &= j Z_0 & &= -j Z_0 \end{aligned}$$

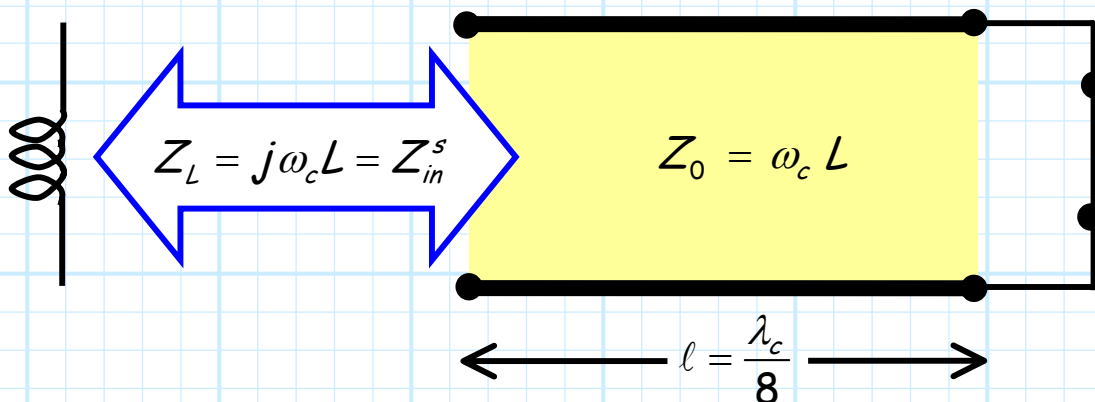Therefore, if we wish to build a **short-circuited** stub with the **same** impedance as an **inductor**  $L$  at frequency  $\omega_c$ , we set the **characteristic impedance** of the stub transmission line to be  $Z_0 = \omega_c L$ :



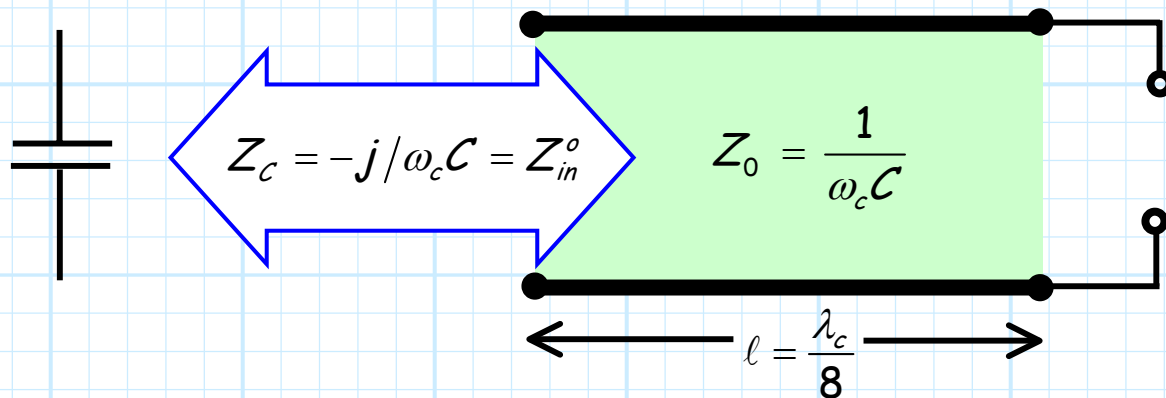Likewise, if we wish to build an **open-circuited** stub with the **same** impedance as an **capacitor**  $C$  at frequency  $\omega_c$ , we set the **characteristic impedance** of the stub transmission line to be  $Z_0 = 1/\omega_c C$ :



We call these two results **Richard's Transformations**.

However, it is important to remember that Richard's Transformations do **not** result in **perfect** replacements for lumped elements—the stubs **do not** behave like capacitors and inductors!

Instead, the transformation is **perfect**—the impedances are **equal**—at **only one frequency** ( $\omega_c$ ).

We can use Richard's transformations to replace the inductors and capacitors of a lumped element filter design. In fact, for **lowpass filter design**, the frequency  $\omega_c$  is the filter's **cutoff frequency**.

Using these stubs to **replace** inductors and capacitors will result in a filter response **similar** to that of the lumped element design—a low pass filter with cutoff frequency  $\omega_c$ .

However, the behavior of the filter in the **stopband** will be **very** different from the lumped element design. For example, at the (high) frequencies where the stub length becomes a **multiple** of  $\lambda/2$ , the filter response will be that of  $\omega = 0$ —near perfect **transmission!**

**Figure 8.37 goes here**

**Q:** *So why does the filter response match the lumped element response so well in the passband?*

**A:** To see why, we first note that the **Taylor Series approximation** for  $\tan \phi$  and  $\cot \phi$  when  $\phi$  is small (i.e.,  $\phi \ll 1$ ) is:

$$\tan \phi \approx \phi \quad \text{and} \quad \cot \phi \approx \frac{1}{\phi} \quad \text{for} \quad \phi \ll 1$$

and  $\phi$  is expressed in **radians**.

The **impedance** of our Richard's transformation shorted stub at some **arbitrary frequency**  $\omega$  is:

$$\begin{aligned}
 Z_{in}^s(\omega) &= j Z_0 \tan\left(\beta \frac{\lambda_c}{8}\right) \\
 &= j(\omega_c L) \tan\left(\frac{\omega}{v_p} \frac{\lambda_c}{8}\right) \\
 &= j(\omega_c L) \tan\left(\frac{\omega}{\omega_c} \frac{\pi}{4}\right)
 \end{aligned}$$

Therefore, when  $\omega \ll \omega_c$  (i.e., frequencies in the **passband** of a low-pass filter!), we can **approximate** this impedance as:

$$\begin{aligned}
 Z_{in}^s(\omega) &= j(\omega_c L) \tan\left(\frac{\omega}{\omega_c} \frac{\pi}{4}\right) \\
 &\approx j \omega_c L \left(\frac{\omega}{\omega_c} \frac{\pi}{4}\right) \\
 &= j \omega L \left(\frac{\pi}{4}\right) \quad \text{when } \omega \ll \omega_c
 \end{aligned}$$

Compare this to a **lumped inductor** impedance:

$$Z_L = j \omega L$$

Since the value  $\pi/4$  is **relatively** close to one, we find that the Richard's Transformation shorted stub has an input impedance **very** close to the lumped element inductor for **all** frequencies **less than**  $\omega_c$  (i.e., all frequencies of the low-pass filter pass-band)!

Similarly, we find that the Richard's transformation **open-circuit** stub has an input impedance of **approximately**:

$$\begin{aligned}Z_{in}^o(\omega) &= \frac{-j}{\omega_c \mathcal{C}} \cot\left(\frac{\omega}{\omega_c} \frac{\pi}{4}\right) \\ &\approx \frac{-j}{\omega_c \mathcal{C}} \left(\frac{\omega_c}{\omega} \frac{4}{\pi}\right) \\ &= \frac{1}{j\omega \mathcal{C}} \left(\frac{4}{\pi}\right) \quad \text{when } \omega \ll \omega_c\end{aligned}$$

Again, when compared to the **lumped element capacitor** impedance:

$$Z_c = \frac{1}{j\omega \mathcal{C}}$$

we find that results are approximately the **same** for all pass-band frequencies (i.e., when  $\omega \ll \omega_c$ ).