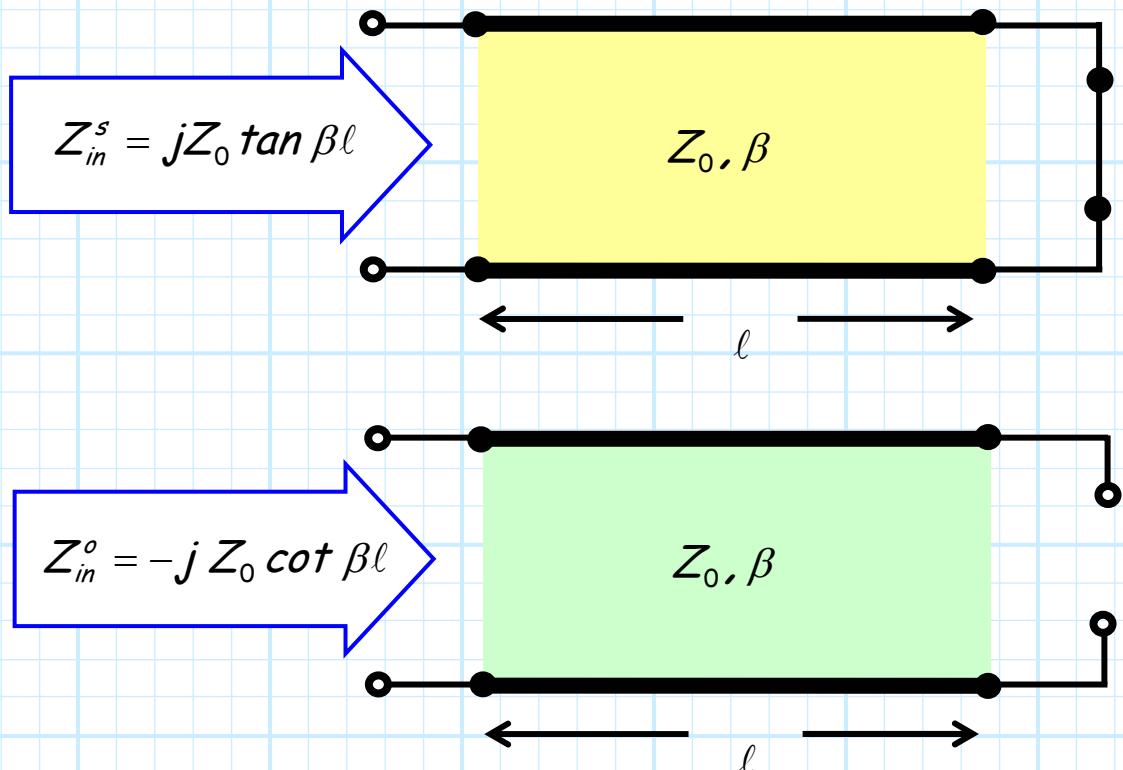



Richard's Transformations

Recall the input impedances of short-circuited and open-circuited transmission line stubs.



Note that the input impedances are purely **reactive**—just like lumped elements!

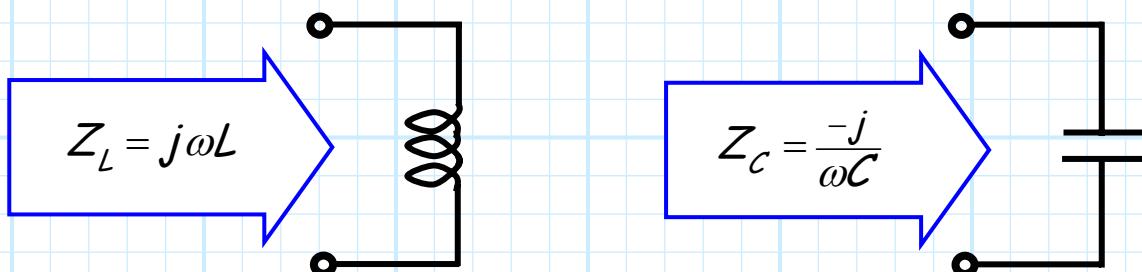However, the reactance of lumped inductors and capacitors have a **much** different mathematical form to that of transmission line stubs:



In other words, the impedance of transmission line stubs and lumped elements (capacitors and inductors) are different functions with respect to **frequency**. Therefore, we can say in general that, for example:

$$Z_{in}^s \neq Z_L$$

$$Z_{in}^o \neq Z_C$$

However, for a given lumped element (L or C) and a given stub (with a given Z_0 and length ℓ) the functions will be equal at precisely one frequency!

For example, there is one frequency—let's call it ω_c —that satisfies this equation for a given L, Z_0 , and ℓ :

$$\begin{aligned} j\omega_c L &= jZ_0 \tan \beta_c \ell \\ &= jZ_0 \tan \left[\frac{\omega_c}{V_p} \ell \right] \end{aligned}$$

or similarly satisfies this equation:

$$\begin{aligned} \frac{-j}{\omega_c C} &= -jZ_0 \cot \beta_c \ell \\ &= -jZ_0 \cot \left[\frac{\omega_c}{V_p} \ell \right] \end{aligned}$$

To make things easier, let's set the length of our transmission line stub to $\lambda_c/8$, where:

$$\lambda_c = \frac{V_p}{\omega_c} = \frac{2\pi}{\beta_c}$$

Q: Why $\ell = \lambda_c/8$?


A: Well, for one reason, $\beta_c \ell = \pi/4$ and therefore $\tan(\pi/4) = 1.0$!

This of course greatly **simplifies** our earlier results:

$$\begin{aligned} j\omega_c L &= jZ_0 \tan\left(\frac{\pi}{4}\right) \\ &= jZ_0 \end{aligned}$$


$$\begin{aligned} \frac{-j}{\omega_c C} &= -jZ_0 \cot\left(\frac{\pi}{4}\right) \\ &= -jZ_0 \end{aligned}$$

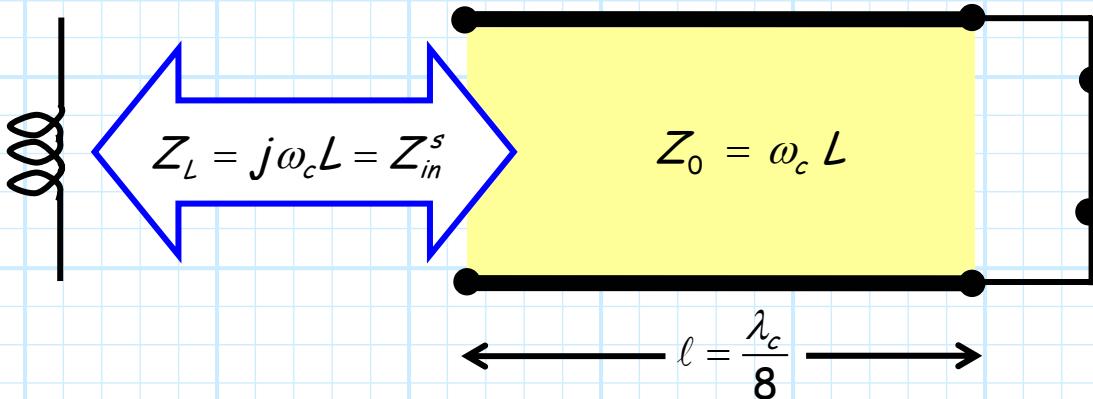Therefore, if we wish to build a **short-circuited** stub with the **same** impedance as an **inductor** L at frequency ω_c , we set the **characteristic impedance** of the stub transmission line to be $Z_0 = \omega_c L$:



Likewise, if we wish to build an **open-circuited** stub with the **same** impedance as an **capacitor** C at frequency ω_c , we set the **characteristic impedance** of the stub transmission line to be

$Z_0 = 1/\omega_c C$:

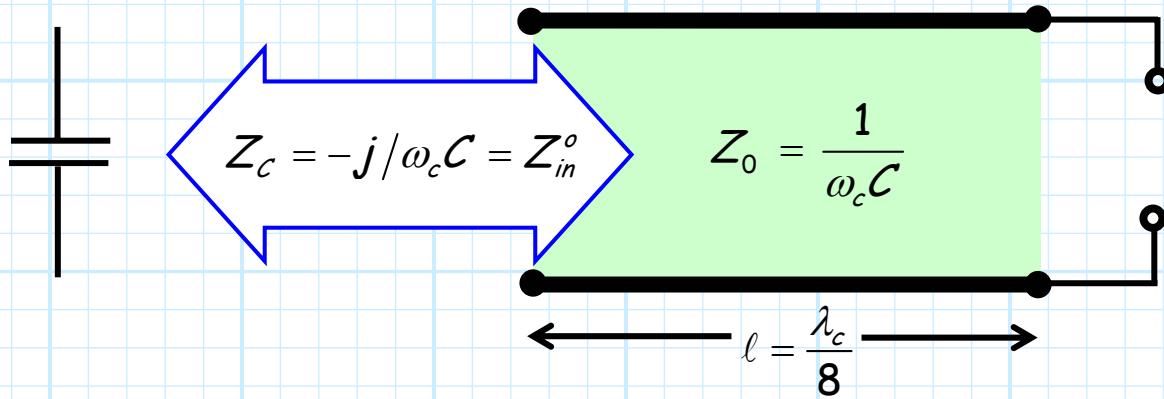

We call these two results **Richard's Transformations**.

However, it is important to remember that Richard's Transformations do **not** result in **perfect** replacements for lumped elements—the stubs **do not** behave like capacitors and inductors!

Instead, the transformation is **perfect**—the impedances are **equal**—at **only one frequency** (ω_c).

We can use Richard's transformations to replace the inductors and capacitors of a lumped element filter design. In fact, for **lowpass filter design**, the frequency ω_c is the filter's **cutoff frequency**.

Using these stubs to **replace** inductors and capacitors will result in a filter response **similar** to that of the lumped element design—a low pass filter with cutoff frequency ω_c .

However, the behavior of the filter in the stopband will be very different from the lumped element design. For example, at the (high) frequencies where the stub length becomes a multiple of $\lambda/2$, the filter response will be that of $\omega = 0$ —near perfect transmission!

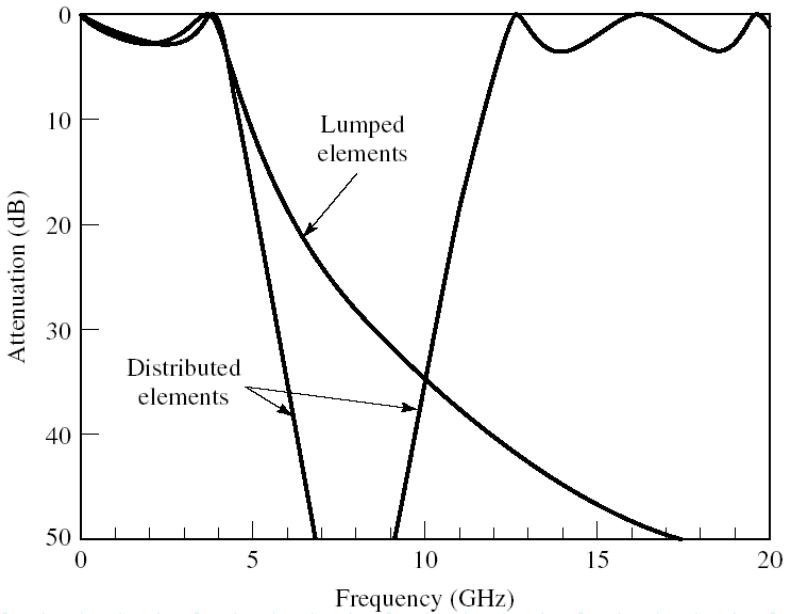


Figure 8.37 (p. 411) Amplitude responses of lumped-element and distributed-element low-pass filter of Example 8.5.

Q: So why does the filter response match the lumped element response so well in the passband?

A: To see why, we first note that the Taylor Series approximation for $\tan \phi$ and $\cot \phi$ when ϕ is small (i.e., $\phi \ll 1$) is:

$$\tan \phi \approx \phi \quad \text{and} \quad \cot \phi \approx \frac{1}{\phi} \quad \text{for} \quad \phi \ll 1$$

and ϕ is expressed in radians.

The **impedance** of our Richard's transformation shorted stub at some **arbitrary frequency** ω is:

$$\begin{aligned} Z_{in}^s(\omega) &= jZ_0 \tan\left(\beta \frac{\lambda_c}{8}\right) \\ &= j(\omega_c L) \tan\left(\frac{\omega}{v_p} \frac{\lambda_c}{8}\right) \\ &= j(\omega_c L) \tan\left(\frac{\omega}{\omega_c} \frac{\pi}{4}\right) \end{aligned}$$

Therefore, when $\omega \ll \omega_c$ (i.e., frequencies in the **passband** of a low-pass filter!), we can **approximate** this impedance as:

$$\begin{aligned} Z_{in}^s(\omega) &= j(\omega_c L) \tan\left(\frac{\omega}{\omega_c} \frac{\pi}{4}\right) \\ &\approx j\omega_c L \left(\frac{\omega}{\omega_c} \frac{\pi}{4}\right) \\ &= j\omega L \left(\frac{\pi}{4}\right) \quad \text{when } \omega \ll \omega_c \end{aligned}$$

Compare this to a **lumped inductor** impedance:

$$Z_L = j\omega L$$

Since the value $\pi/4$ is **relatively close** to one, we find that the Richard's Transformation shorted stub has an input impedance **very close** to the lumped element inductor for **all frequencies less than ω_c** (i.e., all frequencies of the low-pass filter passband)!

Similarly, we find that the Richard's transformation open-circuit stub has an input impedance of approximately:

$$\begin{aligned}
 Z_{in}^o(\omega) &= \frac{-j}{\omega_c C} \cot\left(\frac{\omega}{\omega_c} \frac{\pi}{4}\right) \\
 &\approx \frac{-j}{\omega_c C} \left(\frac{\omega_c}{\omega} \frac{4}{\pi} \right) \\
 &= \frac{1}{j\omega C} \left(\frac{4}{\pi} \right) \quad \text{when } \omega \ll \omega_c
 \end{aligned}$$

Again, when compared to the lumped element capacitor impedance:

$$Z_C = \frac{1}{j\omega C}$$

we find that results are approximately the same for all pass-band frequencies (i.e., when $\omega \ll \omega_c$).