

Special Problem 5.4-1

A **matching network** has been constructed to match a **complex** load to a transmission line with characteristic impedance $Z_0 = 50 \Omega$.


The **design frequency** of this matching network is $f_0 = 10 \text{ MHz}$.

Note that this matching network is **not** specifically one of the standard designs that we studied.

The **capacitor** has a capacitance of value:


$$C = \frac{10^{-9}}{2\pi} \text{ farads}$$

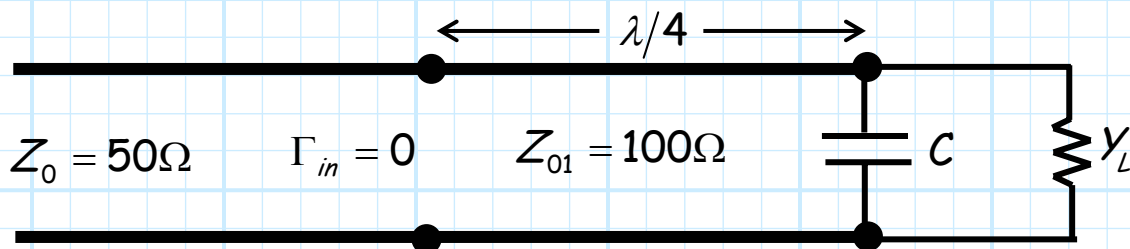Determine the **complex admittance** Y_L of the load.



Solution

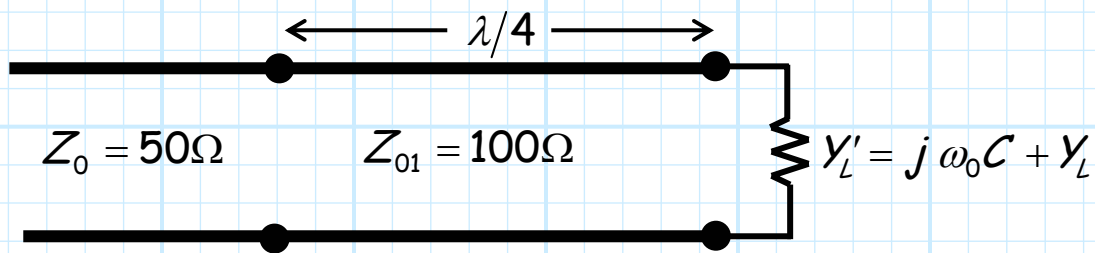First, combine the capacitor and Y_L to form an new load with admittance Y'_L :



where:

$$\begin{aligned} Y'_L &= j\omega_0 C + Y_L \\ &= j2\pi(10^7) \left(\frac{10^{-9}}{2\pi} \right) + Y_L \\ &= j0.01 + Y_L \end{aligned}$$

Now, in order for $\Gamma_{in} = 0$, we know that (because of the $\lambda/4$ transformer):

$$Z'_L = \frac{Z_{01}^2}{Z_0} \quad \Rightarrow \quad Y'_L = \frac{Z_0}{Z_{01}^2}$$

And so if matched:

$$Y'_L = \frac{Z_0}{Z_{01}^2} = \frac{50}{(100)^2} = 0.005$$

Therefore:

$$Y'_L = 0.005 = j0.01 + Y_L \quad \Rightarrow \quad \underline{\underline{Y_L = 0.005 - j0.01}}$$