
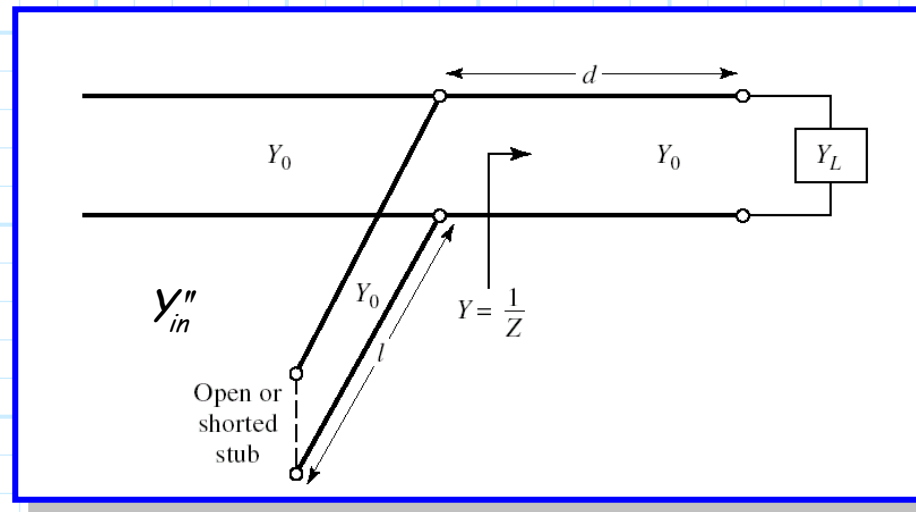


Shunt Stub Tuning

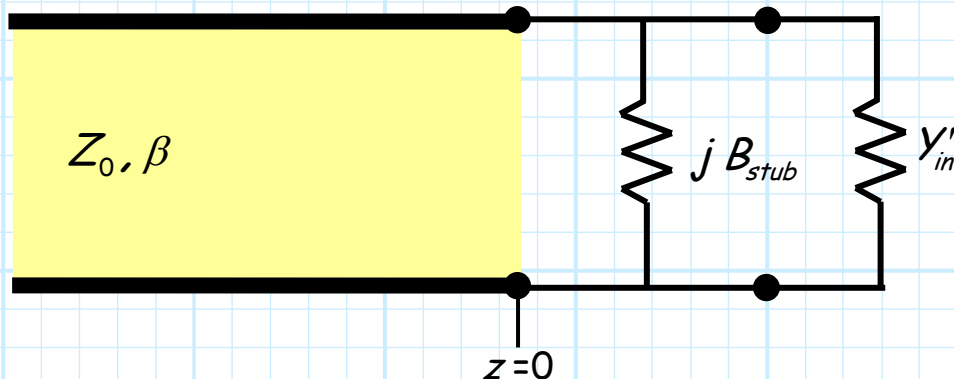Consider the follow transmission line structure, with a **shunt stub**:



The two **design parameters** of this matching network are lengths l and d . An equivalent circuit is:



where:

$$y''_{in} = Y_0 \left(\frac{Y_L + j Y_0 \tan \beta d}{Y_0 + j Y_L \tan \beta d} \right)$$

The reactance jB_{stub} of transmission line **stub** of length l is either:

$$jB_{stub} = \begin{cases} jY_0 \tan \beta l & \text{for an open-circuit stub} \\ -jY_0 \cot \beta l & \text{for an short-circuit stub} \end{cases}$$

Therefore, for a **matched circuit**, we require:

$$jB_{stub} + Y_{in}'' = Y_0$$

Note this complex equation is actually **two real equations!**

i.e.,

$$\text{Re}\{Y_{in}''\} = Y_0$$

and

$$\text{Im}\{jB_{stub} + Y_{in}''\} = 0 \quad \Rightarrow \quad B_{stub} = -B_{in}''$$

where

$$B_{in}'' \doteq \text{Im}\{Y_{in}''\}$$

Since Y_{in}'' is dependent on d only, our **design procedure** is:

- 1) Set d such that $\text{Re}\{Y_{in}''\} = Y_0$.
- 2) Then set ℓ such that $B_{stub} = -B_{in}''$.

We have **two choices** for determining the lengths d and ℓ . We can use the design equations (5.9, 5.10, 5.11) on p. 232,


OR

we can use the **Smith Chart** to determine the lengths!

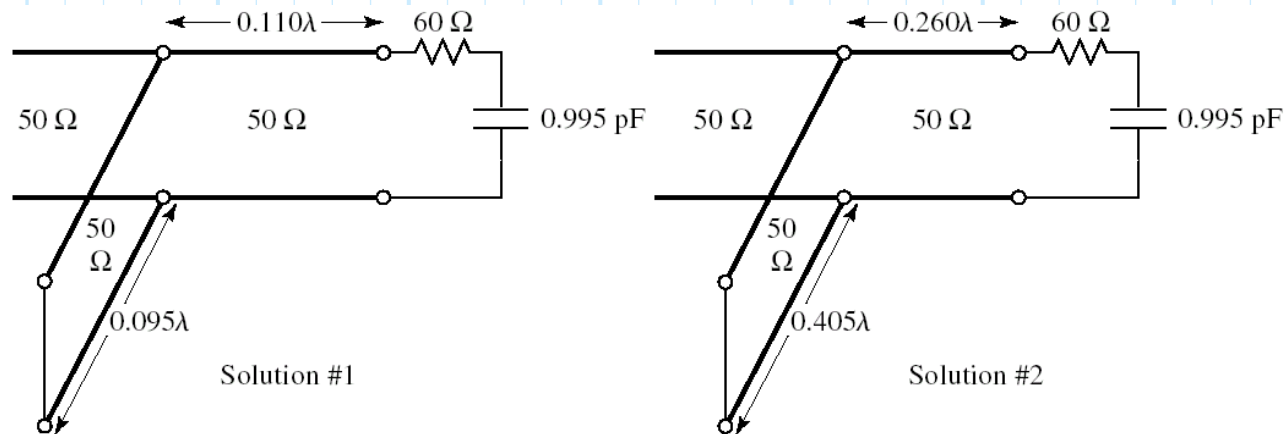
- 1) Rotate **clockwise** around the Smith Chart from y_L until you intersect the **$g = 1$ circle**. The "length" of this rotation determines the value d . Recall there are **two** possible solutions!
- 2) Rotate **clockwise** from the short/open circuit point around the **$g = 0$ circle**, until b_{stub} equals $-b_{in}''$. The "length" of this rotation determines the stub length ℓ .

For example, your **book** describes the case where we want to match a load of $Z_L = 60 - j80$ (at 2 GHz) to a transmission line of $Z_0 = 50\Omega$.

Using **shorted** stubs, we find **two** solutions to this problem:



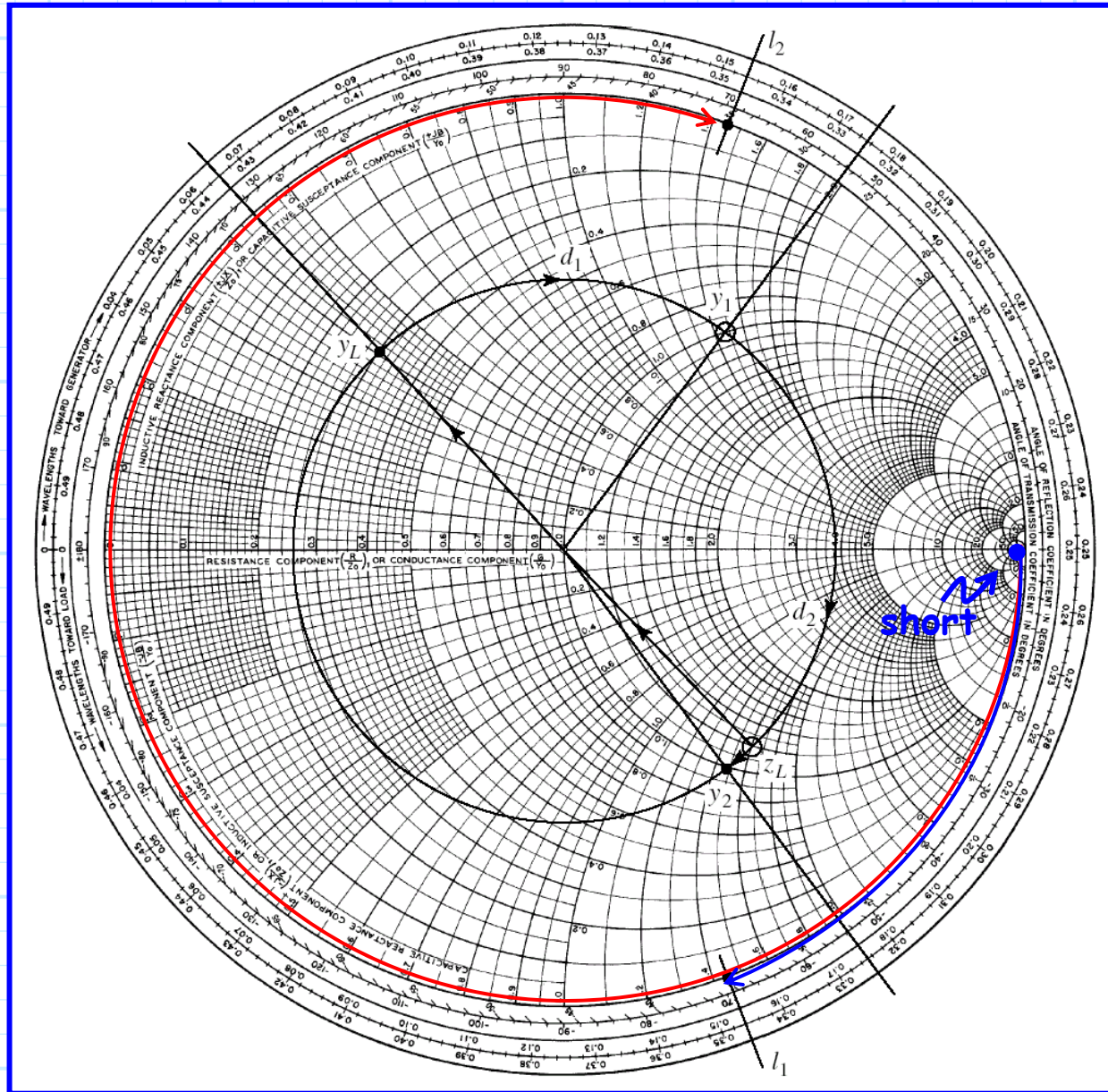Whose length values d and ℓ were determined from a Smith Chart:




Q: *Two solutions! Which one do we use?*

A: The one with the **shortest** lengths of transmission line!

Q: *Oh, I see! Shorter transmission lines provide **smaller** and (slightly) cheaper matching networks.*

A: True! But there is a more **fundamental** reason why we select the solution with the **shortest** lines—the matching **bandwidth** is **larger**!

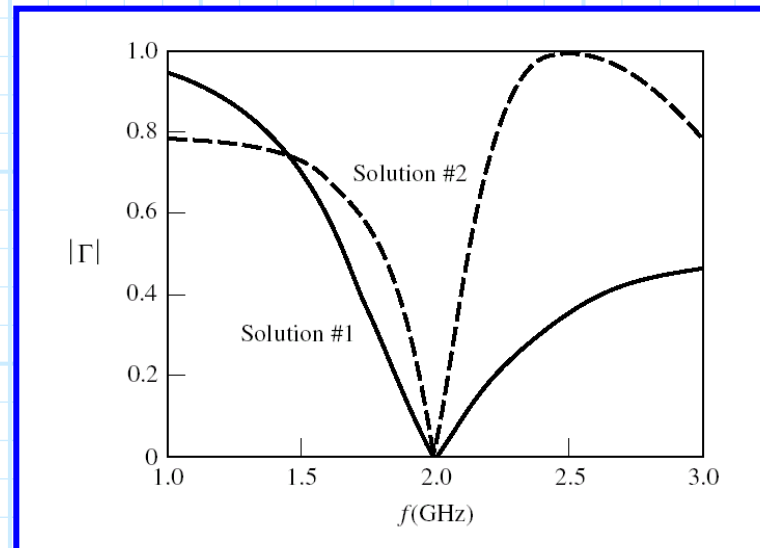For example, consider the **frequency response** of the two examples:



Clearly, solution 1 provides a **wider** bandwidth!