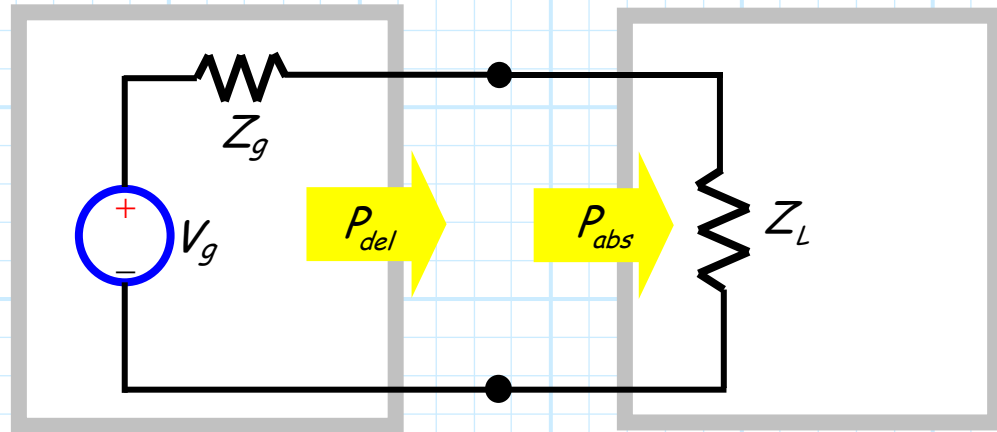


# Special Cases of Source and Load Impedance

Consider again the power **absorbed** by the load (delivered by the source):

$$P_{del} = P_{abs} = \frac{|V_g|^2}{2} \frac{R_L}{|Z_g + Z_L|^2}$$



It is evident that this power transfer is dependent on **each** and **every** element of the equivalent circuit—the **source parameters**  $V_g$  and  $Z_g$ , as well as the **load impedance**  $Z_L$ .


**Q:** *I assume that we want to maximize this power transfer. How can we maximize  $P_{abs}$ ??*

**A:** The answer to that question is among the best known in electrical engineering. Unfortunately, it is also frequently misunderstood and misapplied—**so pay attention!**

# Match the Load to the Source

First, let's ask **this** question:

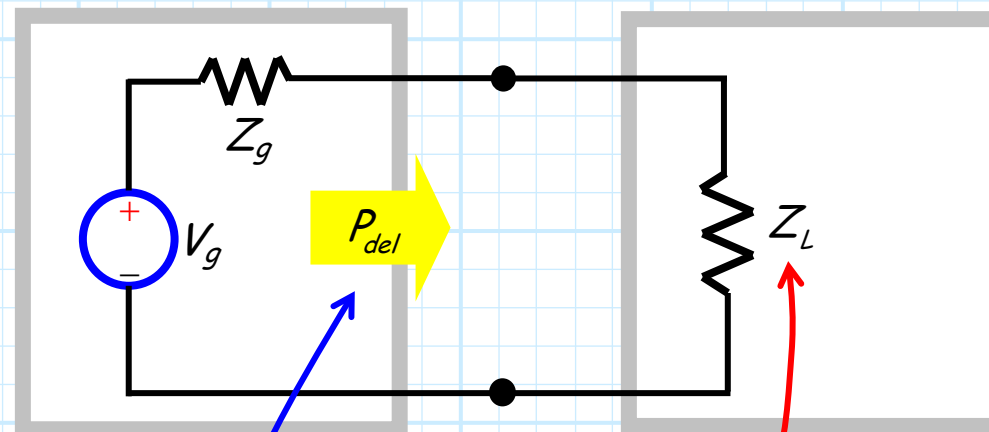**Q1:** What load impedance  $Z_L$  will maximize the power delivered by the source (i.e., maximize  $P_{del}$ )?



What value of this ...

...will maximize this?

**A1:** The load impedance  $Z_L = Z_g^*$  will maximize the power delivered by the source.

## The Available Power of the Source

We can likewise determine what the **value** of this maximum power is. For  $Z_L = Z_g^*$ , we find:

$$P_{del}|_{Z_L=Z_g^*} = \frac{|V_g|^2}{2} \frac{R_g}{|Z_g + Z_g^*|^2} = \frac{|V_g|^2}{2} \frac{R_g}{|2R_g|^2} = \frac{|V_g|^2}{8R_g}$$

This maximum delivered power is **very important** and is dubbed the **available power**  $P_{avl}$  of the **source**:

$$P_{avl} = \frac{|V_g|^2}{8R_g}$$

Note the available power is dependent **just on source parameters** (i.e.,  $V_g$  and  $R_g$ ), and so  $P_{avl}$  is a parameter of the **source only**.


This available power is the **most** that can be **delivered** by the source (i.e.,  $P_{del} \leq P_{avl}$ ), and this available source power can **only** be delivered if a load  $Z_L = Z_g^*$  is connected:

$$P_{del} = P_{avl} = \frac{|V_g|^2}{8R_g} = \quad \text{iff} \quad Z_L = Z_g^*$$

# A Completely Different Question!

Now, let's ask **completely different** question:

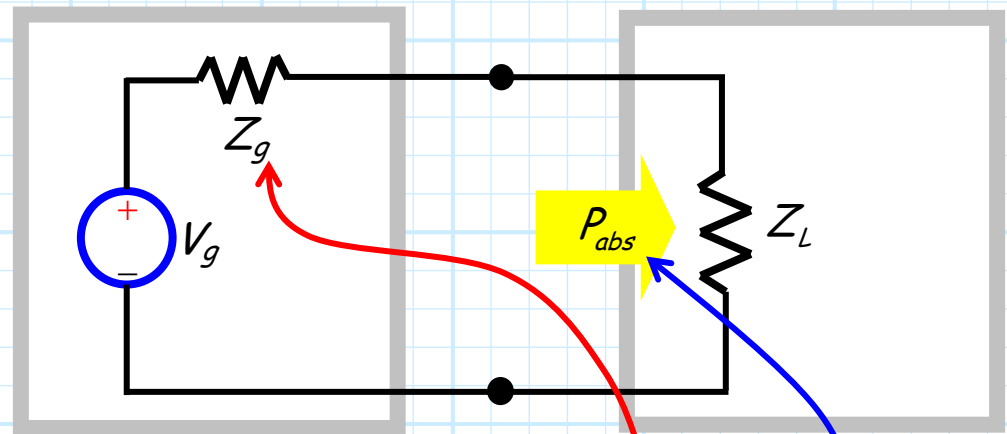**Q2:** What source impedance  $Z_g$  will maximize the power absorbed by the load (i.e., maximize  $P_{abs}$ )?



What value of this ...

...will maximize this?



Like, we already know the answer. Absorbed power is maximized by a conjugate match:

$$Z_g = Z_L^*. \text{ Gosh!}$$

# NOT!

**Not so fast!** It can be shown that the value of  $Z_g$  that **maximizes** the absorbed power:

$$P_{abs} = \frac{|V_g|^2}{2} \frac{R_L}{|Z_g + Z_L|^2}$$

is:

$$Z_g = -jX_L$$

where  $X_L$  is the imaginary (i.e., reactive portion of the load ( $X_L = \text{Im}\{Z_L\}$ )).

Thus, we conclude:

**Q2:** *What source impedance  $Z_g$  will maximize the power absorbed by the load (i.e., maximize  $P_{abs}$ )?*

**A2:** The **source** impedance  $Z_g = -jX_L$  will maximize the power absorbed by the **load** (i.e., maximize  $P_{abs}$ ).

## Don't Make This Mistake!

Although it is **very** common for electrical engineers to incorrectly assume the answer to question **Q2** is the answer to **Q1** (i.e.,  $Z_g = Z_L^*$ ), and this is **far** from the correct answer!

Using the **correct** solution  $Z_g = -jX_L$ , we find:

$$P_{abs}|_{Z_g = -jX_L} = \frac{|V_g|^2}{2} \frac{R_L}{|Z_g + Z_L|^2} = \frac{|V_g|^2}{2 R_L}$$

Whereas if we enforce a "conjugate match"  $Z_g = Z_L^*$  the load instead absorbs:

$$P_{abs}|_{Z_g = Z_L^*} = \frac{|V_g|^2}{2} \frac{R_L}{|Z_L^* + Z_L|^2} = \frac{1}{4} \left( \frac{|V_g|^2}{2 R_L} \right)$$

The power absorbed by the load when  $Z_g = Z_L^*$  is just **25%** of the power absorbed if  $Z_g = -jX_L$ !

## Dazed and Confused

**Q:** *But if  $Z_L$  is not equal to  $Z_g^*$  ( $Z_L \neq Z_g^*$ ) isn't the absorbed power less than the available power ??*

**A:** You bet!

If  $Z_g = -jX_L$ , the absorbed power is **far less** than the **available power**.

**Q:** *I'm so confused!*

*I thought you said that setting  $Z_g = -jX_L$  maximized the absorbed power??*

**A:** See the next page!

## $Z_L$ cannot alter available power— but $Z_g$ sure the heck can!

**A:** Here's the deal; altering the value of **load** impedance  $Z_L$  changes the delivered power  $P_{del}$  but does not alter the available power  $P_{avl}$  of the source.

The best we can do is set  $Z_L$  such that **all available power** is delivered to the load (i.e., set  $Z_L = Z_g^*$ ).

Contrast this with altering the value of **source** impedance  $Z_g$ . Changing  $Z_g$  **will** alter the **available power**  $P_{avl}$  of the source!

Recall:

$$P_{avl} = \frac{|V_g|^2}{8R_g}$$

The ideal source impedance ( $Z_g = -jX_L$ ) is purely reactive, so  $R_g = 0$ —the available power is therefore **infinite!**

Of course, achieving infinite available power is **not practical**—available power  $P_{avl}$  of any **realizable** source is finite.



## Don't ever do this!

Still, engineers attempting to **maximize** the power absorbed by a load should:

1. Attempt to select/design/alter the **source** such that its **available power**  $P_{avl}$  is **maximized**.
2. Attach a **load** that is conjugate matched ( $Z_L = Z_g^*$ ) to this source, such that **all available power is delivered** to the load.

A problem that often arises is a source with a **large available power** has a very **low source impedance**, such that it is **difficult/impractical** to provide a load where  $Z_L = Z_g^*$ .

Engineers sometimes alter/design/select **another source** that it **easier** to "match", but usually this results in a dramatic **decrease in available power!**

## See what I mean?

For **example**, consider two cases:

Source	Available Power	Delivered Power
1	500 mW	200mW
2	100 mW	100 mW

For **which** source is "power transfer maximized"?

For source 2, **100%** of the **available power** is delivered to the load—clearly the **load is matched** to the source impedance.

For source 1, **only 40%** of the available power is delivered to the load—the load is most definitely **not matched** to source impedance.

Yet, the **mismatched load** absorbs **twice** the power of the mismatched case.

It does so because the available power of source 1 is **five times** larger than that of source 2.

→ It's better to have **most of alot** than **all of very little!!**

## Be careful!

Hence, we need to be **careful** when considering a conjugate match (e.g., what does “maximum power transfer” **really** mean?).

- Selecting/altering the **load to match a source** is a **good** idea, but selecting/altering the **source to match a load** is typically **not**.

This question has—and continues to—spark many **arguments** among electrical engineers!!

