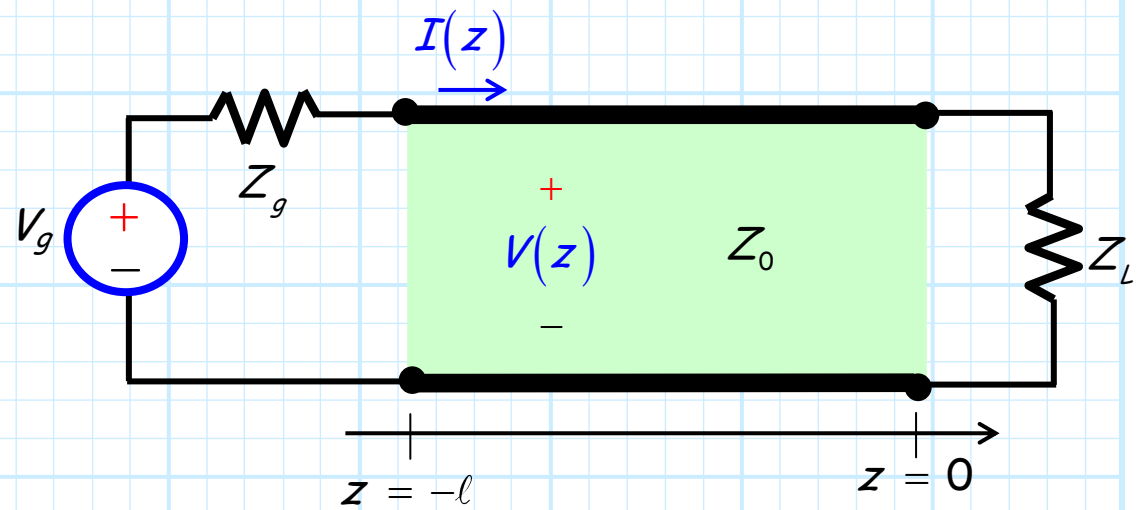


Special Cases of Source and Load Impedance

Let's look at specific cases of:

1. Z_g
2. and Z_L ,




and then determine how they affect:

1. V_0^+
2. and P_{abs} .

The first special case: the matched load

$$Z_L = Z_0 + j0$$

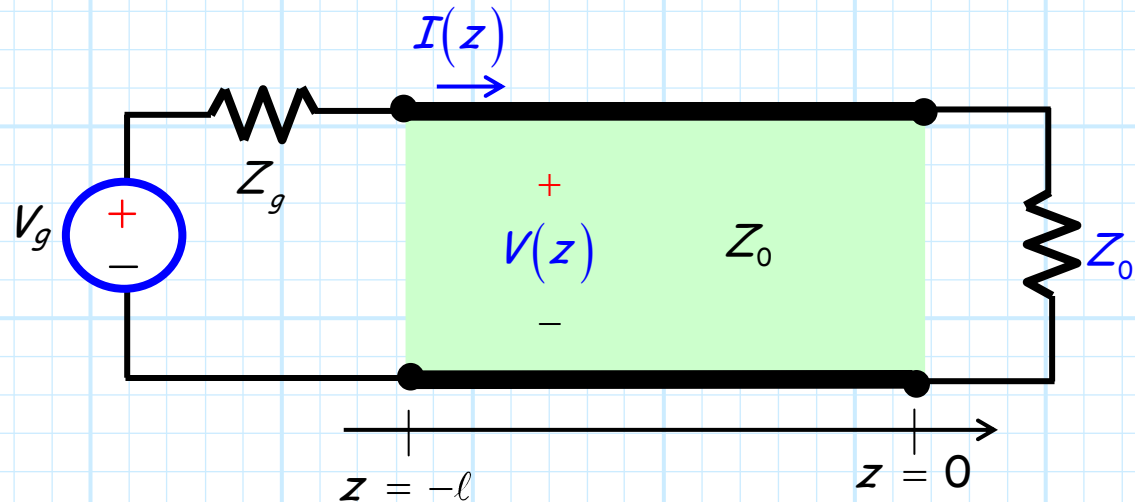

Of course for this case—where the load is “**matched**” to the transmission line—we find that $\Gamma_L = 0$ and thus $\Gamma_{in} = 0$.

As a result, the complex amplitude of the plus-wave **simplifies** to:

$$\begin{aligned} V_0^+ &= V_g e^{-j\beta l} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})} \\ &= V_g e^{-j\beta l} \frac{Z_0}{Z_0 + Z_g} \end{aligned}$$

The absorbed power is just the incident power

Likewise, the absorbed/delivered power is simply that of the **incident** wave:

$$P_{abs} = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_L|^2) = \frac{|V_0^+|^2}{2Z_0}$$

as the **matched** condition causes the reflected power to be **zero** ($P^- = 0$)!

Now, recognizing that the **input impedance** of the transmission line for this case will likewise be $Z_{in} = Z_0$, we can **alternatively** express the **absorbed power** (without determining V_0^+ !):

$$P_{abs} = \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \operatorname{Re}\{Z_{in}\} = \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_0|^2} Z_0 = \frac{|V_g|^2}{2} \frac{Z_0}{|Z_g + Z_0|^2}$$

The 2nd special case: the conjugate match

$$Z_{in} = Z_g^*$$

For this case, we find the load Z_L takes on **whatever** value required to make $Z_{in} = Z_g^*$.

→ The input impedance is a **conjugate match** to the source impedance.


This is of course is a **very** important case!

First, using the fact that:

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z_g^* - Z_0}{Z_g^* + Z_0}$$

We can show that (trust me!) that the plus-wave amplitude **simplifies** to:
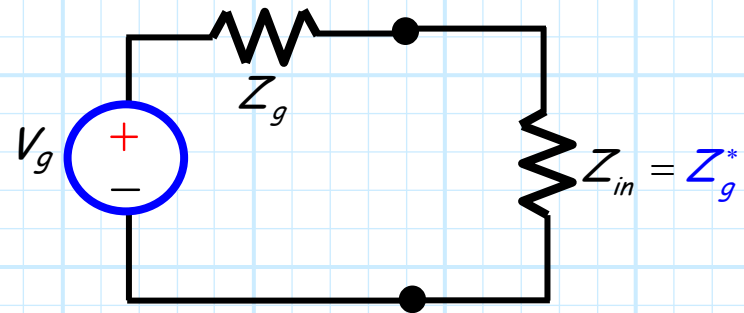
$$V_0^+ = V_g e^{-j\beta l} \frac{Z_g^* + Z_0}{4\text{Re}\{Z_g\}}$$



Yawn: the load absorbs the available power

Not a particularly interesting result, but now let's look at the absorbed power.

$$\begin{aligned}
 P_{abs} &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \operatorname{Re}\{Z_{in}\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_g^*|^2} \operatorname{Re}\{Z_g^*\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|2\operatorname{Re}\{Z_g^*\}|^2} \operatorname{Re}\{Z_g^*\} \\
 &= \frac{1}{2} |V_g|^2 \frac{1}{4\operatorname{Re}\{Z_g^*\}} \\
 &= \frac{|V_g|^2}{8R_g} = P_{avl}
 \end{aligned}$$

The absorbed power is **of course** the **available power** of the source.

Since the input impedance is a **conjugate match** to the source, the source is delivering energy at the **highest rate** it possibly can!

But, the load still reflects power!

Q: *But if the power **delivered** is at a maximum, so too is the power **absorbed** by the load. I.E.:*

$$P_{abs} = P_{del} = P_{avl}$$

*If the power absorbed from the load is at a **maximum**, then the power **reflected** from the load must be at a **minimum**.*

*The load must be absorbing **all** the incident power; **right?***

A: You might think so—and many engineers in fact **do** think so.


→ But those engineers are **incorrect!**

To see why, consider the load Z_L that **minimizes** the reflected power.


We know this load **must** have one specific value—the **matched** load $Z_L = Z_0$.

If the load is Z_0 then so is Z_{in}

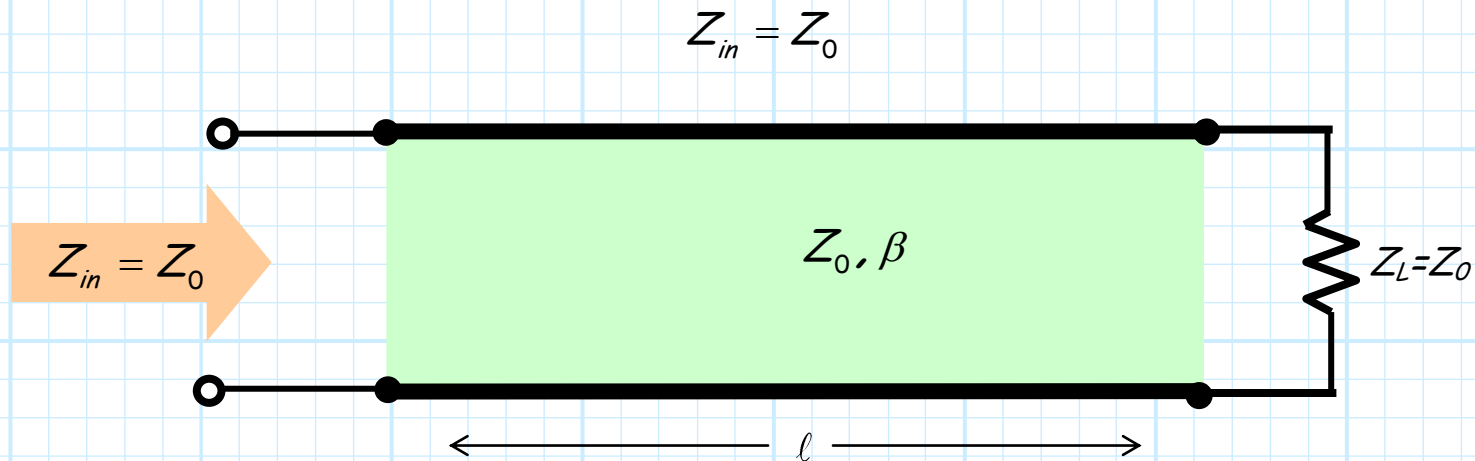But, **if** the load is matched to the transmission line (i.e., $Z_L = Z_0$, then the **input** impedance will likewise be equal to Z_0 :



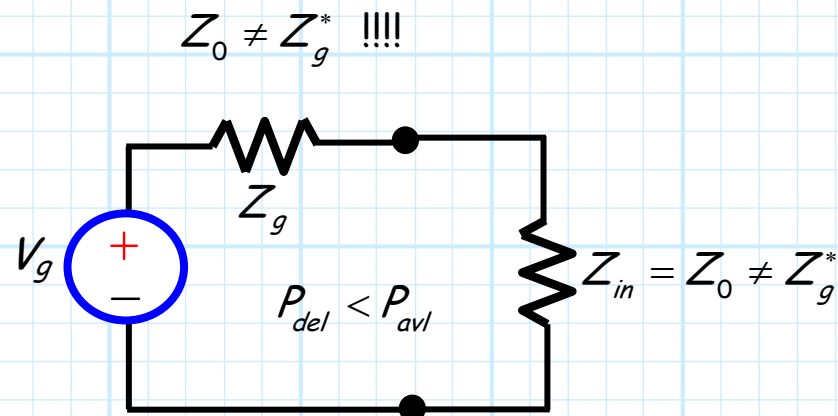And, **generally** speaking, an input impedance of $Z_{in} = Z_0$ will **not** be equal to the complex conjugate of the source impedance:



Look closer at this result

Recall that we **just** determined that for $Z_L = Z_0$, the absorbed power is:

$$P_{abs} = \frac{|V_g|^2}{2} \frac{Z_0}{|Z_0 + Z_g|^2}$$

It can be shown that this value is **less** than the available power of the source:

$$\frac{|V_g|^2}{2} \frac{Z_0}{|Z_0 + Z_g|^2} \leq \frac{|V_g|^2}{8 R_g} = P_{avl}$$

Q: *Huh!? This makes no sense!*

After all, just look at the expression for absorbed power:


$$P_{abs} = \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2)$$

Clearly, this value is maximized when $\Gamma_L = 0$ (i.e., when $Z_L = Z_0$)!!!

Remember, the load affects V^+


A: Let's look closer at this result:

$$P_{abs} = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_L|^2)$$

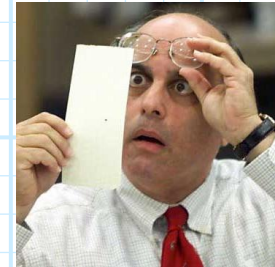

Remember, we can rewrite this to show that the **absorbed** power is simply the **difference** between the power of the **incident** and **reflected** waves:

$$P_{abs} = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_L|^2) = \frac{|V_0^+|^2}{2Z_0} - \frac{|V_0^+ \Gamma_L|^2}{2Z_0} = \frac{|V_0^+|^2}{2Z_0} - \frac{|V_0^-|^2}{2Z_0} = P^+ - P^-$$

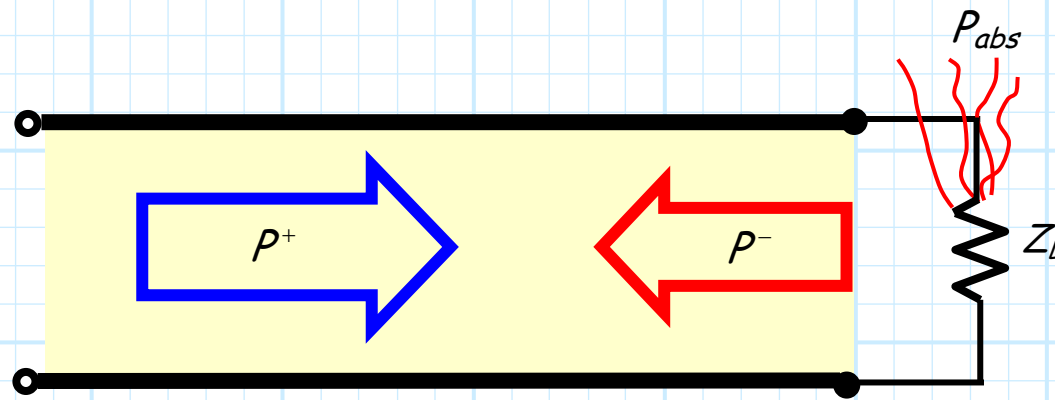

Absorbed power is maximized if the difference between incident and reflected is maximized!


Of course, it is true that the load impedance Z_L affects the **minus-wave** amplitude V_0^- , and thus affects likewise the **reflected** wave power P^- .

Remember however, that the value of Z_L **likewise** affects the **plus-wave** amplitude V_0^+ , and thus affects likewise the **incident** wave power P^+ !

- * Thus, the value of Z_L that minimizes P^- will **not** generally maximize P^+ !
- * **Likewise** the value of Z_L that maximizes P^+ will **not** generally minimize P^- .
- * Instead, the value of Z_L that maximizes the **absorbed** power P_{abs} is, by definition, the value that **maximizes** the **difference** $P^+ - P^-$.

We find that this **ideal** impedance Z_L is the value that results in the **ideal** case of $Z_{in} = Z_g^*$!

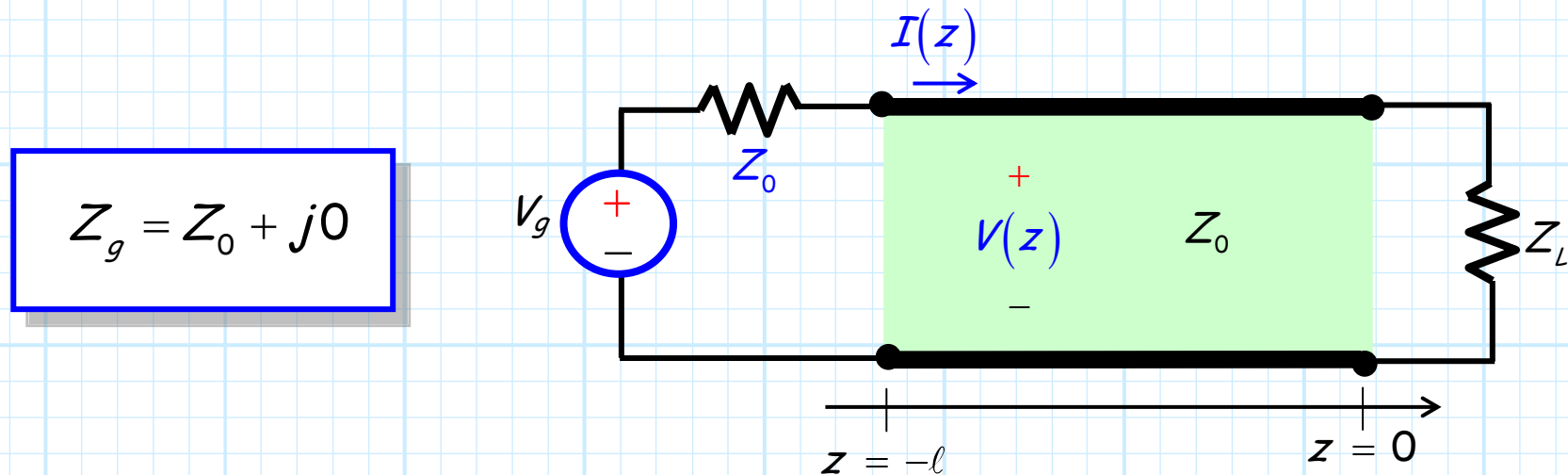The third special case: the matched source



For this case, we find that V_0^+ **simplifies** greatly:

$$\begin{aligned}
 V_0^+ &= V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})} \\
 &= V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_0(1 - \Gamma_{in})} \\
 &= V_g e^{-j\beta\ell} \frac{1}{1 + \Gamma_{in} + 1 - \Gamma_{in}} \\
 &= \frac{1}{2} V_g e^{-j\beta\ell}
 \end{aligned}$$

Look at what **this** says!

This is the answer—regardless of the load!

It says that the incident wave in this case is **independent** of the load attached at the other end (the value Γ_{in} is nowhere to be found)!

Thus, for the **one** case $Z_g = Z_0$, we in fact **can** consider $V^+(z)$ as being the **source wave**.

And then the reflected wave $V^-(z)$ is the **causal result** of this stimulus.

Specifically, for this case we can write **directly** the plus-wave—without knowing **anything** about the load Z_L :

$$V^+(z) = V_0^+ e^{-j\beta z} = \left(\frac{1}{2} V_g e^{-j\beta \ell} \right) e^{-j\beta z} = \frac{V_g}{2} e^{-j\beta(z+\ell)}$$

This blue box equation will
come in quite handy!

Therefore, the value at the **load** (i.e., $z = 0$) is:

$$V^+(z = 0) = \frac{V_g}{2} e^{-j\beta\ell}$$

And the value of the **plus-wave** at the **source** (i.e., $z = -\ell$) is:

$$V^+(z = -\ell) = \frac{V_g}{2}$$

This last result is **very** important.

Remember this result, it will come in **quite handy** later in the course!

All I can say is: wow!

Now consider another **really** important result.

Recall the power associated with the plus-wave is:

$$P^+ = \frac{|V_0^+|^2}{2 Z_0}$$

Inserting the **simplified** expression for V_0^+ (i.e., when $Z_g = Z_0$):

$$P^+ = \frac{|V_0^+|^2}{2 Z_0} = \frac{|V_g e^{-j\beta l}|^2}{8 Z_0} = \frac{|V_g|^2}{8 Z_0} \quad \leftarrow \text{Wow!}$$

Q: *I don't see why this is "wow". Am I missing something?*

A: Apparently you are. Look **closer** at the above result.

Do I have to explain everything?

Remember, this result is for the **special case** where the source impedance is a **real value**, numerically equal to Z_0 :

$$Z_g = Z_0 + j0$$

Therefore:

$$R_g = \text{Re}\{Z_g\} = Z_0$$

The **source** resistance is **numerically equal** to transmission line characteristic impedance Z_0 .

Thus, the **power** of the plus-wave can be alternatively written as:

$$P^+ = \frac{|V_g|^2}{8Z_0} = \frac{|V_g|^2}{8R_g} \quad \leftarrow \text{Wow!}$$

Q: *This result looks vaguely familiar; haven't we seen this before?*

A: Sigh. This result is the **available power of the source**!!!!!!

The incident power is the available power (wow)!

Therefore:

$$P^+ = \frac{|V_g|^2}{8Z_0} = \frac{|V_g|^2}{8R_g} = P_{avl} \quad \leftarrow \text{Wow!}$$


For the special case $Z_g = Z_0 + j0$, the power P^+ associated with the plus-wave (i.e., the **incident** wave) is **equal** to the **available** power P_{avl} of the **source**.

Q: *Wow! Does this mean that the power **absorbed** by the load is **equal** to the **available** power P_{avl} of the source?*

A: **Absolutely not!**

But some of this incident power is reflected (Doh!)

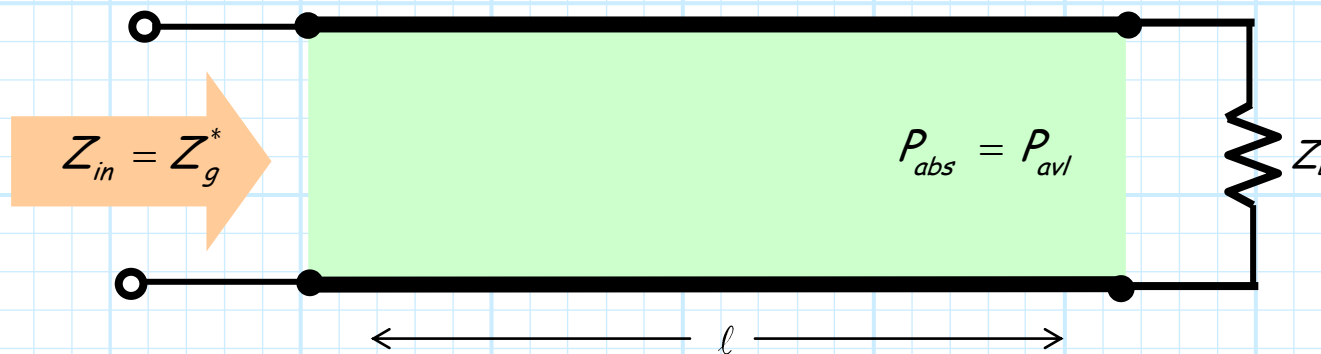Remember, **only** if $Z_{in} = Z_g^*$ does the power absorbed by the load **equal** the **available** power.




- * Making $Z_g = Z_0 + j0$ causes the power of the **incident** wave to be equal to the **available** power.
- * But, the value Z_L of the **load impedance** determines how much of that incident power is absorbed—and how much gets **reflected**.

The really special case!

Q: Hey, that's right!

If the load is matched (i.e., $Z_L = Z_0 + j0$), then wouldn't **none** of the incident power be **reflected** (i.e., $P^- = 0$).

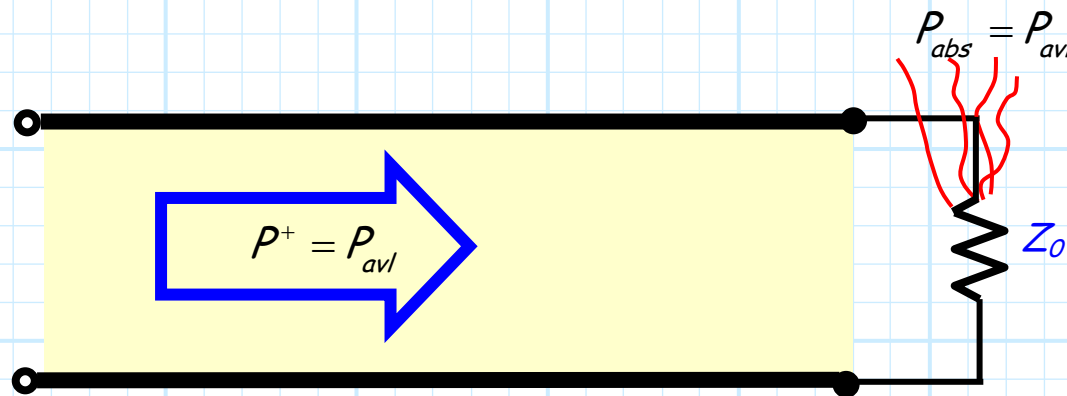And so wouldn't **all** the incident (i.e., available!) power be **absorbed** by the load?



A: That's exactly correct!


Q: But you said earlier that **minimizing** the reflected power would **not** result in **maximizing** the absorbed power. Aren't you contradicting yourself?

A: Not at all.

A conjugate match!

Generally speaking, minimizing the reflected power (i.e., $Z_L = Z_0$) will not result in maximizing the absorbed power.

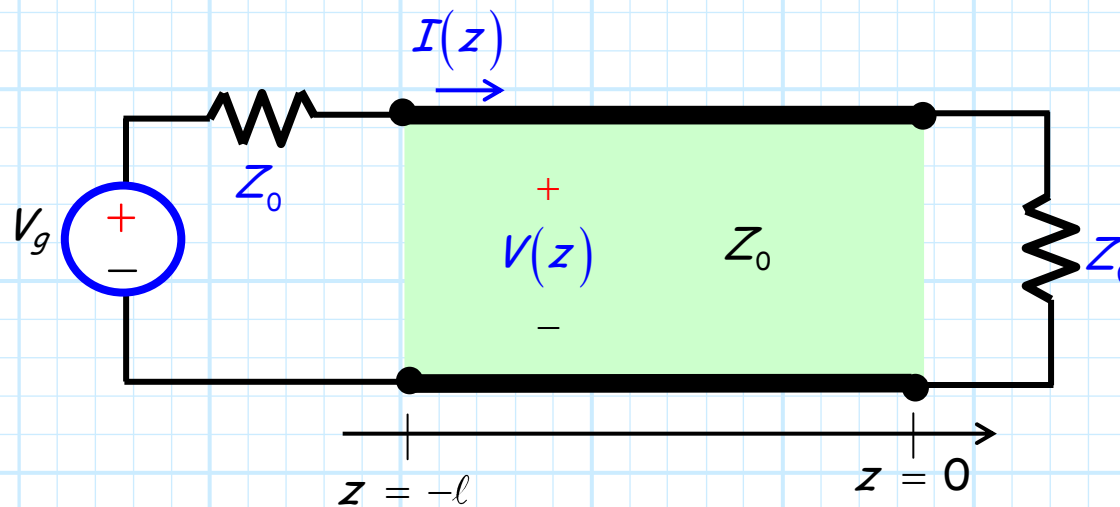However, we are considering the special case where also $Z_g = Z_0!$



Thus, maximum power transfer will occur if there is a conjugate match $Z_{in} = Z_g^*$.

Note for this special case $Z_g^* = Z_0$, meaning that input impedance Z_{in} must be equal to Z_0 for maximum power delivery.


Of course, the input impedance Z_{in} will be equal to Z_0 when the load impedance is matched (i.e., $Z_L = Z_0$)!

"Zee-zeros" everywhere

Thus, in many ways, the case:

$$Z_g = Z_0 = Z_L$$

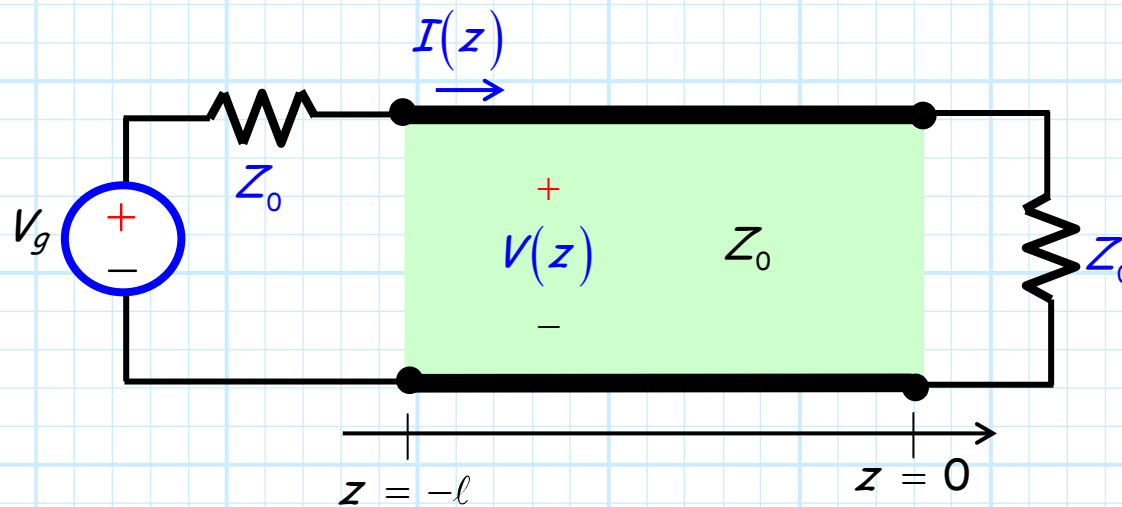(i.e., **both** source and load impedances are numerically equal to Z_0) is **ideal**.



Let's summarize this "ideal case":

- * A **conjugate match** occurs ($Z_{in} = Z_g^*$), and so **all the available power** from the source is **absorbed** by the load:

$$P_{del} = P_{avl} = P_{abs}$$

It's just so simple; you hardly deserve credit for this class

- * The **incident** (plus) wave is **independent** of the load impedance:

$$V^+(z) = \frac{V_g}{2} e^{-j\beta(z+\ell)} \quad V^+(z=0) = \frac{V_g}{2} e^{-j\beta\ell} \quad V^+(z=-\ell) = \frac{V_g}{2}$$

- * And the **power** associated with this **incident** wave is **equal** to the **available power** of the source:

$$P^+ = \frac{|V_g|^2}{8 Z_0} = P_{avl}$$

- * The **reflected** (minus) wave is **zero**:

$$V^-(z) = 0$$

- * So of course, the **power** associated with the reflected wave is likewise **zero**.

$$P^- = 0$$

Load AND source is matched— it's a very good thing

- * This **again** allows us to verify that **all available power** is absorbed by the **load**:

$$P_{abs} = P^+ - P^- = P_{avl} - 0 = P_{avl}$$

- * Finally, the **total current and voltage simplifies nicely**:

$$V(z) = V^+(z) + V^-(z) = \frac{V_g}{2} e^{-j\beta(z+\ell)}$$

$$I(z) = \frac{V^+(z) - V^-(z)}{Z_0} = \frac{V_g}{2Z_0} e^{-j\beta(z+\ell)}$$

