

Special Values of Load Impedance

It's interesting to note that the load Z_L enforces a boundary condition that explicitly determines **neither** $V(z)$ nor $I(z)$ —but **completely specifies line impedance** $Z(z)$!


$$Z(z) = Z_0 \frac{e^{-j\beta z} + \Gamma_L e^{+j\beta z}}{e^{-j\beta z} - \Gamma_L e^{+j\beta z}} = Z_0 \frac{Z_L \cos \beta z - j Z_0 \sin \beta z}{Z_0 \cos \beta z - j Z_L \sin \beta z}$$

Likewise, the load boundary condition leaves $V^+(z)$ and $V^-(z)$ undetermined, but **completely determines reflection coefficient function** $\Gamma(z)$!

$$\Gamma(z) = \Gamma_L e^{+j2\beta z} = \frac{Z_L - Z_0}{Z_L + Z_0} e^{+j2\beta z}$$

Let's look at some **specific** values of load impedance $Z_L = R_L + jX_L$ and see what **functions** $Z(z)$ and $\Gamma(z)$ result!

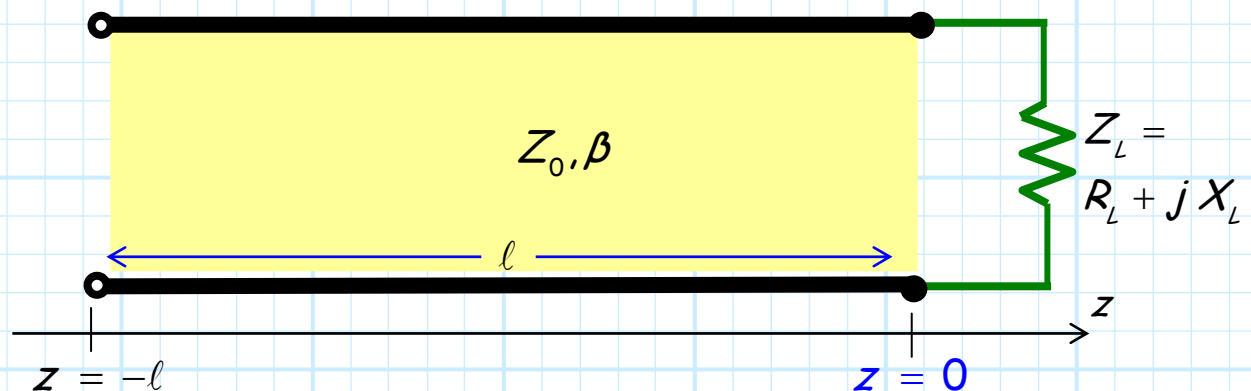We assume that the load is located at $z = 0$
($\therefore \Gamma_L = \Gamma_0$).



The matched case

In this case $Z_L = Z_0$ —the **load impedance is numerically equal to the characteristic impedance of the transmission line**. Assuming the line is **lossless**, then Z_0 is **real**, and thus:

$$R_L = Z_0 \quad \text{and} \quad X_L = 0$$

It is evident that the resulting load reflection coefficient is **zero**:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0$$

As a result, we find that the **reflected wave is zero**, as is the reflection coefficient function:

$$V^+(z) = V_0^+ e^{-j\beta z} \quad V^-(z) = 0 \quad \Gamma(z) = 0$$

Thus, the **total voltage and current along the transmission line is simply voltage and current of the incident wave**, and the line impedance is simply Z_0 at all z :


$$V(z) = V^+(z) = V_0^+ e^{-j\beta z} \quad I(z) = I^+(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} \quad Z(z) = \frac{V(z)}{I(z)} = Z_0$$

Power flow in the matched condition

Note from these results we can conclude that our **boundary conditions** are satisfied:

$$Z(z=0) = Z_0 = Z_L \quad \text{and} \quad \Gamma(z=0) = \Gamma_0 = 0 \quad !!!$$

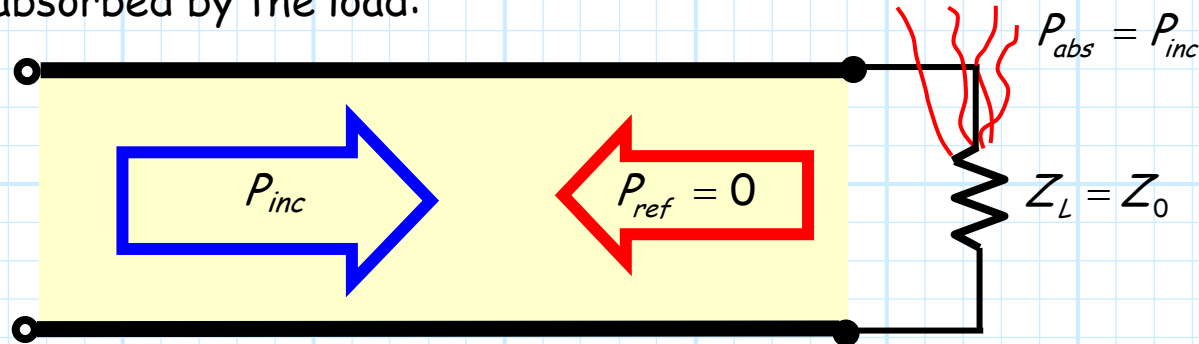Note that since $\Gamma_L = 0$, this is a case where the **reflected power is zero**, and **all the incident power is absorbed by the load**:



Q: *Is there any other load for which this is true?*

A: Nope, $Z_L = Z_0$ is the **only** one!

We call this condition (when $Z_L = Z_0$) the **matched** condition, and the load $Z_L = Z_0$ a **matched load**.

A short-circuit load

A device with **no** impedance ($Z_L = 0$) is called a **short** circuit! I.E.:

$$R_L = 0 \quad \text{and} \quad X_L = 0$$

In this case, the **voltage** across the load—and thus the voltage at the end of the transmission line—is **zero**:

$$V_L = Z_L I_L = 0 \quad \text{and} \quad V(z = 0) = 0$$

Note that this does **not** mean that the **current** is zero!

$$I_L = I(z = 0) \neq 0$$

For a **short**, the resulting load reflection coefficient is therefore:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{0 - Z_0}{0 + Z_0} = -1 = e^{j\pi}$$

A reactive result!

As a result, the **reflected** wave is equal in magnitude to the **incident** wave. The reflection coefficient function thus has a **magnitude of 1!**

$$V^+(z) = V_0^+ e^{-j\beta z} \quad V^-(z) = -V_0^+ e^{+j\beta z} \quad \Gamma(z) = \frac{V^-(z)}{V^+(z)} = -e^{j2\beta z} = e^{j(2\beta z + \pi)}$$

The reflected wave is **just** as big as the incident wave!

The total **voltage** and **current** along a shorted transmission line take an **interesting** form:

$$V(z) = -j2V_0^+ \sin(\beta z) \quad I(z) = \frac{2V_0^+}{Z_0} \cos(\beta z)$$

Meaning that the **line impedance** can likewise be written in terms of a **trigonometric** function:

$$Z(z) = \frac{V(z)}{I(z)} = -jZ_0 \tan(\beta z)$$

Note that this impedance is **purely reactive!**

Boundary conditions are confirmed

From these results we can conclude that our **boundary conditions** are satisfied:

$$Z(z = 0) = -j Z_0 \tan(0) = 0$$

Just as we expected—a **short** circuit!

This is likewise confirmed by evaluating the voltage and current at the **end** of the line (i.e., $z = z_L = 0$):

$$V(z = 0) = -j 2V_0^+ \sin(0) = 0 \qquad I(z = 0) = \frac{2V_0^+}{Z_0} \cos(0) = \frac{2V_0^+}{Z_0}$$

As expected, the voltage is **zero** at the end of the transmission line (i.e. the voltage across the **short**).

Also, the **current** at the end of the line (i.e., the current through the short) is at a **maximum!** Additionally, the **reflection coefficient** at the load is:

$$\Gamma(z = 0) = -e^{j2\beta(0)} = -1 = e^{j\pi} = \Gamma_L$$


Again confirming that the **boundary conditions** are satisfied!

A short cannot absorb energy

Finally, let's determine the **power flow** associated with this short-circuit load.

Since $|\Gamma_L| = 1$, this is a case where the **absorbed** power is **zero**, and all the incident power is **reflected** by the load:
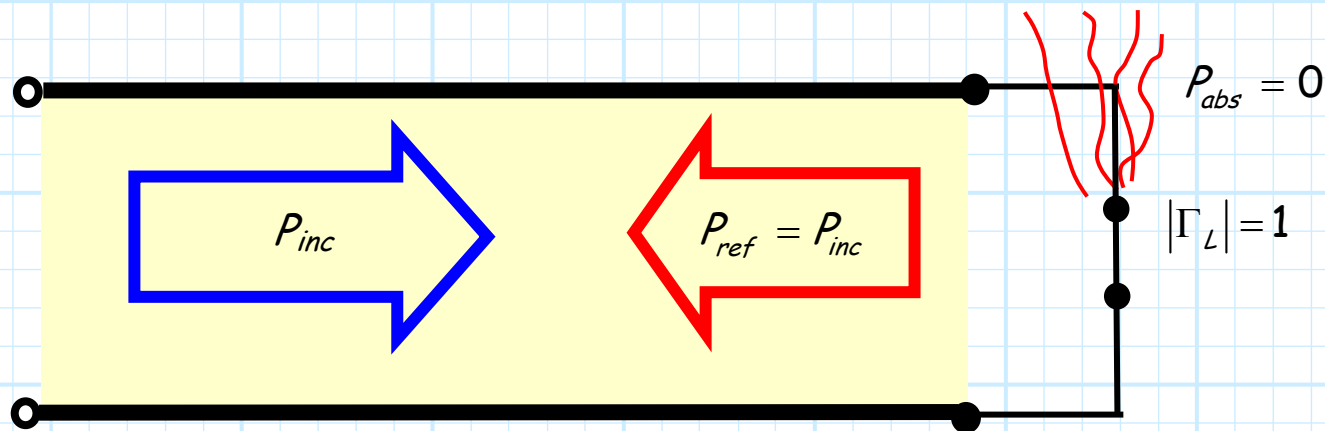
$$P_{abs} = 0 \quad \text{and} \quad P_{ref} = P_{inc}$$



An open-circuit load

A device with **infinite** impedance ($Z_L = \infty$) is called an **open circuit!** I.E.:

$$R_L = \infty \quad \text{and/or} \quad X_L = \pm\infty$$

In this case, the **current** through the load—and thus the current at the end of the transmission line—is **zero**:

$$I_L = \frac{V_L}{Z_L} = 0 \quad \text{and} \quad I(z = z_L) = 0$$

Note that this does **not** mean that the **voltage** is zero!

$$V_L = V(z = z_L) \neq 0$$

For an **open**, the resulting load reflection coefficient is:

$$\Gamma_L = \lim_{Z_L \rightarrow \infty} \frac{Z_L - Z_0}{Z_L + Z_0} = \lim_{Z_L \rightarrow \infty} \frac{Z_L}{Z_L} = 1 = e^{j0}$$

A reactive result!

As a result, the **reflected** wave is **equal** in magnitude to the **incident** wave. The reflection coefficient function thus has a **magnitude of 1!**

$$V^+(z) = V_0^+ e^{-j\beta z} \quad V^-(z) = V_0^+ e^{+j\beta z} \quad \Gamma(z) = \frac{V^-(z)}{V^+(z)} = e^{+j2\beta z}$$

The reflected wave is **just** as big as the incident wave!

The **total** voltage and current along the transmission line is simply (assuming $z_L=0$):

$$V(z) = 2V_0^+ \cos(\beta z) \quad I(z) = -j \frac{2V_0^+}{Z_0} \sin(\beta z)$$

Meaning that the **line impedance** can likewise be written in terms of trigonometric function:

$$Z(z) = \frac{V(z)}{I(z)} = j Z_0 \cot(\beta z)$$

Again note that this impedance is **purely reactive**— $V(z)$ and $I(z)$ are again 90° **out of phase!**

Boundary conditions are confirmed

Note from these results we can conclude that our **boundary conditions** are satisfied:

$$Z(z = 0) = j Z_0 \cot(0) = \infty$$

Just as we expected—an **open** circuit!

This is likewise confirmed by evaluating the voltage and current at the **end** of the line (i.e., $z = z_L = 0$):

$$V(z = 0) = 2V_0^+ \cos(0) = \frac{2V_0^+}{Z_0} \quad I(z = 0) = -j \frac{2V_0^+}{Z_0} \sin(0) = 0$$

As expected, the **current is zero** at the end of the transmission line (i.e. the current through the **open**). Likewise, the **voltage** at the end of the line (i.e., the voltage across the open) is at a **maximum**!

Additionally, the **reflection coefficient** at the load is:

$$\Gamma(z = 0) = e^{j2\beta(0)} = 1 = e^{j0} = \Gamma_L$$


Again confirming that the **boundary conditions** are satisfied!

An open cannot absorb energy

Finally, let's determine the **power flow** associated with this open circuit load.

Since $|\Gamma_L| = 1$, this is again a case where the **absorbed** power is **zero**, and all the incident power is **reflected** by the load:
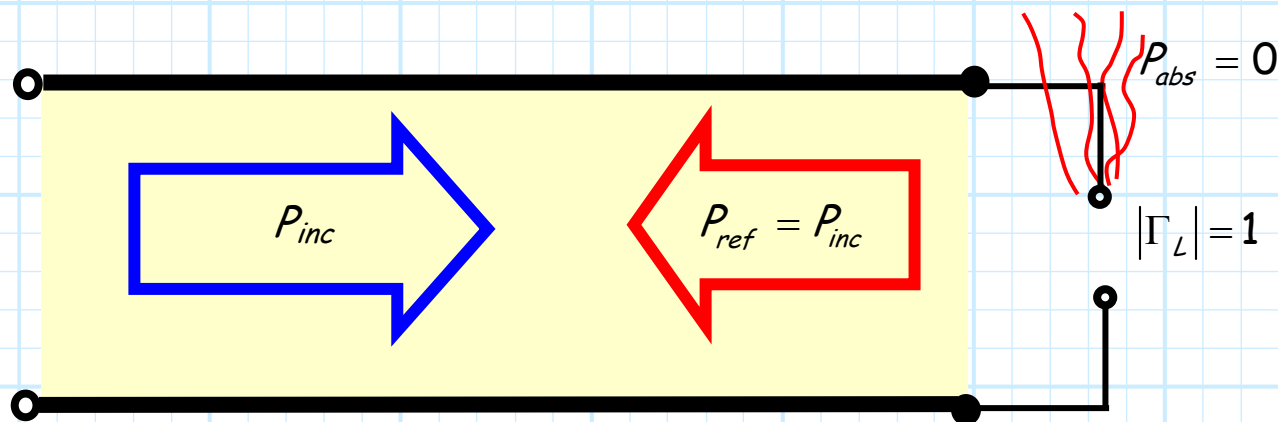
$$P_{abs} = 0 \quad \text{and} \quad P_{ref} = P_{inc}$$



A purely reactive load

For this case, the load impedance is **purely reactive** $Z_L = jX_L$ (e.g. a capacitor or inductor), and thus the resistive portion is zero:

$$R_L = 0$$

Thus, **both** the current through the load, and voltage across the load, are **non-zero**:

$$I_L = I(z = z_L) \neq 0 \qquad V_L = V(z = z_L) \neq 0$$

The resulting load reflection coefficient is:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{jX_L - Z_0}{jX_L + Z_0}$$

Given that Z_0 is real (i.e., the line is **lossless**), we find that this load reflection coefficient is a **complex** number.

V^+ , V^- and Γ

However, we find that the magnitude of **this (reactive)** load reflection coefficient is:

$$|\Gamma_L|^2 = \frac{|jX_L - Z_0|^2}{|jX_L + Z_0|^2} = \frac{X_L^2 + Z_0^2}{X_L^2 + Z_0^2} = 1$$

Its magnitude is **one!**

Thus, we find that for reactive loads, the reflection coefficient can be simply expressed as:

$$\Gamma_L = e^{j\theta} \quad \text{where} \quad \theta = \tan^{-1} \left[\frac{2Z_0 X_L}{X_L^2 - Z_0^2} \right]$$

We can therefore conclude that $V_0^- = e^{j\theta} V_0^+$, and so for a **reactive load**, :

$$V^+(z) = V_0^+ e^{-j\beta z} \quad V^-(z) = e^{j\theta} V_0^+ e^{+j\beta z} \quad \Gamma(z) = \frac{V^-(z)}{V^+(z)} = e^{+j2\beta z}$$

The reflected wave is again **just** as big as the incident wave!

I, V, and Z

The **total** voltage and current along the transmission line are **complex** (assuming $z_L = 0$):

$$V(z) = 2V_0^+ e^{+j\theta_r/2} \cos(\beta z + \theta_r/2) \quad I(z) = -j \frac{2V_0^+}{Z_0} e^{+j\theta_r/2} \sin(\beta z + \theta_r/2)$$

Meaning that the **line impedance** can again be written in terms of trigonometric function:

$$Z(z) = \frac{V(z)}{I(z)} = j Z_0 \cot(\beta z + \theta_r/2)$$

Again note that this impedance is **purely reactive**— $V(z)$ and $I(z)$ are once again 90° out of phase!

Boundary Conditions!

Note at the **end** of the line (i.e., $z = z_L = 0$), we find that

$$V(z = 0) = 2V_0^+ \cos(\theta_r/2) \quad I(z = 0) = -j \frac{2V_0^+}{Z_0} \sin(\theta_r/2)$$

As expected, **neither** the current **nor** voltage at the end of the line is zero.

We also note that the line impedance at the **end** of the transmission line is:

$$Z(z = 0) = j Z_0 \cot(\theta_r/2)$$

With a little trigonometry, we can show (trust me!) that:

$$\cot(\theta_r/2) = \frac{X_L}{Z_0}$$

and therefore:

$$Z(z = 0) = j Z_0 \cot(\theta_r/2) = j X_L = Z_L$$

Just as we **expected!**

Déjà vu All Over Again

Q: Gee, a **reactive** load leads to results very **similar** to that of an **open** or **short** circuit. Is this just **coincidence**?


A: Hardly! An open and short **are** in fact reactive loads—they **cannot absorb power** (think about this!).

Specifically, for an **open**, we find $\theta_r = 0$, so that: $\Gamma_L = e^{j\theta} = 1$

Likewise, for a **short**, we find that $\theta_r = \pi$, so that: $\Gamma_L = e^{j\theta} = -1$

The **power flow** associated with a reactive load is the same as for an open or short.

Since $|\Gamma_L| = 1$, it is again a case where the **absorbed** power is **zero**, and all the incident power is **reflected** by the load:

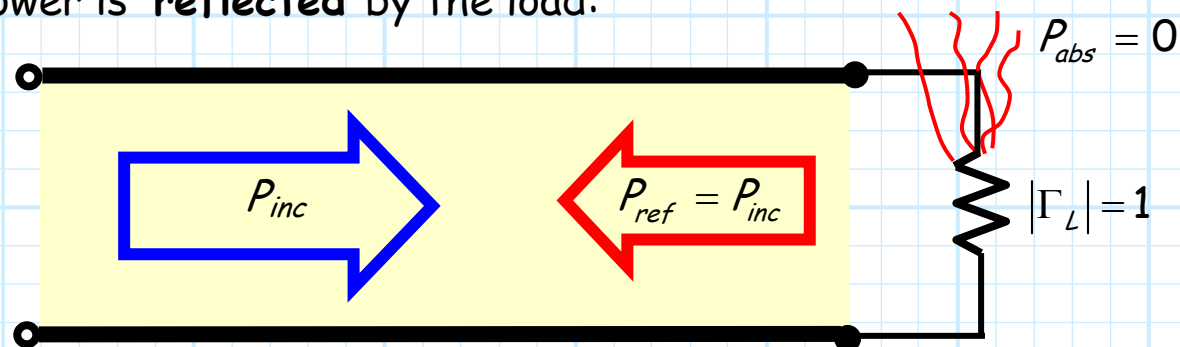

Resistive Load

For this case $Z_L = R_L$, so the load impedance is **purely real** (e.g. a resistor), meaning its reactive portion is zero:

$$X_L = 0$$

The resulting **load reflection coefficient** is:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{R - Z_0}{R + Z_0}$$

Given that Z_0 is real (i.e., the line is **lossless**), we find that this load reflection coefficient must be a purely **real** value!

In other words:

$$\operatorname{Re}\{\Gamma_L\} = \frac{R - Z_0}{R + Z_0} \quad \operatorname{Im}\{\Gamma_L\} = 0$$

Phase difference is either 0 or π

The magnitude is thus:

$$|\Gamma_L| = \left| \frac{R - Z_0}{R + Z_0} \right|$$

whereas the phase θ_r can take on one of two values:

$$\theta_r = \begin{cases} 0 & \text{if } \operatorname{Re}\{\Gamma_L\} > 0 \text{ (i.e., if } R_L > Z_0) \\ \pi & \text{if } \operatorname{Re}\{\Gamma_L\} < 0 \text{ (i.e., if } R_L < Z_0) \end{cases}$$

For this case, the impedance at the **end** of the line must be **real** ($Z(z = z_L) = R_L$).

Thus, the current and the voltage at this point are precisely **in phase**, or precisely 180 degrees **out of phase**!

The load is real; why isn't the line impedance?

However, even though the **load** impedance is real, the **line** impedance at all other points on the line is generally **complex**!

Moreover, the **general** current and voltage expressions, as well as reflection coefficient function, **cannot** be further simplified for the case where $Z_L = R_L$.

Q: *Why is that?*

*When the load was purely **imaginary** (reactive), we were able to **simply** our general expressions, and likewise deduce all sorts of interesting results!*

A: True! And here's **why**.

Remember, a **lossless** transmission line has series inductance and shunt capacitance **only**.

In other words, a length of lossless transmission line is a **purely reactive** device (it absorbs **no** energy!).

Remember, a lossless line is purely reactive!

- * If we attach a **purely reactive** load at the end of the transmission line, we still have a **completely** reactive system (load and transmission line).
- * Because this system has **no** resistive (i.e., real) component, the general expressions for line impedance, line voltage, etc. can be significantly **simplified**.
- * However, if we attach a **purely real** load to our reactive transmission line, we now have a **complex** system, with **both** real and imaginary (i.e., resistive and reactive) components.
- * This **complex** case is exactly what our general expressions **already** describes—**no** further simplification is possible!

The "General" Load

Now, let's look at the **general** case $Z_L = R_L + jX_L$, where the load has both a **real** (resistive) and **imaginary** (reactive) component.

Q: Haven't we **already** determined all the **general** expressions (e.g., $\Gamma_L, V(z), I(z), Z(z), \Gamma(z)$) for this general case?

*Is there **anything** else left to be determined?*

A: There is **one** last thing we need to discuss.

It seems trivial, but its ramifications are **very** important!

For you see, the "general" case is **not**, in reality, quite so **general**.

Although the reactive component of the load can be **either** positive or negative ($-\infty < X_L < \infty$), the resistive component of a passive load **must** be positive ($R_L > 0$)—there's **no** such thing as a (passive) **negative** resistor!



Complex arithmetic—is there anything funner?

This leads to one **very** important and **very** useful result.

Consider the **load reflection coefficient**:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(R_L + jX_L) - Z_0}{(R_L + jX_L) + Z_0} = \frac{(R_L - Z_0) + jX_L}{(R_L + Z_0) + jX_L}$$

Now let's look at the **magnitude** of this value:

$$\begin{aligned} |\Gamma_L|^2 &= \left| \frac{(R_L - Z_0) + jX_L}{(R_L + Z_0) + jX_L} \right|^2 \\ &= \frac{(R_L - Z_0)^2 + X_L^2}{(R_L + Z_0)^2 + X_L^2} \\ &= \frac{(R_L^2 - 2R_L Z_0 + Z_0^2) + X_L^2}{(R_L^2 + 2R_L Z_0 + Z_0^2) + X_L^2} \\ &= \frac{(R_L^2 + Z_0^2 + X_L^2) - 2R_L Z_0}{(R_L^2 + Z_0^2 + X_L^2) + 2R_L Z_0} \end{aligned}$$

A passive load? Then $|\Gamma| < 1!$

It is apparent that since both R_L and Z_0 are **positive**, the **numerator** of the above expression must be **less** than (or equal to) the **denominator** of the above expression.

→ In other words, the magnitude of the load reflection coefficient is always **less** than or equal to one!

$$|\Gamma_L| \leq 1 \quad (\text{for } R_L \geq 0)$$

Moreover, we find that this means the reflection coefficient **function** likewise always has a magnitude **less** than or equal to one, for **all** values of position z .

$$|\Gamma(z)| \leq 1 \quad (\text{for all } z)$$

A passive load? Then the reflected wave will always be less than the incident!

Which means, of course, that the **reflected** wave will always have a magnitude **less** than that of the **incident** wave magnitude:

$$|V^-(z)| \leq |V^+(z)| \quad (\text{for all } z)$$

Recall this result is consistent with **conservation of energy**—the reflected wave from a **passive** load **cannot** be larger than the wave incident on it.