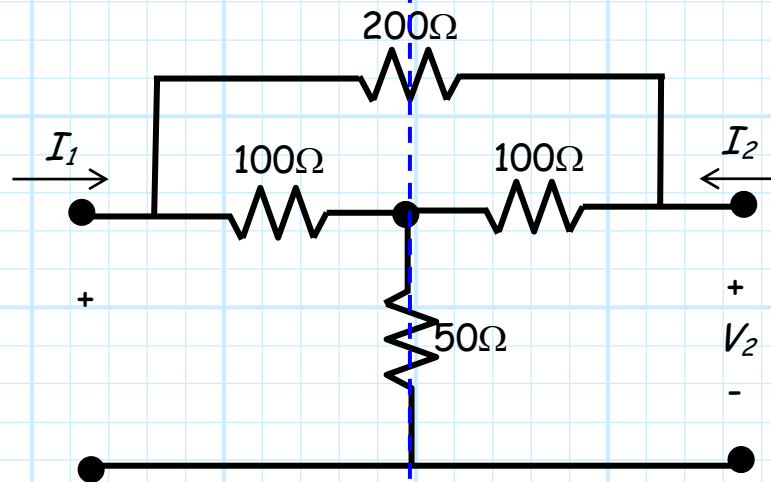



Symmetric Circuit Analysis

Consider the following D_1 symmetric two-port device:



Q: *Yikes! The plane of reflection symmetry slices through two resistors. What can we do about that?*

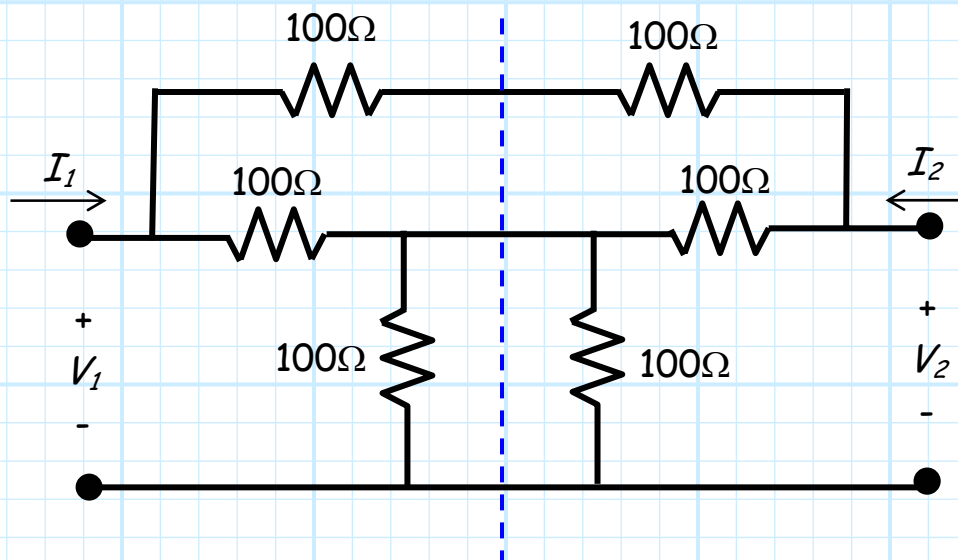A: Resistors are easily split into two equal pieces: the 200Ω resistor into two 100Ω resistors in **series**, and the 50Ω resistor as two 100Ω resistors in **parallel**.




Recall that the **symmetry** of this 2-port device leads to **simplified** network matrices:

$$\mathbf{S} = \begin{bmatrix} S_{11} & S_{21} \\ S_{21} & S_{11} \end{bmatrix} \quad \mathbf{Z} = \begin{bmatrix} Z_{11} & Z_{21} \\ Z_{21} & Z_{11} \end{bmatrix} \quad \mathbf{Y} = \begin{bmatrix} Y_{11} & Y_{21} \\ Y_{21} & Y_{11} \end{bmatrix}$$


Q: *Yes, but can circuit symmetry likewise simplify the procedure of **determining** these elements? In other words, can symmetry be used to **simplify circuit analysis**?*

A: You bet!

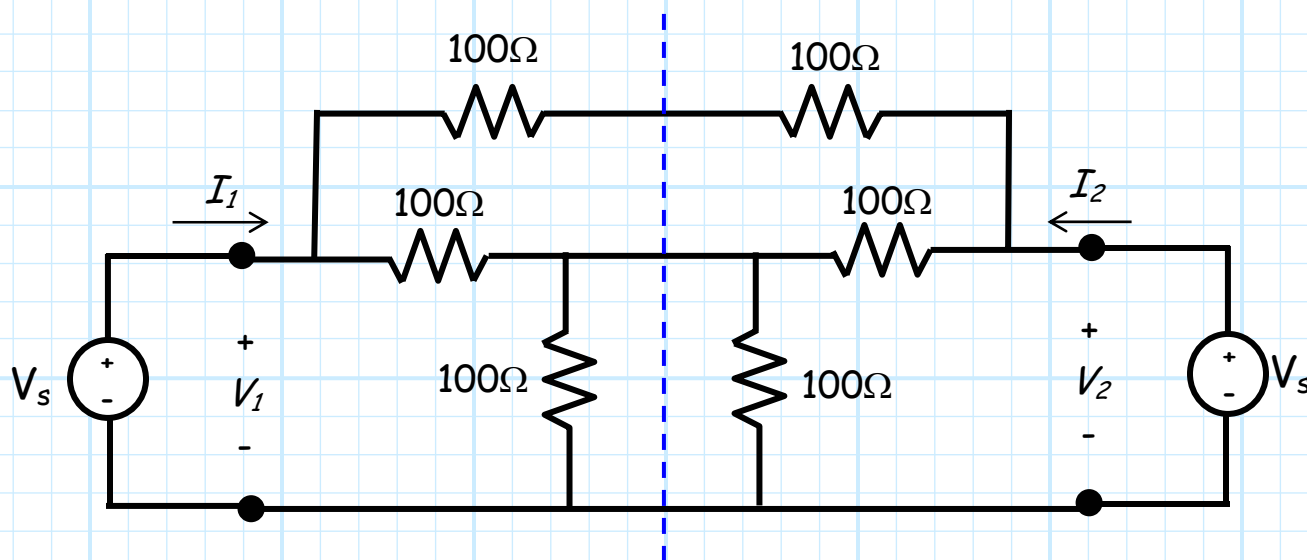
First, consider the case where we **attach sources** to circuit in a way that **preserves** the circuit **symmetry**:



Or,

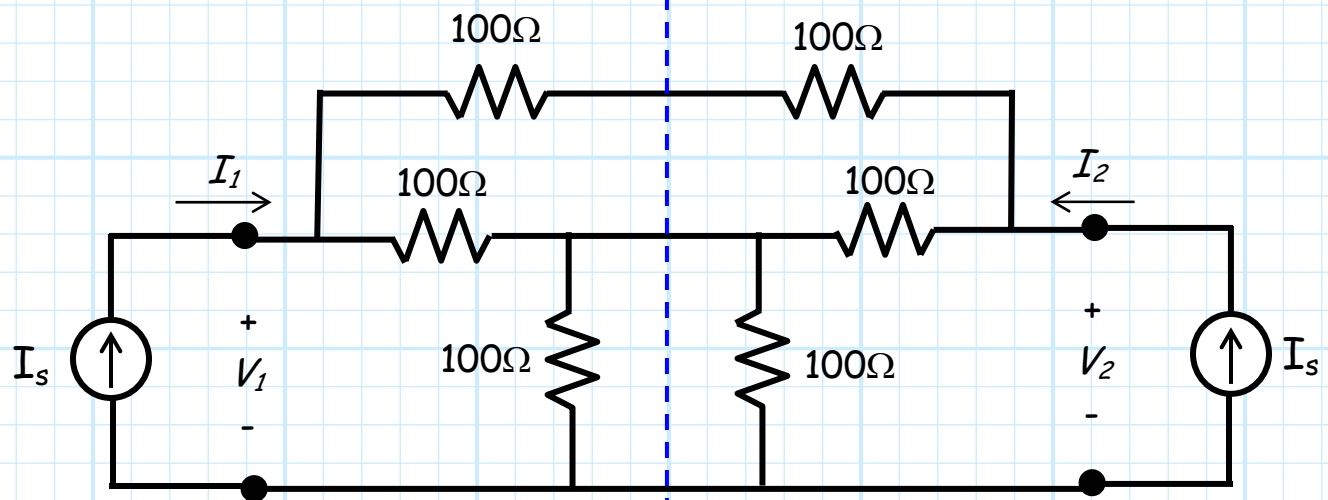


Or,

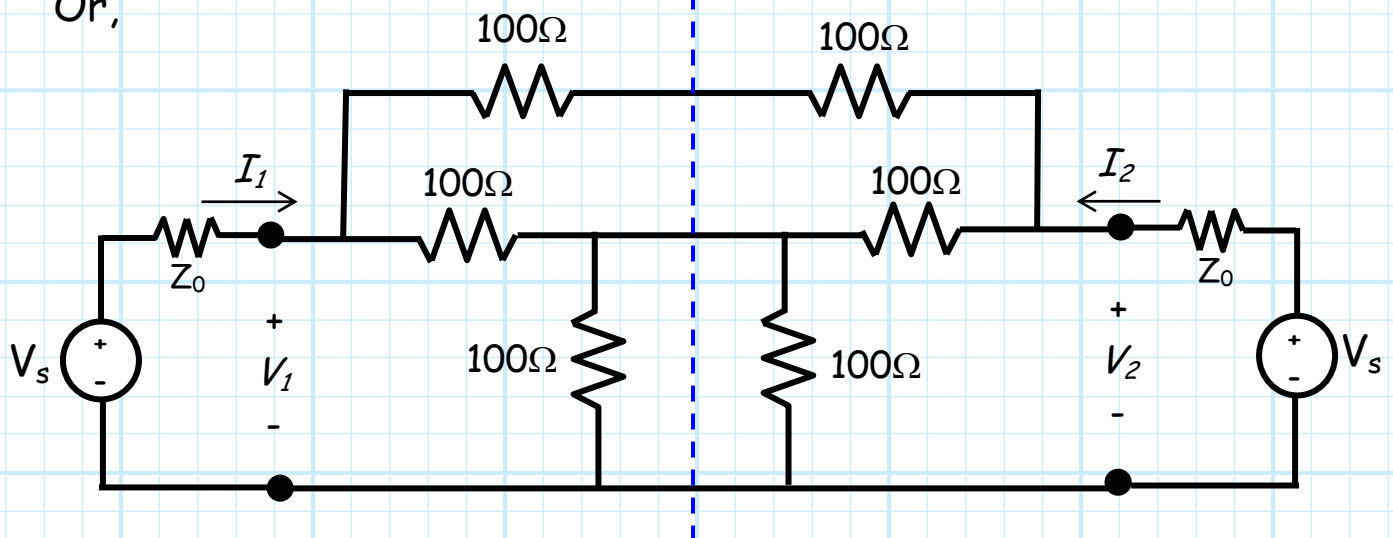

But remember! In order for **symmetry to be preserved**, the source values on both sides (i.e., I_s, V_s, Z_0) must be **identical**!

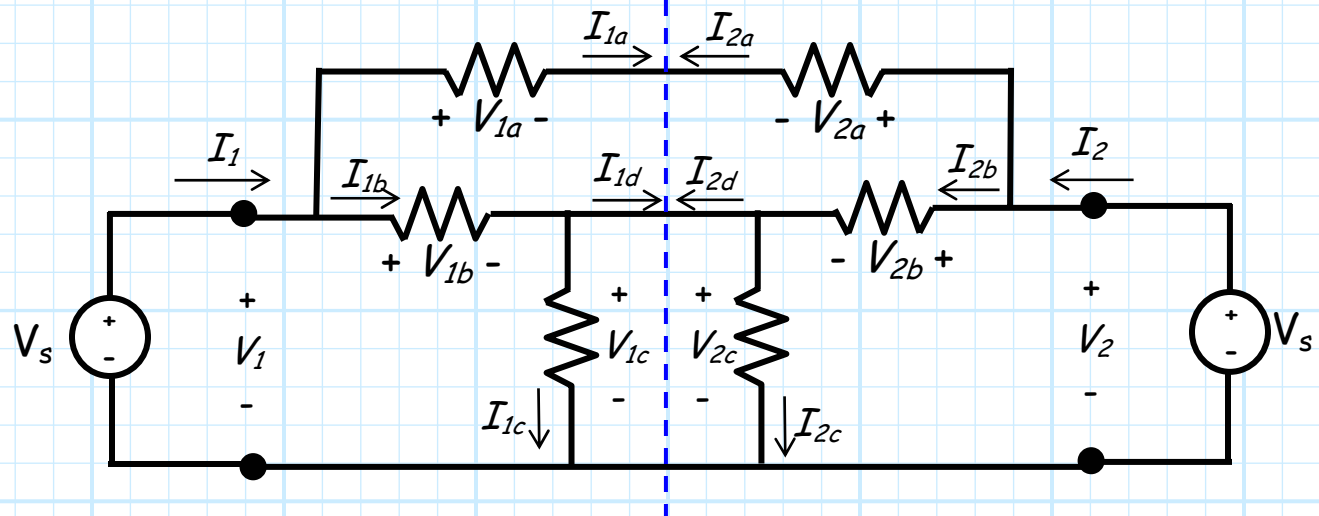Now, consider the **voltages** and **currents** within this circuit under this symmetric configuration:



Since this circuit possesses **bilateral** (reflection) symmetry ($1 \rightarrow 2, 2 \rightarrow 1$), symmetric currents and voltages must be equal:

$$V_1 = V_2$$

$$V_{1a} = V_{2a}$$

$$V_{1b} = V_{2b}$$

$$V_{1c} = V_{2c}$$

$$I_1 = I_2$$

$$I_{1a} = I_{2a}$$

$$I_{1b} = I_{2b}$$

$$I_{1c} = I_{2c}$$

$$I_{1d} = I_{2d}$$

Q: Wait! This can't possibly be correct! Look at currents I_{1a} and I_{2a} , as well as currents I_{1d} and I_{2d} . From KCL, this must be true:

$$I_{1a} = -I_{2a}$$

$$I_{1d} = -I_{2d}$$

Yet you say that **this** must be true:

$$I_{1a} = I_{2a}$$


$$I_{1d} = I_{2d}$$

There is an obvious contradiction here! There is no way that both sets of equations can simultaneously be correct, is there?

A: Actually there is! There is **one** solution that will satisfy **both** sets of equations:

$$I_{1a} = I_{2a} = 0 \qquad I_{1d} = I_{2d} = 0$$

The currents are **zero!**

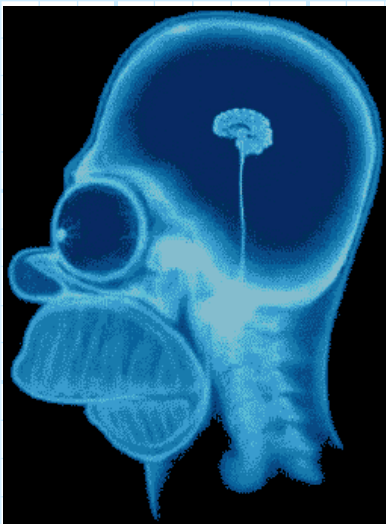


If you **think** about it, this makes **perfect sense!** The result says that **no current** will flow from one side of the symmetric circuit into the other.

If current **did** flow across the symmetry plane, then the circuit symmetry would be **destroyed**—one side would effectively become the “**source side**”, and the other the “**load side**” (i.e., the source side delivers current to the load side).


Thus, **no current** will flow **across** the reflection symmetry plane of a **symmetric circuit**—the symmetry plane thus acts as a **open circuit!**

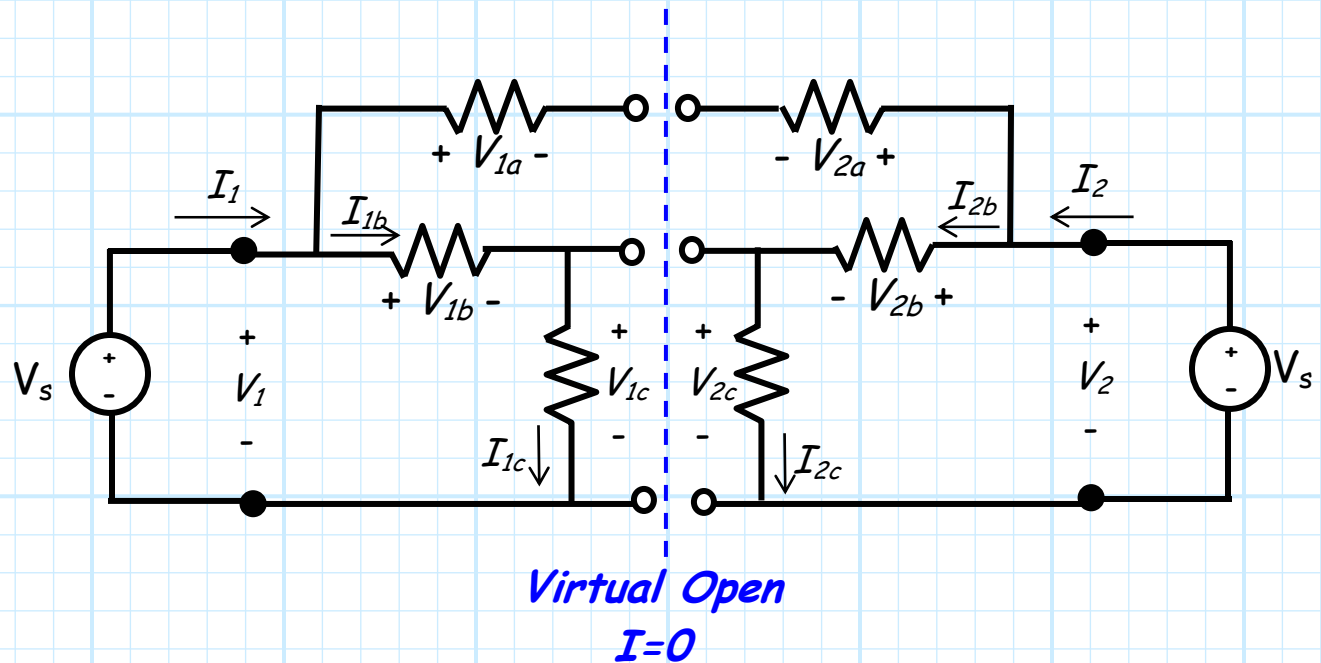The plane of symmetry thus becomes a **virtual open!**



Q: So what?

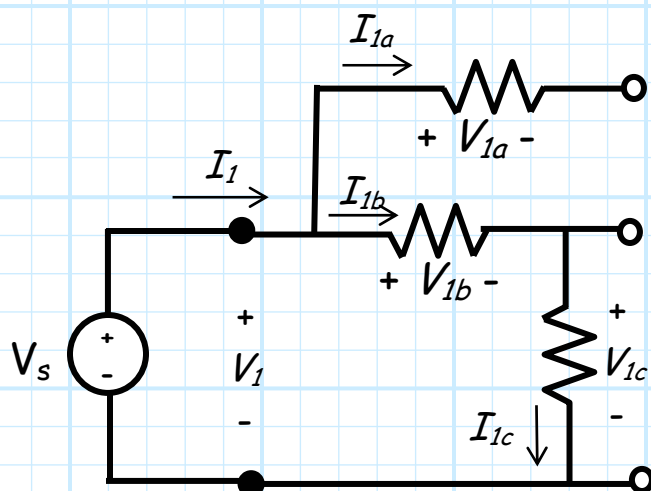A: So what! This means that our circuit can be **split apart** into **two separate** but **identical** circuits. Solve **one** half-circuit, and you have **solved** the other!



$$V_1 = V_2 = V_s$$

$$V_{1a} = V_{2a} = 0$$

$$V_{1b} = V_{2b} = V_s/2$$

$$V_{1c} = V_{2c} = V_s/2$$

$$I_1 = I_2 = V_s/200$$


$$I_{1a} = I_{2a} = 0$$

$$I_{1b} = I_{2b} = V_s/200$$


$$I_{1c} = I_{2c} = V_s/200$$

$$I_{1d} = I_{2d} = 0$$

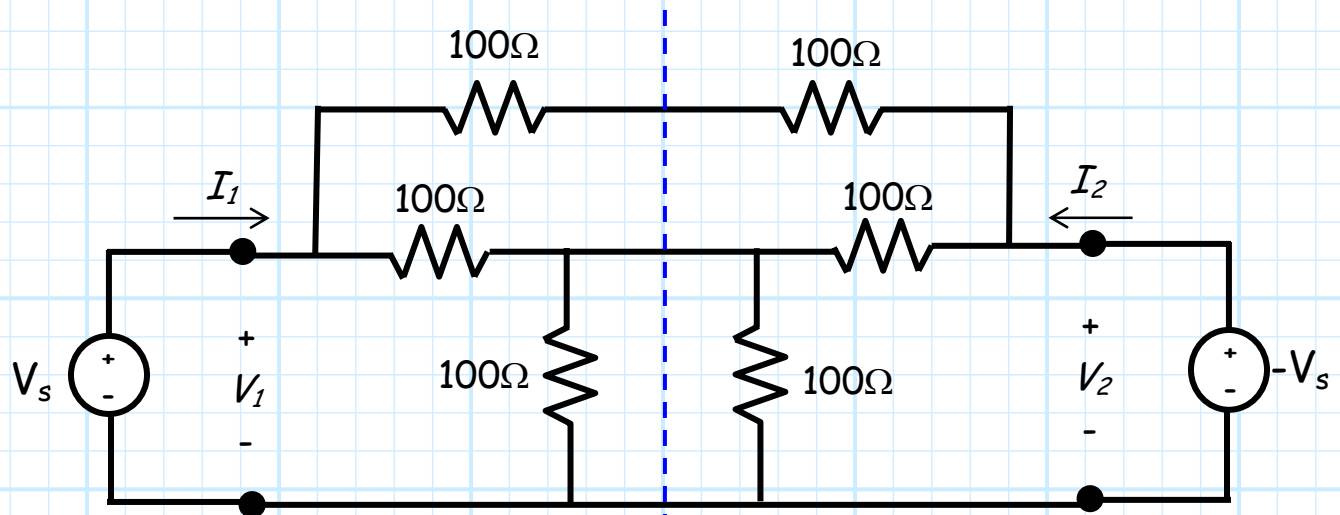
Now, consider **another** type of symmetry, where the sources are **equal but opposite** (i.e., **180 degrees** out of phase).




Or,

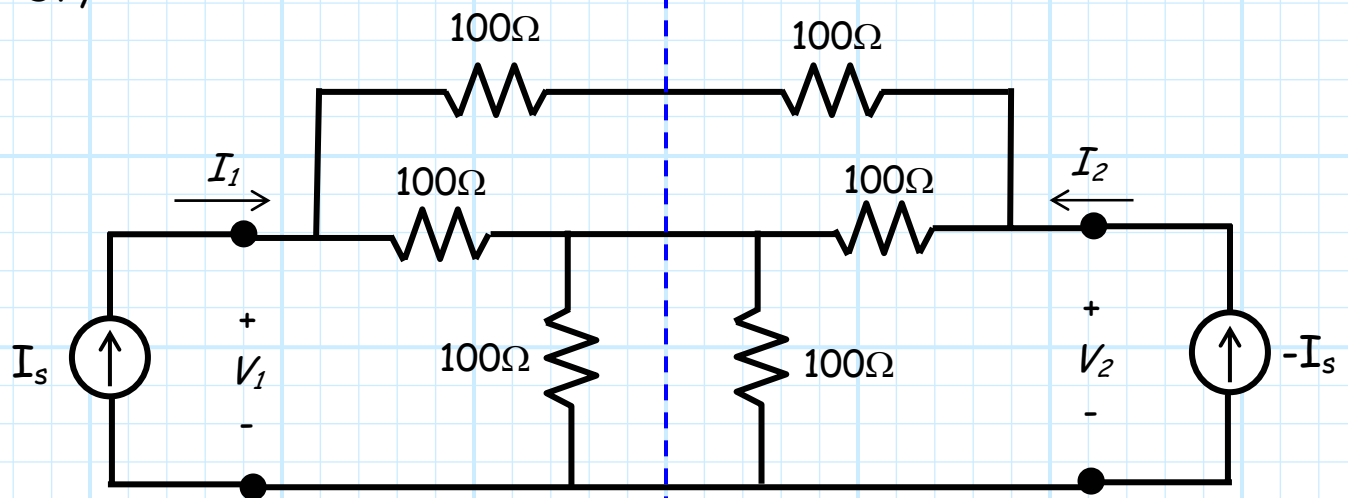

Or,

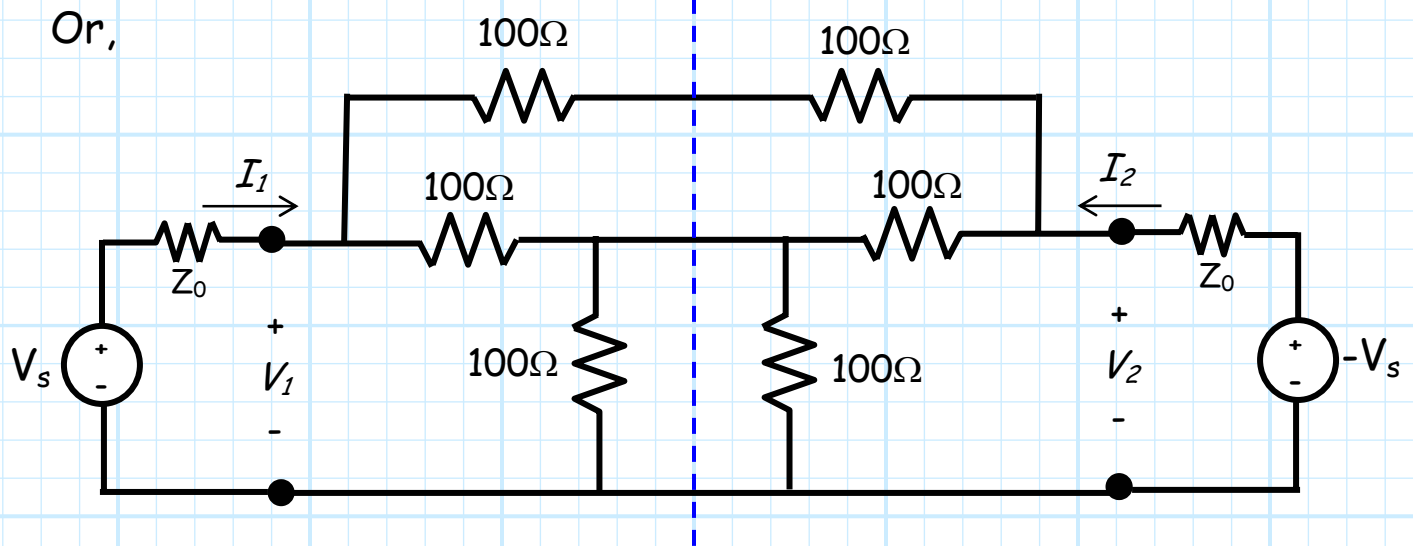

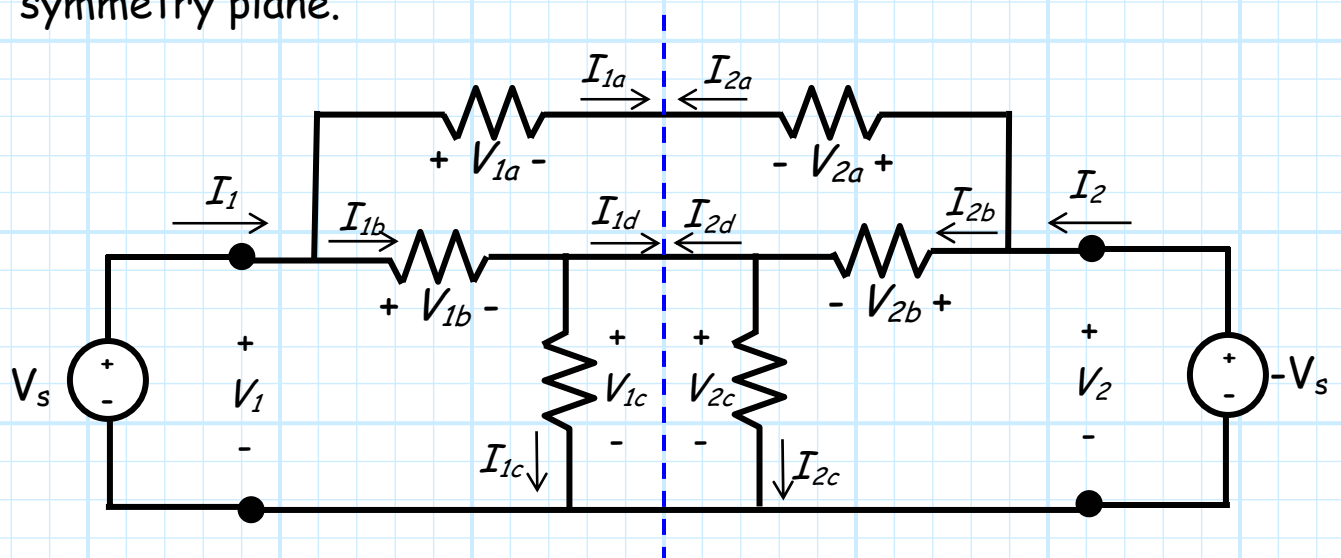
This situation still preserves the **symmetry** of the circuit—**somewhat**. The **voltages** and **currents** in the circuit will now possess **odd symmetry**—they will be **equal but opposite** (180 degrees out of phase) at symmetric points across the symmetry plane.



$$\begin{aligned} V_1 &= -V_2 \\ V_{1a} &= -V_{2a} \\ V_{1b} &= -V_{2b} \\ V_{1c} &= -V_{2c} \end{aligned}$$

$$\begin{aligned} I_1 &= -I_2 \\ I_{1a} &= -I_{2a} \\ I_{1b} &= -I_{2b} \\ I_{1c} &= -I_{2c} \\ I_{1d} &= -I_{2d} \end{aligned}$$

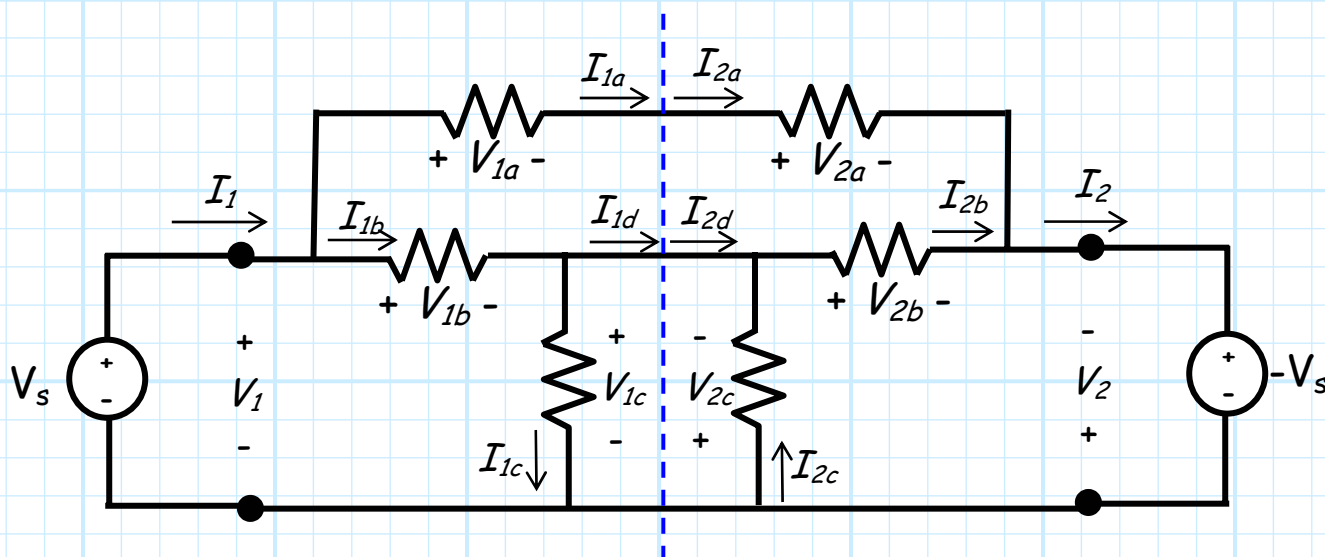Perhaps it would be easier to **redefine** the circuit variables as:



$$V_1 = V_2$$

$$V_{1a} = V_{2a}$$

$$V_{1b} = V_{2b}$$

$$V_{1c} = V_{2c}$$

$$I_1 = I_2$$

$$I_{1a} = I_{2a}$$

$$I_{1b} = I_{2b}$$

$$I_{1c} = I_{2c}$$

$$I_{1d} = I_{2d}$$

Q: But wait! *Again* I see a problem. By KVL it is evident that:

$$V_{1c} = -V_{2c}$$


Yet you say that $V_{1c} = V_{2c}$ must be true!

A: Again, the solution to **both** equations is **zero**!


$$V_{1c} = V_{2c} = 0$$

For the case of **odd symmetry**, the symmetric plane must be a plane of **constant potential** (i.e., constant voltage)—just like a **short circuit!**

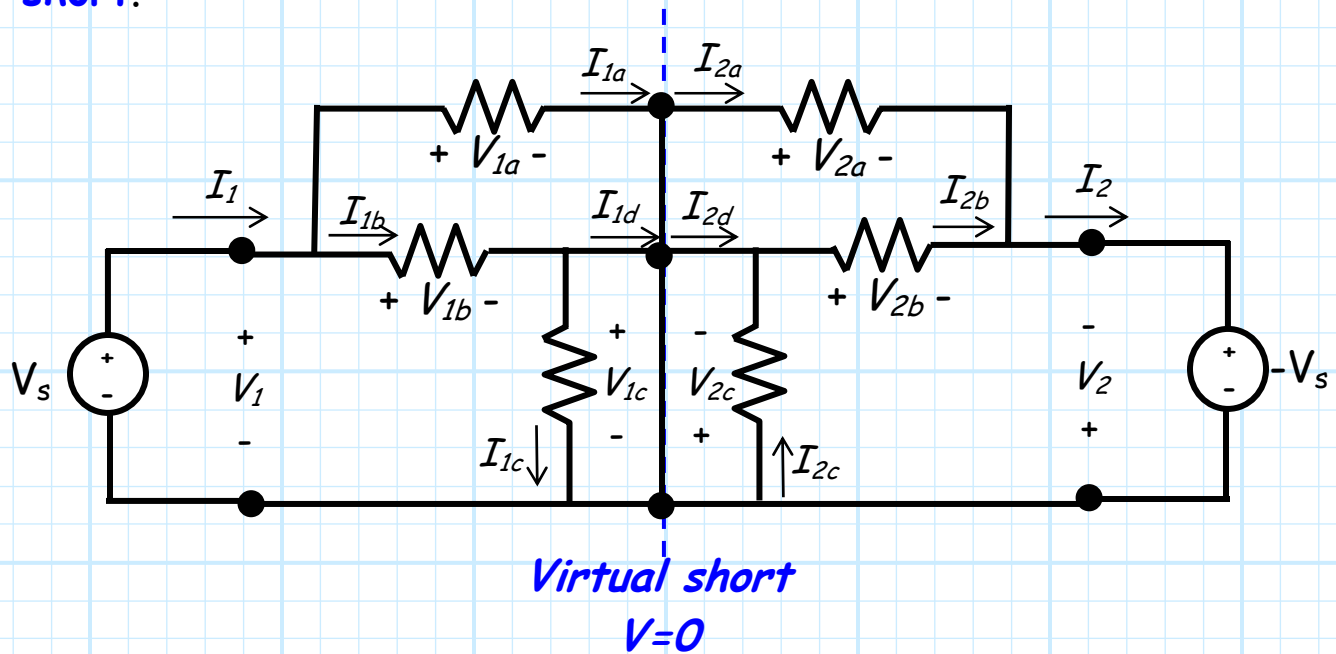Thus, for odd symmetry, the symmetric plane forms a **virtual short**.



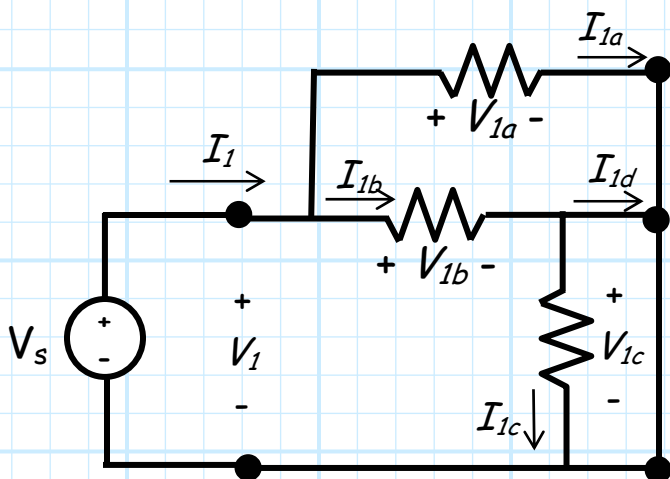This **greatly** simplifies things, as we can again **break** the circuit into **two** independent and (effectively) identical circuits!



$$\begin{aligned} V_1 &= V_s \\ V_{1a} &= V_s \\ V_{1b} &= V_s \\ V_{1c} &= 0 \end{aligned}$$

$$\begin{aligned} I_1 &= V_s/50 \\ I_{1a} &= V_s/100 \\ I_{1b} &= V_s/100 \\ I_{1c} &= 0 \\ I_{1d} &= V_s/100 \end{aligned}$$