

# The Binomial Multi-Section Transformer


Recall that a **multi-section matching network** can be described using the theory of small reflections as:

$$\begin{aligned}\Gamma_{in}(\omega) &= \Gamma_0 + \Gamma_1 e^{-j2\omega T} + \Gamma_2 e^{-j4\omega T} + \dots + \Gamma_N e^{-j2N\omega T} \\ &= \sum_{n=0}^N \Gamma_n e^{-j2n\omega T}\end{aligned}$$

where:

$$T \doteq \frac{\ell}{v_p} = \text{propagation time through 1 section}$$

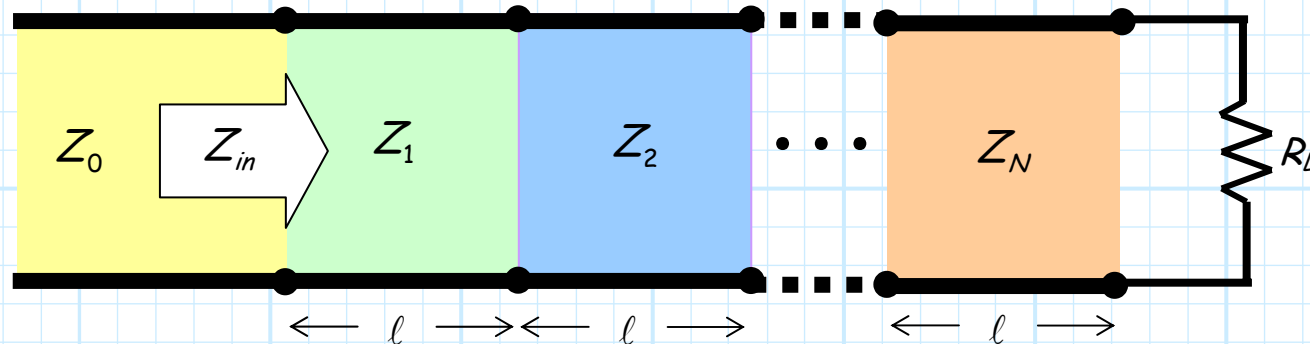Note that for a multi-section transformer, we have  $N$  **degrees of design freedom**, corresponding to the  $N$  characteristic impedance values  $Z_n$ .



# Behold the Binomial Function!

**Q:** *What should the values of  $\Gamma_n$  (i.e.,  $Z_n$ ) be?*

**A:** We need to define  $N$  independent **design equations**, which we can then use to solve for the  $N$  values of **characteristic impedance**  $Z_n$ .

First, we start with a single **design frequency**  $\omega_0$ , where we wish to achieve a **perfect match**:

$$\Gamma_{in}(\omega = \omega_0) = 0$$

That's just **one** design equation: we need  $N - 1$  more!

These additional equations can be selected using **many** criteria—one such criterion is to make the function  $\Gamma_{in}(\omega)$  **maximally flat** at the point  $\omega = \omega_0$ .

To accomplish this, we first consider the **Binomial Function**:

$$\Gamma(\theta) = A(1 + e^{-j2\theta})^N$$

# What's so special about the Binomial Function!

The Binomial Function has the desirable **properties** that:

$$\begin{aligned}\Gamma(\theta = \pi/2) &= A(1 + e^{-j\pi})^N \\ &= A(1 - 1)^N \\ &= 0\end{aligned}$$

and that:

$$\left. \frac{d^n \Gamma(\theta)}{d\theta^n} \right|_{\theta=\pi/2} = 0 \text{ for } n = 1, 2, 3, \dots, N-1$$

In other words, this Binomial Function is **maximally flat** at the point  $\theta = \pi/2$ , where it has a value of  $\Gamma(\theta = \pi/2) = 0$ .

**Q:** *So? What does this have to do with our multi-section matching network?*

## A: Plenty!

Let's **expand** (multiply out the  $N$  identical product terms) of the Binomial Function:

$$\begin{aligned}\Gamma(\theta) &= A(1 + e^{-j2\theta})^N \\ &= A(C_0^N + C_1^N e^{-j2\theta} + C_2^N e^{-j4\theta} + C_3^N e^{-j6\theta} + \dots + C_N^N e^{-j2N\theta})\end{aligned}$$

where:

$$C_n^N = \frac{N!}{(N-n)!n!}$$

Compare this to an  $N$ -section transformer function:

$$\Gamma_{in}(\omega) = \Gamma_0 + \Gamma_1 e^{-j2\omega T} + \Gamma_2 e^{-j4\omega T} + \dots + \Gamma_N e^{-j2N\omega T}$$

and it is obvious the two functions have **identical** forms, **provided** that:

$$\Gamma_n = A C_n^N \quad \text{and} \quad \omega T = \theta$$

## See, the Binomial Function is very useful!

Moreover, we find that this function is very **desirable** from the standpoint of a matching network. Recall that  $\Gamma(\theta) = 0$  at  $\theta = \pi/2$ --a **perfect** match!

Additionally, the function is **maximally flat** at  $\theta = \pi/2$ , therefore  $\Gamma(\theta) \approx 0$  over a wide range around  $\theta = \pi/2$ --a **wide bandwidth!**

**Q:** *But how does  $\theta = \pi/2$  relate to frequency  $\omega$ ?*

**A:** Remember that  $\omega T = \theta$ , so the value  $\theta = \pi/2$  corresponds to the frequency:

$$\omega_0 = \frac{1}{T} \frac{\pi}{2} = \frac{v_p}{\ell} \frac{\pi}{2}$$

This frequency ( $\omega_0$ ) is therefore our **design** frequency—the frequency where we have a **perfect** match.

## What about the length of each section?

Note that the section-length  $\ell$  has an interesting relationship with this frequency:

$$\ell = \frac{V_p}{\omega_0} \frac{\pi}{2} = \frac{1}{\beta_0} \frac{\pi}{2} = \frac{\lambda_0}{2\pi} \frac{\pi}{2} = \frac{\lambda_0}{4}$$

In other words, a **Binomial** Multi-section matching network will have a **perfect** match at the frequency where the section lengths  $\ell$  are a **quarter wavelength!**

Thus, we have our **first design rule**:


Set section lengths  $\ell$  so that they are a **quarter-wavelength** ( $\lambda_0/4$ ) at the design frequency  $\omega_0$ .

## And that pesky constant $A$ ?

**Q:** *I see! And then we select all the values  $Z_n$  such that  $\Gamma_n = A C_n^N$ . But wait! **What is the value of  $A$  ??***

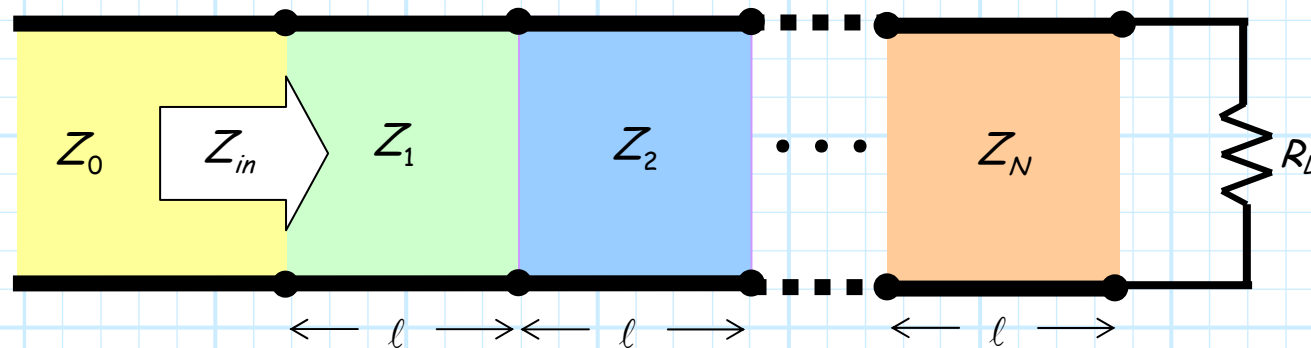**A:** *We can determine this value by evaluating a **boundary condition!***

Specifically, we can **easily** determine the value of  $\Gamma(\omega)$  at  $\omega = 0$ .



Note as  $\omega$  approaches **zero**, the electrical length  $\beta l$  of each section will **likewise** approach zero. Thus, the input impedance  $Z_{in}$  will simply be equal to  $R_L$  as  $\omega \rightarrow 0$ .

As a result, the input reflection coefficient  $\Gamma(\omega = 0)$  **must** be:

$$\Gamma(\omega = 0) = \frac{Z_{in}(\omega = 0) - Z_0}{Z_{in}(\omega = 0) + Z_0} = \frac{R_L - Z_0}{R_L + Z_0}$$

## Aren't boundary conditions great ?

However, we likewise know that:

$$\begin{aligned}\Gamma(0) &= A(1 + e^{-j2(0)})^N \\ &= A(1 + 1)^N \\ &= A2^N\end{aligned}$$

Equating the two expressions:

$$\Gamma(0) = A2^N = \frac{R_L - Z_0}{R_L + Z_0}$$

And therefore:

$$A = 2^{-N} \frac{R_L - Z_0}{R_L + Z_0} \quad (A \text{ can be negative!}) \quad \triangle$$

We now have a form to calculate the **required marginal reflection coefficients**  $\Gamma_n$ :

$$\Gamma_n = AC_n^N = \frac{A N!}{(N-n)!n!}$$



## How do I determine characteristic impedance?

Of course, we **also** know that these marginal reflection coefficients are physically related to the characteristic impedances of each section as:

$$\Gamma_n = \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n}$$

Equating the two and solving, we find that that the section characteristic impedances must satisfy:

$$Z_{n+1} = Z_n \frac{1 + \Gamma_n}{1 - \Gamma_n} = Z_n \frac{1 + AC_n^N}{1 - AC_n^N}$$

Note this is an **iterative** result—we determine  $Z_1$  from  $Z_0$ ,  $Z_2$  from  $Z_1$ , and so forth.

**Q:** *This result **appears** to be our second design equation. Is there some reason why you didn't draw a big blue box around it?*

**A:** Alas, there is a **big problem** with this result.

## The BIG problem with this result!

Note that there are  $N+1$  coefficients  $\Gamma_n$  (i.e.,  $n \in \{0, 1, \dots, N\}$ ) in the Binomial series, yet there are only  $N$  design degrees of freedom (i.e., there are only  $N$  transmission line sections!).

Thus, our design is a bit **over constrained**, a result that manifests itself the finally marginal reflection coefficient  $\Gamma_N$ .

Note from the iterative solution above, the **last** transmission line impedance  $Z_N$  is selected to satisfy the **mathematical** requirement of the **penultimate** reflection coefficient  $\Gamma_{N-1}$ :

$$\Gamma_{N-1} = \frac{Z_N - Z_{N-1}}{Z_N + Z_{N-1}} = AC_{N-1}^N$$

Thus the last impedance must be:

$$Z_N = Z_{N-1} \frac{1 + AC_{N-1}^N}{1 - AC_{N-1}^N}$$

## Our degrees of freedom have run out!

But there is **one more** mathematical requirement! The last marginal reflection coefficient **must** likewise satisfy:

$$\Gamma_N = A C_N^N = 2^{-N} \frac{R_L - Z_0}{R_L + Z_0}$$

where we have used the fact that  $C_N^N = 1$ .

But, we **just** selected  $Z_N$  to satisfy the requirement for  $\Gamma_{N-1}$ ,—we have no **physical** design parameter to satisfy this last **mathematical** requirement!

As a result, we find to our great consternation that the last requirement is not satisfied:

$$\Gamma_N = \frac{R_L - Z_N}{R_L + Z_N} \neq A C_N^N \text{ !!!!!}$$

**Q:** *Yikes! Does this mean that the resulting matching network will **not** have the desired Binomial frequency response?*

**A:** That's **exactly** what it means!


## &\*#@\*!&!!!!

**Q:** You big #%#@#\$%&!!!! Why did you waste all my time by discussing an over-constrained design problem that can't be built?

**A:** Relax; there is a **solution** to our dilemma—albeit an **approximate** one. You undoubtedly have previously used the **approximation**:

$$\frac{y-x}{y+x} \approx \frac{1}{2} \ln \left( \frac{y}{x} \right)$$

An approximation that is especially **accurate** when  $|y-x|$  is small (i.e., when  $y/x \simeq 1$ ).

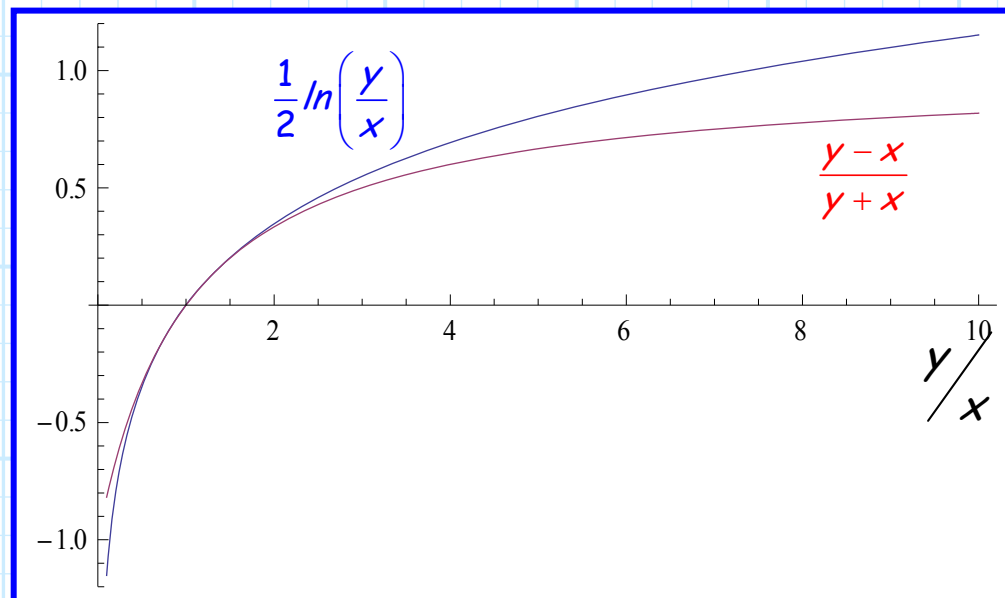

## Use this approximation for value $A$ !

Now, we know that the values of  $Z_{n+1}$  and  $Z_n$  in a multi-section matching network are typically **very close**, such that  $|Z_{n+1} - Z_n|$  is small.

Thus, we use the approximation:

$$\Gamma_n = \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n} \approx \frac{1}{2} \ln \left( \frac{Z_{n+1}}{Z_n} \right)$$

Likewise, we can **also** apply this approximation (although not as accurately) to the value of  $A$ :

$$A = 2^{-N} \frac{R_L - Z_0}{R_L + Z_0} \approx 2^{-(N+1)} \ln \left( \frac{R_L}{Z_0} \right)$$

## Let's try this again—with approximations!

So, let's **start over**, only this time we'll use these **approximations**. First, determine  $A$ :

$$A \approx 2^{-(N+1)} \ln \left( \frac{R_L}{Z_0} \right) \quad (A \text{ can be negative!}) \quad \triangle!$$

Now use this result to calculate the **mathematically required** marginal reflection coefficients  $\Gamma_n$ :

$$\Gamma_n = A C_n^N = \frac{A N!}{(N-n)! n!}$$

## Here's (finally) our second design rule!

Of course, we **also** know that these marginal reflection coefficients are **physically** related to the **characteristic impedances** of each section as:

$$\Gamma_n \approx \frac{1}{2} \ln \left( \frac{Z_{n+1}}{Z_n} \right)$$

Equating the two and solving, we find that that the section characteristic impedances **must** satisfy:

$$Z_{n+1} = Z_n \exp[2\Gamma_n]$$

Now **this** is our **second design rule**. Note it is an **iterative** rule—we determine  $Z_1$  from  $Z_0$ ,  $Z_2$  from  $Z_1$ , and so forth.

# I don't understand what just happened

**Q:** *Huh? How is this any better? How does applying **approximate** math lead to a **better** design result??*

**A:** Applying these approximations help **resolve** our over-constrained problem. Recall that the over-constraint resulted in:

$$\Gamma_N = \frac{R_L - Z_N}{R_L + Z_N} \neq A C_N^N$$

But, as it turns out, these approximations leads to the **happy situation** where:

$$\Gamma_N \approx \frac{1}{2} \ln \left( \frac{R_L}{Z_N} \right) = A C_N^N \quad \leftarrow \text{A Sanity check!!}$$

**provided** that the value  $A$  is likewise the **approximation** given above.





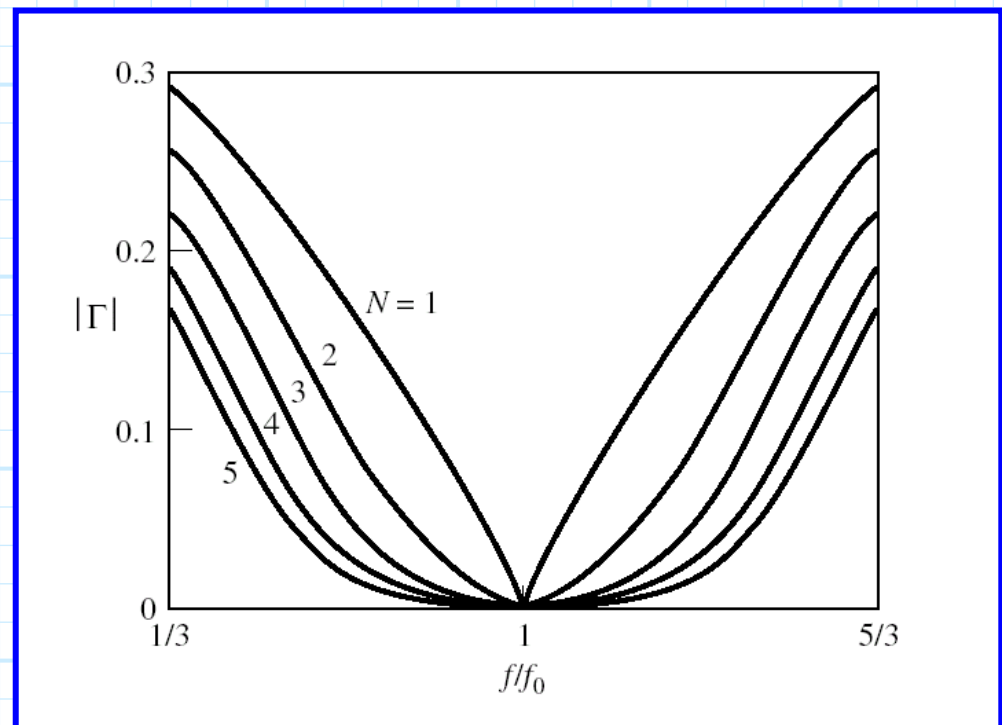
## I still don't understand what just happened

Effectively, these approximations couple the results, such that each value of characteristic impedance  $Z_n$  **approximately** satisfies both  $\Gamma_n$  and  $\Gamma_{n+1}$ . Summarizing:

- \* If you use the “**exact**” design equations to determine the characteristic impedances  $Z_n$ , the **last** value  $\Gamma_N$  will exhibit a **significant** numeric error, and your design **will not** appear to be maximally flat.
- \* If you instead use the “**approximate**” design equations to determine the characteristic impedances  $Z_n$ , **all** values  $\Gamma_n$  will exhibit a **slight** error, but the resulting design **will** appear to be **maximally flat**, Binomial reflection coefficient function  $\Gamma(\omega)$ !



*Note that as we increase the number of sections, the matching bandwidth increases.*

# Bandwidth: How do we define it?


**band-width** (band'width', -witt'h') - noun

1. the range of frequencies within a ....

**Q:** *Can we determine the **value** of this bandwidth?*

**A:** Sure! But we first must **define** what we mean by bandwidth.

As we move from the design (perfect match) frequency  $f_0$  the value  $|\Gamma(f)|$  will **increase**. At some frequency ( $f_m$ , say) the magnitude of the reflection coefficient will increase to some **unacceptably** high value ( $\Gamma_m$ , say). At that point, we **no longer** consider the device to be matched.

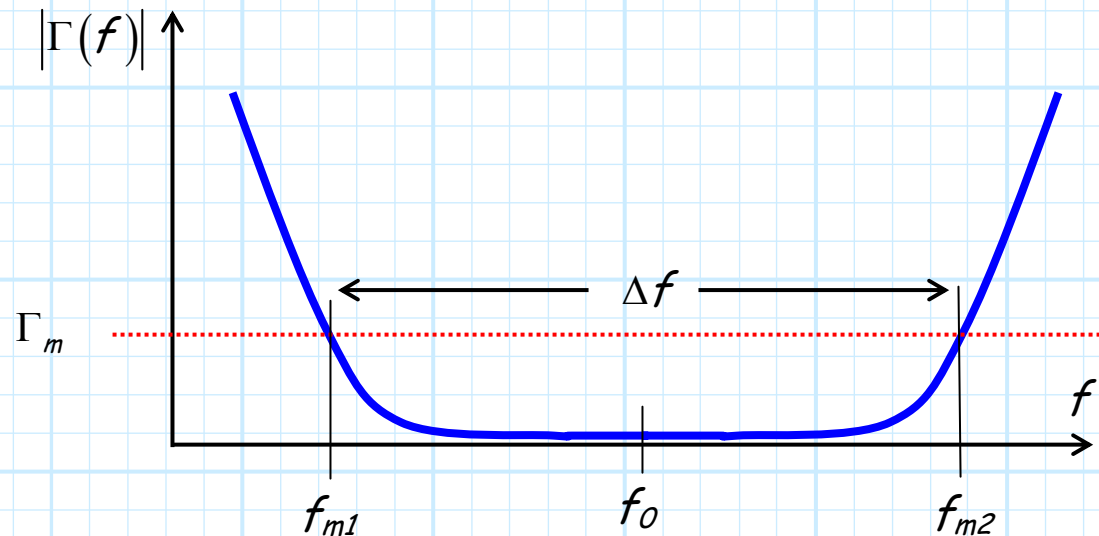

## Bandwidth: How do we calculate it?

Note there are **two** values of frequency  $f_m$ —one value **less** than design frequency  $f_0$ , and one value **greater** than design frequency  $f_0$ .

These two values define the **bandwidth**  $\Delta f$  of the matching network:

$$\Delta f = f_{m2} - f_{m1} = 2(f_0 - f_{m1}) = 2(f_{m2} - f_0)$$


**Q:** So what is the **numerical** value of  $\Gamma_m$ ?

**A:** I don't know—it's up to you to decide!

Every engineer must determine what **they** consider to be an acceptable match (i.e., decide  $\Gamma_m$ ).

This decision depends on the **application** involved, and the **specifications** of the overall microwave system being designed.

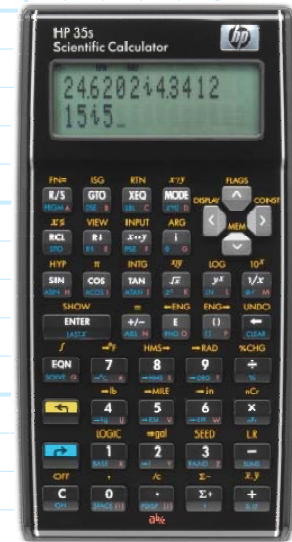However, we **typically** set  $\Gamma_m$  to be 0.2 or less.



## We get to perform some Algebra!!

**Q:** *OK, after we have selected  $\Gamma_m$ , can we determine the two frequencies  $f_m$ ?*

**A:** Sure! We just have to do a little **algebra**.

We start by **rewriting** the Binomial function:

$$\begin{aligned}\Gamma(\theta) &= A(1 + e^{-j2\theta})^N \\ &= Ae^{-jN\theta} (e^{+j\theta} + e^{-j\theta})^N \\ &= Ae^{-jN\theta} (e^{+j\theta} + e^{-j\theta})^N \\ &= Ae^{-jN\theta} (2\cos\theta)^N\end{aligned}$$

Now, we take the **magnitude** of this function:

$$\begin{aligned}|\Gamma(\theta)| &= 2^N |A| |e^{-jN\theta}| |\cos\theta|^N \\ &= 2^N |A| |\cos\theta|^N\end{aligned}$$



## It gets better—even more algebra!

Now, we **define** the values  $\theta$  where  $|\Gamma(\theta)| = \Gamma_m$  as  $\theta_m$ . I.E., :

$$\begin{aligned}\Gamma_m &= |\Gamma(\theta = \theta_m)| \\ &= 2^N |A| |\cos \theta_m|^N\end{aligned}$$



We can now solve for  $\theta_m$  (in **radians!**) in terms of  $\Gamma_m$ :

$$\theta_{m1} = \cos^{-1} \left[ \frac{1}{2} \left( \frac{\Gamma_m}{|A|} \right)^{1/N} \right] \qquad \theta_{m2} = \cos^{-1} \left[ -\frac{1}{2} \left( \frac{\Gamma_m}{|A|} \right)^{1/N} \right]$$

Note that there are **two solutions** to the above equation (one **less** than  $\pi/2$  and one **greater** than  $\pi/2$ )!

Now, we can **convert** the values of  $\theta_m$  into specific **frequencies**.

## Converting $\theta_m$ to $f_m$

Recall that  $\omega T = \theta$ , therefore:

$$\omega_m = \frac{1}{T} \theta_m = \frac{v_p}{\ell} \theta_m$$

But recall also that  $\ell = \lambda_0/4$ , where  $\lambda_0$  is the wavelength at the **design frequency**  $f_0$  (not  $f_m$ !), and where  $\lambda_0 = v_p/f_0$ .

Thus we can conclude:

$$\omega_m = \frac{v_p}{\ell} \theta_m = \frac{4v_p}{\lambda_0} \theta_m = (4f_0) \theta_m$$

or:

$$f_m = \frac{1}{2\pi} \frac{v_p}{\ell} \theta_m = \frac{(4f_0) \theta_m}{2\pi} = \frac{(2f_0) \theta_m}{\pi}$$

where  $\theta_m$  is expressed in **radians**.

## And thus the bandwidth is...

Therefore:

$$f_{m1} = \frac{2f_0}{\pi} \cos^{-1} \left[ + \frac{1}{2} \left( \frac{\Gamma_m}{|A|} \right)^{1/N} \right] \quad f_{m2} = \frac{2f_0}{\pi} \cos^{-1} \left[ - \frac{1}{2} \left( \frac{\Gamma_m}{|A|} \right)^{1/N} \right]$$

Thus, the **bandwidth** of the binomial matching network can be determined as:

$$\begin{aligned} \Delta f &= 2(f_0 - f_{m1}) \\ &= 2f_0 - \frac{4f_0}{\pi} \cos^{-1} \left[ + \frac{1}{2} \left( \frac{\Gamma_m}{|A|} \right)^{1/N} \right] \end{aligned}$$

Note that this equation can be used to determine the **bandwidth** of a binomial matching network, given  $\Gamma_m$  and number of sections  $N$ .

However, it can likewise be used to determine the **number of sections  $N$**  required to meet a specific bandwidth requirement!

## In summary, our design steps

Finally, we can list the **design steps** for a binomial matching network:

1. **Determine** the value  $N$  required to meet the bandwidth ( $\Delta f$  and  $\Gamma_m$ ) requirements.
2. Determine the **approximate** value  $A$  from  $Z_0, R_L$  and  $N$ .
3. Determine the **marginal reflection coefficients**  $\Gamma_n = A C_n^N$  required by the **binomial function**.
4. Determine the characteristic impedance of each section using the **iterative approximation**:

$$Z_{n+1} = Z_n \exp[2\Gamma_n]$$

5. Perform the **sanity check**:

$$\Gamma_N \approx \frac{1}{2} \ln\left(\frac{R_L}{Z_N}\right) = A C_N^N$$

6. Determine section **length**  $l = \lambda_0/4$  for design frequency  $f_0$ .