

# The Directional Coupler

A **directional coupler** is a 4-port network that is designed to **divide** and **distribute** power.



Although this would seem to be a particularly **mundane** and simple task, these devices are both very **important** in microwave systems, and very **difficult** to design and construct.

Two of the **reasons** for this difficulty are our desire for the device to be:

1. Matched
- B. Lossless

Thus, we require a **matched**, **lossless**, and (to make it simple) **reciprocal** 4-port device!

Recall that a matched, lossless, reciprocal, 4-port device was difficult to even **mathematically** determine, as the resulting scattering matrix must be (among other things) **unitary**.



## You must remember this...

However, we were able to determine two possible mathematical solutions, which we called the **symmetric** solution:

$$\mathcal{S} = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$

And the **asymmetric** solution:

$$\mathcal{S} = \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$

wherein for both cases, the relationship:

$$|\alpha|^2 + |\beta|^2 = 1$$

must be true in order for the device to be **lossless** (i.e., for  $\mathcal{S}$  to be unitary).

# The coupling coefficient defines all!


For most couplers we will find that  $\alpha$  and  $\beta$  can (at least ideally) be represented by a real value  $c$ , known as the **coupling coefficient**.

$$\beta = c$$

$$\alpha = \sqrt{1 - c^2}$$


The **symmetric** solution is thus described as:
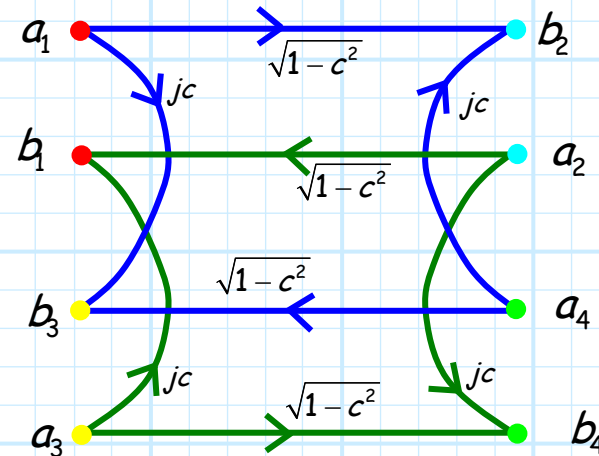
$$\mathbf{S} = \begin{bmatrix} 0 & \sqrt{1-c^2} & jc & 0 \\ \sqrt{1-c^2} & 0 & 0 & jc \\ jc & 0 & 0 & \sqrt{1-c^2} \\ 0 & jc & \sqrt{1-c^2} & 0 \end{bmatrix}$$



And the **asymmetric** solution is:
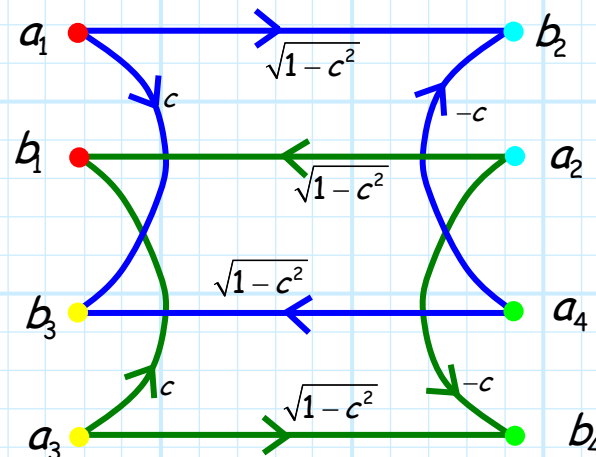
$$\mathbf{S} = \begin{bmatrix} 0 & \sqrt{1-c^2} & c & 0 \\ \sqrt{1-c^2} & 0 & 0 & -c \\ c & 0 & 0 & \sqrt{1-c^2} \\ 0 & -c & \sqrt{1-c^2} & 0 \end{bmatrix}$$



## Let's see how power is divided!

Additionally, for a directional coupler, the coupling coefficient  $c$  will be less than  $1/\sqrt{2}$  **always**. Therefore, we find that:

$$0 \leq c \leq \frac{1}{\sqrt{2}} \quad \text{and} \quad \frac{1}{\sqrt{2}} \leq \sqrt{1-c^2} \leq 1$$

Let's see what this means in terms of the **physical behavior** of a directional coupler!

First, consider the case where some signal is incident on **port 1**, with power  $P_1^+$ . If all other ports are matched, we find that the power flowing out of **port 1** is **zero**:

$$P_1^- = |S_{11}|^2 P_1^+ = 0^2 P_1^+ = 0$$

while **a lot** of power leaves **port 2**:

$$P_2^- = |S_{21}|^2 P_1^+ = (1-c^2) P_1^+$$


and **a little** power is coupled out of **port 3**:

$$P_3^- = |S_{31}|^2 P_1^+ = c^2 P_1^+$$

Finally, we find there is **no power** flowing out of **port 4**:  $P_4^- = |S_{41}|^2 P_1^+ = 0^2 P_1^+ = 0$

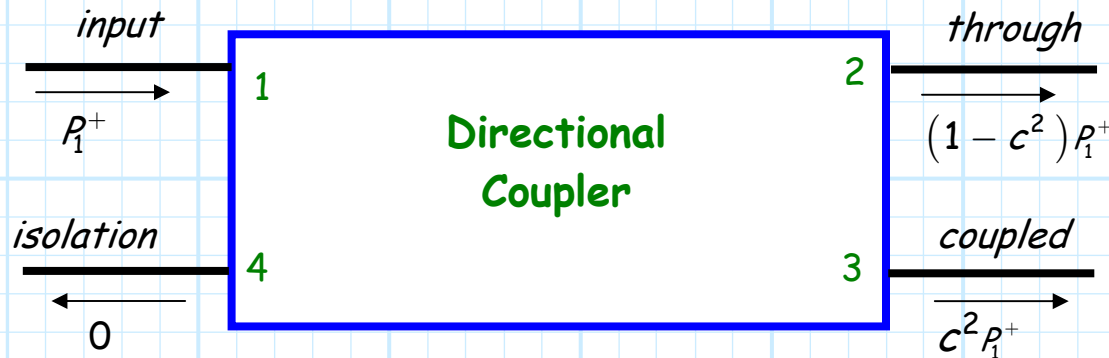
## Remember, the device has $D_2$ symmetry

In the terminology of the directional coupler, we say that port 1 is the **input** port, port 2 is the **through** port, port 3 is the **coupled** port, and port 4 is the **isolation** port.



Note however, that **any** of the coupler ports can be an input, with a different through, coupled and isolation port for each case.

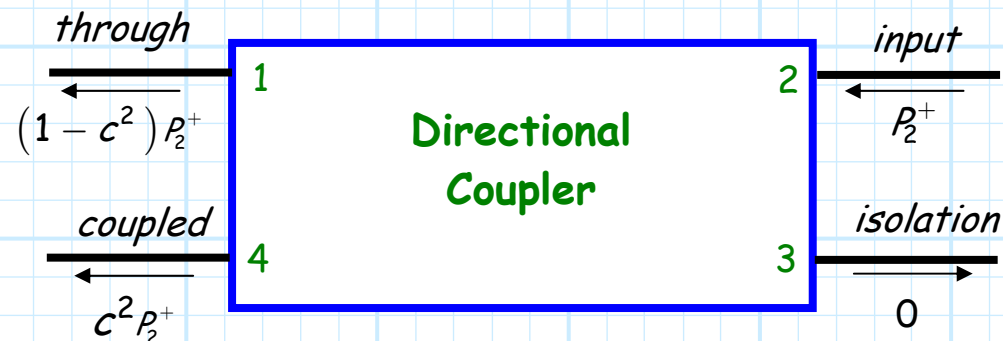For example, if a signal is incident on **port 2**, while all other ports are matched, we find that:



## A big table to reinforce the point

Thus, from the scattering matrix of a directional coupler, we can form the following table:

<i>Input</i>	<i>Through</i>	<i>Coupled</i>	<i>Isolation</i>
Port 1	Port 2	Port 3	Port 4
Port 2	Port 1	Port 4	Port 3
Port 3	Port 4	Port 1	Port 2
Port 4	Port 3	Port 2	Port 1

## Really; is this thing at all useful?

Typically, the coupling coefficients for a directional coupler are in the range of approximately:

$$0.25 > c^2 > 0.0001$$

As a result, we find that  $\sqrt{1 - c^2} \approx 1$ . What this means is that the power out of the **through** port is just **slightly smaller** (typically) than the power incident on the input port.

Likewise, the power out of the **coupling** port is typically a **small fraction** of the power incident on the input port.



**Q:** *Pffft! Just a **small fraction** of the input power! What is the use in doing that??*

**A:** A directional coupler is often used for **sampling** a small portion of the signal power. For example, we might **measure** the output power of the **coupled** port (e.g.,  $P_3^-$ ) and then we can determine the amount of signal power flowing through the device (e.g.,  $P_1^+ = P_3^- / c^2$ )

# Alas, the ideal device is a mythical device



Unfortunately, the **ideal** directional coupler **cannot** be built! For example, the input match is never **perfect**, so that the diagonal elements of the scattering matrix, although **very small**, are not zero.

Likewise, the isolation port is never **perfectly** isolated, so that the values  $S_{41}$ ,  $S_{32}$ ,  $S_{23}$  and  $S_{14}$  are also non-zero—some **small** amount of power leaks out!

As a result, the through port will be **slightly less** than the value  $\sqrt{1 - c^2}$ . The scattering matrix for a **non-ideal coupler** would therefore be:

$$\mathcal{S} = \begin{bmatrix} S_{11} & S_{21} & jc & S_{41} \\ S_{21} & S_{11} & S_{41} & jc \\ jc & S_{41} & S_{11} & S_{21} \\ S_{41} & jc & S_{21} & S_{11} \end{bmatrix}$$

From **this** scattering matrix, we can extract **some important parameters** about directional couplers!



## Coupling $C$

The **coupling** value is the ratio of the coupled output power ( $P_3^-$ ) to the input power ( $P_1^+$ ), expressed in decibels:

$$C \text{ (dB)} = 10 \log_{10} \left[ \frac{P_1^+}{P_3^-} \right] = -10 \log_{10} |jc|^2$$

This is the **primary** specification of a directional coupler!

Note the **larger** the coupling value, the **smaller** the coupled power!

For example:

A **6 dB** coupler couples out **25%** of the input power.

A **10 dB** coupler couples out **10%** of the input power.

A **20 dB** coupler couples out **1.0%** of the input power.

A **30 dB** coupler couples out **0.1%** of the input power.

## Directivity $D$

The **directivity** is the ratio of the power **out** of the coupling port ( $P_3^-$ ) to the power **out** of the isolation port ( $P_4^-$ ), expressed in decibels.

$$D(dB) = 10 \log_{10} \left[ \frac{P_3^-}{P_4^-} \right] = 10 \log_{10} \left[ \frac{|j_c|^2}{|S_{41}|^2} \right]$$

This value indicates how effective the device is in "**directing**" the coupled energy into the correct port (i.e., into the coupled port, **not** the isolation port).

**Ideally** this is infinite (i.e.,  $P_4^- = 0$ ), so the **higher** the directivity, the **better**.

## Isolation $I$

**Isolation** is the ratio of the **input power** ( $P_1^+$ ) to the power out of the **isolation port** ( $P_4^-$ ), expressed in decibels.

$$I (dB) = 10 \log_{10} \left[ \frac{P_1^+}{P_4^-} \right] = -10 \log_{10} [ |S_{41}|^2 ]$$

This value indicates how "isolated" the isolation port actually is.

**Ideally** this is infinite (i.e.,  $P_4^- = 0$ ), so the **higher** the isolation, the better.

Note that isolation, directivity, and coupling are **not** independent values! **You** should be able to quickly show that:

$$I (dB) = C (dB) + D (dB)$$

## Mainline Loss $ML$

The **mainline loss** is the ratio of the **input** power ( $P_1^+$ ) to the power out of the **through** port ( $P_2^-$ ), expressed in decibels.

$$ML(dB) = 10 \log_{10} \left[ \frac{P_1^+}{P_2^-} \right] = -10 \log_{10} [ |S_{21}|^2 ]$$

It indicates how much power the signal **loses** as it travels from the input to the through port.

## Coupling Loss $CL$

The **coupling loss** indicates the **portion** of the mainline loss that is due to coupling some of the input power into the coupling port.

$$CL(dB) = 10 \log_{10} \left[ \frac{P_1^+}{P_1^+ - P_3^-} \right] = -10 \log_{10} \left[ 1 - |jc|^2 \right]$$

Conservation of energy makes this loss is **unavoidable**.

Note this value can be **very small**, for example:

The coupling loss of a **10dB** coupler is **0.44 dB**

The coupling loss of a **20dB** coupler is **0.044 dB**

The coupling loss of a **30dB** coupler is **0.0044 dB**

## Insertion Loss $IL$

**Q:** *But wait, shouldn't  $P_1^+ - P_3^- = P_2^-$ , meaning the coupling loss and the mainline loss will be the same exact value?*

**A:** Ideally this would be true.


But, the reality is that couplers are **not perfectly lossless**, so there will additionally be loss due to **absorbed** energy (i.e., heat). This loss is called **insertion loss** and is simply the **difference** between the mainline loss and coupling loss:

$$IL(dB) = ML(dB) - CL(dB)$$

The insertion loss thus indicates the portion of the mainline loss that is **not** due to coupling some input power to the coupling port. This insertion loss is avoidable, and thus the **smaller** the insertion loss, the better.

For couplers with **very small coupling** coefficients (e.g.,  $C(dB) > 20$ ) the coupling loss is so small that the mainline loss is almost entirely due to insertion loss (i.e.,  $ML = IL$ )—often then, the two terms are used **interchangeably**.

## A photo of a microstrip coupler

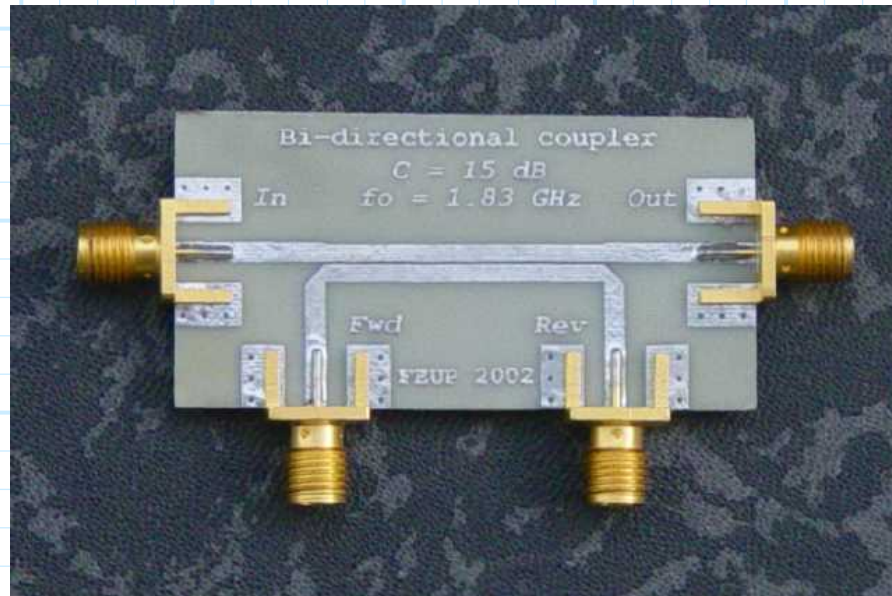

From: [paginas.fe.up.pt/~hmiranda/etele/microstrip/](http://paginas.fe.up.pt/~hmiranda/etele/microstrip/)