

# The Ideal Gain Element

Recall that the maximum possible transducer gain, **given a specific gain element**, and a source and load impedance of  $Z_0$  is:

$$G_{Tmax} = \frac{1}{1 - |\Gamma_s|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_L S_{22}|^2}$$

By properly constructing input and output matching networks, we can maximize the transducer gain—it's the largest value that we can get for **that particular gain element**.

→ But what if this gain is insufficient?


In that case we must **change the gain element**, but what should we change the gain element to? What are the characteristics of an **ideal gain element**?

The answers to these questions are best determined by examining the maximum **unilateral** transducer gain:

$$G_{UTmax} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}$$

Recall that for most gain elements,  $|S_{12}|$  is small (i.e., approximately unilateral), and in fact  $S_{12} = 0$  is **one** ideal characteristic of an **ideal gain element**.

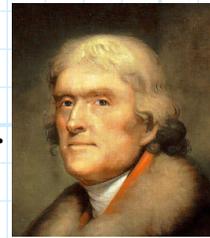From the maximum unilateral gain expression, we can determine the remaining **ideal characteristics** of a gain element. Some of these results are rather **self-evident**, but others are a bit **surprising!**



For example, it is clear that **gain** is increased as  $|S_{21}|$  is **maximized**—no surprise here. What might catch you off guard are the conclusions we reach when we observe the **denominator** of  $G_{UTmax}$ :



$$G_{UTmax} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}$$

It appears that the gain will go to **infinity** if  $|S_{11}| = 1$  and/or  $|S_{22}| = 1$ !

**Q:** *But that would mean the input and/or output impedance of the gain element is **purely reactive** (e.g. and open or a short). Is this conclusion **accurate**?*

**A:** Yes and no.

Remember, this maximum gain is achieved when we establish a **conjugate match**. The equation above says that this maximum gain will increase to infinity if we match to a **reactive** input/output impedance.

And **that's** the catch.

→ It is **impossible** to match  $Z_0$  to load that is purely reactive!


We can only match to an impedance that has a **non-zero resistive component** (i.e.,  $|\Gamma| < 1$ ); otherwise, there's no way for the available power can be **absorbed!**

Still, it is quite evident that—all other things being equal—a gain element with **larger values** of  $|S_{11}|$  and  $|S_{22}|$  will produce **more gain** than gain elements with smaller values of  $|S_{11}|$  and  $|S_{22}|$ .

**Q:** *This seems very counter intuitive; I would think that an inherently **better-matched** gain element (e.g.,  $|S_{11}| \approx 0$  and  $|S_{22}| \approx 0$ ) would provide **more gain**.*

**A:** It does doesn't it?

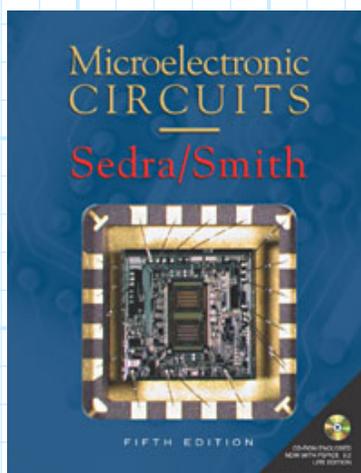
**But** remember back to your initial academic discussion of amplifiers (probably **way** back in an undergraduate **electronics course**).



Recall you studied **four types** of amplifier (gain element) models: voltage gain, current gain, trans-impedance, and trans-conductance. Each of these amplifiers was likewise characterized in terms of its **input impedance** and its **output impedance**.

Recall also that for each of these models, the **ideal** values of input/output impedance was **always** either zero (a short) or infinity (an open)!

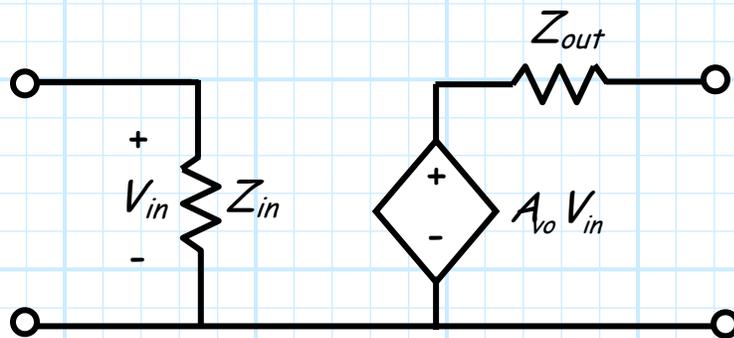In other words, **ideal amplifiers (gain elements)** always have  $S_{11} = S_{22} = 0$ !



Ideally:

$|Z_{in}|$  very small

$|Z_{out}|$  very small

$|A_{vo}|$  very small

For example, an **ideal voltage amplifier** has a **high input impedance** ( $|S_{11}| \approx 1$ ) and a **low output impedance** ( $|S_{22}| \approx 1$ ). If we construct matching networks on either side of this ideal gain element, the result is an amplifier with **very high transducer gain**!

**Q:** So how do we "**change**" a gain element to a **more ideal** one?

**A:** Of course we could always select a **different** transistor, but we also could simply change the **DC bias** of the transistor we are using!

Recall the **small-signal parameters** (and thus the scattering parameters) of a transistor change as we modify the **DC bias** values. We can select our DC bias such that the value of  $G_{TUmax}$  **is maximized**.

**Q:** *Is there any **downside** to this approach?*

**A:** Absolutely! Recall that we can theoretically match to a very low or very high resistance—at precisely **one frequency!** But we found that the resulting match will typically be **extremely narrowband** for these cases.

Thus, we might consider **reducing** the amplifier gain (i.e., reducing the values  $|S_{11}|$  and  $|S_{22}|$ ), in return for achieving a more moderate gain over a **wider frequency bandwidth!**

Additionally, DC bias likewise affects **other** amplifier characteristics, including compression points and noise figure!