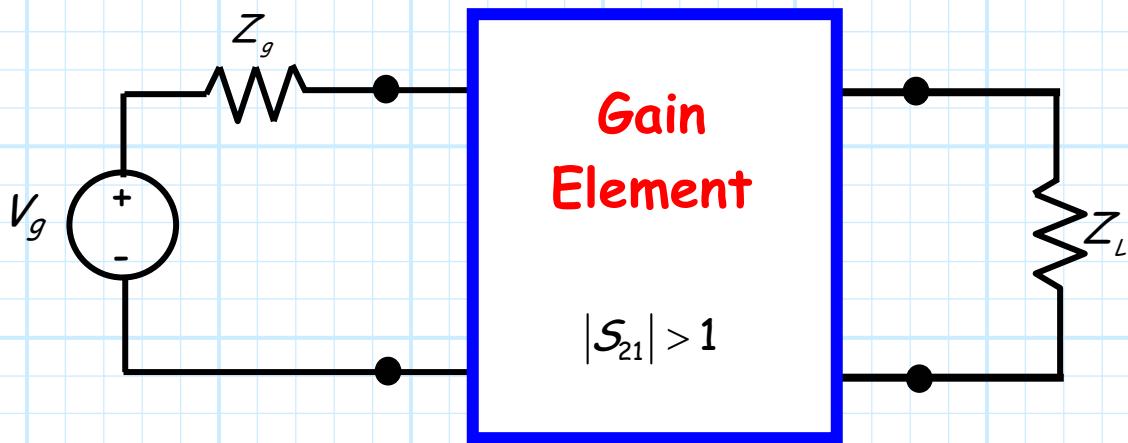



# The Powers that Be

To begin our discussion of **amplifiers**, we first must define and derive a number of quantities that describe the **rate of energy flow** (i.e., power).

Consider a source and a load that are connected together by some gain element:




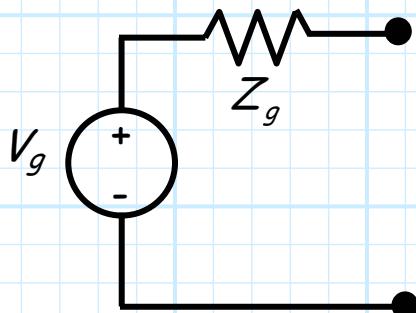The first power we consider is the **available power from the source**:




$P_{avs} \doteq$  available power from the source

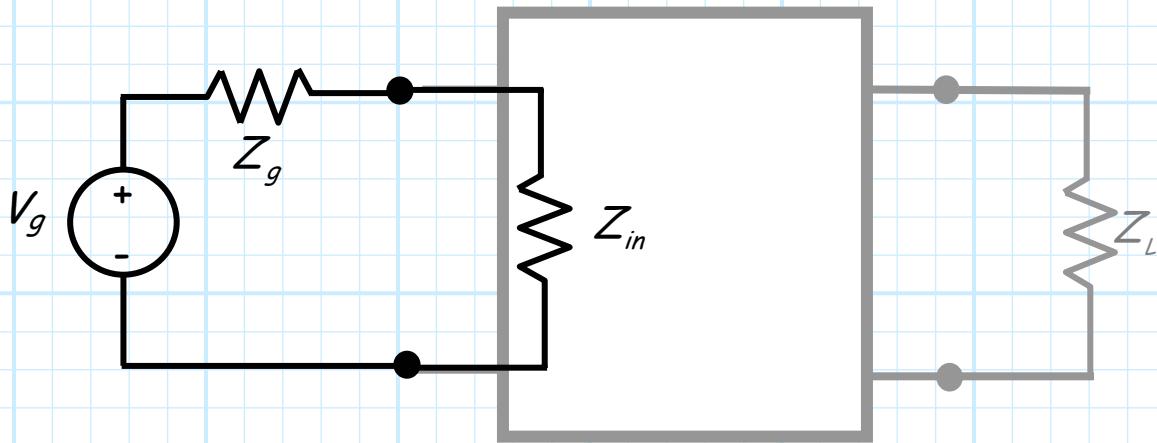
We likewise consider the power  $P_{in}$  delivered by the source; in other words the power **absorbed** by the input impedance of the gain element with a load attached:



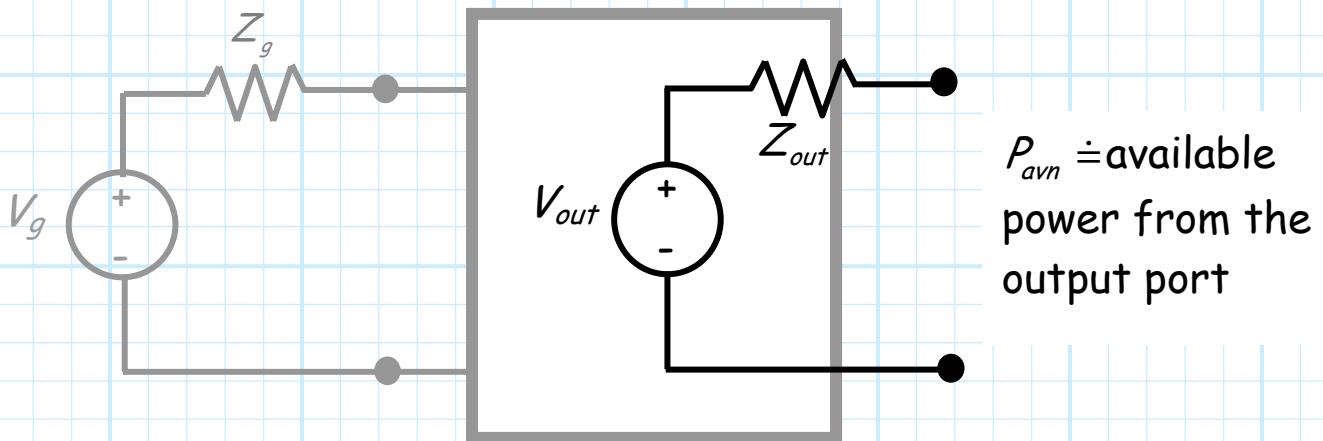On the output, we consider the power **available** from the **output** of the gain element:



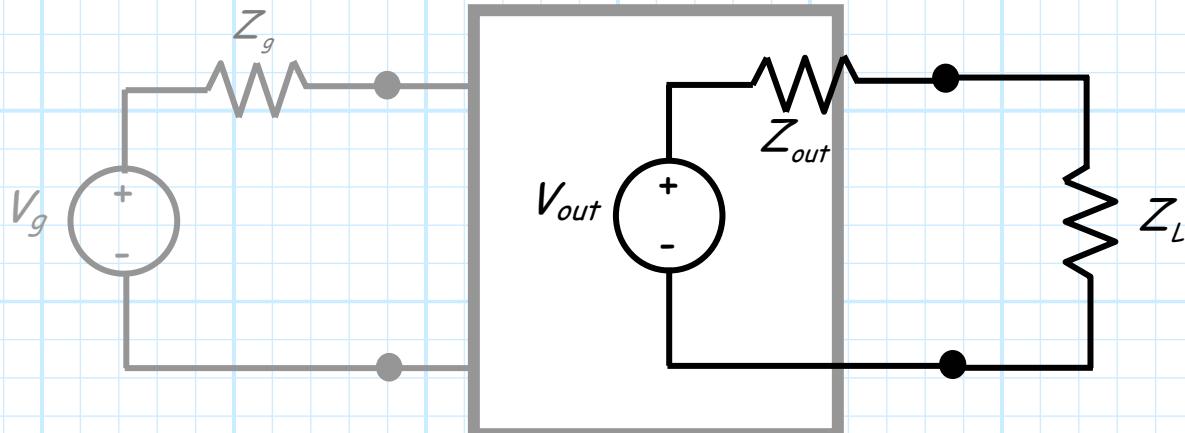And finally, we consider the power  $P_L$  **delivered** by the output port—the power absorbed by load  $Z_L$ :



These four power quantities depend (at least in part) on the source parameters  $V_g$  and  $Z_g$ , load  $Z_L$ , and the scattering parameters of  $S_{11}, S_{21}, S_{22}, S_{12}$  the gain element.


**Q:** Yikes! How can we possibly determine the power values in terms of these circuit parameters?

**A:** Remember, the source, load and gain element (i.e. its scattering matrix) each are described by a set of equations. We simply need to solve these simultaneous equations!

Your text (pages 537-539) provides an algebraic solution. But you know me; I prefer to graphically solve the algebra using signal flow graphs!

**Q:** But there's a source in our circuit: How do we handle that in a signal flow graph?

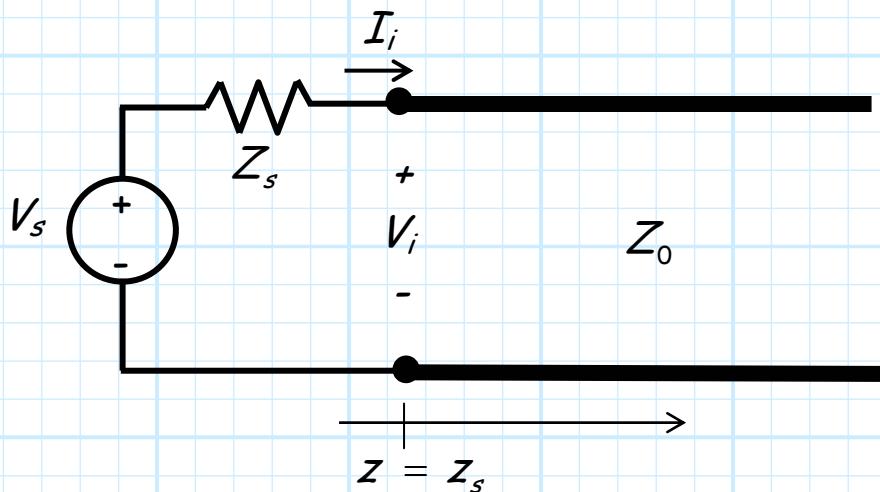**A:** Consider a simple source connected to a transmission line:



From KVL we know that:

$$V_s = V_i + Z_s I_i$$

Whereas, from the telegraphers equations we know that:

$$V_i = V(z = z_s) = V_0^+ e^{-j\beta z_s} + V_0^- e^{+j\beta z_s}$$

$$I_i = I(z = z_s) = \frac{V_0^+}{Z_0} e^{-j\beta z_s} - \frac{V_0^-}{Z_0} e^{+j\beta z_s}$$

Substituting the definitions:

$$a_s \doteq V_0^- e^{+j\beta z_g} \text{ (complex amplitude of voltage wave incident on source)}$$

$$b_s \doteq V_0^+ e^{-j\beta z_g} \text{ (complex amplitude of voltage wave exiting source)}$$

we get:

$$V_i = V(z = z_s) = b_s + a_s$$

$$I_i = I(z = z_s) = \frac{b_s}{Z_0} - \frac{a_s}{Z_0}$$

And then our KVL equation can be written as:

$$V_s = (b_s + a_s) + \frac{Z_s}{Z_0} (b_s - a_s)$$

And rearranging:

$$b_g = \left( \frac{Z_0}{Z_g + Z_0} \right) V_g + \Gamma_g a_g$$

**Reluctantly defining a "reflection coefficient":**

$$\Gamma_s \doteq \frac{Z_s - Z_0}{Z_s + Z_0} \quad (\text{Doh!})$$


we find by rearranging:

$$\frac{Z_0}{Z_0 + Z_s} = \frac{1 - \Gamma_s}{2}$$


and so:

$$b_s = \left( \frac{1 - \Gamma_s}{2} \right) V_s + \Gamma_s a_s$$

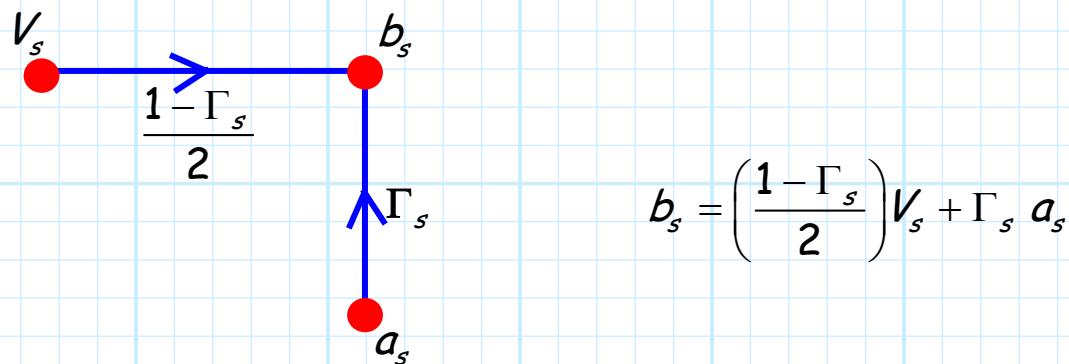We can express the above result graphically using a signal-flow graph:



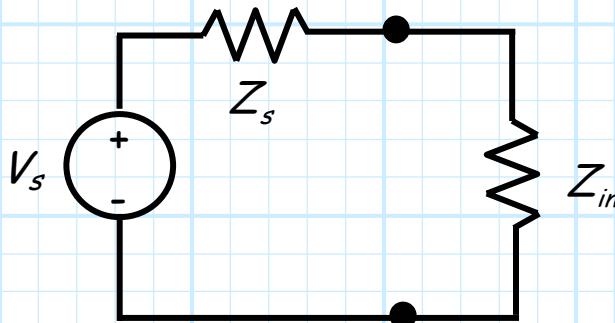
Now, consider the case where we place a load (e.g., the input impedance of a two port network) at this source port:




We know from transmission line theory that:

$$\Gamma_{in} = \frac{V_0^- e^{+j\beta z_s}}{V_0^+ e^{-j\beta z_s}} = \frac{a_s}{b_s} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

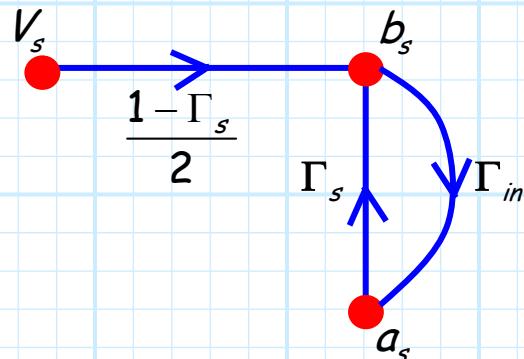
Thus, the relationship  $a_s = \Gamma_{in} b_s$  can be added to the signal flow graph:



Using the splitting rule:

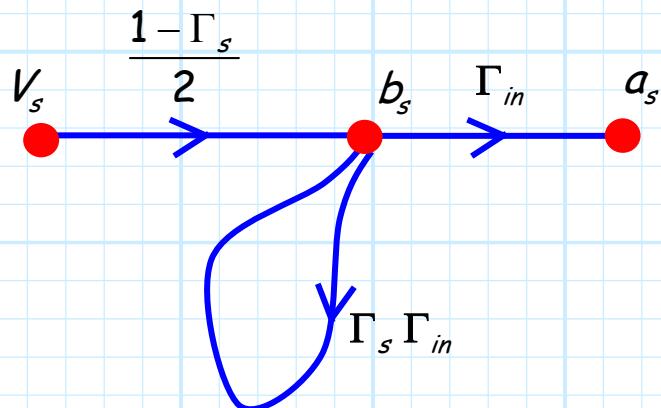

and then the self-loop rule:

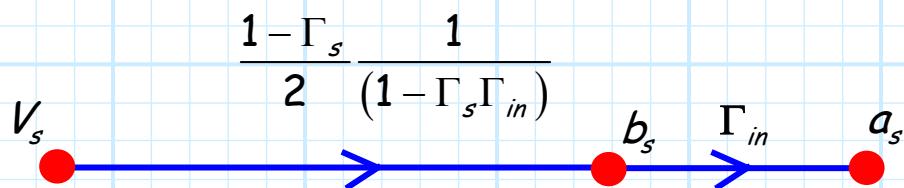

we can directly conclude that:

$$b_s = V_s \frac{1 - \Gamma_s}{2} \frac{1}{1 - \Gamma_s \Gamma_{in}}$$

$$a_s = V_s \frac{1 - \Gamma_s}{2} \frac{\Gamma_{in}}{1 - \Gamma_s \Gamma_{in}}$$

Note that the power **incident** on the load can now be determined:

$$P_{inc} = \frac{|b_s|^2}{2Z_0} = \frac{|V_s|^2}{8Z_0} \frac{|1 - \Gamma_s|^2}{|1 - \Gamma_s \Gamma_{in}|^2}$$

as well as the power **reflected** from the load:

$$P_{ref} = \frac{|a_s|^2}{2Z_0} = \frac{|V_s|^2}{8Z_0} \frac{|1 - \Gamma_s|^2}{|1 - \Gamma_s \Gamma_{in}|^2} |\Gamma_{in}|^2$$

so that the power absorbed by the load (i.e. the power **delivered** by the source) is:

$$\begin{aligned} P_{in} &= P_{inc} - P_{ref} \\ &= \frac{|b_s|^2 - |a_s|^2}{2Z_0} \\ &= \frac{|V_s|^2}{8Z_0} \frac{|1 - \Gamma_s|^2}{|1 - \Gamma_s \Gamma_{in}|^2} (1 - |\Gamma_{in}|^2) \\ &= \frac{|V_s|^2}{2Z_0} \left| \frac{Z_0}{Z_0 + Z_s} \right|^2 \frac{1 - |\Gamma_{in}|^2}{|1 - \Gamma_s \Gamma_{in}|^2} \end{aligned}$$


It is evident from the result above that the amount of power delivered is **dependent** on the value of **load impedance**. To maximize this power, we must find the value  $\Gamma_{in}$  that maximizes the term:

$$\frac{1 - |\Gamma_{in}|^2}{|1 - \Gamma_s \Gamma_{in}|^2}$$


It can be shown that this term is maximized when  $\Gamma_{in} = \Gamma_s^*$ . No surprise here; the load must be **conjugate matched** to the source in order to maximize power transfer. This maximum value—resulting only when the load is conjugate matched to the source—is referred to as the **available power** of the source:

$$\begin{aligned}
 P_{avS} &= P_{in} \Big|_{\Gamma_{in}=\Gamma_s^*} \\
 &= \frac{|V_s|^2}{8Z_0} \frac{|1-\Gamma_s|^2}{1-|\Gamma_s|^2} \\
 &= \frac{|V_s|^2}{2Z_0} \left| \frac{Z_0}{Z_0 + Z_s} \right|^2 \frac{1}{1-|\Gamma_s|^2} \\
 &= \frac{1}{2} |V_s|^2 \frac{1}{4 \operatorname{Re}\{Z_s^*\}}
 \end{aligned}$$

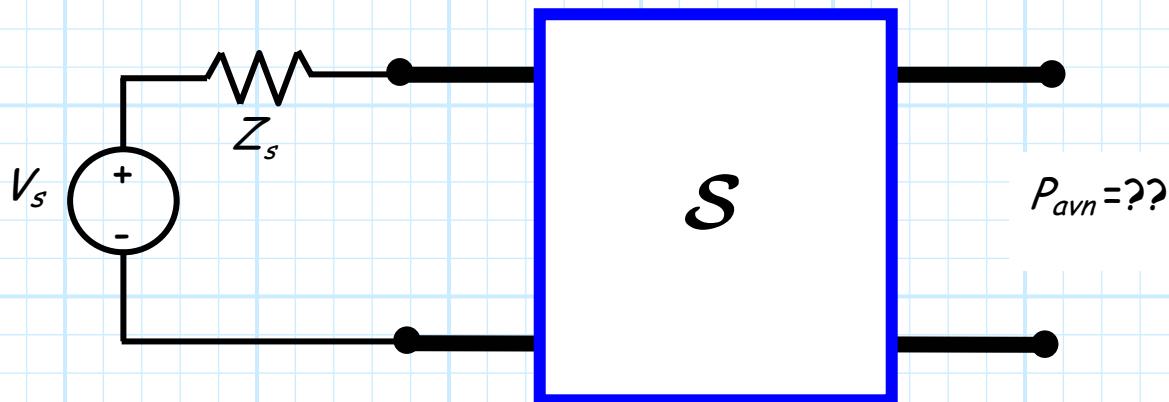
Now, consider the case where we connect some arbitrary **two-port device** to the source. We would like to determine the **available power**  $P_{avn}$  from the output port of this two-port device.




The signal-flow graph for this network:

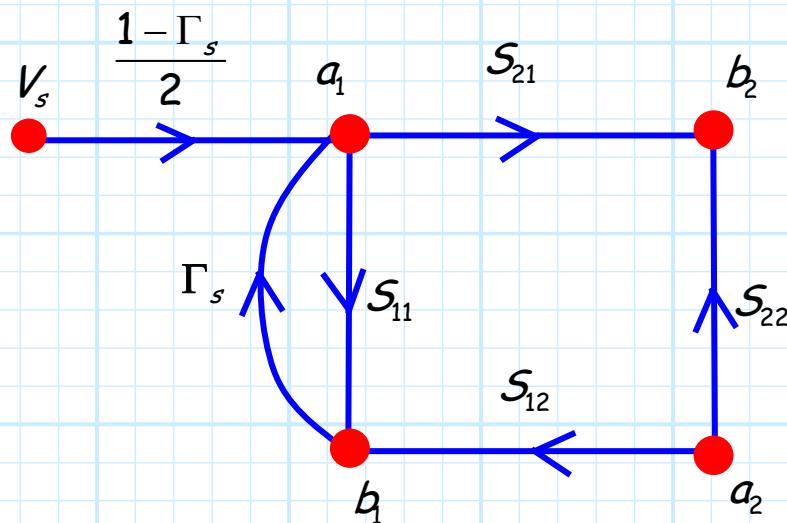


We can reduce this signal-flow graph:

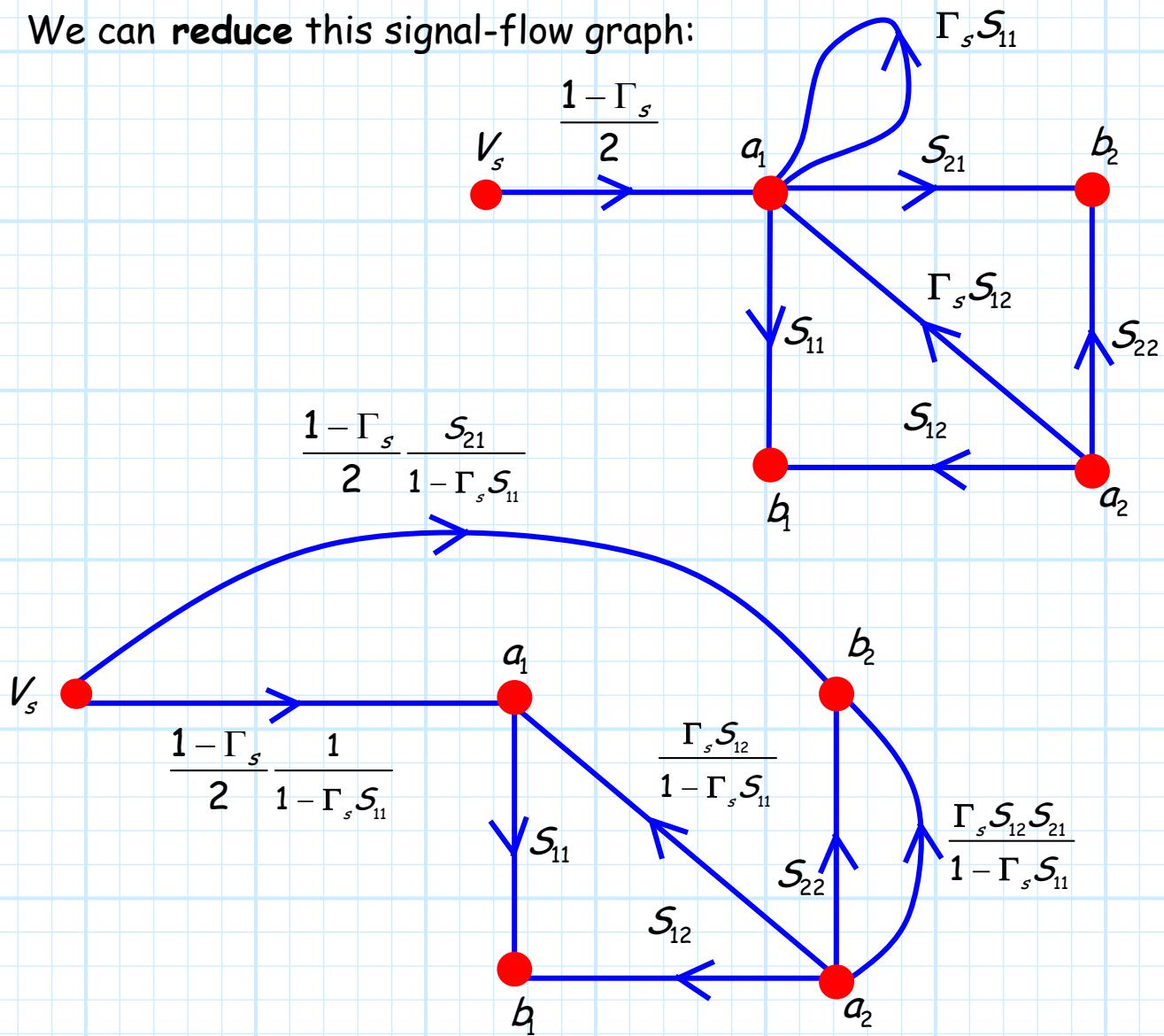


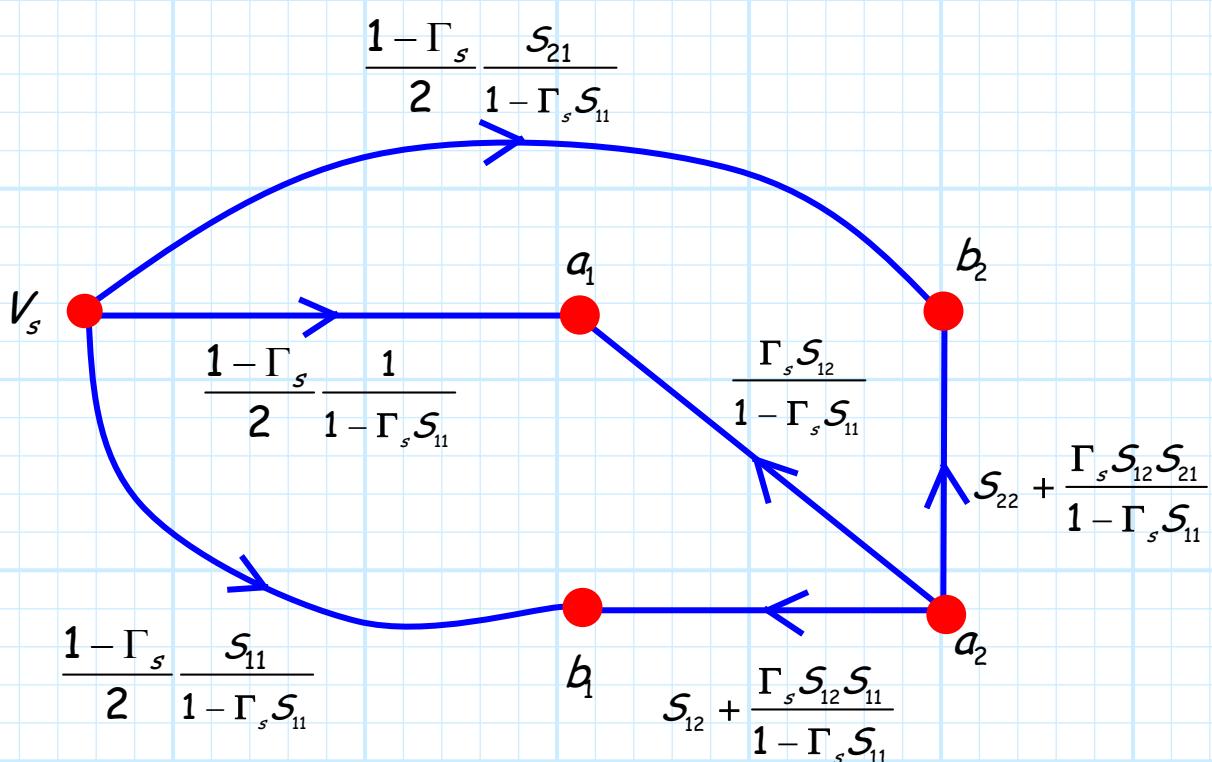

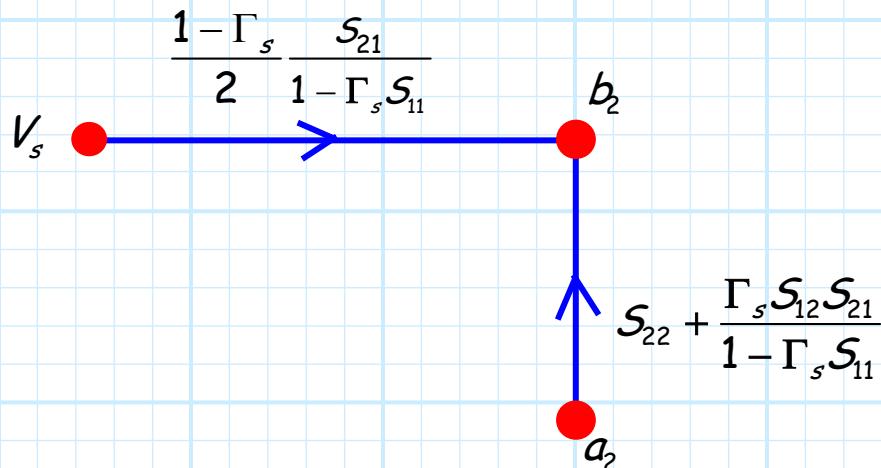Now, for the purposes of determining the output power at port 2, we can ignore nodes  $a_1$  and  $b_1$  (in the final signal flow-graph above they are terminal nodes, no branches are leaving these nodes). Thus, the relevant portion of the reduced signal flow graph is:



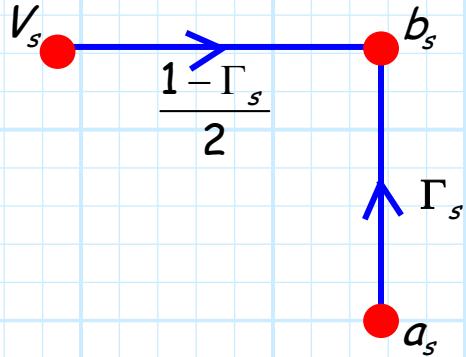Notice this signal flow graph has the same form as the source signal-flow graph:




To make this comparison more specific, we **define** variables:

$$V_{out} \doteq V_s \frac{1 - \Gamma_s}{1 - \Gamma_{out}} \frac{S_{21}}{1 - \Gamma_s S_{11}}$$


$$\Gamma_{out} \doteq S_{22} + \frac{\Gamma_s S_{12} S_{21}}{1 - \Gamma_s S_{11}}$$

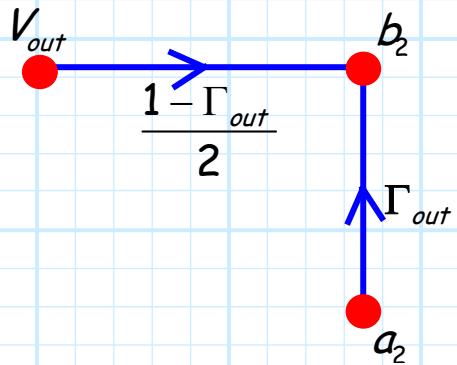And thus, using these definitions, our signal flow graph can be **equivalently** written as:




It is apparent that  $V_{out}$  and  $\Gamma_{out}$  define an **equivalent source** created when the original source is connected to a two-port device.

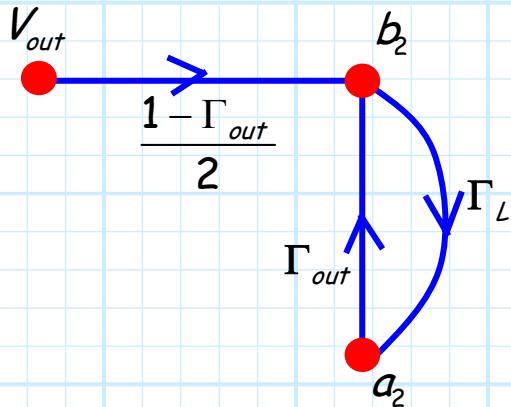Thus, when some load is connected to the output of the two-port device, the signal-flow graph is:



Which has precisely the same form as:

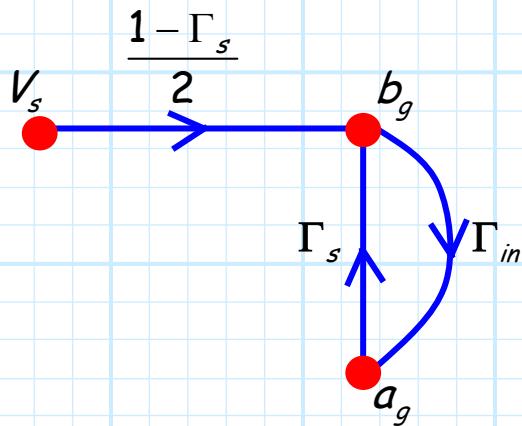

As a result, the delivered power is precisely the same as the original case, with the exception that we use the equivalent values defined above:

$$\begin{aligned}
 P_L &= \frac{|b_2|^2 - |a_2|^2}{2Z_0} \\
 &= \frac{|V_{out}|^2}{8Z_0} \frac{|1 - \Gamma_{out}|^2}{|1 - \Gamma_{out} \Gamma_L|^2} (1 - |\Gamma_L|^2) \\
 &= \frac{|V_s|^2}{8Z_0} \frac{|S_{21}|^2}{|1 - \Gamma_s S_{11}|^2} \frac{|1 - \Gamma_s|^2}{|1 - \Gamma_{out} \Gamma_L|^2} (1 - |\Gamma_L|^2)
 \end{aligned}$$

Likewise, the **available power** from port 2 is simply the maximum possible power absorbed by a load  $\Gamma_L$ . This again is found by maximizing the term:

$$\frac{1 - |\Gamma_L|^2}{|1 - \Gamma_{out} \Gamma_L|^2}$$

which **again** occurs when  $\Gamma_L = \Gamma_{out}^*$ . Thus, maximum power transfer occurs when the load is **conjugate matched** to the **equivalent source impedance**  $Z_{out}$  ( $\Gamma_{out}$ ). As a result the **available power** from port 2 is:

$$\begin{aligned} P_{avn} &= P_L \Big|_{\Gamma_L = \Gamma_{out}^*} \\ &= \frac{|V_s|^2}{8Z_0} \frac{|\mathcal{S}_{21}|^2}{|1 - \Gamma_s \mathcal{S}_{11}|^2} \frac{|1 - \Gamma_s|^2}{|1 - \Gamma_{out} \Gamma_{out}^*|^2} (1 - |\Gamma_{out}|^2) \\ &= \frac{|V_s|^2}{8Z_0} \frac{|\mathcal{S}_{21}|^2}{|1 - \Gamma_s \mathcal{S}_{11}|^2} \frac{|1 - \Gamma_s|^2}{(1 - |\Gamma_{out}|^2)^2} (1 - |\Gamma_{out}|^2) \\ &= \frac{|V_s|^2}{8Z_0} \frac{|\mathcal{S}_{21}|^2}{|1 - \Gamma_s \mathcal{S}_{11}|^2} \frac{|1 - \Gamma_s|^2}{1 - |\Gamma_{out}|^2} \end{aligned}$$