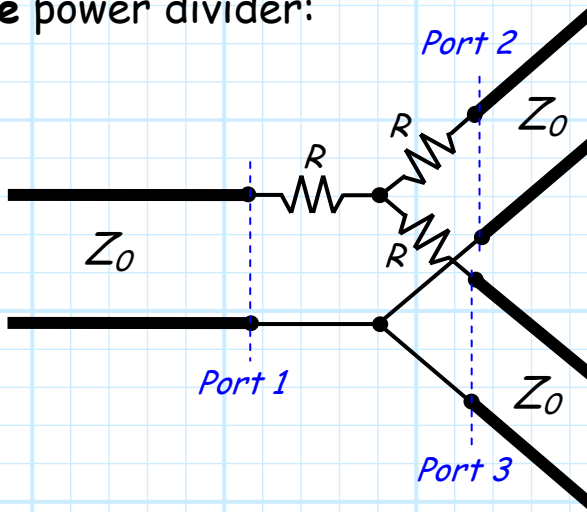



# The Resistive Divider

Consider the **resistive** power divider:



This symmetric power divider will be matched at port 1 if  $R$  is selected as:
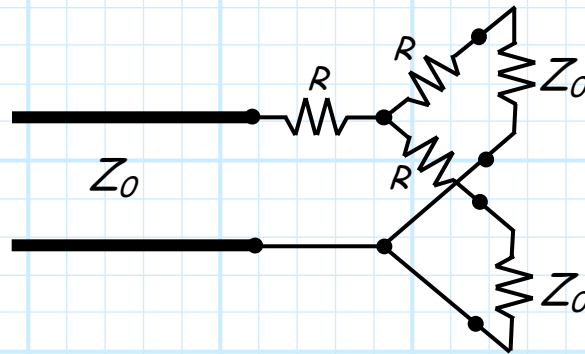
$$\begin{aligned} Z_0 &= R + (R + Z_0) \parallel (R + Z_0) \\ &= R + \frac{R + Z_0}{2} \\ &= 1.5R + \frac{Z_0}{2} \end{aligned}$$



Solving this equation, we find that port 1 is matched if:


$$R = \frac{Z_0}{3}$$

From the **symmetry** of the circuit, we find that all the **other** ports will be matched as well (i.e.,  $S_{11} = S_{22} = S_{33} = 0$ ).  
Moreover, it can be shown that:

$$S_{12} = S_{21} = S_{31} = S_{31} = S_{23} = S_{32} = \frac{1}{2}$$

So:
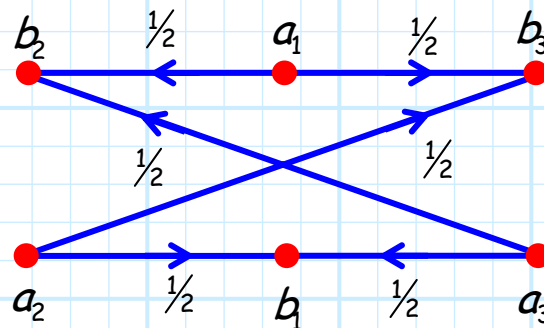
$$\mathbf{S} = \begin{bmatrix} 0 & \frac{1}{2} & \frac{1}{2} \\ \frac{1}{2} & 0 & \frac{1}{2} \\ \frac{1}{2} & \frac{1}{2} & 0 \end{bmatrix}$$



Note the magnitude of each column is less than one. E.G.,:

$$|S_{21}|^2 + |S_{31}|^2 = \frac{1}{2} < 1$$

Therefore this power divider is **lossy**!

In fact, we find that the power out of each port is just **one-quarter** of the input power:

$$P_2^- = P_3^+ = \frac{P_1^+}{4}$$

In other words, **half** the input power is **absorbed** by the divider!