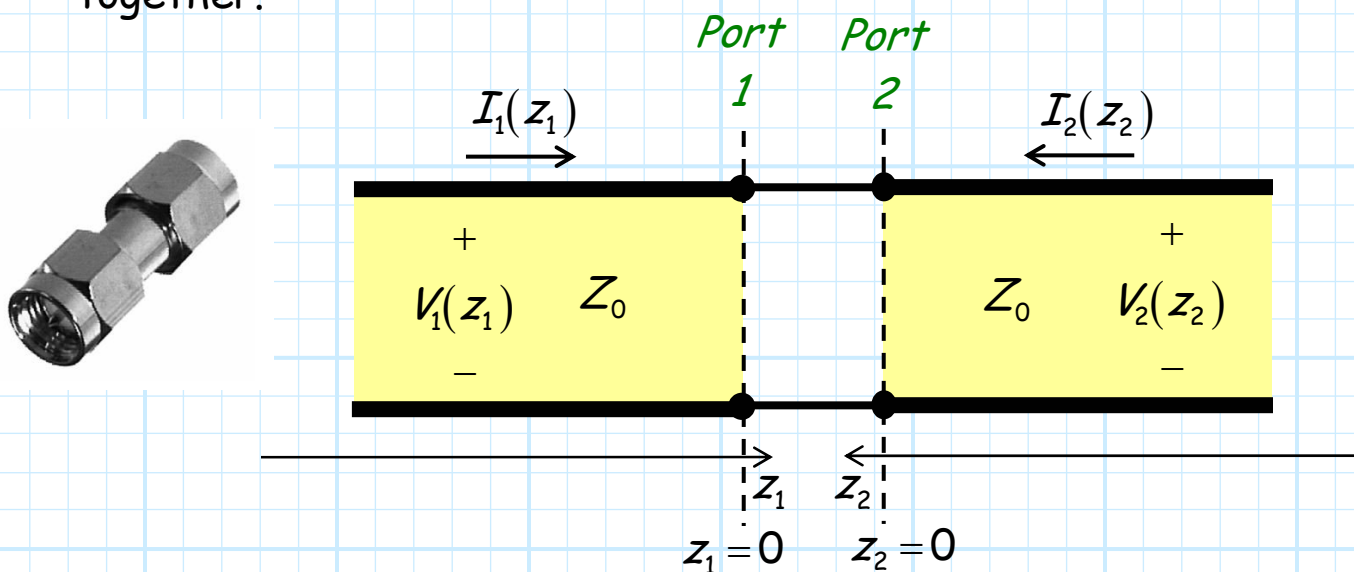


# Example: The Scattering Matrix of a Connector

First, let's consider the scattering matrix of a **perfect connector**—an electrically **very small** two-port device that allows us to connect the ends of different transmission lines together.



If the connector is ideal, then it will exhibit **no series inductance nor shunt capacitance**, and thus from KVL and KCL:

$$V_1(z_1=0) = V_2(z_2=0) \quad I_1(z_1=0) = -I_2(z_2=0)$$

Terminating **port 2 in a matched load**, and then analyzing the resulting circuit, we find that (not surprisingly!):

$$V_{01}^- = 0 \quad \text{and} \quad V_{02}^- = V_{01}^+$$

From this we conclude that (since  $V_{02}^+ = 0$ ):

$$S_{11} = \frac{V_{01}^-}{V_{01}^+} = \frac{0}{V_{01}^+} = 0.0$$

$$S_{21} = \frac{V_{02}^-}{V_{01}^+} = \frac{V_{01}^+}{V_{01}^+} = 1.0$$


This two-port device has  $D_2$  symmetry (a plane of bilateral symmetry), meaning:

$$S_{22} = S_{11} = 0.0 \quad \text{and} \quad S_{21} = S_{12} = 1.0$$


The **scattering matrix** for such this ideal connector is therefore:

$$S = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$$

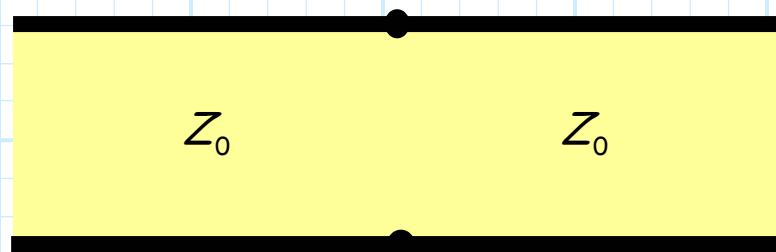As a result, the perfect connector allows two transmission lines of **identical characteristic impedance** to be connected together into one "seamless" transmission line.



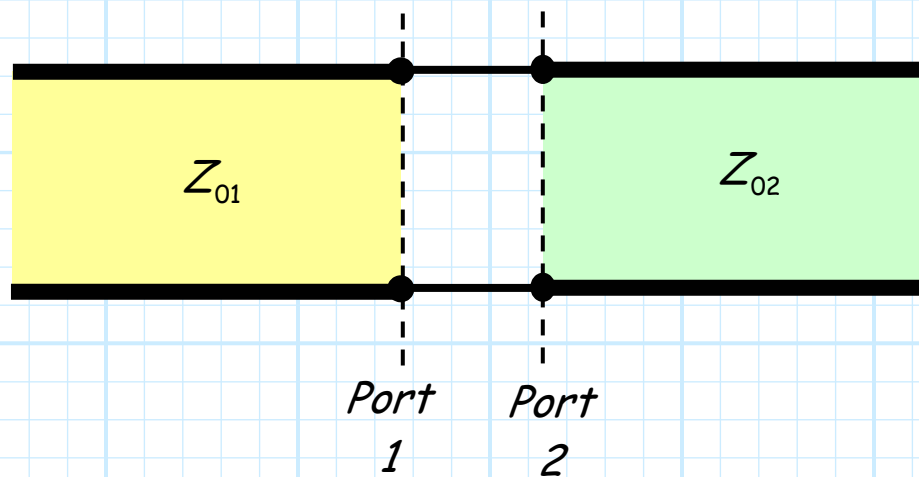Now, however, consider the case where the transmission lines connected together have **dissimilar** characteristic impedances (i.e.,  $Z_0 \neq Z_1$ ):




**Q:** *Won't the scattering matrix of this ideal connector remain the **same**? After all, the **device itself** has not changed!*

**A:** The impedance, admittance, and transmission matrix **will** remain unchanged—these matrix quantities **do not** depend on the characteristics of the transmission lines connected to the device.


But remember, the **scattering matrix** depends on **both** the device **and** the characteristic impedance of the transmission lines attached to it.

**➔** After all, the **incident** and **exiting** waves are traveling on these transmission lines!

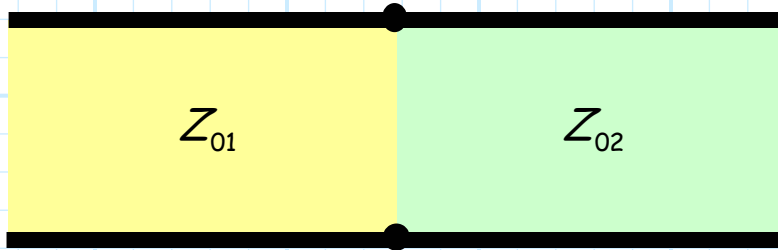The ideal connector in this case establishes a "seamless" **interface** between two **dissimilar** transmission lines.



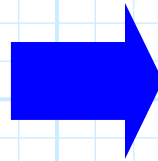Remember, this is the **same** structure that we evaluated in an **earlier** handout!



1/31/2007 The Transmission Coefficient T 5/6

### Example: The Transmission Coefficient T

Consider this circuit:

I.E., a transmission line with characteristic impedance  $Z_1$  transitions to a different transmission line at location  $z=0$ . This second transmission line has different characteristic impedance  $Z_2$  ( $Z_1 \neq Z_2$ ). This second line is terminated with a load  $Z_L = Z_2$  (i.e., the second line is matched).

**Q:** What is the voltage and current along each of these two transmission lines? More specifically, what are  $V_{01}^-$ ,  $V_{01}^+$ ,  $V_{02}^-$  and  $V_{02}^+$ ??

**A:** Since a source has not been specified, we can only determine  $V_{01}^-$ ,  $V_{02}^-$  and  $V_{02}^+$  in terms of complex constant  $V_{01}^+$ . To accomplish this, we must apply a boundary condition at  $z=0!$

Jim Stiles The Univ. of Kansas Dept. of EECS

In that analysis we found that—when  $V_{02}^+ = 0$ :

$$\frac{V_{01}^-}{V_{01}^+} = \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}} \quad \text{and} \quad \frac{V_{02}^-}{V_{01}^+} = \frac{2Z_{02}}{Z_{02} + Z_{01}}$$

And so the (generalized) scattering parameters  $S_{11}$  and  $S_{21}$  are:

$$S_{11} = \frac{V_{01}^-}{V_{01}^+} \frac{\sqrt{Z_{01}}}{\sqrt{Z_{01}}} = \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}} \quad \text{and} \quad S_{21} = \frac{V_{02}^-}{V_{01}^+} \frac{\sqrt{Z_{01}}}{\sqrt{Z_{02}}} = \frac{2\sqrt{Z_{01}Z_{02}}}{Z_{02} + Z_{01}}$$

As a result we can conclude that the **scattering matrix** of the ideal connector (when connecting dissimilar transmission lines) is:

$$S = \begin{bmatrix} \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}} & \frac{2\sqrt{Z_{01}Z_{02}}}{Z_{01} + Z_{02}} \\ \frac{2\sqrt{Z_{01}Z_{02}}}{Z_{01} + Z_{02}} & \frac{Z_{01} - Z_{02}}{Z_{01} + Z_{02}} \end{bmatrix}$$