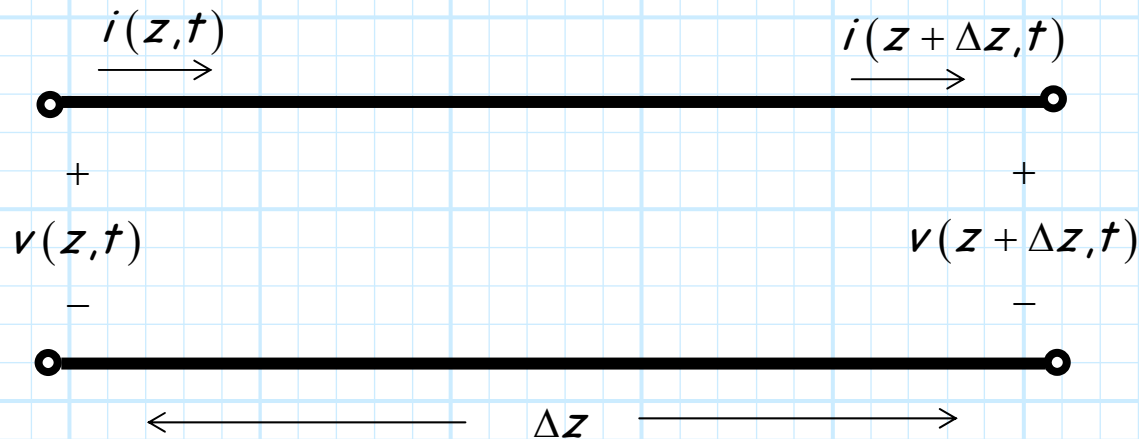


The Telegrapher Equations

Consider a section of "wire":



Where:

$$i(z, t) \neq i(z + \Delta z, t)$$


$$v(z, t) \neq v(z + \Delta z, t)$$

Q: No way! Kirchoff's Laws tells me that:

$$i(z, t) = i(z + \Delta z, t)$$

$$v(z, t) = v(z + \Delta z, t)$$

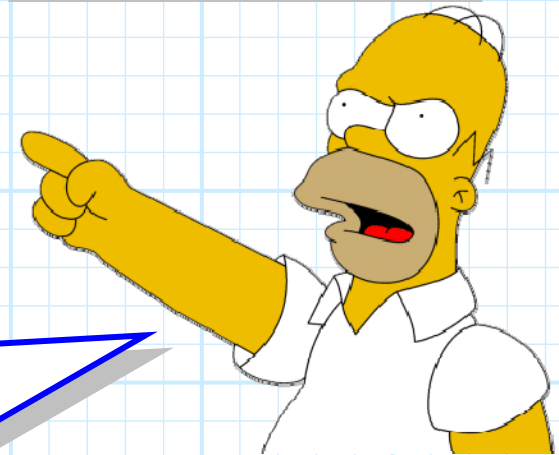
How can the voltage/current at the **end** of the line (at $z + \Delta z$) be **different** than the voltage/current at the **beginning** of the line (at z)??



A: Way. The structure above actually exhibits some non-zero value of **inductance, capacitance, conductance, and admittance!**

An Accurate Model

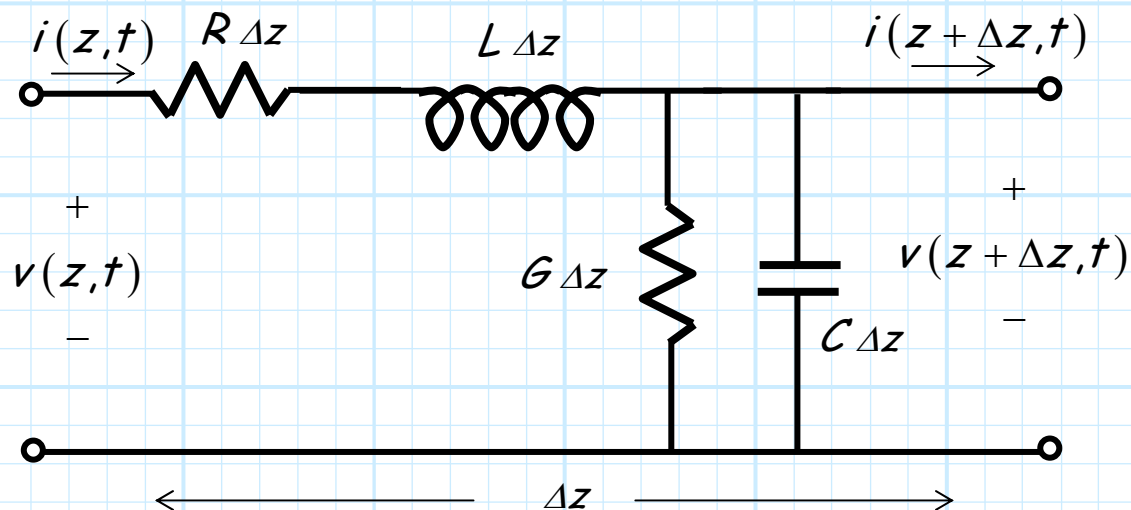A more accurate transmission line model is:



Where:

R = resistance/unit length

L = inductance/unit length

C = capacitance/unit length

G = conductance/unit length

\therefore resistance of wire length Δz is $R\Delta z$

Now evaluating KVL, we find:

$$v(z+\Delta z,t) - v(z,t) = -R\Delta z i(z,t) - L\Delta z \frac{\partial i(z,t)}{\partial t} \neq 0$$

and from KCL:


$$i(z+\Delta z,t) - i(z,t) = -G\Delta z v(z,t) - C\Delta z \frac{\partial v(z,t)}{\partial t} \neq 0$$

The Telegrapher's Equations


Dividing these equations by Δz , and then taking the **limit as** $\Delta z \rightarrow 0$, we find a set of **differential equations** that describe the voltage $v(z,t)$ and current $i(z,t)$ along a transmission line:

$$\frac{\partial v(z,t)}{\partial z} = -Ri(z,t) - L \frac{\partial i(z,t)}{\partial t}$$
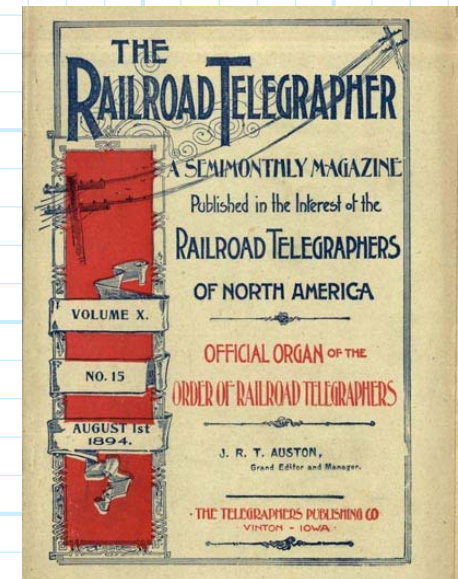
$$\frac{\partial i(z,t)}{\partial z} = -Gv(z,t) - C \frac{\partial v(z,t)}{\partial t}$$



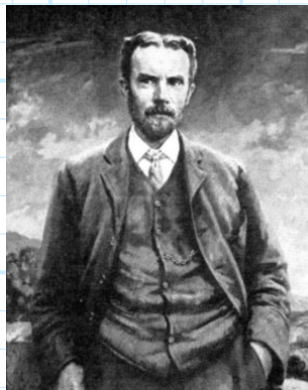These equations are known as the **telegrapher's equations**.



Derived by **Oliver Heaviside**, the telegrapher's equations are essentially the Maxwell's equations of transmission lines.

Although **mathematically** the functions $v(z,t)$ and current $i(z,t)$ can take any form, they can **physically exist only** if they satisfy the both of the differential equations shown above!