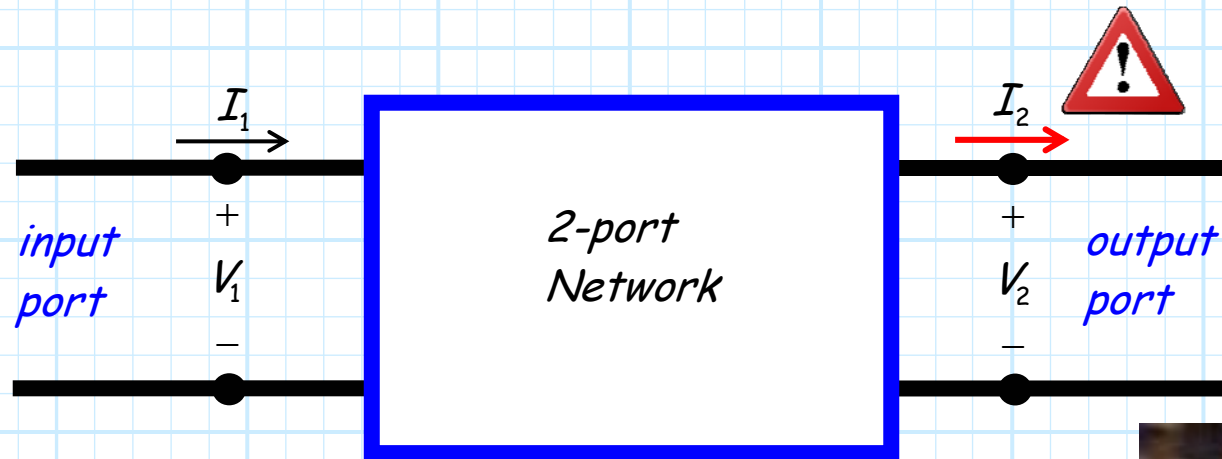


# The Transmission Matrix

If a network has **two** ports, then we can **alternatively** define the voltages and currents at each port as:



**Q:** Say, can we somehow relate the two *input* parameters  $(I_1, V_1)$  to the two *output* parameters  $(I_2, V_2)$ ?

**A:** Yes we can! We can relate them with **four** parameters  $A, B, C, D$ :

$$V_1 = A V_2 + B I_2$$

$$I_1 = C V_2 + D I_2$$



Or, using linear algebra:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

The matrix is defined as the **transmission matrix**  $\mathcal{T}$ , otherwise known as the **ABCD matrix** :

$$\mathcal{T} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$



**Q:** Great. But what exactly **are** the values  $A$ ,  $B$ ,  $C$ ,  $D$ , and how do we determine them?

**A:** Similar to the impedance and admittance matrices, we determine the elements of the transmission matrix using **shorts** and **opens**.


A

Note when  $I_2 = 0$  then:

$$V_1 = AV_2$$

Therefore, to find value  $A$ , place an **open** on port 2, and then determine voltage  $V_1$  in terms of  $V_2$ . We find that:
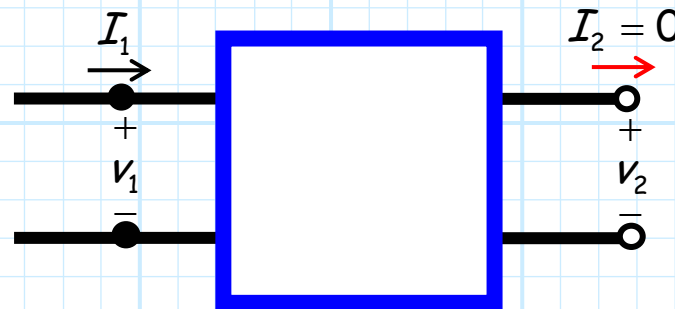
$$A = \frac{V_1}{V_2} \quad (\text{port 2 open})$$



Note the parameter  $A$  is unitless (i.e., it is a coefficient).


B

Note when  $V_2 = 0$  then:

$$V_1 = B I_2$$

Therefore, to find value  $B$ , place a **short** on port 2, and then determine voltage  $V_1$  in terms of  $I_2$ . We find that:
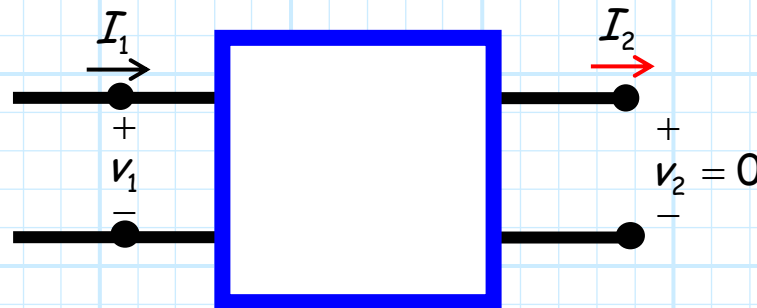
$$B = \frac{V_1}{I_2} \quad (\text{port 2 short})$$



Note parameter  $B$  has units of **impedance** (i.e., Ohms).


C

Note when  $I_2 = 0$  then:

$$I_1 = C V_2$$

Therefore, to find value  $C$ , place an **open** on port 2, and then determine current  $I_1$  in terms of voltage  $V_2$ . We find that:
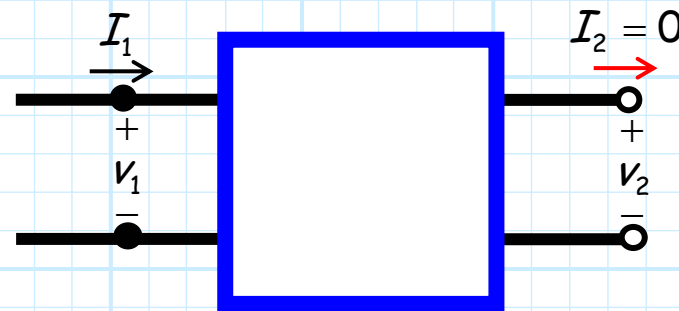
$$C = \frac{I_1}{V_2} \quad (\text{port 2 open})$$



Note parameter  $C$  has units of **admittance** (i.e., mhos).


D

Note when  $V_2 = 0$  then:

$$I_1 = D I_2$$

Therefore, to find value D, place a **short** on port 2, and then determine current  $I_1$  in terms of current  $I_2$ . We find that:
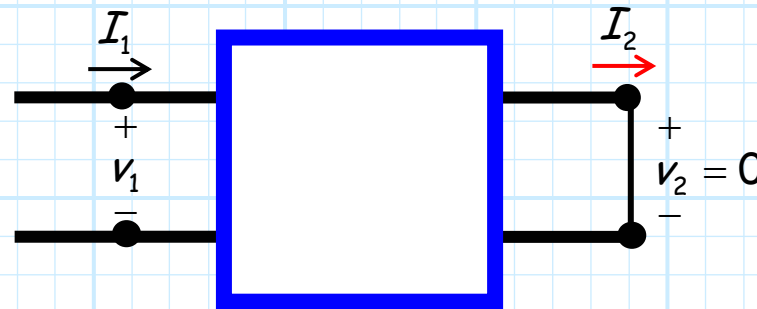
$$D = \frac{I_1}{I_2} \quad (\text{port 2 short})$$




Note parameter D is unitless (another coefficient!).

**Q:** For cryin' out loud! We already have the impedance matrix, the scattering matrix, **and** the admittance matrix. **Why** do we need the transmission matrix **also**? Is it somehow **uniquely** useful?



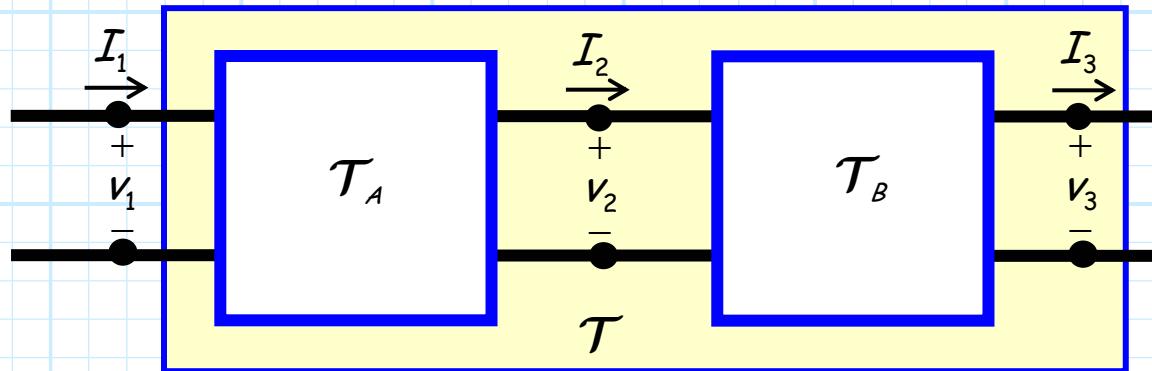**A:** Consider the case where a 2-port network is created by connecting (i.e., cascading) two networks:



Note

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \mathcal{T}_A \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

and

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \mathcal{T}_B \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

also

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \mathcal{T} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

Combining the first two equations:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \mathcal{T}_A \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \mathcal{T}_A \mathcal{T}_B \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

and comparing to the third:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \mathcal{T}_A \mathcal{T}_B \begin{bmatrix} V_3 \\ I_3 \end{bmatrix} = \mathcal{T} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

we conclude that:

$$\mathcal{T} = \mathcal{T}_A \mathcal{T}_B$$

Likewise, for  $N$  cascaded networks, the **total** transmission matrix  $\mathcal{T}$  can be determined as the product of all  $N$  networks!

$$\mathcal{T} = \mathcal{T}_1 \mathcal{T}_2 \mathcal{T}_3 \mathcal{T}_4 \cdots \mathcal{T}_N = \prod_{n=1}^N \mathcal{T}_n$$



Note this result is **only** true for the **transmission** matrix  $\mathcal{T}$ . **No** equivalent result exists for  $\mathcal{S}, \mathcal{Z}, \mathcal{Y}$ !

Thus, the transmission matrix can greatly **simplify** the analysis of **complex** networks constructed from **two**-port devices. We find that the  $\mathcal{T}$  matrix is particularly useful when creating design software for **CAD** applications.