

# The Binomial Multi-Section Transformer

Recall that a **multi-section matching network** can be described using the theory of small reflections as:

$$\begin{aligned}\Gamma_{in}(\omega) &= \Gamma_0 + \Gamma_1 e^{-j2\omega T} + \Gamma_2 e^{-j4\omega T} + \dots + \Gamma_N e^{-j2N\omega T} \\ &= \sum_{n=0}^N \Gamma_n e^{-j2n\omega T}\end{aligned}$$

where:

$$T \doteq \frac{\ell}{v_p} = \text{propagation time through 1 section}$$

Note that for a multi-section transformer, we have  $N$  **degrees of design freedom**, corresponding to the  $N$  characteristic impedance values  $Z_n$ .

**Q:** *What should the values of  $\Gamma_n$  (i.e.,  $Z_n$ ) be?*

**A:** We need to define  $N$  independent **design equations**, which we can then use to solve for the  $N$  values of **characteristic impedance  $Z_n$** .

First, we start with a single **design frequency**  $\omega_0$ , where we wish to achieve a **perfect match**:

$$\Gamma_{in}(\omega = \omega_0) = 0$$

That's just **one** design equation: we need  **$N - 1$**  more!

These addition equations can be selected using **many** criteria—one such criterion is to make the function  $\Gamma_{in}(\omega)$  **maximally flat** at the point  $\omega = \omega_0$ .

To accomplish this, we first consider the **Binomial Function**:

$$\Gamma(\theta) = A(1 + e^{-j2\theta})^N$$

This function has the desirable **properties** that:

$$\begin{aligned}\Gamma(\theta = \pi/2) &= A(1 + e^{-j\pi})^N \\ &= A(1 - 1)^N \\ &= 0\end{aligned}$$

and that:

$$\left. \frac{d^n \Gamma(\theta)}{d\theta^n} \right|_{\theta=\pi/2} = 0 \text{ for } n = 1, 2, 3, \dots, N - 1$$

In other words, this Binomial Function is **maximally flat** at the point  $\theta = \pi/2$ , where it has a value of  $\Gamma(\theta = \pi/2) = 0$ .

**Q:** *So? What does **this** have to do with our multi-section matching network?*

**A:** Let's **expand** (multiply out the  $N$  identical product terms) of the Binomial Function:

$$\begin{aligned}\Gamma(\theta) &= A(1 + e^{-j2\theta})^N \\ &= A(C_0^N + C_1^N e^{-j2\theta} + C_2^N e^{-j4\theta} + C_3^N e^{-j6\theta} + \dots + C_N^N e^{-j2N\theta})\end{aligned}$$

where:

$$C_n^N \doteq \frac{N!}{(N-n)!n!}$$

Compare this to an  $N$ -section transformer function:

$$\Gamma_{in}(\omega) = \Gamma_0 + \Gamma_1 e^{-j2\omega T} + \Gamma_2 e^{-j4\omega T} + \dots + \Gamma_N e^{-j2N\omega T}$$

and it is obvious the two functions have **identical** forms, **provided** that:

$$\Gamma_n = A C_n^N \quad \text{and} \quad \omega T = \theta$$

Moreover, we find that this function is very **desirable** from the standpoint of the a matching network. Recall that  $\Gamma(\theta) = 0$  at  $\theta = \pi/2$ --a **perfect** match!

Additionally, the function is **maximally flat** at  $\theta = \pi/2$ , therefore  $\Gamma(\theta) \approx 0$  over a wide range around  $\theta = \pi/2$ --a **wide bandwidth!**

**Q:** *But how does  $\theta = \pi/2$  relate to frequency  $\omega$ ?*

**A:** Remember that  $\omega T = \theta$ , so the value  $\theta = \pi/2$  corresponds to the frequency:

$$\omega_0 = \frac{1}{T} \frac{\pi}{2} = \frac{v_p}{\ell} \frac{\pi}{2}$$

This frequency ( $\omega_0$ ) is therefore our **design** frequency—the frequency where we have a **perfect** match.

Note that the length  $\ell$  has an interesting **relationship** with this frequency:

$$\ell = \frac{v_p}{\omega_0} \frac{\pi}{2} = \frac{1}{\beta_0} \frac{\pi}{2} = \frac{\lambda_0}{2\pi} \frac{\pi}{2} = \frac{\lambda_0}{4}$$

In other words, a **Binomial** Multi-section matching network will have a **perfect** match at the frequency where the section lengths  $\ell$  are a **quarter wavelength!**


Thus, we have our **first design rule:**

Set section lengths  $\ell$  so that they are a **quarter-wavelength** ( $\lambda_0/4$ ) at the design frequency  $\omega_0$ .

**Q:** *I see! And then we select all the values  $Z_n$  such that  $\Gamma_n = A C_n^N$ . But wait! What is the value of  $A$  ??*

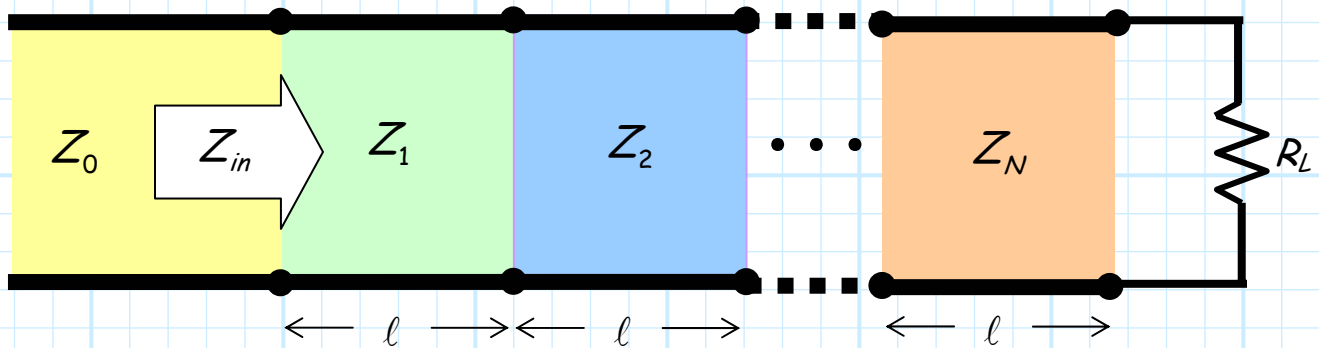**A:** We can determine this value by evaluating a **boundary condition!**

Specifically, we can **easily** determine the value of  $\Gamma(\omega)$  at  $\omega = 0$ .



Note as  $\omega$  approaches **zero**, the electrical length  $\beta l$  of each section will **likewise** approach zero. Thus, the input impedance  $Z_{in}$  will simply be equal to  $R_L$  as  $\omega \rightarrow 0$ .

As a result, the input reflection coefficient  $\Gamma(\omega = 0)$  **must** be:

$$\begin{aligned}\Gamma(\omega = 0) &= \frac{Z_{in}(\omega = 0) - Z_0}{Z_{in}(\omega = 0) + Z_0} \\ &= \frac{R_L - Z_0}{R_L + Z_0}\end{aligned}$$

However, we **likewise** know that:

$$\begin{aligned}\Gamma(0) &= A(1 + e^{-j2(0)})^N \\ &= A(1 + 1)^N \\ &= A2^N\end{aligned}$$

Equating the two expressions:

$$\Gamma(0) = A 2^N = \frac{R_L - Z_0}{R_L + Z_0}$$

And therefore:

$$A = 2^{-N} \frac{R_L - Z_0}{R_L + Z_0} \quad (A \text{ can be negative!})$$



We now have a form for the **marginal reflection coefficients**

$\Gamma_n$ :

$$\Gamma_n = A C_n^N = 2^{-N} \frac{R_L - Z_0}{R_L + Z_0} \frac{N!}{(N-n)!n!}$$

Of course, we **also** know that these marginal reflection coefficients are:

$$\Gamma_n = \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n}$$

Now, we know that the values of  $Z_{n+1}$  and  $Z_n$  are typically very close, such that  $Z_{n+1} - Z_n$  is **small**. It turns out for this case that we can use a helpful **approximation** for the marginal reflection coefficient:

$$\Gamma_n = \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n} \approx \frac{1}{2} \ln \left( \frac{Z_{n+1}}{Z_n} \right) \quad (\text{for } |\Gamma_n| \text{ small})$$

Therefore we can conclude:

$$\Gamma_n = \frac{1}{2} \ln \left( \frac{Z_{n+1}}{Z_n} \right) = 2^{-N} \frac{R_L - Z_0}{R_L + Z_0} C_n^N$$

Solving for  $Z_{n+1}$ , we find:


$$Z_{n+1} = Z_n \exp \left[ 2^{-N+1} \frac{R_L - Z_0}{R_L + Z_0} C_n^N \right]$$

We can further simplify this with yet **another approximation**:

$$Z_{n+1} \approx Z_n \exp \left[ 2^{-N} \ln \left( \frac{R_L}{Z_0} \right) C_n^N \right]$$

This is our **second design rule**. Note it is an **iterative rule**—we determine  $Z_1$  from  $Z_0$ ,  $Z_2$  from  $Z_1$ , and so forth.

The result is a **maximally flat, Binomial** reflection coefficient function  $\Gamma(\omega)$ .

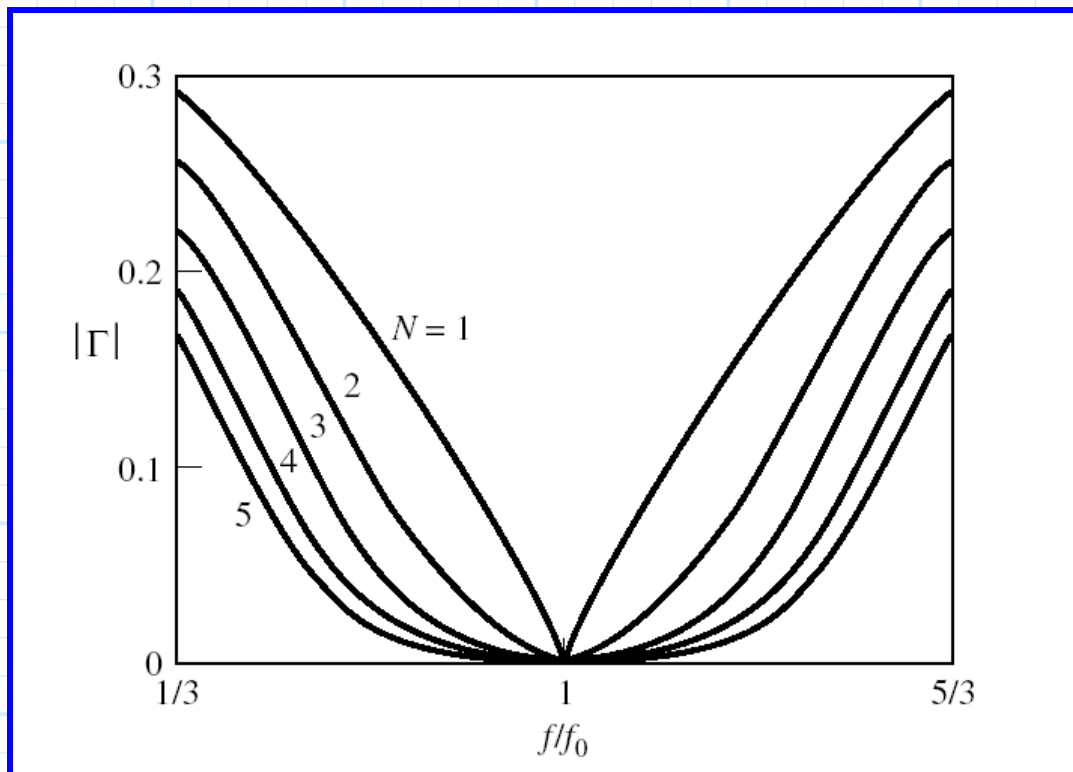

**Figure 5.15** (p. 250)

*Reflection coefficient magnitude versus frequency for multisection binomial matching transformers of Example 5.6  $Z_L = 50\Omega$  and  $Z_0 = 100\Omega$ .*

Note that as we **increase** the number of **sections**, the matching **bandwidth** increases.


**Q:** *Can we determine the **value** of this bandwidth?*

**A:** Sure! But we first must **define** what we mean by bandwidth.

As we move from the design (perfect match) frequency  $f_0$  the value  $|\Gamma(f)|$  will **increase**. At some frequency ( $f_m$ , say) the magnitude of the reflection coefficient will increase to some



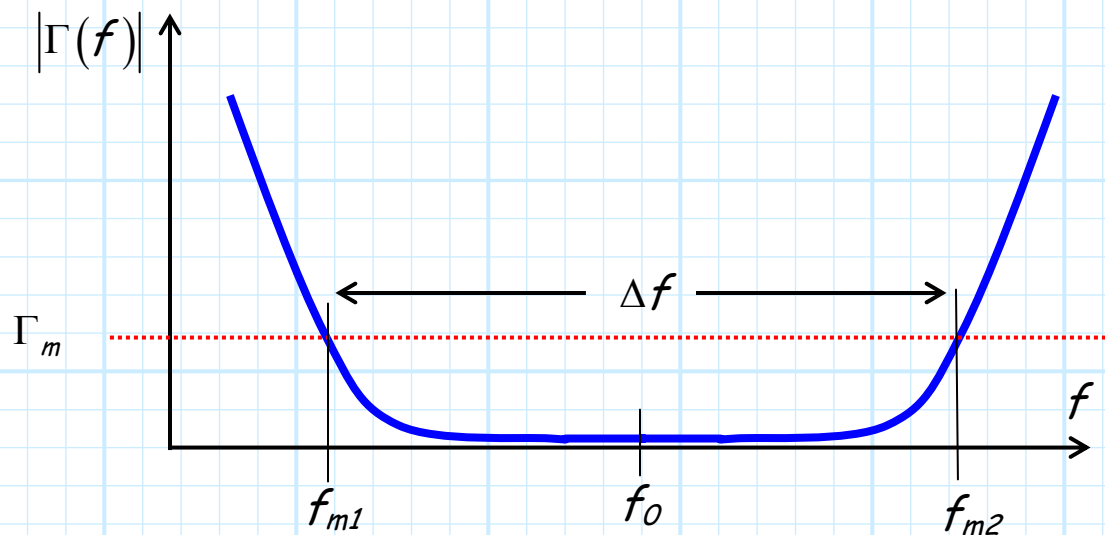**unacceptably** high value ( $\Gamma_m$ , say). At that point, we no longer consider the device to be matched.



Note there are **two** values of frequency  $f_m$ —one value **less** than design frequency  $f_0$ , and one value **greater** than design frequency  $f_0$ . These two values define the **bandwidth**  $\Delta f$  of the matching network:

$$\Delta f = f_{m2} - f_{m1} = 2(f_0 - f_{m1}) = 2(f_{m2} - f_0)$$

**Q:** *So what is the **numerical** value of  $\Gamma_m$ ?*

**A:** **I don't know**—it's up to **you** to decide!

Every engineer must determine what **they** consider to be an acceptable match (i.e., decide  $\Gamma_m$ ). This decision depends on the **application** involved, and the **specifications** of the overall microwave system being designed.

However, we **typically** set  $\Gamma_m$  to be 0.2 or less.

**Q:** OK, after we have selected  $\Gamma_m$ , can we determine the two frequencies  $f_m$ ?

**A:** Sure! We just have to do a little algebra.

We start by rewriting the **Binomial function**:

$$\begin{aligned}\Gamma(\theta) &= A(1 + e^{-j2\theta})^N \\ &= Ae^{-jN\theta} (e^{+j\theta} + e^{-j\theta})^N \\ &= Ae^{-jN\theta} (e^{+j\theta} + e^{-j\theta})^N \\ &= Ae^{-jN\theta} (2\cos\theta)^N\end{aligned}$$

Now, we take the **magnitude** of this function:

$$\begin{aligned}|\Gamma(\theta)| &= 2^N |A| |e^{-jN\theta}| |\cos\theta|^N \\ &= 2^N |A| |\cos\theta|^N\end{aligned}$$

Now, we **define** the values  $\theta$  where  $|\Gamma(\theta)| = \Gamma_m$  as  $\theta_m$ . I.E., :

$$\begin{aligned}\Gamma_m &= |\Gamma(\theta = \theta_m)| \\ &= 2^N |A| |\cos\theta_m|^N\end{aligned}$$

We can now solve for  $\theta_m$  (in radians!) in terms of  $\Gamma_m$ :

$$\theta_{m1} = \cos^{-1} \left[ \frac{1}{2} \left( \frac{\Gamma_m}{|A|} \right)^{1/N} \right] \qquad \theta_{m2} = \cos^{-1} \left[ -\frac{1}{2} \left( \frac{\Gamma_m}{|A|} \right)^{1/N} \right]$$

Note that there are **two solutions** to the above equation (one **less** than  $\pi/2$  and one **greater** than  $\pi/2$ )!

Now, we can convert the values of  $\theta_m$  into specific frequencies.

Recall that  $\omega T = \theta$ , therefore:

$$\omega_m = \frac{1}{T} \theta_m = \frac{v_p}{\ell} \theta_m$$

But recall also that  $\ell = \lambda_0/4$ , where  $\lambda_0$  is the wavelength at the **design frequency**  $f_0$  (not  $f_m$ !), and where  $\lambda_0 = v_p/f_0$ .

Thus we can conclude:

$$\omega_m = \frac{v_p}{\ell} \theta_m = \frac{4v_p}{\lambda_0} \theta_m = (4f_0) \theta_m$$

or:

$$f_m = \frac{1}{2\pi} \frac{v_p}{\ell} \theta_m = \frac{(4f_0) \theta_m}{2\pi} = \frac{(2f_0) \theta_m}{\pi}$$

where  $\theta_m$  is expressed in **radians**. Therefore:

$$f_{m1} = \frac{2f_0}{\pi} \cos^{-1} \left[ + \frac{1}{2} \left( \frac{\Gamma_m}{|A|} \right)^{1/N} \right] \quad f_{m2} = \frac{2f_0}{\pi} \cos^{-1} \left[ - \frac{1}{2} \left( \frac{\Gamma_m}{|A|} \right)^{1/N} \right]$$

Thus, the **bandwidth** of the binomial matching network can be determined as:

$$\begin{aligned}\Delta f &= 2(f_0 - f_{m1}) \\ &= 2f_0 - \frac{4f_0}{\pi} \cos^{-1} \left[ + \frac{1}{2} \left( \frac{\Gamma_m}{|A|} \right)^{1/N} \right]\end{aligned}$$

Note that this equation can be used to determine the **bandwidth** of a binomial matching network, given  $\Gamma_m$  and number of sections  $N$ .

However, it can likewise be used to determine the **number of sections**  $N$  required to meet a specific bandwidth requirement!

Finally, we can list the **design steps** for a binomial matching network:

1. **Determine** the value  $N$  required to meet the bandwidth ( $\Delta f$  and  $\Gamma_m$ ) requirements.
2. Determine the impedance of each section using the iterative approximation:

$$Z_{n+1} \approx Z_n \exp \left[ 2^{-N} \ln \left( \frac{R_L}{Z_0} \right) C_n^N \right]$$

3. Determine section **length**  $\ell = \lambda_0/4$  for frequency  $f_0$ .