

# Transistors as Gain Elements

A quiz!

1. To construct a small-signal amplifier, a **BJT** must be **DC biased** to which mode:

- A. Active
- B. Triode
- C. Cutoff
- D. Saturation

2. To construct a small-signal amplifier, a **FET** must be **DC biased** to which mode:

- A. Active
- B. Triode
- C. Cutoff
- D. Saturation


3. The **BJT** amplifier **configuration** that typically provides the highest open-circuit **voltage gain** is the:

- A. common emitter
- B. common source
- C. common base
- D. common collector
- E. common drain
- F. common gate

4. The **FET** amplifier configuration that typically provides the highest open-circuit voltage gain is the:

- |                   |                     |
|-------------------|---------------------|
| A. common emitter | B. common source    |
| C. common base    | D. common collector |
| E. common drain   | F. common gate      |

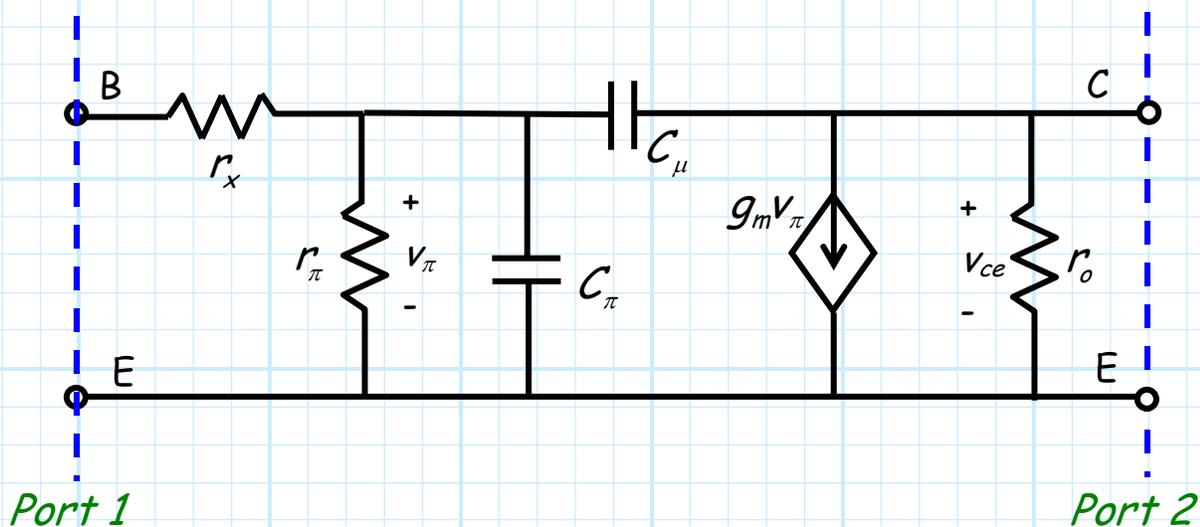
The high-frequency small-signal (hybrid-pi) **model** for a **BJT** in the **common emitter** configuration is:



Here the values  $g_m, r_\pi, r_o$  are all **small-signal parameters**—values determined in part by the **DC bias** of the transistor.

The values  $r_x, C_\pi, C_\mu$  are **parasitic elements**. Generally too small to consider for low-frequency operation, these value make a great difference at microwave frequencies!

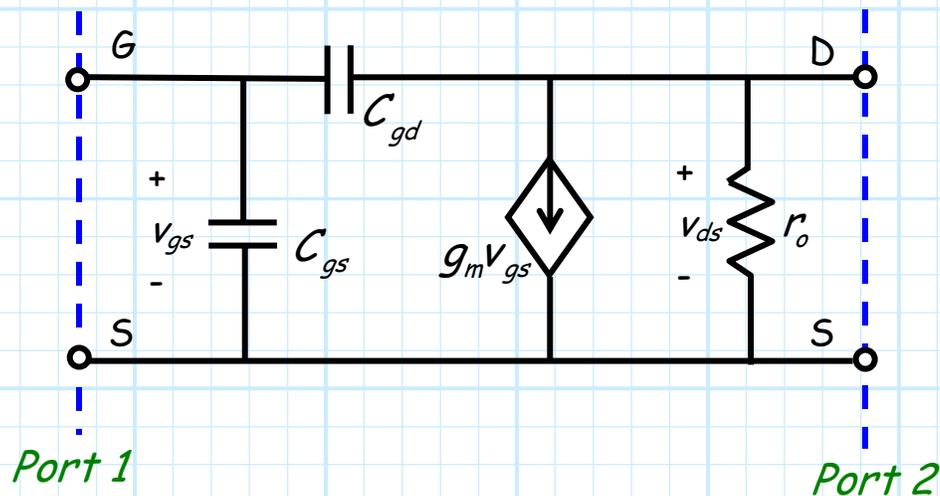Likewise, the high-frequency small-signal model for a MOSFET device in a common-source configuration is:




where again  $g_m$ ,  $r_o$  are small-signal parameters and  $C_{gs}$ ,  $C_{gd}$  are parasitic elements.

Note that each of these circuits form a **two-port network**!

This network we will define as a **gain stage**, where port 1 is the **input** port and port 2 the **output** port.

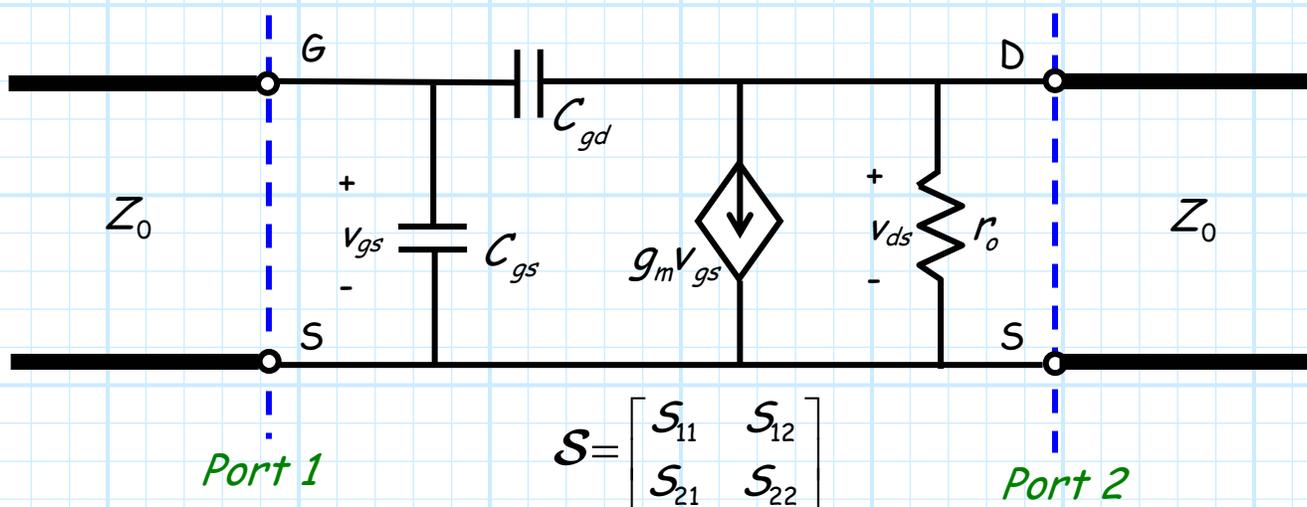Since they are two-port networks, we can describe them with a **scattering matrix**:



We can determine this scattering matrix either by direct **measurement** (using a network analyzer) or by **analysis** of the small-signal circuit.

Either way, we will find that this two-port network has some **interesting** characteristics!

1. We will typically find that both  $|S_{11}|$  and  $|S_{22}|$  are relatively large (e.g.  $0.6 < |S_{11}| < 1.0$ ).
2. We will typically find that  $|S_{12}|$  is relatively small (e.g.  $|S_{12}| = 0.01$ ).
3. We will typically find that  $|S_{21}|$  is much greater than one (e.g.  $|S_{21}| = 3.5$ )!

As a result, it is evident that this **gain stage** is:

- a. **not** matched (just look at  $|S_{11}|$  and  $|S_{22}|$ )
- b. **not** reciprocal (just look at  $|S_{12}|$  and  $|S_{21}|$ )
- c. **not** lossless—but neither is it lossy ( $|S_{11}|^2 + |S_{21}|^2 > 1$ )!

This gain stage is an **active** device—the DC bias supplies energy that is converted into RF signal power at the output port. In other words, **more** RF power flows **out** than flows **in**!

**Q:** *So, is this gain stage a microwave amplifier?*

**A:** It could be used as such, but generally we start with this **gain stage** and then carefully design **two** additional networks—one for the **input** and one for the **output**. These three networks together form a typical (low-power) microwave amplifier!