

Turning a Gain Element into an Amplifier

Say the design criteria for our amplifier is to maximize the power delivered to the load (i.e., maximize P_L). This power is maximized when:

1. The available power from the **source** is entirely delivered to the **input** of the gain element $P_{in} = P_{av}$.
2. The available power from the **output** of the gain element is entirely delivered to the **load** $P_L = P_{av}$.

Recall this happy occurrence results when $\Gamma_{in} = \Gamma_s^*$ and $\Gamma_L = \Gamma_{out}^*$.

Q: But what if this is not the case? What if our gain element is not matched to our source, or to our load? Must we simply accept inferior power transfer?

A: Nope! Remember, we can always build **lossless matching networks** to efficiently transfer power between mismatched sources and loads.


Q: I see! We need to **modify** the source impedance Z_s and modify the output impedance Z_{out} such that $Z_s = Z_{in}^*$ and $Z_{out} = Z_L^*$. Right?

A: Not exactly.

Remember, it is true that a lossless matching network can change the source impedance to match a specific load. But the lossless matching network likewise alters the source voltage V_s such that the available power is preserved!


Messing around **directly** with the source impedance will undoubtedly **reduce** the available power of the source (this is bad!).

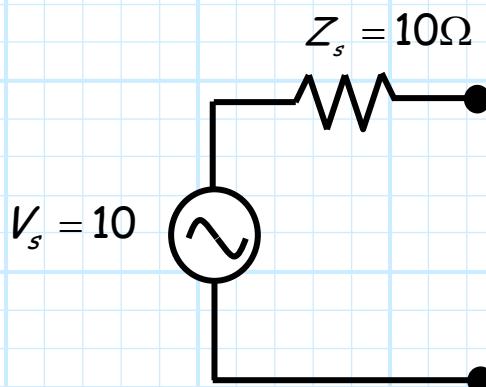For **example**, consider this simple problem. Say we have this source, with a robust **available power** of 1.25 W:




$$\begin{aligned} P_{avs} &= \frac{|V_s|^2}{8 \operatorname{Re}\{Z_s\}} \\ &= \frac{10^2}{8(10)} \\ &= 1.25 \text{ W} \end{aligned}$$

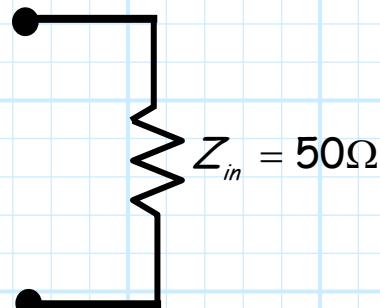and wish to deliver this power to an impedance of $Z_{in} = 50\Omega$:



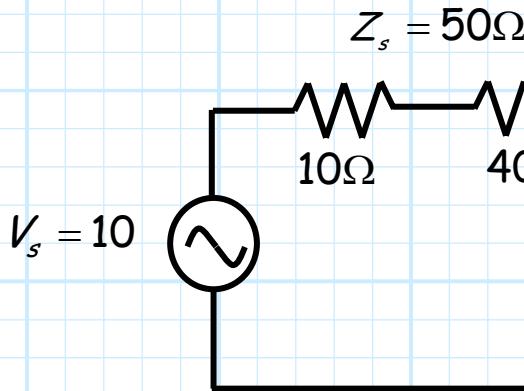
Although increasing the source impedance by 40Ω would result in a **conjugate match**, it would likewise **reduce** the available power to a measly **0.25 Watts**.



$$\begin{aligned} P_{av} &= \frac{|V_s|^2}{8 \operatorname{Re}\{Z_s\}} \\ &= \frac{10^2}{8(50)} \\ &= 0.25 \text{ W} \end{aligned}$$


Thus, although finagling the source impedance does result in extracting **all** the available power from the resulting source, it likewise **decreases** this available power by 80% !

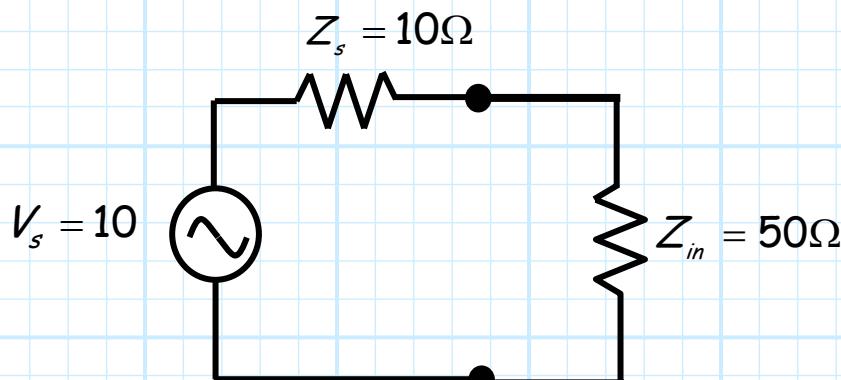Moreover, we find that the delivered power to would be greater if we simply left the darn thing **alone**!




$$\begin{aligned} P_L &= \frac{1}{2} |V_g|^2 \frac{\operatorname{Re}\{Z_L\}}{|Z_g + Z_L|^2} \\ &= \frac{10^2}{2} \frac{50}{(20 + 50)^2} \\ &= \frac{50^2}{70^2} \\ &= 0.51 \text{ W} \end{aligned}$$

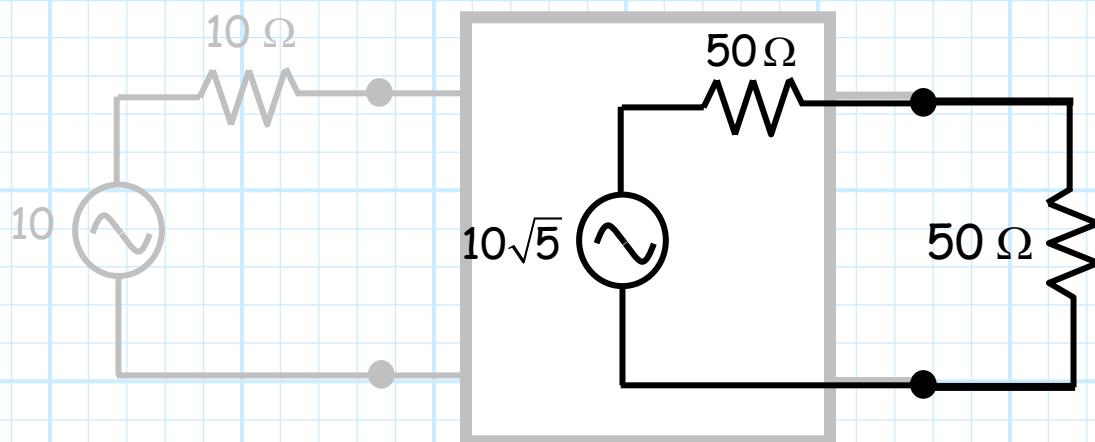In contrast, a properly designed matching network will transform the source impedance to a matched value of 50Ω , but it **likewise** transforms the source **voltage** such that the absorbed power remains the **same**—1.25 Watts is delivered to the 50Ω load!




We have our cake. We eat it too.

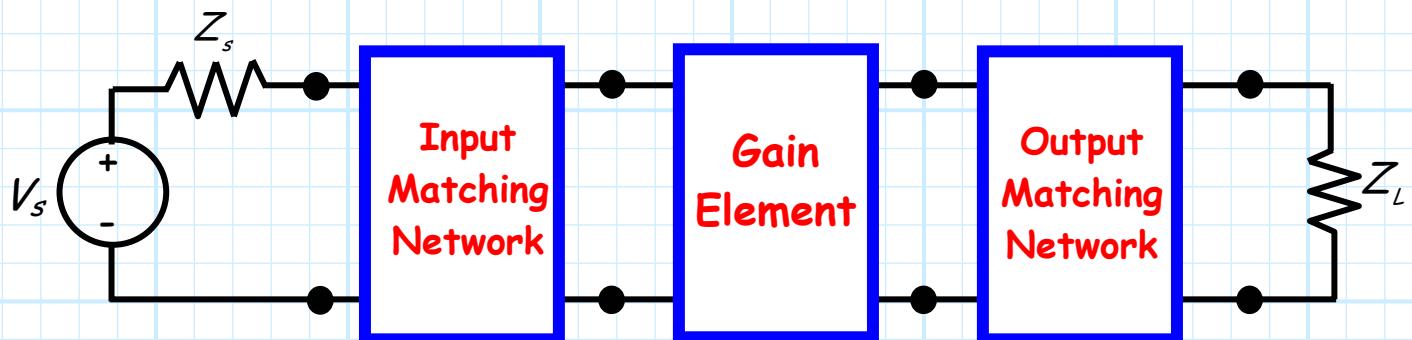So, to maximize the power delivered to a load, we need to insert **lossless matching networks** between the source and gain element, and between the gain element and the load:




The **three stages** together—input matching network, gain element, and output matching network—form a **microwave amplifier**!


A Microwave Amplifier

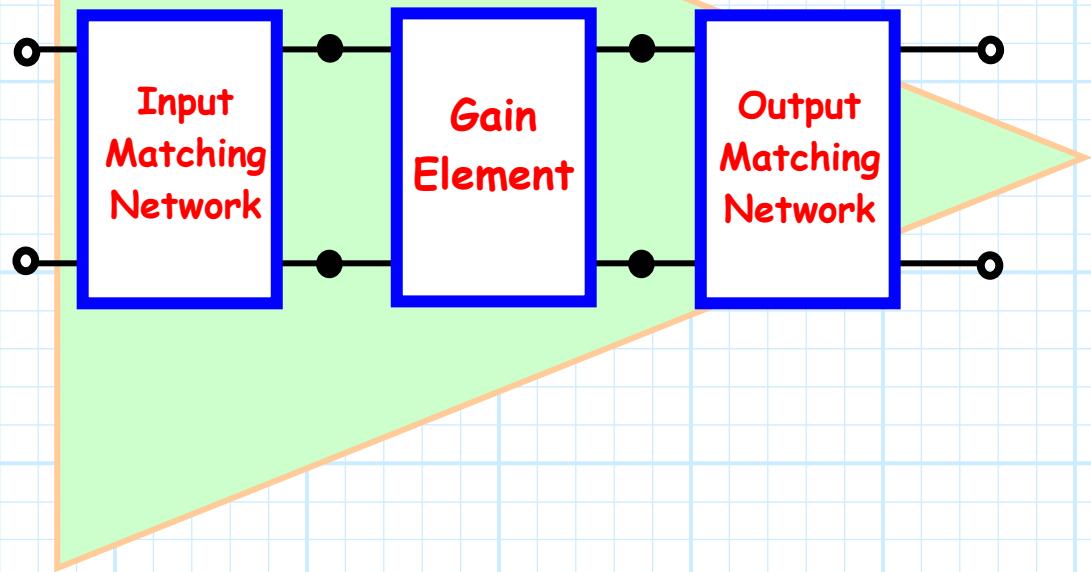

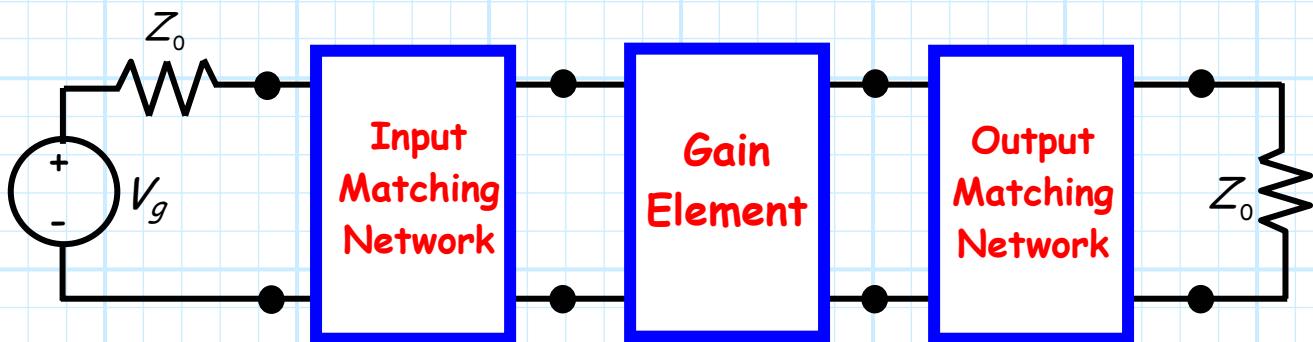Of course, the impedance of both the source and the load connected to this amp will most certainly be that of transmission line **characteristic impedance** Z_0 . Thus, our amplifier circuit is typically:



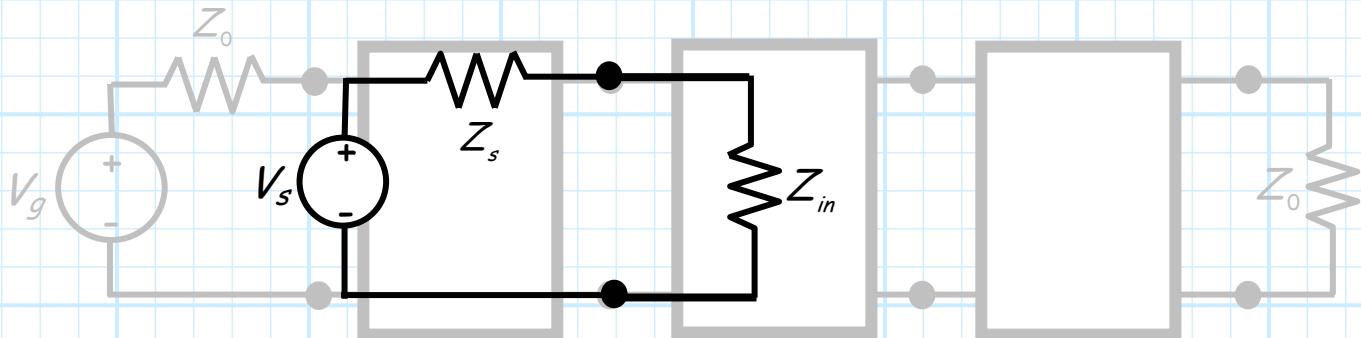
The **input network** is thus required to match Z_0 to the gain element input impedance Z_{in} . For the purposes of amplifier design, we view the input matching network as one that transforms the source impedance Z_0 into a new source impedance Z_s , one that is conjugate matched to the gain element input impedance Z_{in} :



If our input matching network is properly designed, we then find:

$$Z_s = Z_{in} \quad \text{and so} \quad \Gamma_s = \Gamma_{in}^*$$

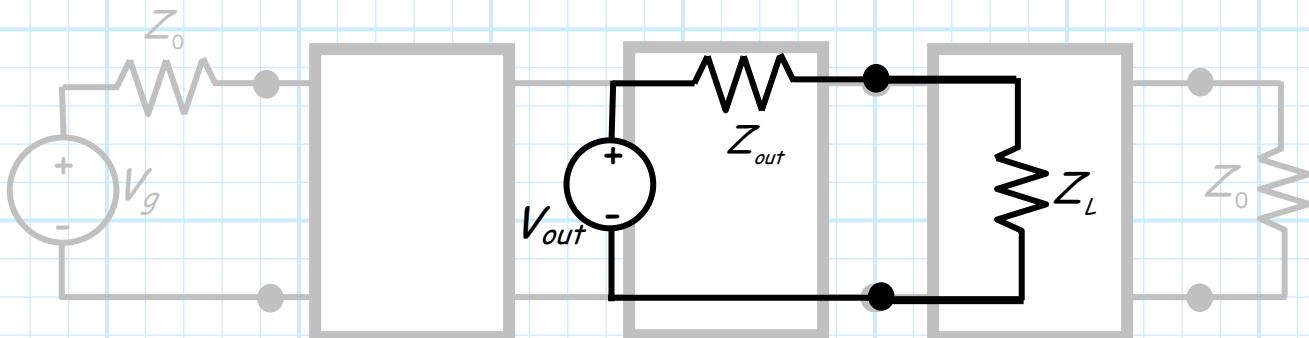
Likewise, the **output matching network** is used to match Z_0 to the gain element output impedance Z_{out} . For the purposes of amplifier design, we view the output matching network as one that transforms the load impedance Z_0 into a new load impedance Z_L , one that is conjugate matched to the gain element output impedance Z_{out} :



Thus, if our input matching network is properly designed, then we find:

$$Z_L = Z_{out}^* \quad \text{and so} \quad \Gamma_L = \Gamma_{out}^*$$

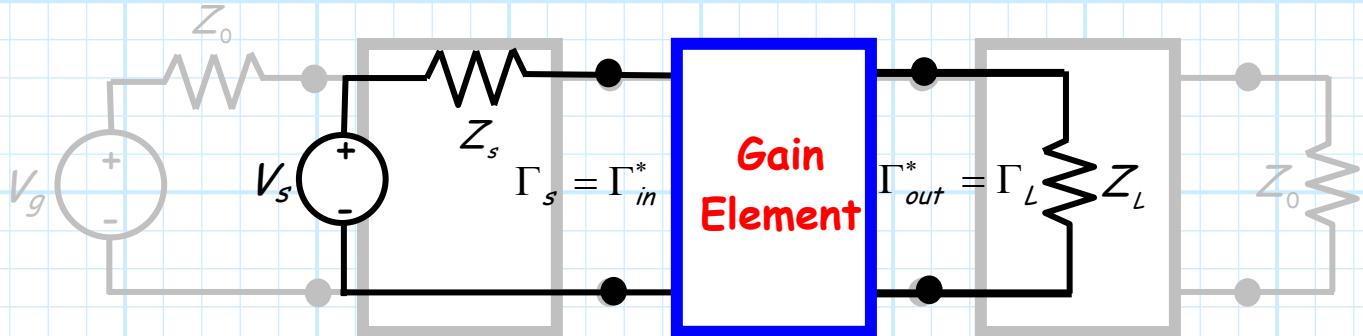And so, our amplifier design problem can be described as:




where the values of Γ_s and Γ_L depend on the input and output matching networks.


Q: Alright, we get it. We know how to make matching networks. Can't we move on to something else?

A: Not so fast! There's one little **problem** that makes this procedure more difficult than it otherwise might appear.

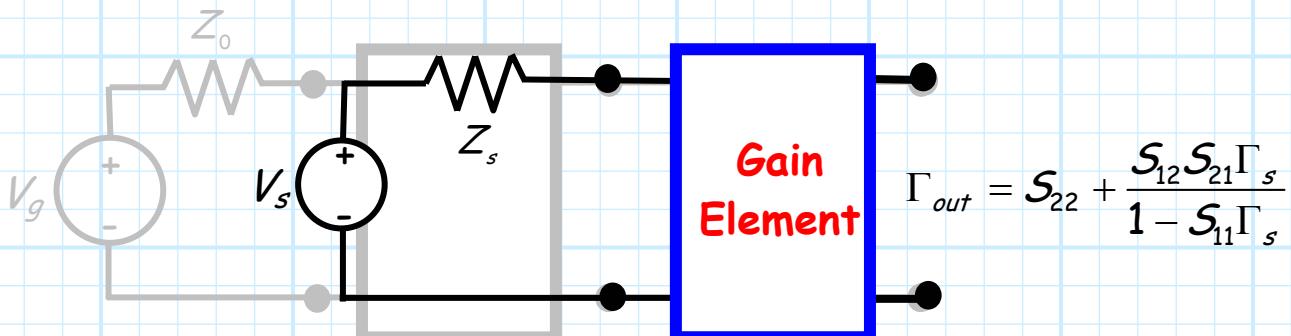Note that the value of Γ_{out} depends on the value of Z_s (i.e., depends on Γ_s).



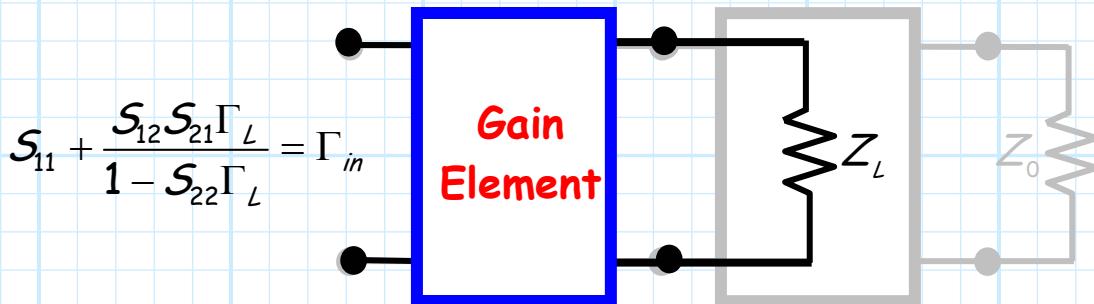Likewise, the value of Γ_{in} depends on the value of Z_L (i.e., depends on Γ_L).



It's a classic **chicken and egg!**

1. We can't design the input matching network until we determine Γ_{in} .
2. We can't determine Γ_{in} until we design the output matching network.
3. We can't determine the output matching network until we determine Γ_{out} .
4. We can't determine Γ_{out} until we design the input matching network.
5. But we can't design the input matching network until we determine Γ_{in} !

Our matching network design problems are thus **coupled**. The solution to this coupled problem is provided in your textbook

on page 550, and provides simultaneous solutions for $\Gamma_s = \Gamma_{in}^*$ and $\Gamma_L = \Gamma_{out}^*$.

Now for some good news!

Recall that for many gain elements, the value of S_{12} is exceedingly small. Often it is so small that we can approximate as zero.

Q: So?

A: Look at what this does to the value of Γ_{in} and Γ_{out} !

$$\Gamma_{out} \Big|_{S_{12}=0} = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s} \Big|_{S_{12}=0} = S_{22}$$

$$\Gamma_{in} \Big|_{S_{12}=0} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \Big|_{S_{12}=0} = S_{11}$$

Thus, for this **unilateral** gain element, the matching network design problem decouples, and our matching network design simplifies to these two independent equations:

$$\Gamma_s = \Gamma_{in}^*$$

and

$$\Gamma_L = \Gamma_{out}^*$$