

# The Matched, Lossless, Reciprocal Network

Often, we describe a network as **matched**, **lossless**, or **reciprocal**.

Q: *What do these three terms mean??*

A: Let's explain each of them **one at a time!**

## Matched

A matched device is another way of saying that the **input impedance** at each port is **equal to  $Z_0$**  when all other ports are terminated in matched loads. As a result, the **reflection coefficient** of each port is **zero**—no signal will be come out of a port if a signal is incident on that port (and only that port).

In other words, we want:

$$V_m^- = S_{mm} V_m^+ = 0 \quad \text{for all } m$$

a result that occurs when:

$$S_{mm} = 0 \quad \text{for all } m$$

We find therefore that a matched device will exhibit a scattering matrix where all **diagonal elements** are **zero**.

Therefore:

$$\bar{\mathbf{S}} = \begin{bmatrix} 0 & 0.1 & j0.2 \\ 0.1 & 0 & 0.3 \\ j0.2 & 0.3 & 0 \end{bmatrix}$$

is an example of a scattering matrix for a **matched**, three port device.

### Lossless

For a lossless device, all of the power that delivered to each device port must eventually finds its way **out**!

In other words, power is not **absorbed** by the network—no power to be **converted to heat**!

Consider, for example, a **four-port** device. Say a signal is incident on port 1, and that **all** other ports are **terminated**. The power **incident** on port 1 is therefore:

$$P_1^+ = \frac{|V_1^+|^2}{2Z_0}$$

while the power **leaving** the device at each port is:

$$P_m^- = \frac{|V_m^-|^2}{2Z_0} = \frac{|S_{m1}V_1^-|^2}{2Z_0} = |S_{m1}|^2 P_1^+$$

The **total** power leaving the device is therefore:

$$\begin{aligned} P_{out} &= P_1^- + P_2^- + P_3^- + P_4^- \\ &= |S_{11}|^2 P_1^+ + |S_{21}|^2 P_1^+ + |S_{31}|^2 P_1^+ + |S_{41}|^2 P_1^+ \\ &= (|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 + |S_{41}|^2) P_1^+ \end{aligned}$$

Note therefore that if the device is **lossless**, the output power will be **equal** to the input power, i.e.,  $P_{out} = P_1^+$ . This is true **only** if:

$$|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 + |S_{41}|^2 = 1$$

If the device is lossless, this will likewise be true for each of the **other** ports:

$$|S_{12}|^2 + |S_{22}|^2 + |S_{32}|^2 + |S_{42}|^2 = 1$$

$$|S_{13}|^2 + |S_{23}|^2 + |S_{33}|^2 + |S_{43}|^2 = 1$$

$$|S_{14}|^2 + |S_{24}|^2 + |S_{34}|^2 + |S_{44}|^2 = 1$$

We can state in general then:

$$\sum_{m=1}^N |S_{mn}|^2 = 1 \quad \text{for all } n$$

In fact, it can be shown that a lossless device will have a **unitary** scattering matrix, i.e.:

$$\bar{\bar{S}}^H \bar{\bar{S}} = \bar{\bar{I}}$$

where  $H$  indicates **conjugate transpose** and  $\bar{\bar{\mathbf{I}}}$  is the **identity** matrix.

The columns of a unitary matrix form an **orthonormal set**—that is, the **magnitude** of each column is 1 (as shown above) and dissimilar column vector are mutually **orthogonal**. I.E.:

$$S_{1m}S_{1n}^* + S_{2m}S_{2n}^* + \cdots + S_{Nm}S_{Nn}^* = 0 \quad \text{for all } m \neq n$$

### Reciprocal

Reciprocity results when we build a **passive** (i.e., unpowered) device with **simple** materials.

For a reciprocal network, we find that the elements of the scattering matrix are **related** as:

$$S_{mn} = S_{nm}$$

For example, a reciprocal device will have  $S_{21} = S_{12}$  or  $S_{32} = S_{23}$ . We can write reciprocity in matrix form as:

$$\bar{\bar{\mathbf{S}}}^T = \bar{\bar{\mathbf{S}}}$$

where  $T$  indicates (non-conjugate) transpose.