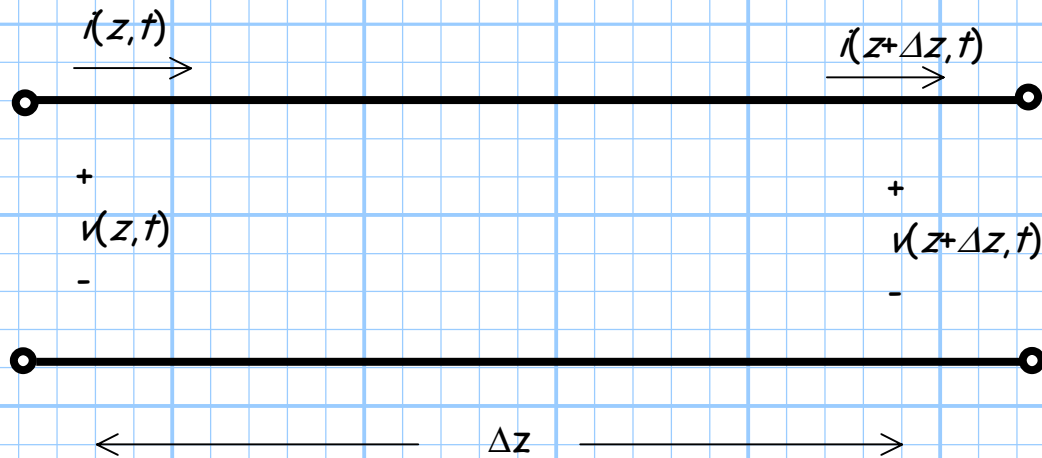


The Telegrapher Equations

Consider a section of "wire":




Q: Huh ?! Current i and voltage v are a function of **position** z ??
Shouldn't $i(z, t) = i(z + \Delta z, t)$ and $v(z, t) = v(z + \Delta z, t)$?

A: NO ! Because a wire is never a **perfect** conductor.

A "wire" will have:

- 1) Inductance
- 2) Resistance
- 3) Capacitance
- 4) Conductance

i.e.,

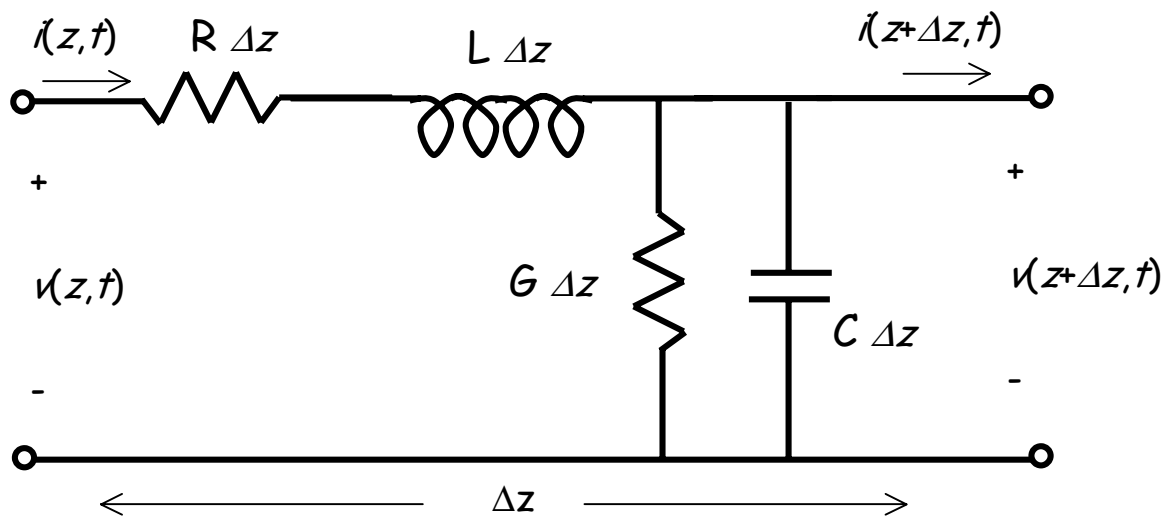

Where:

R = resistance/unit length

L = inductance/unit length

C = capacitance/unit length

G = conductance/unit length

\therefore resistance of wire length Δz is $R\Delta z$.

Using KVL, we find:

$$v(z + \Delta z, t) - v(z, t) = -R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t}$$

and from KCL:

$$i(z + \Delta z, t) - i(z, t) = -G\Delta z v(z, t) - C\Delta z \frac{\partial v(z, t)}{\partial t}$$

Dividing the first equation by Δz , and then taking the limit as $\Delta z \rightarrow 0$:

$$\lim_{\Delta z \rightarrow 0} \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

which, by definition of the derivative, becomes:

$$\frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

Similarly, the KCL equation becomes:

$$\frac{\partial i(z, t)}{\partial z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t}$$

If $v(z, t)$ and $i(z, t)$ have the form:

$$v(z, t) = \text{Re}\{V(z)e^{j\omega t}\} \quad \text{and} \quad i(z, t) = \text{Re}\{I(z)e^{j\omega t}\}$$

then these equations become:

$$\frac{\partial V(z)}{\partial z} = -(R + j\omega L) I(z)$$

$$\frac{\partial I(z)}{\partial z} = -(G + j\omega C) V(z)$$

These equations are known as the **telegrapher's equations** !

- * The functions $I(z)$ and $V(z)$ are **complex**, where the **magnitude** and **phase** of the complex functions describe the **magnitude** and **phase** of the sinusoidal time function $e^{j\omega t}$.
- * Thus, $I(z)$ and $V(z)$ describe the current and voltage along the transmission line, as a function of position z .
- * **Remember**, not just **any** function $I(z)$ and $V(z)$ can exist on a transmission line, but rather **only** those functions that satisfy the **telegrapher's equations**.

Our task, therefore, is to **solve** the telegrapher equations and find **all** solutions $I(z)$ and $V(z)$!

