I(z)

+

V(z)


 $Z_{L}$ 

 $V_{L}$ 

## <u>The Terminated, Lossless</u> <u>Transmission Line</u>

Consider a lossless line, length  $\ell$ , terminated with a load  $Z_L$ .

 $Z_0, \beta$ 

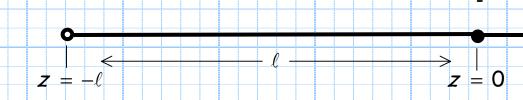

We know from the telegrapher's equations that:

$$V(z=0) = V_0^+ e^{-\beta(0)} + V_0^- e^{+\beta(0)} = V_0^+ + V_0^-$$

$$I(z=0) = \frac{V_0^+}{Z_0} e^{-\beta(0)} - \frac{V_0^-}{Z_0} e^{+\beta(0)} = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}$$

We also know that the load voltage and current must be related by "Ohms Law":  $\frac{V_{L}}{I_{L}} = Z_{L}$  **BUT**, we notice that the transmission line current at z=0 is the current flowing into the load, while the transmission line voltage at *z=0* is the voltage across the load:

$$V(z=0)=V_{L}$$

$$I(z=0)=I_{t}$$

These are the **boundary conditions** of transmission line problem, and result in yet another equation that I(z) and V(z) must satisfy:


$$Z_{L} = \frac{V_{L}}{I_{L}} = \frac{V(z = 0)}{I(z = 0)} = \frac{(V_{0}^{+} + V_{0}^{-})}{\left(\frac{V_{0}^{+} - V_{0}^{-}}{Z_{0}^{-}}\right)}$$

Rearranging, we find that the two complex coefficients  $V_0^+$  and  $V_0^-$  are no longer **independent**, but instead must satisfy the following:

$$\frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \doteq \Gamma$$

The value  $\Gamma$  is a complex coefficient known as the **reflection coefficient**. It relates the magnitude and phase of the wave **incident** on the load  $(V_0^+)$  to the magnitude and phase of the wave emerging (i.e., **reflected** from ) the load  $(V_0^-)$ .

$$V_0^- = \Gamma V_0^+$$

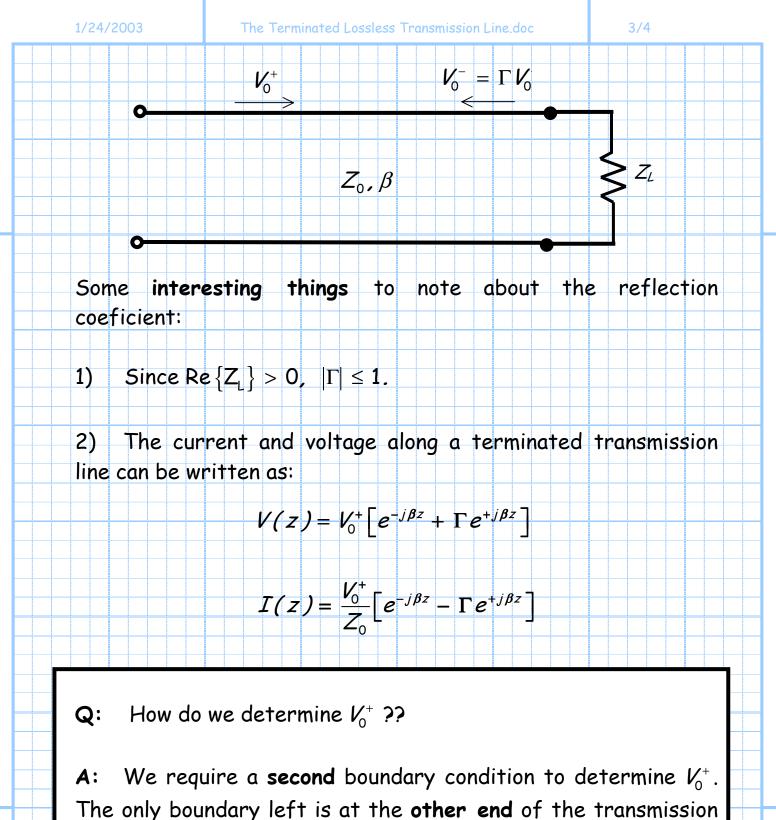

The only boundary left is at the **other end** of the transmission line. Typically, a **source** of some sort is located there. This makes physical sense, as something must generate the **incident** wave !