

# EECS 723-Microwave Engineering

**Teacher:** "*Bart, do you even know your multiplication tables?*"

**Bart:** "*Well, I know of them*".

Like Bart and his multiplication tables, many electrical engineers know **of** the concepts of microwave engineering.

Concepts such as characteristic impedance, scattering parameters, Smith Charts and the like are familiar, but often we find that a **complete, thorough and unambiguous** understanding of these concepts can be somewhat lacking.

Thus, the goals of this class are for **you** to:

- 1.** Obtain a complete, thorough, and unambiguous understanding of the fundamental concepts on microwave engineering.
- 2.** Apply these concepts to the **design and analysis** of useful microwave devices.

## 2.1 - The Lumped Element Circuit Model for Transmission Lines

**Reading Assignment:** pp. 1-5, 48-51

The most important fact about microwave devices is that they are connected together using transmission lines.

**Q:** *So just what is a transmission line?*

**A:** A passive, linear, two port device that allows bounded E. M. energy to flow from one device to another.

→ Sort of an "electromagnetic pipe" !



**Q:** *Oh, so it's simply a conducting wire, right?*

**A:** NO! At high frequencies, things get much more complicated!

**HO: THE TELEGRAPHERS EQUATIONS**

**HO: TIME-HARMONIC SOLUTIONS FOR TRANSMISSION LINES**

**Q:** *So, what complex functions  $I(z)$  and  $V(z)$  do satisfy both telegrapher equations?*

**A:** The solutions to the transmission line **wave equations!**

## HO: THE TRANSMISSION LINE WAVE EQUATIONS

**Q:** *Are the solutions for  $I(z)$  and  $V(z)$  completely independent, or are they related in any way?*

**A:** The two solutions are related by the transmission line characteristic impedance.

## HO: THE TRANSMISSION LINE CHARACTERISTIC IMPEDANCE

**Q:** *So what is the significance of the complex constant  $\gamma$ ? What does it tell us?*

**A:** It describes the **propagation** of each **wave** along the transmission line.

## HO: THE COMPLEX PROPAGATION CONSTANT

**Q:** *Now, you said earlier that **characteristic impedance  $Z_0$**  is a **complex** value. But I recall engineers referring to a transmission line as simply a "50 Ohm line", or a "300 Ohm line". But these are **real** values; are they **not** referring to characteristic impedance  $Z_0$ ??*

**A:** These real values are in fact some **standard  $Z_0$**  values. They are **real** values because the transmission line is **lossless** (or nearly so!).

## HO: THE LOSSLESS TRANSMISSION LINE

**Q:** *Is characteristic impedance  $Z_0$  the same as the concept of impedance I learned about in circuits class?*

**A:** **NO!** The  $Z_0$  is a **wave** impedance. However, we can also define **line impedance**, which is the same as that used in circuits.

### HO: LINE IMPEDANCE

**Q:** *These wave functions  $V^+(z)$  and  $V^-(z)$  seem to be important. How are they related?*

**A:** They are in fact **very** important! They are related by a function called the **reflection coefficient**.

### HO: THE REFLECTION COEFFICIENT


**Q:** *Does this mean I can describe transmission line activity in terms of (complex) voltage, current, and impedance, **or alternatively** in terms of an incident wave, reflected wave, and reflection coefficient?*

**A:** Absolutely! A microwave engineer has a **choice** to make when describing transmission line activity.

### HO: $V, I, Z$ OR $V^+, V^-, \Gamma$ ?

# The Telegrapher Equations

Consider a section of "wire":

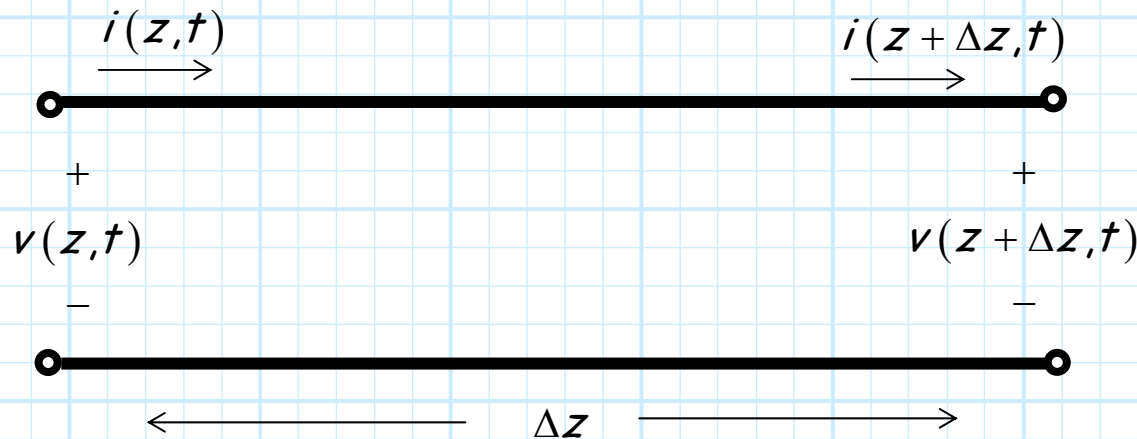

Where:

$$i(z, t) \neq i(z + \Delta z, t)$$


$$v(z, t) \neq v(z + \Delta z, t)$$

**Q:** No way! Kirchoff's Laws tells me that:

$$i(z, t) = i(z + \Delta z, t)$$

$$v(z, t) = v(z + \Delta z, t)$$

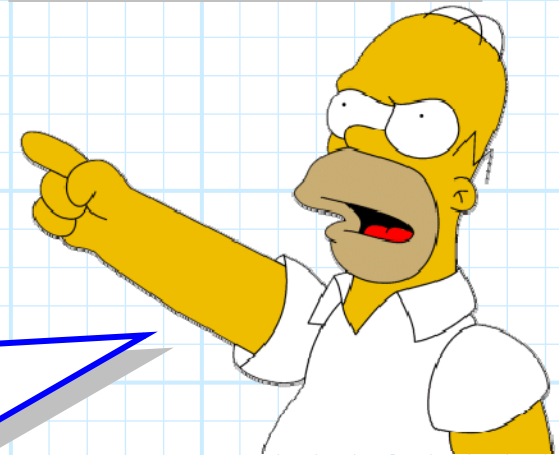
How can the voltage/current at the **end** of the line (at  $z + \Delta z$ ) be **different** than the voltage/current at the **beginning** of the line (at  $z$ )??



**A:** Way. The structure above actually exhibits some non-zero value of **inductance, capacitance, conductance, and admittance!**
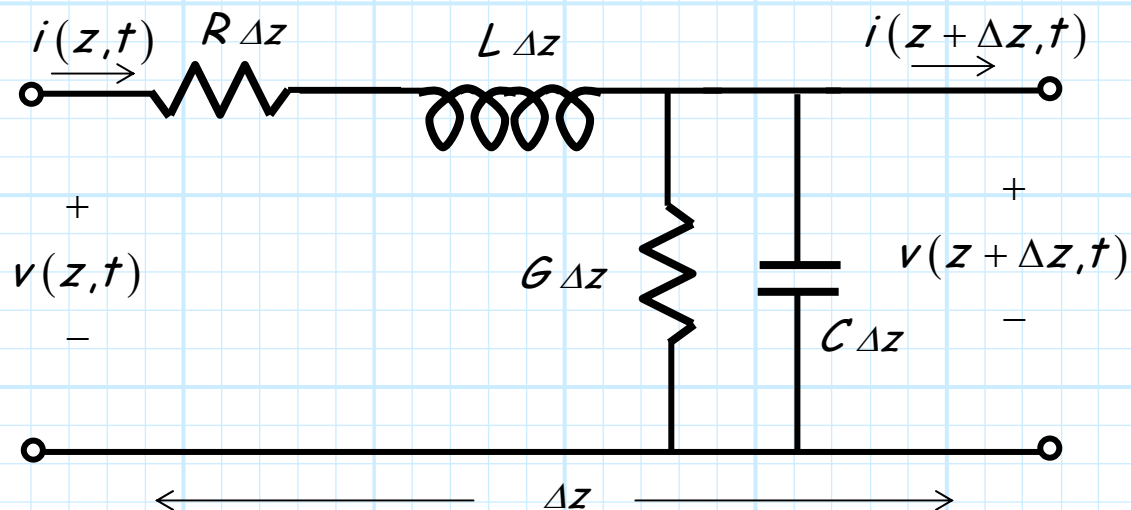
## An Accurate Model

A more accurate transmission line model is:



Where:

$R$  = resistance/unit length

$L$  = inductance/unit length

$C$  = capacitance/unit length

$G$  = conductance/unit length

$\therefore$  resistance of wire length  $\Delta z$  is  $R\Delta z$

Now evaluating KVL, we find:

$$v(z + \Delta z, t) - v(z, t) = -R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t} \neq 0$$

and from KCL:


$$i(z + \Delta z, t) - i(z, t) = -G\Delta z v(z, t) - C\Delta z \frac{\partial v(z, t)}{\partial t} \neq 0$$

# The Telegrapher's Equations


Dividing these equations by  $\Delta z$ , and then taking the limit as  $\Delta z \rightarrow 0$ , we find a set of **differential equations** that describe the voltage  $v(z,t)$  and current  $i(z,t)$  along a transmission line:

$$\frac{\partial v(z,t)}{\partial z} = -Ri(z,t) - L \frac{\partial i(z,t)}{\partial t}$$
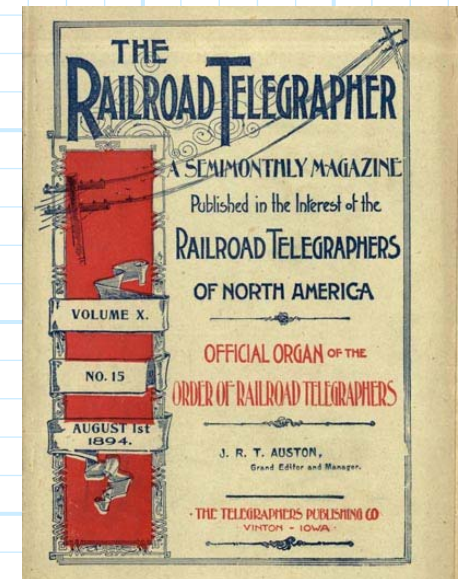
$$\frac{\partial i(z,t)}{\partial z} = -Gv(z,t) - C \frac{\partial v(z,t)}{\partial t}$$



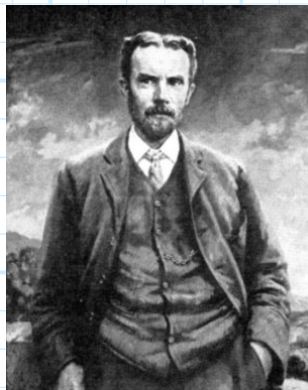These equations are known as the **telegrapher's equations**.



Derived by **Oliver Heaviside**, the telegrapher's equations are essentially the Maxwell's equations of transmission lines.

Although **mathematically** the functions  $v(z,t)$  and current  $i(z,t)$  can take any form, they can **physically exist only** if they satisfy the both of the differential equations shown above!

# Time-Harmonic Solutions for Transmission Lines


There are an unaccountably **infinite** number of solutions  $v(z,t)$  and  $i(z,t)$  for the telegrapher's equations!

However, we can simplify the problem by assuming that the function of time is **time harmonic** (i.e., sinusoidal), oscillating at some radial **frequency**  $\omega$  (e.g.,  $\cos \omega t$ ).

**Q:** *Why on earth would we assume a **sinusoidal** function of time?*

*Why not a **square wave**, or **triangle wave**, or a "sawtooth" function?*

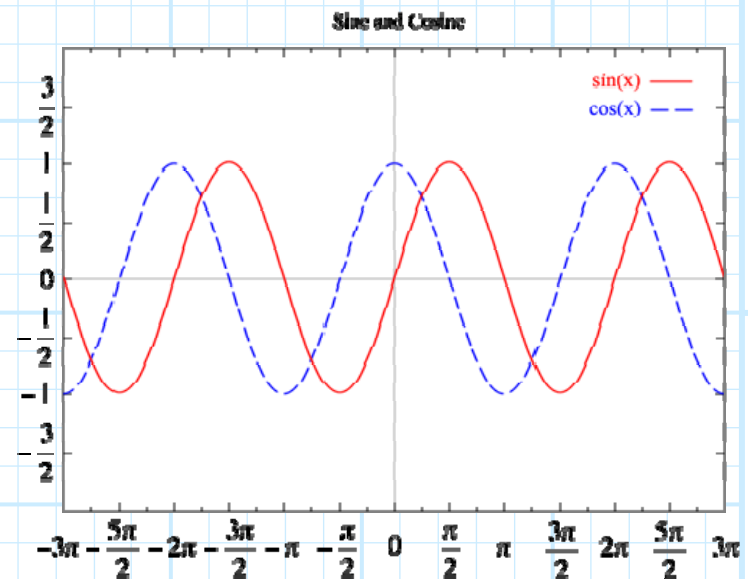**A:** We assume **sinusoids** because they have a **very special property!**





# Eigen Functions

Sinusoidal time functions—and **only** a sinusoidal time functions—are the **eigen functions** of **linear, time-invariant** systems.

→ If a sinusoidal voltage source with frequency  $\omega$  is used to excite a linear, time-invariant circuit (and a transmission line is **both** linear **and** time invariant!), then the voltage at each and **every** point with the circuit will likewise vary sinusoidally—at the same frequency  $\omega$ !

**Q:** *So, the sinusoidal function at every point in the circuit is **exactly** the same as the input sinusoid?*


**A:** Not quite **exactly** the same.

Although at every point within the circuit the voltage will be **precisely** sinusoidal (with frequency  $\omega$ ), the **magnitude** and **relative phase** of the sinusoid will generally be **different** at each and every point within the circuit.
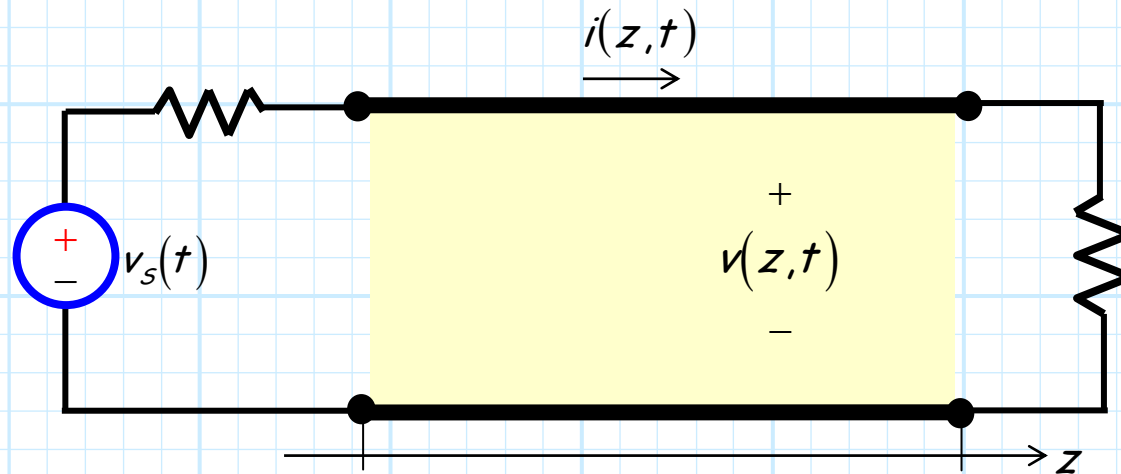
# Eigen Functions and Transmission Lines

Thus, the voltage along a transmission line—**when** excited by a sinusoidal source—**must** have the form:

$$v(z,t) = v(z) \cos(\omega t + \varphi(z))$$



In other words, at some arbitrary location  $z$  along the transmission line, we **must** find a time-harmonic oscillation of **magnitude**  $v(z)$  and **relative phase**  $\varphi(z)$ .

For a given frequency  $\omega$ , the **two functions**  $v(z)$  and  $\varphi(z)$  (functions of position  $z$  only!) **completely** describe the oscillating voltage at each and **every** point along the transmission line.

# A Complex Representation of $v(z, t)$

**Q:** *I just thought of something!*

*Our sinusoidal oscillations are described by a **magnitude** ( $v(z)$ ) and a **phase** ( $\varphi(z)$ )—but a complex value is **also** defined by its magnitude and phase (i.e.,  $c = |c|e^{j\varphi_c}$ ).*

*Is there a **connection** between our oscillations and a **complex value**?*

**A:** Absolutely! A connection made by **Euler's Identity**

$$e^{j\psi} = \cos \psi + j \sin \psi$$

From this it is apparent that:

$$\operatorname{Re} \{ e^{j\psi} \} = \cos \psi$$



*I hope I  
got this  
right...*

and so we conclude that the real **voltage** on a transmission line can be expressed as:

$$v(z, t) = v(z) \cos(\omega t + \varphi(z)) = \operatorname{Re} \left\{ v(z) e^{j(\omega t + \varphi(z))} \right\} = \operatorname{Re} \left\{ v(z) e^{+j\varphi(z)} e^{j\omega t} \right\}$$

# The Complex Function $V(z)$

It is apparent that we can specify the time-harmonic voltage at each and every location  $z$  along a transmission line with the **complex** function  $V(z)$ :

$$V(z) = v(z) e^{-j\phi(z)}$$

So that:


$$v(z, t) = v(z) \cos(\omega t + \phi(z)) = \text{Re} \{ v(z) e^{+j\phi(z)} e^{j\omega t} \} = \text{Re} \{ V(z) e^{j\omega t} \}$$

where the **magnitude** of the complex function is the **magnitude** of the sinusoid:

$$v(z) = |V(z)|$$

and the **phase** of the complex function is the **relative phase** of the sinusoid :

$$\phi(z) = \arg \{ V(z) \}$$

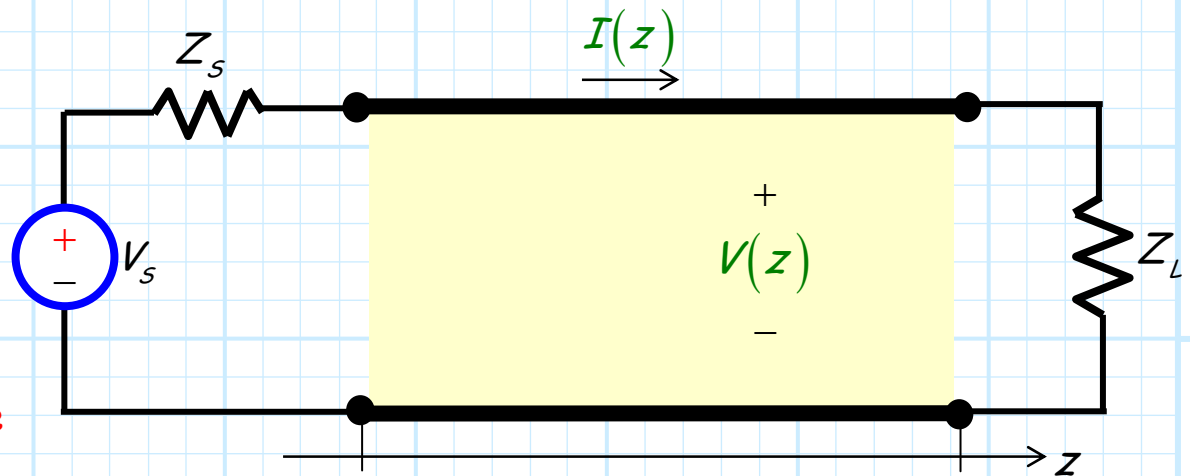

## All we need to determine is $V(z)$

Note then that only **unknown** is the **complex** function  $V(z)$ .

Once we determine  $V(z)$ , we can always (if we so desire) "recover" the **real** function  $v(z, t)$  as:

$$v(z, t) = \operatorname{Re} \left\{ V(z) e^{j\omega t} \right\} = v(z) \cos(\omega t + \varphi(z))$$

Thus, if we assume a **time-harmonic source**, finding the transmission line solution  $v(z, t)$  reduces to solving for the **complex function  $V(z)$** !


## Make this make sense to you

Microwave engineers almost **always** describe the activity of a transmission line (if excited by time harmonic sources) in terms of **complex functions of position  $z$**  — and **only** in terms of complex functions of position  $z$  !!




As a result, it is **unfathomably important** that you understand what these complex functions **mean**.

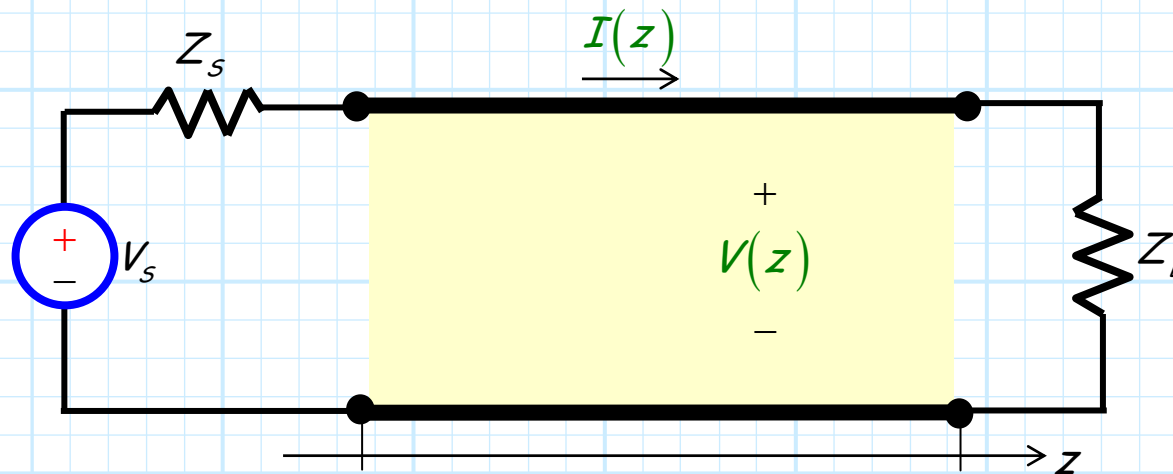You **must understand** what these complex functions are telling you about the currents, voltages, etc. along a transmission line.



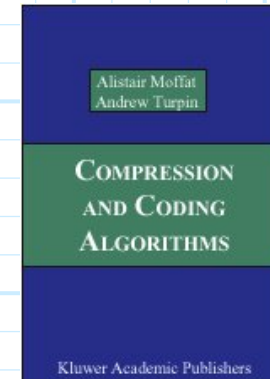
# The Complex Function $V(z)$ and You

Perhaps it's helpful to think about these functions as sort of a **compression algorithm**, with the important information "embedded" in the complex values.



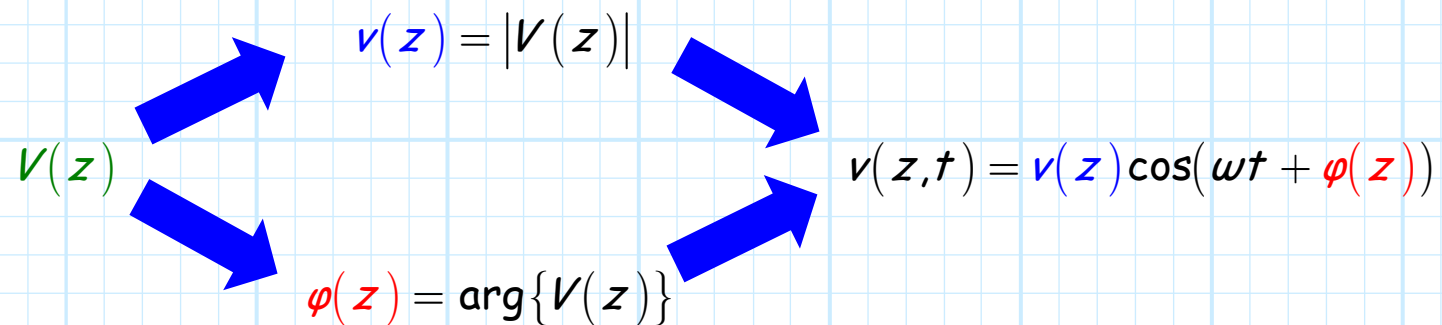To recover the information, we simply take the magnitude and phase of these complex values.



Note that the complex function  $V(z)$  is a function of position  $z$  only!

# Why we Love our Eigen Functions



**Q:** *Hey wait a minute! What happened to the time-harmonic function  $e^{j\omega t}$  ??*

**A:** There really is no reason to **explicitly** write the complex function  $e^{j\omega t}$ , since we know in fact (being the eigen function of linear systems and all) that if this is the time function at any **one** location (such as the excitation source) then this must be time function at **all** transmission line locations  $z$ .

The only **unknown** is the **complex function**  $V(z)$ !

Once we determine  $V(z)$ , we can always (if we so desire) "recover" the **real** function  $v(z, t)$  as:

$$\text{Re}\{V(z)e^{j\omega t}\} = v(z, t) = v(z)\cos(\omega t + \phi(z))$$

Thus, if we assume a **time-harmonic source**, finding the transmission line solution  $v(z, t)$  reduces to solving for the **complex function**  $V(z)$ !!!






## Quiz !!


See if **you** can determine what these complex values tell you about the **voltage** at different points  $z$  along a transmission line:

$$V(z = 0) = 3$$

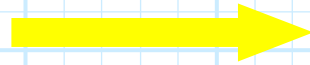


$$v(z = 0, t) = \cos(\omega t + \quad)$$

$$V(z = 1) = j$$

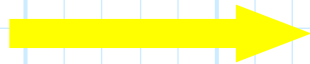


$$v(z = 1, t) = \cos(\omega t + \quad)$$

$$V(z = 2) = e^{j\pi/4}$$

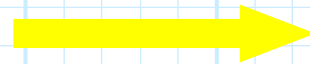


$$v(z = 2, t) = \cos(\omega t + \quad)$$

$$V(z = 3) = -2$$

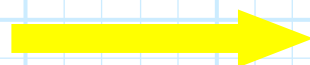


$$v(z = 3, t) = \cos(\omega t + \quad)$$

$$V(z = 4) = \sqrt{2} + j\sqrt{2}$$

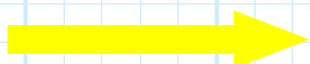

$$v(z = 4, t) = \cos(\omega t + \quad)$$

$$V(z = 5) = 3e^{-j\pi/4}$$

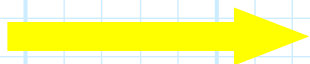

$$v(z = 5, t) = \cos(\omega t + \quad)$$

# The Transmission Line Wave Equations

So let's assume that  $v(z,t)$  and  $i(z,t)$  each have the **time-harmonic** form:

$$v(z,t) = \text{Re} \left\{ V(z) e^{j\omega t} \right\} \quad \text{and} \quad i(z,t) = \text{Re} \left\{ I(z) e^{j\omega t} \right\}$$

The **time-derivative** of these **eigen** functions are easily determined. E.G., :


$$\frac{\partial v(z,t)}{\partial t} = \text{Re} \left\{ V(z) \frac{\partial e^{j\omega t}}{\partial t} \right\} = \text{Re} \left\{ j\omega V(z) e^{j\omega t} \right\}$$

From this we can show that the **telegrapher equations** relate  $I(z)$  and  $V(z)$  as:

$$\frac{\partial V(z)}{\partial z} = -(R + j\omega L) I(z) \quad \frac{\partial I(z)}{\partial z} = -(G + j\omega C) V(z)$$

These are the **complex form** of the **telegrapher equations**.

# What's your quest?

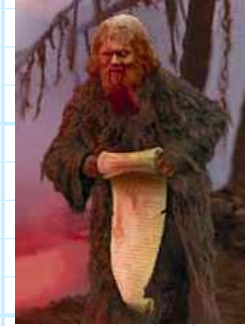

Note that these complex differential equations are **not** a function of **time  $t$** !

$$\frac{\partial V(z)}{\partial z} = -(R + j\omega L) I(z)$$

$$\frac{\partial I(z)}{\partial z} = -(G + j\omega C) V(z)$$



\* The functions  $I(z)$  and  $V(z)$  are **complex**, where the **magnitude** and **phase** of the complex functions describe the **magnitude** and **phase** of the sinusoidal time function  $e^{j\omega t}$ .

\* Thus,  $I(z)$  and  $V(z)$  describe the current and voltage along the transmission line, as a function as position  $z$ .

\* **Remember**, not just **any** function  $I(z)$  and  $V(z)$  can exist on a transmission line, but rather **only** those functions that satisfy the **telegraphers equations**.

Our quest, therefore, is to **solve** the telegrapher equations and find **all** solutions  $I(z)$  and  $V(z)$ !

# The Transmission Line Wave Equations

**Q:** So, what functions  $I(z)$  and  $V(z)$  **do** satisfy both telegrapher's equations??

**A:** The complex telegrapher's equations are a pair of **coupled** differential equations.

With a little mathematical elbow grease, we can **decouple** the telegrapher's equations, such that we now have **two** equations involving **one** function only:

$$\frac{\partial^2 V(z)}{\partial z^2} = \gamma^2 V(z)$$

$$\frac{\partial^2 I(z)}{\partial z^2} = \gamma^2 I(z)$$

where

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

These equations are known as the transmission line **wave equations**. Since they each involve only **one** unknown function they are **easily** solved!

# The (one and only) solution to the Wave Equations

The **solutions** to these wave equations are:

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} \qquad I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

where  $V_0^+$ ,  $V_0^-$ ,  $I_0^+$ , and  $I_0^-$  are **complex constants**.

→ It is **unfathomably** important that **you** understand what this result means!

It means that the functions  $V(z)$  and  $I(z)$ , describing the current and voltage at **all** points  $z$  along a transmission line, can **always** be **completely** specified with just **four complex constants** ( $V_0^+$ ,  $V_0^-$ ,  $I_0^+$ ,  $I_0^-$ )!!



# The wave interpretation

We can **alternatively** write these solutions as:

$$V(z) = V^+(z) + V^-(z)$$

$$I(z) = I^+(z) + I^-(z)$$

where:

$$V^+(z) \doteq V_0^+ e^{-\gamma z}$$

$$V^-(z) \doteq V_0^- e^{+\gamma z}$$

$$I^+(z) \doteq I_0^+ e^{-\gamma z}$$


$$I^-(z) \doteq I_0^- e^{+\gamma z}$$



**Q:** *Just what do the two functions  $V^+(z)$  and  $V^-(z)$  tell us? Do they have any physical meaning?*

**A:** An incredibly important physical meaning!

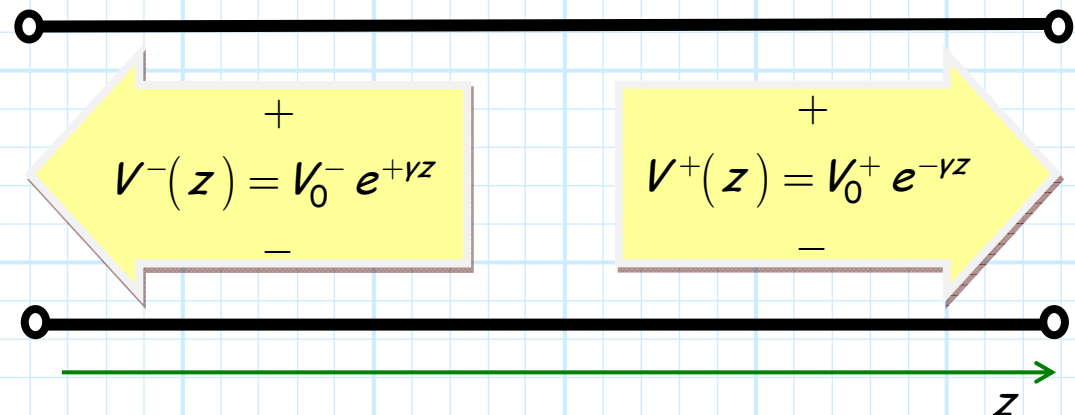Function  $V^+(z)$  describes a **wave propagating** in the direction of **increasing  $z$** , and  $V^-(z)$  describes a **wave** in the **opposite direction**.



## Complex amplitudes

**Q:** So just what *are* the complex values  $V_0^+$ ,  $V_0^-$ ,  $I_0^+$ ,  $I_0^-$  ?

**A:** They are called the **complex amplitudes** of each propagating wave.

**Q:** Do they have any *physical meaning*?

**A:** Consider the wave solutions at **one** specific point on the transmission line—the point where  $z=0$ . We find that the **complex value** of the wave at that point is:

$$\begin{aligned} V^+(z=0) &= V_0^+ e^{-\gamma(z=0)} \\ &= V_0^+ e^{-(0)} \\ &= V_0^+ (1) \\ &= V_0^+ \end{aligned}$$

likewise:

$$V_0^- = V^-(z=0)$$

$$I_0^+ = I^+(z=0)$$

$$I_0^- = I^-(z=0)$$


So, the complex **wave amplitude**  $V_0^+$  is simply the **complex** value of the wave function  $V^+(z=0)$  at the point  $z=0$  on the transmission line (that's what the **subscript**  $_0$  means—the value at  $z=0$ )!
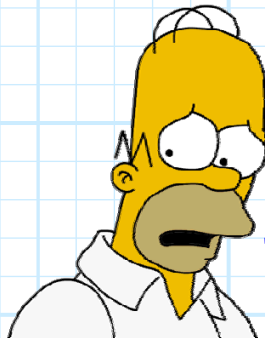
## Determining the 4 complex wave amplitudes



Again, the **four** complex values  $V_0^+$ ,  $I_0^+$ ,  $V_0^-$ ,  $I_0^-$  are **all** that is needed to determine the voltage and current at **any and all** points on the transmission line!

More specifically, **each** of these four complex constants completely specifies **one** of the four transmission line wave functions  $V^+(z)$ ,  $I^+(z)$ ,  $V^-(z)$ ,  $I^-(z)$ .



**Q:** *But what **determines** these wave functions? How do we **find** the values of constants  $V_0^+$ ,  $I_0^+$ ,  $V_0^-$ ,  $I_0^-$ ?*

**A:** As you might expect, the voltage and current on a transmission line is determined by the devices **attached** to it on either end (e.g., active **sources** and/or passive **loads**)!

The precise values of  $V_0^+$ ,  $I_0^+$ ,  $V_0^-$ ,  $I_0^-$  are therefore determined by satisfying the **boundary conditions** applied at **each end** of the transmission line—much more on this **later**!



# The Characteristic Impedance of a Transmission Line

So, from the **telegrapher's** differential equations, we know that the complex current  $I(z)$  and voltage  $V(z)$  **must** have the form:

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} \quad I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

Let's insert the expression for  $V(z)$  into the first telegrapher's equation, and **see what happens!**

$$\frac{dV(z)}{dz} = -\gamma V_0^+ e^{-\gamma z} + \gamma V_0^- e^{+\gamma z} = -(R + j\omega L)I(z)$$

Therefore, rearranging, current  $I(z)$  must be:

$$I(z) = \frac{\gamma}{R + j\omega L} (V_0^+ e^{-\gamma z} - V_0^- e^{+\gamma z})$$

## *I thought we knew this?!*

**Q:** *But wait! I thought we already knew current  $I(z)$ .*

*Isn't it:*

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z} \quad ??$$

*How can **both** expressions for  $I(z)$  be true??*



**A:** Easy! Both expressions for current are **equal** to each other.

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z} = \frac{\gamma}{R + j\omega L} (V_0^+ e^{-\gamma z} - V_0^- e^{+\gamma z})$$

For the above equation to be true for **all**  $z$ ,  $I_0$  and  $V_0$  must be related as:

$$I_0^+ e^{-\gamma z} = \left( \frac{\gamma}{R + j\omega L} \right) V_0^+ e^{-\gamma z} \quad \text{and} \quad I_0^- e^{+\gamma z} = \left( \frac{-\gamma}{R + j\omega L} \right) V_0^- e^{+\gamma z}$$

## A startling conclusion

Or—recalling that  $V_0^+ e^{-\gamma z} = V^+(z)$  (etc.)—we can express this in terms of the **two propagating waves**:

$$I^+(z) = \left( \frac{+\gamma}{R + j\omega L} \right) V^+(z) \quad \text{and} \quad I^-(z) = \left( \frac{-\gamma}{R + j\omega L} \right) V^-(z)$$

Now, we note that since:

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

We find that:

$$\frac{\gamma}{R + j\omega L} = \frac{\sqrt{(R + j\omega L)(G + j\omega C)}}{R + j\omega L} = \sqrt{\frac{G + j\omega C}{R + j\omega L}}$$

Thus, we come to the **startling** conclusion that:

$$\frac{V^+(z)}{I^+(z)} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad \text{and} \quad \frac{-V^-(z)}{I^-(z)} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

# Characteristic Impedance

**Q:** *What's so startling about this conclusion?*

**A:** Note that although each propagating wave is a **function** of transmission line **position**  $z$  (e.g.,  $V^+(z)$  and  $I^+(z)$ ), the **ratio** of the voltage and current of **each wave** is independent of position—a **constant** with respect to position  $z$ !

Although  $V_0^\pm$  and  $I_0^\pm$  are determined by **boundary conditions** (i.e., what's **connected** to either end of the transmission line), the **ratio**  $V_0^\pm/I_0^\pm$  is determined by the parameters of the **transmission line only** (i.e.,  $R, L, G, C$ ).

→ This ratio is an important **characteristic of a transmission line**, called its **Characteristic Impedance  $Z_0$** .

$$Z_0 \doteq \frac{V^+(z)}{I^+(z)} = \frac{-V_0^-(z)}{I_0^-(z)} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

## An alternative transmission line description

We can therefore describe the **current and voltage** along a transmission line as:

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{+\gamma z}$$

or equivalently:


$$V(z) = Z_0 I_0^+ e^{-\gamma z} - Z_0 I_0^- e^{+\gamma z}$$

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

→ Note that instead of characterizing a transmission line with **real** parameters  $R$ ,  $G$ ,  $L$ , and  $C$ , we can (and typically do!) describe a transmission line using **complex** parameters  $Z_0$  and  $\gamma$ .
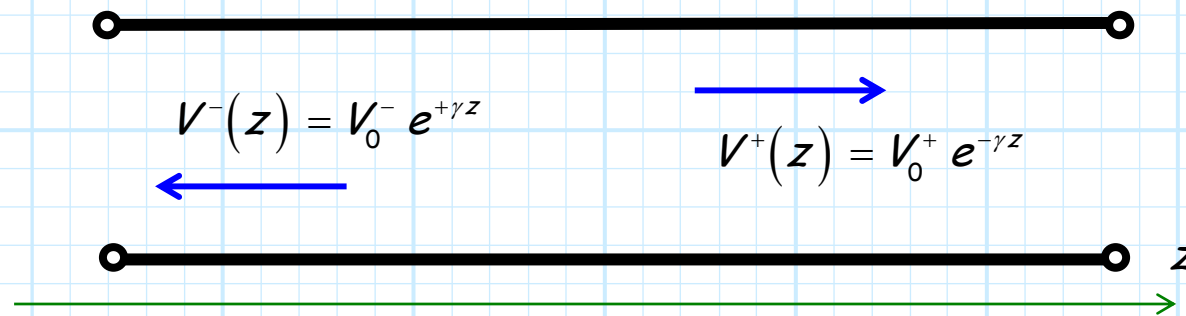
# Complex Propagation Constant $\gamma$

Recall that the activity along a transmission line can be expressed in terms of two functions, functions that we have described as **wave** functions:



where  $\gamma$  is a **complex constant** that describe the properties of a transmission line. Since  $\gamma$  is complex, we can consider both its **real** and **imaginary** components.

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} \doteq \alpha + j\beta$$

where  $\alpha = \text{Re}\{\gamma\}$  and  $\beta = \text{Im}\{\gamma\}$ . Therefore, we can write:

$$V^+(z) = V_0^+ e^{-\gamma z} = V_0^+ e^{-(\alpha + j\beta)z} = V_0^+ e^{-\alpha z} e^{-j\beta z}$$

## The value $\alpha$

**Q:** *What are these constants  $\alpha$  and  $\beta$ ? What do they physically represent?*

**A:** Remember, a complex value can be expressed in terms of its **magnitude** and **phase**.

For example:

$$V_0^+ = |V_0^+| e^{j\varphi_0^+}$$

Likewise:

$$V^+(z) = |V^+(z)| e^{j\varphi^+(z)}$$

And since:


$$\begin{aligned} V^+(z) &= V_0^+ e^{-\alpha z} e^{-j\beta z} \\ &= |V_0^+| e^{j\varphi_0^+} e^{-\alpha z} e^{-j\beta z} \\ &= |V_0^+| e^{-\alpha z} e^{j(\varphi_0^+ - \beta z)} \end{aligned}$$

we find:

$$|V^+(z)| = |V_0^+| e^{-\alpha z} \quad \varphi^+(z) = \varphi_0^+ - \beta z$$
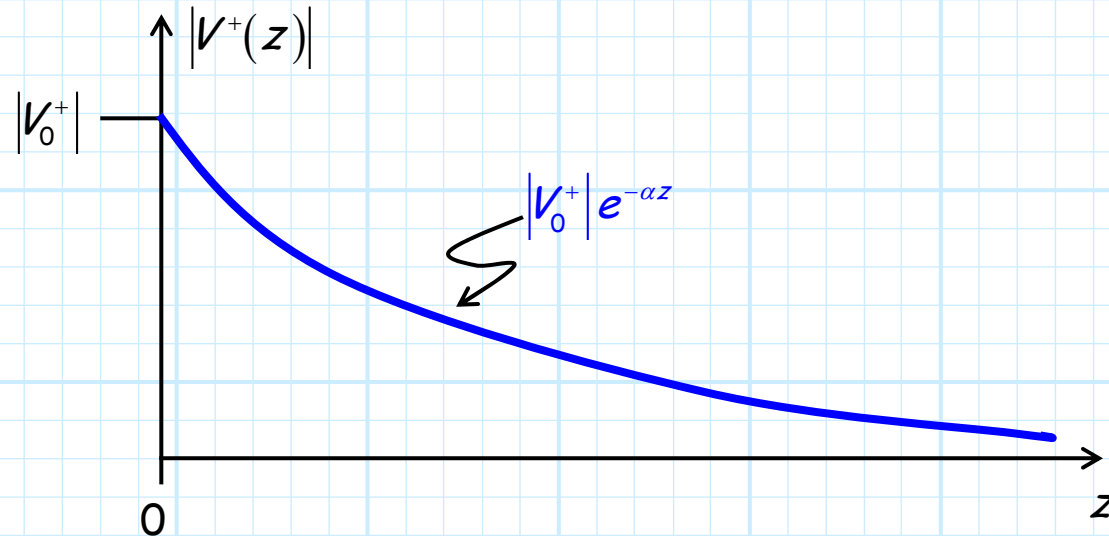
## The value $\alpha$ specifies attenuation

It is thus evident that  $e^{-\alpha z}$  **alone** determines the **magnitude** of wave  $V^+(z) = V_0^+ e^{-\gamma z}$  as a function of position  $z$ .



Therefore,  $\alpha$  expresses the **attenuation** of the signal due to the **loss** in the transmission line.

The **larger** the value of  $\alpha$ , the **greater** the exponential attenuation.

**Q:** *So just why does the wave attenuate as it propagates down the transmission line?*

**A:**



## The value $\beta$

**Q:** So what is the constant  $\beta$ ? What does it physically mean?

**A:** Recall the function;

$$\varphi^+(z) = \varphi_0^+ - \beta z$$

represents the relative **phase** of wave  $V^+(z)$ ; a **function** of transmission line **position**  $z$ .

Since phase  $\varphi$  is expressed in **radians**, and  $z$  is distance (in meters), the value  $\beta$  must have **units** of:

$$\beta = \frac{\varphi}{z} \quad \frac{\text{radians}}{\text{meter}}$$

Thus, if the value  $\beta$  is **small**, we will need to move a **significant distance**  $\Delta z$  down the transmission line in order to observe a change in the relative phase of the oscillation.

Conversely, if the value  $\beta$  is **large**, a significant change in relative phase can be observed if traveling a **short distance**  $\Delta z_{2\pi}$  down the transmission line.

## The Wavelength $\lambda$

**Q:** *How far must we move along a transmission line in order to observe a change in relative phase of  $2\pi$  radians?*

**A:** We can easily determine this distance ( $\Delta z_{2\pi}$ , say) from the transmission line characteristic  $\beta$ .

$$2\pi = \varphi(z + \Delta z_{2\pi}) - \varphi(z) = \beta \Delta z_{2\pi}$$

or, rearranging:

$$\Delta z_{2\pi} = \frac{2\pi}{\beta} \quad \Rightarrow \quad \beta = \frac{2\pi}{\Delta z_{2\pi}}$$

The **distance**  $\Delta z_{2\pi}$  over which the relative phase changes by  $2\pi$  **radians**, is more specifically known as the **wavelength**  $\lambda$  of the propagating wave (i.e.,  $\lambda \doteq \Delta z_{2\pi}$ ):

$$\lambda = \frac{2\pi}{\beta} \quad \Rightarrow \quad \beta = \frac{2\pi}{\lambda}$$

## $\beta$ is Spatial Frequency

The value  $\beta$  is thus essentially a **spatial frequency**, in the same way that  $\omega$  is a **temporal frequency**:

$$\omega = \frac{2\pi}{T}$$

Note  $T$  is the **time** required for the phase of the oscillating signal to change by a value of  $2\pi$  radians, i.e.:

$$\omega T = 2\pi$$

And the **period** of a sinewave, and related to its **frequency** in Hertz (cycles/second) as:

$$T = \frac{2\pi}{\omega} = \frac{1}{f}$$

Compare these results to:

$$\beta = \frac{2\pi}{\lambda} \quad 2\pi = \beta\lambda \quad \lambda = \frac{2\pi}{\beta}$$

# Propagation Velocity

**Q:** *So, just how fast does this wave propagate down a transmission line?*

**A:** We describe wave velocity in terms of its **phase velocity**—in other words, how **fast** does a specific value of absolute phase  $\varphi$  seem to **propagate** down the transmission line.

It can be shown that this velocity is:

$$v_p = \frac{dz}{dt} = \frac{\omega}{\beta}$$

From this we can conclude:

$$v_p = f\lambda$$


as well as:

$$\beta = \frac{\omega}{v_p}$$
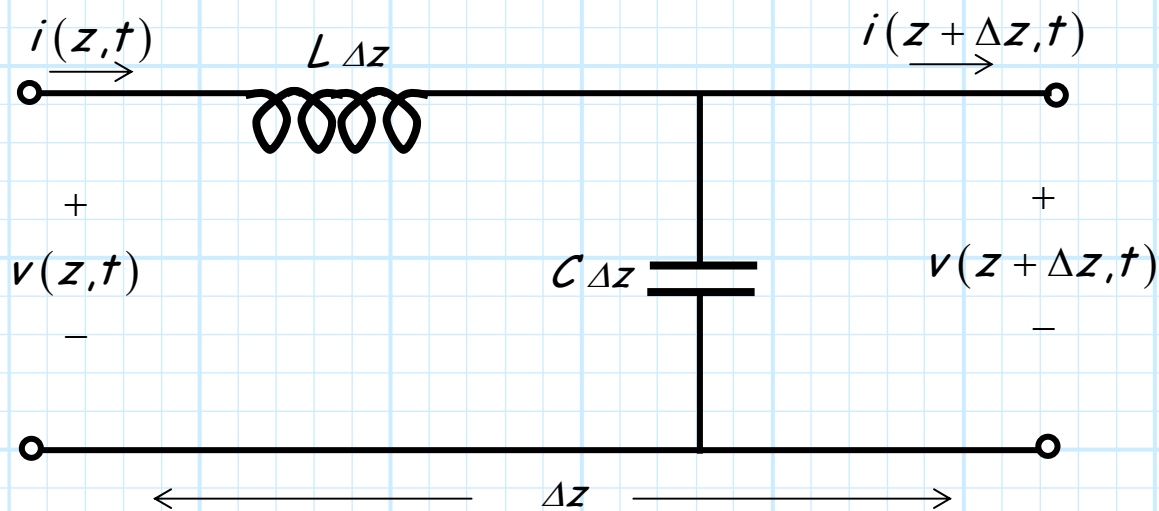
# The Lossless Transmission Line

Say a transmission line is **lossless** (i.e.,  $R = G = 0$ ).

Thus, this lossless transmission line is a **purely reactive** two port device—it exhibits only **capacitance** and **inductance**!!!



As a result, the transmission line equations are then **significantly** simplified!

## The characteristic impedance of the lossless transmission line

For example, the **characteristic impedance** of a lossless lines simply becomes:

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{j\omega L}{j\omega C}} = \sqrt{\frac{L}{C}}$$

Ironically, the characteristic **impedance** of a **lossless** (i.e., purely reactive) transmission line is—**purely real!**

## The propagation constant

Moreover, the **propagation constant** of a lossless line is purely **imaginary**:

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{(j\omega L)(j\omega C)} = \sqrt{-\omega^2 LC} = j\omega\sqrt{LC}$$

In other words, for a **lossless** transmission line:

$$\alpha = 0 \quad \text{and} \quad \beta = \omega\sqrt{LC}$$

Note that since  $\alpha = 0$ , **neither** propagating wave is **attenuated** as they travel down the line—a wave at the **end** of the line is as large as it was at the **beginning**!

→ And this makes sense!

Wave attenuation occurs when **energy is extracted** from the propagating wave and turned into **heat**.

This can **only** occur if resistance and/or conductance are present in the line.

If  $R = G = 0$ , then **no attenuation** occurs—that's why we call the line **lossless**.

## Velocity and Wavelength

The **complex functions** describing the magnitude and phase of the **voltage/current** at every location  $z$  along a transmission line are for a **lossless** line are:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$


$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

We can now **explicitly** write the **wavelength** and propagation **velocity** of the two transmission line waves in terms of transmission line parameters  $L$  and  $C$ :

$$\lambda = \frac{2\pi}{\beta} = \frac{1}{f\sqrt{LC}} \qquad v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$



## The low-loss approximation

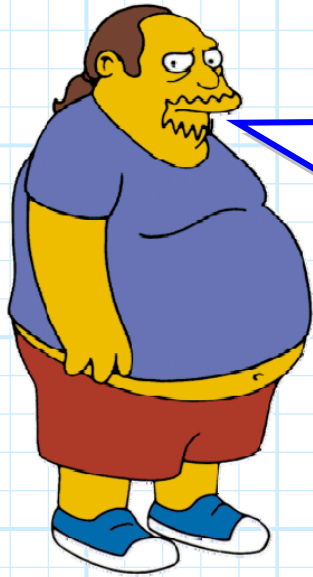

**Q:** *Oh please, continue wasting my valuable time.*

*We both know that a perfectly lossless transmission line is a physical impossibility.*

**A:** True! However, a **low-loss** line is possible—in fact, it is **typical!**

If  $R \ll \omega L$  and  $G \ll \omega C$ , we find that the lossless transmission line equations are excellent **approximations!**

Unless **otherwise** indicated, **we will use the lossless equations** to approximate the behavior of a **low-loss** transmission line.


The lone **exception** is when determining the attenuation of a **long** transmission line. For that case we will use the approximation:

$$\alpha \approx \frac{1}{2} \left( \frac{R}{Z_0} + GZ_0 \right)$$

where  $Z_0 = \sqrt{L/C}$ .
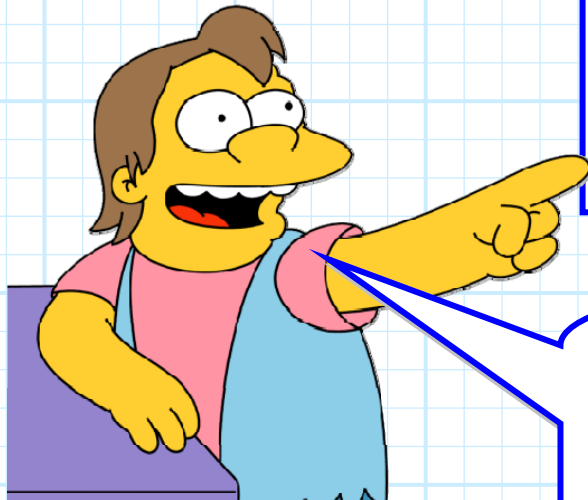
# Line Impedance

Now let's define **line impedance**  $Z(z)$ , a **complex** function which is simply the ratio of the complex line **voltage** and complex line **current**:



$$Z(z) = \frac{V(z)}{I(z)}$$

**Q:** *Hey! I know what this is!*

*The ratio of the voltage to current is simply the characteristic impedance  $Z_0$ , right ???*

**A:** **NO!** The line impedance  $Z(z)$  is (generally speaking) **NOT** the transmission line **characteristic impedance**  $Z_0$ !!!

→ It is **unfathomably important** that you understand this!!!! ←

## Why Line Impedance is not $Z_0$

To see why line impedance  $Z(z)$  is different than characteristic impedance  $Z_0$ , recall that:

$$V(z) = V^+(z) + V^-(z) \quad \text{and that} \quad I(z) = \frac{V^+(z) - V^-(z)}{Z_0}$$

Therefore, line impedance is:

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \left( \frac{V^+(z) + V^-(z)}{V^+(z) - V^-(z)} \right) \neq Z_0$$

Or, more specifically, we can write:

$$Z(z) = Z_0 \left( \frac{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}} \right)$$

## What then is $Z_0$ ?

**Q:** *I'm confused! Isn't:*

$$V^+(z)/I^+(z) = Z_0 ???$$



**A:** Yes! That is true! The ratio of the voltage to current for **each** of the two propagating waves is  $\pm Z_0$ .

However, the ratio of the **sum** of the two voltages, to the **sum** of the two currents, is **not** equal to  $Z_0$  (generally speaking)!

→ This is actually confirmed by the expression of  $Z(z)$  above.

Say that  $V^-(z) = 0$ , so that only **one** wave ( $V^+(z)$ ) is propagating on the line.

In this case, the ratio of the **total** voltage to the total current is simply the ratio of the voltage and current of the **one** remaining wave—the **characteristic impedance**  $Z_0$ !

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \left( \frac{V^+(z)}{I^+(z)} \right) = \frac{V^+(z)}{I^+(z)} = Z_0 \quad (\text{when } V^-(z) = 0)$$

## Let's Summarize!!

**Q:** *So, it appears to me that characteristic impedance  $Z_0$  is a transmission line parameter, depending **only** on the transmission line values  $L$  and  $C$ .*

*Whereas line impedance is  $Z(z)$  depends the magnitude and phase of the two propagating waves  $V^+(z)$  and  $V^-(z)$  —values that depend **not only** on the transmission line, but also on the two things **attached** to either **end** of the transmission line!*

*Right !?*



**A:** Exactly!

Moreover, note that characteristic impedance  $Z_0$  is simply a **number**, whereas line impedance  $Z(z)$  is a **function** of position ( $z$ ) on the transmission line.


# The Reflection Coefficient

So, we know that the transmission line **voltage**  $V(z)$  and the transmission line **current**  $I(z)$  can be related by the **line impedance**  $Z(z)$ :

$$V(z) = Z(z) I(z) \quad \text{or equivalently} \quad I(z) = \frac{V(z)}{Z(z)}$$

**Q:** *Piece of cake! I fully understand the concepts of **voltage**, **current** and **impedance** from my **circuits** classes.*

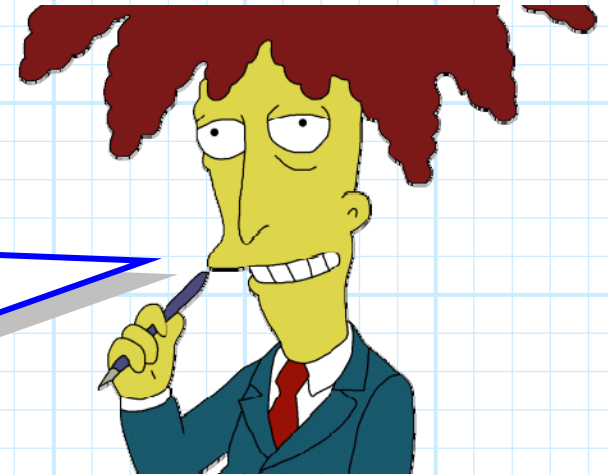*Let's move on to something more important (or, at the very least, more **interesting**).*



Expressing the "activity" on a transmission line in terms of **voltage**, **current** and **impedance** is of course **perfectly** valid.



→ However, there is an **alternative** (and much simpler!) way to describe transmission line activity !!!!

# Wave Functions $V^+(z)$ and $V^-(z)$ Describe All!

Look closely at the expressions for **voltage**, **current**, and **impedance**:

$$V(z) = V^+(z) + V^-(z) \quad I(z) = \frac{V^+(z) - V^-(z)}{Z_0} \quad Z(z) = Z_0 \left( \frac{V^+(z) + V^-(z)}{V^+(z) - V^-(z)} \right)$$

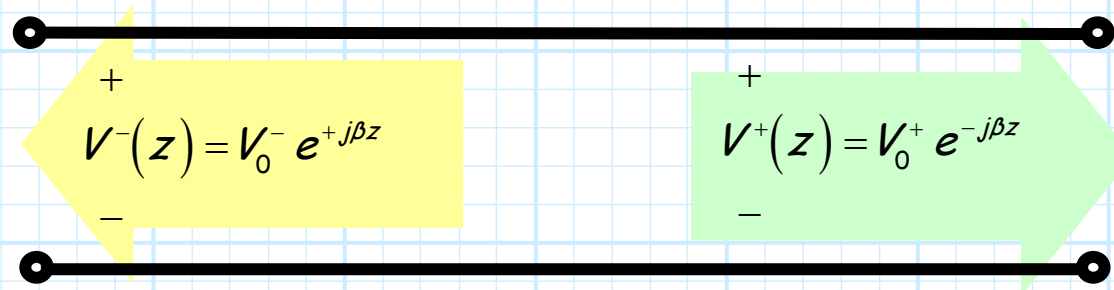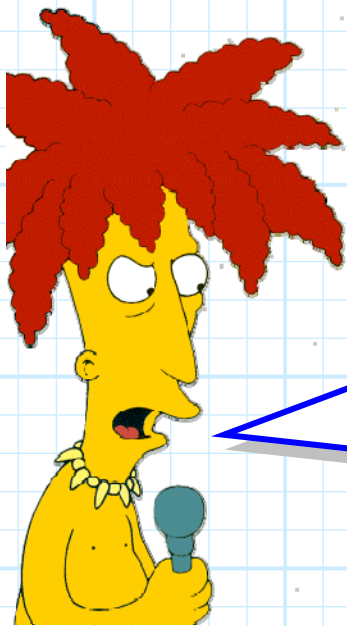It is evident that we can **alternatively** express all "activity" on the transmission line in terms of the two transmission line **waves**  $V^+(z)$  and  $V^-(z)$ .



**Q:** I know  $V(z)$  and  $I(z)$  are **related** by line impedance  $Z(z)$ :

$$Z(z) = \frac{V(z)}{I(z)}$$

But how are  $V^+(z)$  and  $V^-(z)$  related?

# The Reflection Coefficient Function

**A:** Similar to line impedance, we can define a new parameter—the **reflection coefficient**  $\Gamma(z)$ —as the **ratio** of the two quantities:

$$\Gamma(z) \doteq \frac{V^-(z)}{V^+(z)} \quad \Rightarrow \quad V^-(z) = \Gamma(z) V^+(z)$$

More **specifically**, we can express  $\Gamma(z)$  as:

$$\Gamma(z) = \frac{V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z}} = \frac{V_0^-}{V_0^+} e^{+j2\beta z}$$

Note then, the value of the reflection coefficient at  $z = 0$  is:

$$\Gamma(z=0) = \frac{V^-(z=0)}{V^+(z=0)} e^{+j2\beta(0)} = \frac{V_0^-}{V_0^+}$$



## The Value $\Gamma_0$

We define this value as  $\Gamma_0$ , where:

$$\Gamma_0 \doteq \Gamma(z=0) = \frac{V_0^-}{V_0^+}$$

Note then that we can **alternatively** write  $\Gamma(z)$  as:

$$\Gamma(z) = \Gamma_0 e^{+j2\beta z}$$

So we have **two different**, but equivalent ways, to describe transmission line activity!

We can use (total) **voltage** and **current**, related by **line impedance**:


$$Z(z) = \frac{V(z)}{I(z)} \quad \therefore \quad V(z) = Z(z) I(z)$$

Or, ...
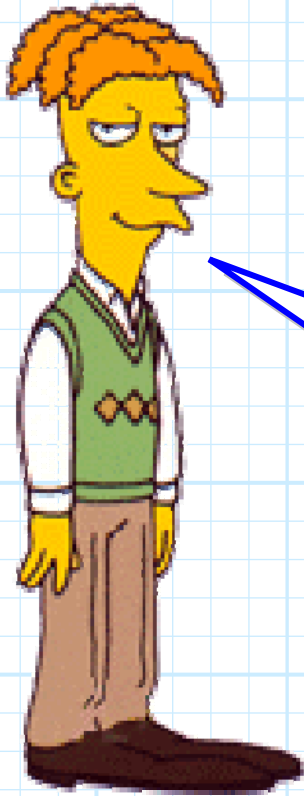
# The Wave Description of Transmission Line Activity

.....we can use the two propagating **voltage waves**, related by the **reflection coefficient**:

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} \quad \therefore \quad V^-(z) = \Gamma(z) V^+(z)$$



These are **equivalent** relationships—we can use **either** when describing a transmission line.

*Based on your **circuits** experience, you might well be **tempted** to always use the **first** relationship.*

*However, we will find it useful (as well as simple) indeed to describe activity on a transmission line in terms of the **second** relationship—in terms of the **two** propagating transmission line **waves**!*

# V, I, Z or V<sup>+</sup>, V<sup>-</sup>, Γ?

**Q:** How do I choose *which* relationship to use when describing/analyzing transmission line activity? What if I make the **wrong** choice? How will I know if my analysis is correct?

**A:** Remember, the two relationships are **equivalent**.

There is **no** explicitly wrong or right choice—**both** will provide you with precisely the **same** correct answer!

For example, we know that the total voltage and current can be determined from knowledge wave representation:

$$\begin{aligned}
 V(z) &= V^+(z) + V^-(z) \\
 &= V^+(z)(1 + \Gamma(z))
 \end{aligned}
 \qquad
 \begin{aligned}
 I(z) &= \frac{V^+(z) - V^-(z)}{Z_0} \\
 &= \frac{V^+(z)(1 - \Gamma(z))}{Z_0}
 \end{aligned}$$



## A direct mapping from $Z$ to $\Gamma$

More importantly, we find that **line impedance**  $Z(z) = V(z)/I(z)$  can be expressed as:

$$\begin{aligned} Z(z) &= Z_0 \frac{V^+(z) + V^-(z)}{V^+(z) - V^-(z)} \\ &= Z_0 \left( \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \right) \end{aligned}$$

→ **Look** what happened—the line impedance can be **completely** and unambiguously expressed in terms of **reflection coefficient**  $\Gamma(z)$ !

## And a mapping from $\Gamma$ to $Z$

With a little **algebra**, we find likewise that the wave functions can be determined from  $V(z)$ ,  $I(z)$  and  $Z(z)$ :

$$\begin{aligned}
 V^+(z) &= \frac{V(z) + I(z)Z_0}{2} & V^-(z) &= \frac{V(z) - I(z)Z_0}{2} \\
 &= \frac{V(z)}{Z(z)} \left( \frac{Z(z) + Z_0}{2} \right) & &= \frac{V(z)}{Z(z)} \left( \frac{Z(z) - Z_0}{2} \right)
 \end{aligned}$$

From this result we easily find that the reflection coefficient  $\Gamma(z)$  can **likewise** be written directly in terms of **line impedance**:

$$\Gamma(z) = \frac{Z(z) - Z_0}{Z(z) + Z_0}$$

# The two representations are equivalent!

Thus, the values  $\Gamma(z)$  and  $Z(z)$  are **equivalent** parameters—if we know **one**, then we can directly determine the **other**—each is dependent on transmission line parameters  $(L, C, R, G)$  **only!**



**Q:** *So, if they are equivalent, why wouldn't I **always** use the current, voltage, line impedance representation?*

*After all, I am more **familiar** and more confident those quantities.*

*The **wave** representation sort of **scares** me!*

**A:** Perhaps I can **convince** you of the value of the **wave** representation.

Remember, the time-harmonic solution to the telegraphers equation simply boils down to **two complex constants**— $V_0^+$  and  $V_0^-$ .

Once these complex values have been determined, we can describe **completely** the activity **all** points along our transmission line.

## Look how simple this is!

For the **wave representation** we find:

$$V^+(z) = V_0^+ e^{-j\beta z} \quad V^-(z) = V_0^- e^{+j\beta z} \quad \Gamma(z) = \frac{V_0^-}{V_0^+} e^{+j2\beta z}$$

Note that the **magnitudes** of the complex functions are in fact **constants** (with respect to position  $z$ ):

$$|V^+(z)| = |V_0^+| \quad |V^-(z)| = |V_0^-| \quad |\Gamma(z)| = \left| \frac{V_0^-}{V_0^+} \right|$$

While the **relative phase** of these complex functions are expressed as a **simple** linear relationship with respect to  $z$ :

$$\arg\{V^+(z)\} = -\beta z \quad \arg\{V^-(z)\} = +\beta z \quad \arg\{\Gamma(z)\} = +2\beta z$$

# Yuck!

Now, contrast this with the complex **current, voltage, impedance** functions:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = \frac{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}}{Z_0}$$

$$Z(z) = Z_0 \frac{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}}$$

With magnitudes:

$$|V(z)| = |V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}| = ??$$

$$|I(z)| = \frac{|V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}|}{Z_0} = ??$$

$$|Z(z)| = Z_0 \frac{|V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}|}{|V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}|} = ??$$



## $V^+$ , $V^-$ , $\Gamma$ is much simpler

And likewise phase:

$$\arg\{V(z)\} = \arg\{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}\} = ??$$

$$\arg\{I(z)\} = \arg\{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}\} = ??$$

$$\begin{aligned} \arg\{Z(z)\} &= \arg\{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}\} \\ &\quad - \arg\{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}\} \\ &= ?? \end{aligned}$$



**Q:** *It appears to me that when attempting to describe the activity along a transmission line—as a function of **position**  $z$ —it is much **easier** and more **straightforward** to use the **wave** representation(nyuck, nyuck, nyuck).*

**A:** That's right! However, this does **not** mean that we **never** determine  $V(z)$ ,  $I(z)$ , or  $Z(z)$ ; these quantities are still **fundamental** and very important—particularly at each **end** of the transmission line!