

2.3 - The Terminated, Lossless Transmission Line

Reading Assignment: pp. 57-64

We now know that a **lossless** transmission line is **completely** characterized by **real** constants Z_0 and β .

Likewise, the **2 waves** propagating on a transmission line are **completely** characterized by **complex** constants V_0^+ and V_0^- .

Q: Z_0 and β are determined from L , C , and ω . How do we find V_0^+ and V_0^- ?

A: Apply **Boundary Conditions!**

Every transmission line has **2 "boundaries"**

- 1) At one end of the transmission line.
- 2) At the **other** end of the trans line!

Typically, there is a **source** at one end of the line, and a **load** at the other.

→ The purpose of the transmission line is to get power **from** the source, **to** the load!

Let's apply the **load** boundary condition!

HO: THE TERMINATED, LOSSLESS TRANSMISSION LINE

Q: *So, the purpose of the transmission line is to transfer E.M. energy from the source to the load. Exactly how much power is flowing in the transmission line, and how much is delivered to the load?*

A: HO: INCIDENT, REFLECTED, AND ABSORBED POWER

Let's look at several "special" values of **load impedance**, as well as the interesting transmission line behavior they create.

HO: SPECIAL VALUES OF LOAD IMPEDANCE

Q: *So the line impedance at the **end** of a line must be load impedance Z_L (i.e., $Z(z = z_L) = Z_L$); what is the line impedance at the **beginning** of the line (i.e., $Z(z = z_L - \ell) = ?$)?*

A: The input impedance !

HO: TRANSMISSION LINE INPUT IMPEDANCE

EXAMPLE: INPUT IMPEDANCE

Q: *For a given Z_L we can determine an equivalent Γ_L . Is there an equivalent Γ_{in} for each Z_{in} ?*

A: HO: THE REFLECTION COEFFICIENT TRANSFORMATION

Note that we can **specify** a load with its impedance Z_L or equivalently, its reflection coefficient Γ_L .

Q: *But these are both complex values. Isn't there a way of specifying a load with a real value?*

A: Yes (sort of)! The two most common methods are Return Loss and **VSWR**.

HO: RETURN LOSS AND VSWR

Q: *What happens if our transmission line is terminated by something **other** than a load? Is our transmission line theory **still** valid?*

A: As long as a transmission line is connected to linear devices our theory is valid. However, we must be careful to properly apply the **boundary conditions** associated with each linear device!


EXAMPLE: THE TRANSMISSION COEFFICIENT

EXAMPLE: APPLYING BOUNDARY CONDITIONS

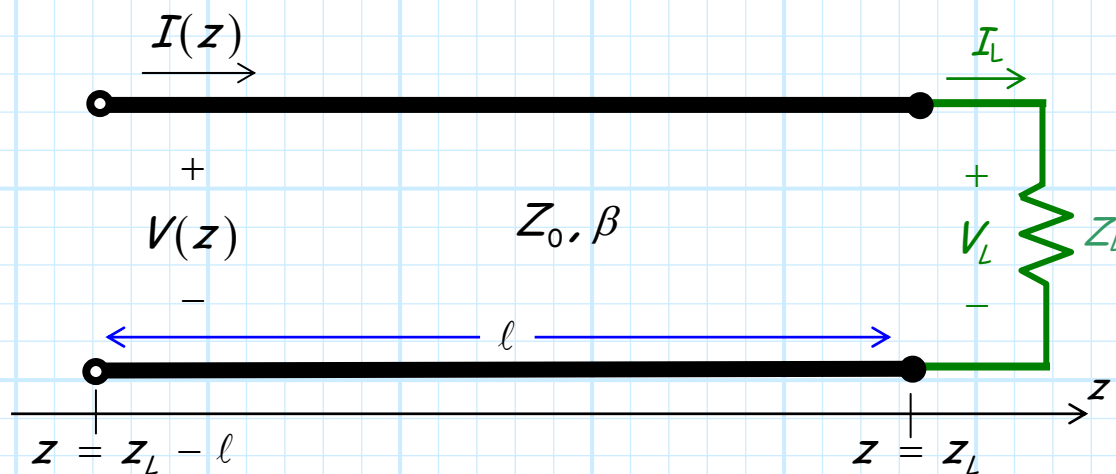EXAMPLE: ANOTHER BOUNDARY CONDITION PROBLEM

The Terminated, Lossless Transmission Line

Now let's **attach** something to our transmission line. Consider a lossless line, length ℓ , terminated with a load Z_L .



Q: What is the **current and voltage** at each and **every** point on the transmission line (i.e., what is $I(z)$ and $V(z)$ for **all** points z where $z_L - \ell \leq z \leq z_L$?)?

A: To find out, we must apply **boundary conditions!**

In other words, at the **end** of the transmission line ($z = z_L$)—where the load is **attached**—we have **many** requirements that **all** must be satisfied!

Requirement 1. To begin with, the voltage and current ($I(z = z_L)$ and $V(z = z_L)$) must be consistent with a valid transmission line solution:



$$\begin{aligned} V(z = z_L) &= V^+(z = z_L) + V^-(z = z_L) \\ &= V_0^+ e^{-j\beta z_L} + V_0^- e^{+j\beta z_L} \end{aligned}$$


$$\begin{aligned} I(z = z_L) &= \frac{V_0^+(z = z_L)}{Z_0} - \frac{V_0^-(z = z_L)}{Z_0} \\ &= \frac{V_0^+}{Z_0} e^{-j\beta z_L} - \frac{V_0^-}{Z_0} e^{+j\beta z_L} \end{aligned}$$

Requirement 2. Likewise, the load voltage and current must be related by **Ohm's law**:

$$V_L = Z_L I_L$$



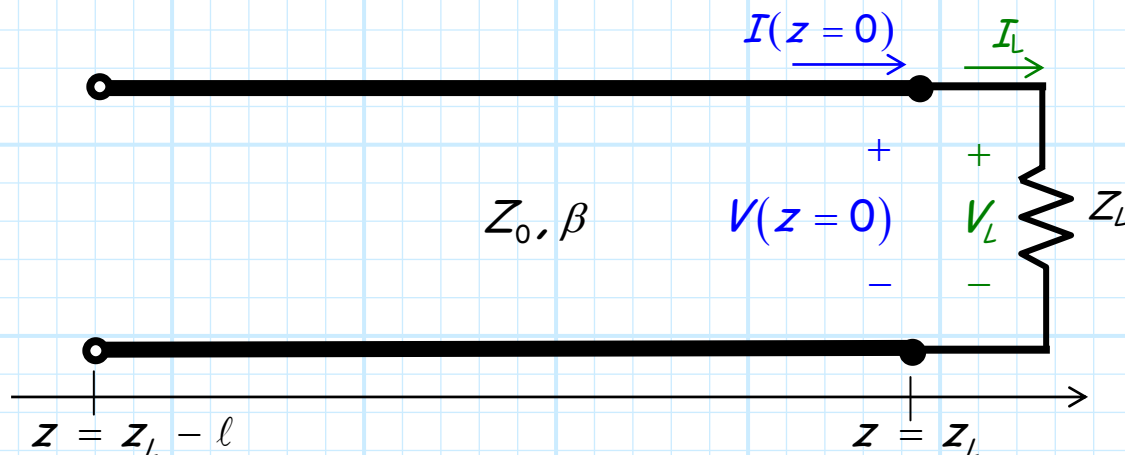Requirement 3. Most importantly, we recognize that the values $I(z = z_L)$, $V(z = z_L)$ and I_L , V_L are **not** independent, but in fact are strictly related by **Kirchoff's Laws**!




From KVL and KCL we find these requirements:



$$V(z = z_L) = V_L$$

$$I(z = z_L) = I_L$$

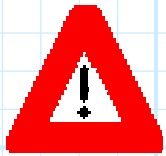These are the **boundary conditions** for **this** particular problem.



→ **Careful!** Different transmission line problems lead to **different** boundary conditions—you must access each problem **individually** and **independently!**

Combining these equations and boundary conditions, we find that:

$$V_L = Z_L I_L$$

$$V(z = z_L) = Z_L I(z = z_L)$$

$$V^+(z = z_L) + V^-(z = z_L) = \frac{Z_L}{Z_0} (V^+(z = z_L) - V^-(z = z_L))$$

Rearranging, we can conclude:

$$\frac{V^-(z = z_L)}{V^+(z = z_L)} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Q: *Hey wait as second! We earlier defined $V^-(z)/V^+(z)$ as reflection coefficient $\Gamma(z)$. How does this relate to the expression above?*

A: Recall that $\Gamma(z)$ is a **function** of transmission line position z . The value $V^-(z = z_L)/V^+(z = z_L)$ is simply the value of function $\Gamma(z)$ **evaluated** at $z = z_L$ (i.e., evaluated at the **end** of the line):

$$\frac{V^-(z = z_L)}{V^+(z = z_L)} = \Gamma(z = z_L) = \frac{Z_L - Z_0}{Z_L + Z_0}$$

This value is of **fundamental** importance for the terminated transmission line problem, so we provide it with its **own** special symbol (Γ_L)!

$$\Gamma_L \doteq \Gamma(z = z_L) = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Q: *Wait! We earlier determined that:*

$$\Gamma(z) = \frac{Z(z) - Z_0}{Z(z) + Z_0}$$

so it would seem that:

$$\Gamma_L = \Gamma(z = z_L) = \frac{Z(z = z_L) - Z_0}{Z(z = z_L) + Z_0}$$

Which expression is correct??

A: They **both** are! It is evident that the two expressions:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{and} \quad \Gamma_L = \frac{Z(z = z_L) - Z_0}{Z(z = z_L) + Z_0}$$

are **equal** if:

$$Z(z = z_L) = Z_L$$

And since we know that from **Ohm's Law**:

$$Z_L = \frac{V_L}{I_L}$$

and from **Kirchoff's Laws**:

$$\frac{V_L}{I_L} = \frac{V(z = z_L)}{I(z = z_L)}$$

and that **line impedance** is:


$$\frac{V(z = z_L)}{I(z = z_L)} = Z(z = z_L)$$

we find it apparent that the **line impedance** at the **end** of the transmission line is **equal** to the **load impedance**:

$$Z(z = z_L) = Z_L$$

The above expression is essentially **another** expression of the **boundary condition** applied at the **end** of the transmission line.

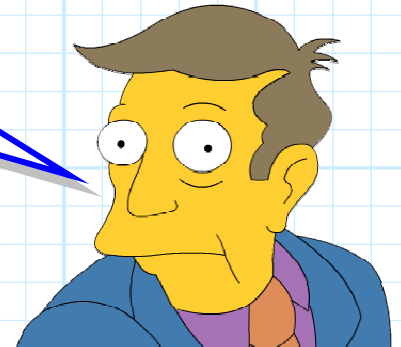Q: *I'm confused! Just what are we trying to accomplish in this handout?*



A: We are trying to find $V(z)$ and $I(z)$ when a lossless transmission line is terminated by a load Z_L !

We can now determine the value of V_0^- in terms of V_0^+ . Since:

$$\Gamma_L = \frac{V^-(z=z_L)}{V^+(z=z_L)} = \frac{V_0^- e^{j\beta z_L}}{V_0^+ e^{-j\beta z_L}}$$

We find:

$$V_0^- = e^{-2j\beta z_L} \Gamma_L V_0^+$$

And therefore we find:

$$V^-(z) = \left(e^{-2j\beta z_L} \Gamma_L V_0^+ \right) e^{j\beta z}$$

$$V(z) = V_0^+ \left[e^{-j\beta z} + \left(e^{-2j\beta z_L} \Gamma_L \right) e^{j\beta z} \right]$$


$$I(z) = \frac{V_0^+}{Z_0} \left[e^{-j\beta z} - \left(e^{-2j\beta z_L} \Gamma_L \right) e^{j\beta z} \right]$$

where:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$z_L = 0$$

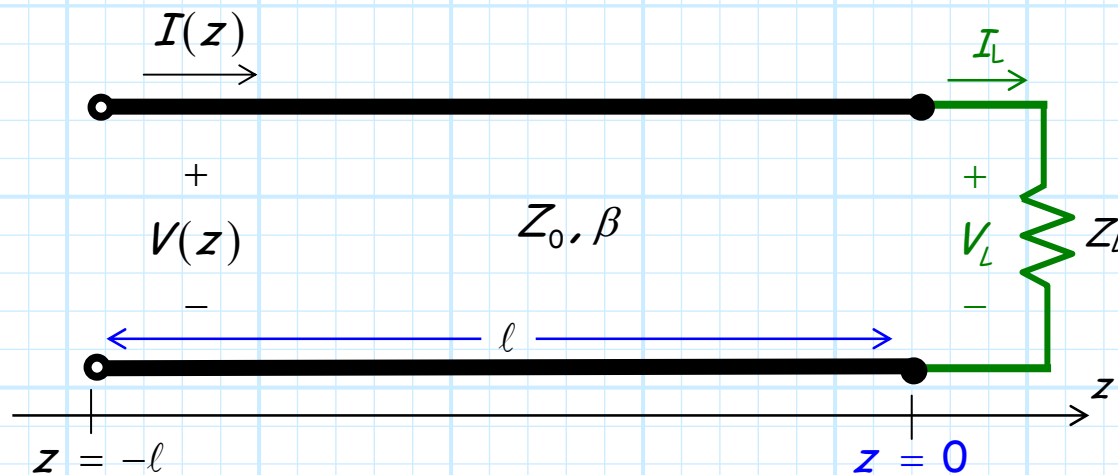Now, we can further **simplify** our analysis by **arbitrarily** assigning the end point z_L a **zero** value (i.e., $z_L = 0$):



If the load is located at $z=0$ (i.e., if $z_L = 0$), we find that:

$$\begin{aligned} V(z=0) &= V^+(z=0) + V^-(z=0) \\ &= V_0^+ e^{-j\beta(0)} + V_0^- e^{+j\beta(0)} \\ &= V_0^+ + V_0^- \end{aligned}$$

$$\begin{aligned} I(z=0) &= \frac{V_0^+(z=0)}{Z_0} - \frac{V_0^-(z=0)}{Z_0} \\ &= \frac{V_0^+}{Z_0} e^{-j\beta(0)} - \frac{V_0^-}{Z_0} e^{+j\beta(0)} \\ &= \frac{V_0^+ - V_0^-}{Z_0} \end{aligned}$$

$$Z(z=0) = Z_0 \left(\frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right)$$

Likewise, it is apparent that if $z_L = 0$, Γ_L and Γ_0 are the same:

$$\Gamma_L = \Gamma(z = z_L) = \frac{V^-(z = 0)}{V^+(z = 0)} = \frac{V_0^-}{V_0^+} = \Gamma_0$$

Therefore if $z_L = 0$:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \Gamma_0$$

Thus, we can write the line current and voltage simply as:

$$V(z) = V_0^+ [e^{-j\beta z} + \Gamma_0 e^{+j\beta z}]$$

$$I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma_0 e^{+j\beta z}]$$


[for $z_L = 0$]

Q: *But, how do we determine V_0^+ ??*

A: We require a **second** boundary condition to determine V_0^+ . The only boundary left is at the **other end** of the transmission line. Typically, a **source** of some sort is located there. This makes physical sense, as something must generate the **incident wave**!

Incident, Reflected, and Absorbed Power

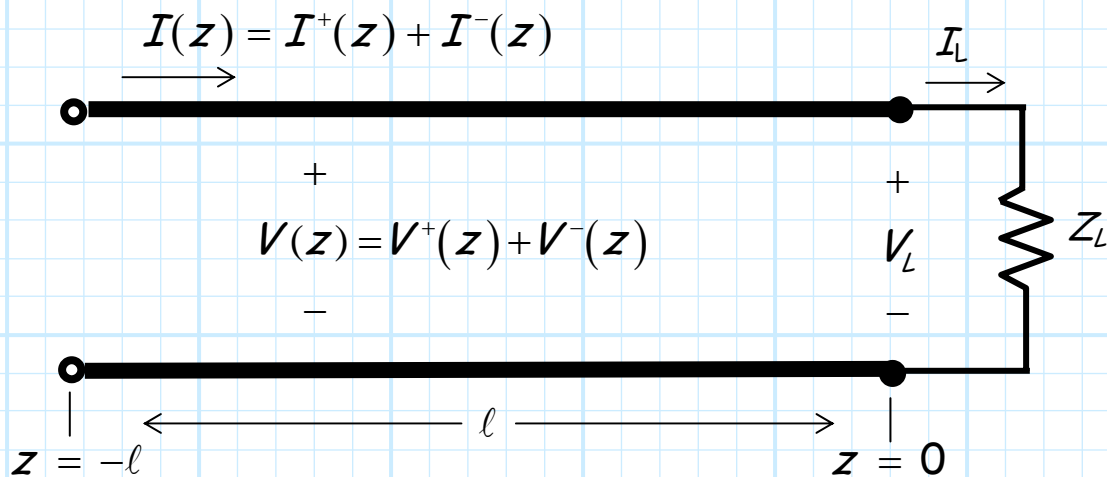We have discovered that **two waves propagate** along a transmission line, one in each direction ($V^+(z)$ and $V^-(z)$).



The result is that electromagnetic energy flows along the transmission line at a given rate (i.e., **power**).

Q: *How much power flows along a transmission line, and where does that power go?*

A: We can answer that question by determining the **power absorbed** by the load!

You of course recall that the **time-averaged** power (a **real** value!) absorbed by a **complex** impedance Z_L is:

$$P_{abs} = \frac{1}{2} \operatorname{Re}\{V_L I_L^*\}$$

Of course, the **load** voltage and current is simply the voltage and current at the **end** of the transmission line (at $z = 0$). A **happy** result is that we can then use our **transmission line theory** to determine this absorbed power:

$$\begin{aligned} P_{abs} &= \frac{1}{2} \operatorname{Re}\{V_L I_L^*\} \\ &= \frac{1}{2} \operatorname{Re}\{V(z=0) I(z=0)^*\} \\ &= \frac{1}{2 Z_0} \operatorname{Re}\left\{ \left(V_0^+ [e^{-j\beta 0} + \Gamma_0 e^{+j\beta 0}] \right) \left(V_0^+ [e^{-j\beta 0} - \Gamma_0 e^{+j\beta 0}] \right)^* \right\} \\ &= \frac{|V_0^+|^2}{2 Z_0} \operatorname{Re}\left\{ 1 - (\Gamma_0^* - \Gamma_0) - |\Gamma_0|^2 \right\} \\ &= \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_0|^2) \end{aligned}$$

The significance of this result can be seen by **rewriting** the expression as:

$$P_{abs} = \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_0|^2) = \frac{|V_0^+|^2}{2 Z_0} - \frac{|V_0^+ \Gamma_0|^2}{2 Z_0} = \frac{|V_0^+|^2}{2 Z_0} - \frac{|V_0^-|^2}{2 Z_0}$$

The two terms in above expression have a very definite **physical meaning**. The **first term** is the time-averaged **power of the wave** propagating along the transmission line **toward the load**.

We say that this wave is **incident** on the load:

$$P_{inc} = P_+ = \frac{|V_0^+|^2}{2Z_0}$$

Likewise, the second term of the P_{abs} equation describes the **power of the wave** moving in the other direction (**away from the load**). We refer to this as the wave **reflected** from the load:

$$P_{ref} = P_- = \frac{|V_0^-|^2}{2Z_0} = \frac{|\Gamma_L V_0^+|^2}{2Z_0} = |\Gamma_L|^2 \frac{|V_0^+|^2}{2Z_0} = |\Gamma_L|^2 P_{inc}$$

Thus, the power **absorbed** by the load (i.e., the power **delivered to the load**) is simply:


$$P_{abs} = \frac{|V_0^+|^2}{2Z_0} - \frac{|V_0^-|^2}{2Z_0} = P_{inc} - P_{ref}$$

or, rearranging, we find:

$$P_{inc} = P_{abs} + P_{ref}$$

This equation is simply an expression of the **conservation of energy** !

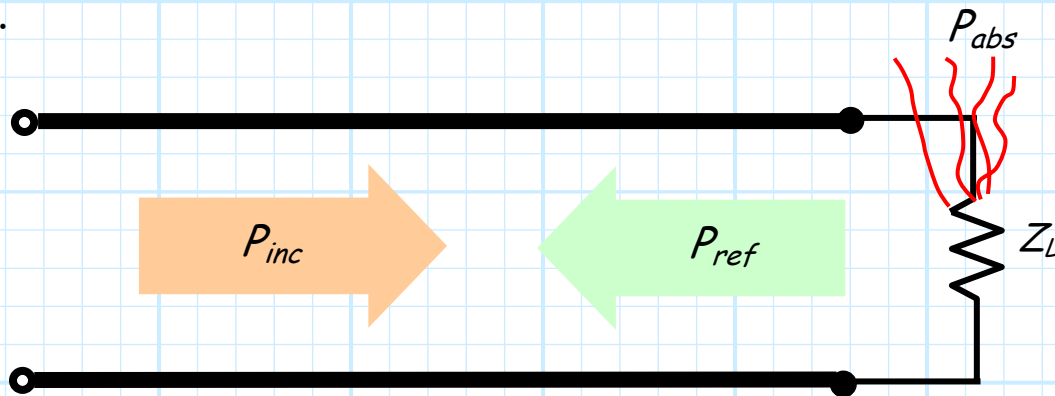It says that power flowing **toward** the load (P_{inc}) is either **absorbed** by the load (P_{abs}) or **reflected** back from the load (P_{ref}).



Now let's consider some special cases:

- $|\Gamma_L|^2 = 1$

For this case, we find that the load absorbs **no power!**

$$P_{abs} = P_{inc} (1 - |\Gamma_L|^2) = P_{inc} (1 - 1) = 0$$


Likewise, we find that the reflected power is **equal** to the incident:

$$P_{ref} = |\Gamma_L|^2 P_{inc} = (1) P_{inc} = P_{inc}$$

Note these two results are completely **consistent**—by conservation of energy, if one is true the other **must** also be:

$$P_{inc} = P_{abs} + P_{ref} = 0 + P_{ref} = P_{ref}$$

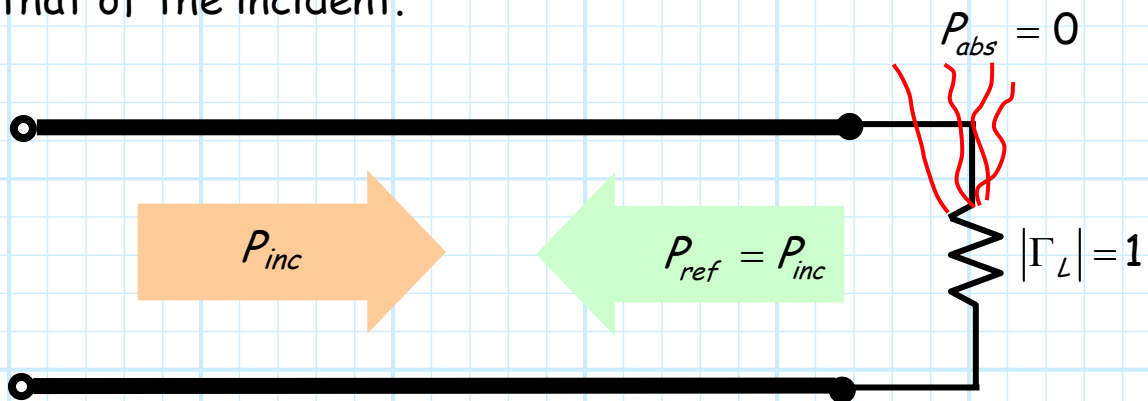In this case, **no power** is absorbed by the load. **All** of the incident power is **reflected**, so that the reflected power is **equal** to that of the incident.



2. $|\Gamma_L| = 0$

For this case, we find that there is **no reflected power!**

$$P_{ref} = |\Gamma_L|^2 P_{inc} = (0) P_{inc} = 0$$


Likewise, we find that the absorbed power is **equal** to the incident:

$$P_{abs} = P_{inc} (1 - |\Gamma_0|^2) = P_{inc} (1 - 0) = P_{inc}$$

Note these two results are completely **consistent**—by conservation of energy, if one is true the other **must** also be:

$$P_{inc} = P_{abs} + P_{ref} = P_{abs} + 0 = P_{abs}$$

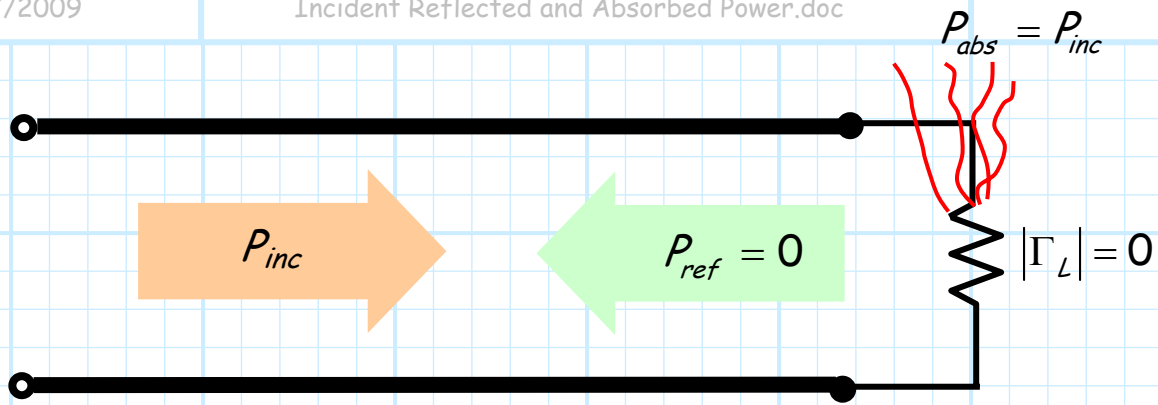In this case, **all** the incident power is absorbed by the load. **None** of the incident power is **reflected**, so that the absorbed power is **equal** to that of the incident.



3. $0 < |\Gamma_L| < 1$

For this case, we find that the **reflected** power is greater than zero, but **less** than the incident power.

$$0 < P_{ref} = |\Gamma_L|^2 P_{inc} < P_{inc}$$


Likewise, we find that the **absorbed** power is **also** greater than zero, but **less** than the incident power.

$$0 < P_{abs} = P_{inc} (1 - |\Gamma_L|^2) < P_{inc}$$

Note these two results are completely **consistent**—by conservation of energy, if one is true the other **must** also be:

$$0 < P_{ref} = P_{inc} - P_{abs} < P_{inc} \quad \text{and} \quad 0 < P_{abs} = P_{inc} - P_{ref} < P_{inc}$$

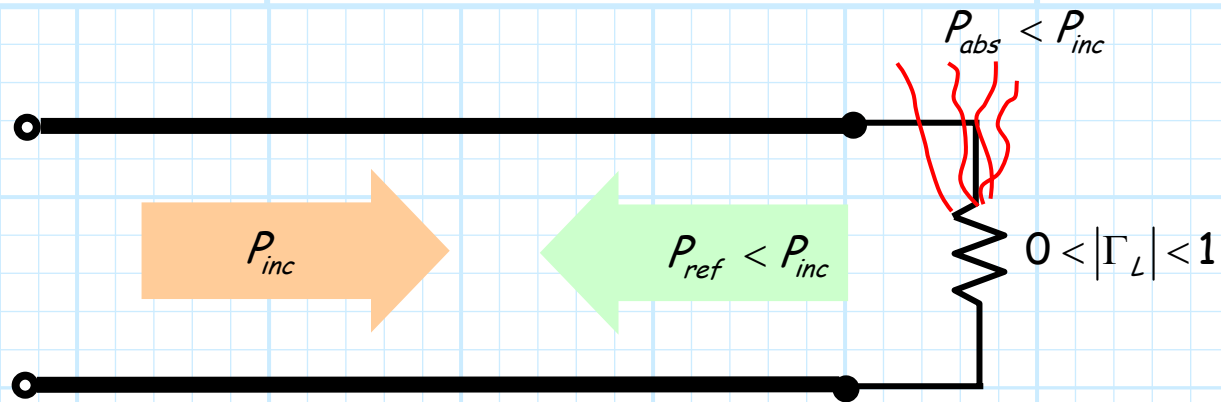In this case, the incident power is divided. Some of the incident power is absorbed by the load, while the remainder is reflected from the load.



4. $|\Gamma_L| > 1$

For this case, we find that the **reflected** power is **greater** than the **incident** power.

$$0 < P_{ref} = |\Gamma_L|^2 P_{inc} < P_{inc}$$

Q: *Yikes! What's up with that? This result does **not** seem at all consistent with your conservation of energy argument. How can the reflected power be **larger** than the incident?*

A: Quite insightful! It is indeed a result quite **askew** with our conservation of energy analysis. To see why, let's determine the **absorbed** power for this case.

$$P_{abs} = P_{inc} (1 - |\Gamma_L|^2) < 0$$

The power absorbed by the load is **negative**!

This result actually has a **physical interpretation**. A negative absorbed power indicates that the load is not absorbing power at all—it is instead **producing** power!

This makes sense if **you think** about it. The power flowing away from the load (the reflected power) can be larger than the power flowing toward the load (the incident power) **only** if the load itself is creating this extra power. The load is not a power **sink**, it is a power **source**.

Q: *But how could a **passive** load be a power source?*

A: It **can't**. A passive device cannot produce power. Thus, we have come to an important conclusion. The reflection coefficient of any and all passive loads **must** have a **magnitude** that is **less than one**.

$$|\Gamma_L| \leq 1 \quad \text{for all passive loads}$$

Q: *Can $|\Gamma_L|$ every be **greater** than one?*

A: Sure, if the "load" is an **active** device. In other words, the load must have some **external power** source connected to it.

Q: *What about the case where $|\Gamma_L| < 0$, shouldn't we examine **that** situation as well?*

A: That would be just plain **silly**; do **you** see why?

Special Values of Load Impedance

It's interesting to note that the load Z_L enforces a boundary condition that explicitly determines neither $V(z)$ nor $I(z)$ —but **completely specifies line impedance $Z(z)$** !

$$Z(z) = Z_0 \frac{e^{-j\beta z} + \Gamma_L e^{+j\beta z}}{e^{-j\beta z} - \Gamma_L e^{+j\beta z}} = Z_0 \frac{Z_L \cos \beta z - jZ_0 \sin \beta z}{Z_0 \cos \beta z - jZ_L \sin \beta z}$$

$$\Gamma(z) = \Gamma_L e^{+j2\beta z} = \frac{Z_L - Z_0}{Z_L + Z_0} e^{+j2\beta z}$$

Likewise, the load boundary condition leaves $V^+(z)$ and $V^-(z)$ undetermined, but **completely determines reflection coefficient function $\Gamma(z)$** !

Let's look at some **specific** values of load impedance $Z_L = R_L + jX_L$ and see what functions $Z(z)$ and $\Gamma(z)$ result!

- $Z_L = Z_0$

In this case, the **load impedance is numerically equal to the characteristic impedance** of the transmission line. Assuming the line is **lossless**, then Z_0 is **real**, and thus:

$$R_L = Z_0 \quad \text{and} \quad X_L = 0$$

It is evident that the resulting load reflection coefficient is **zero**:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0$$

This result is very interesting, as it means that there is **no reflected wave** $V^-(z)$!

$$\begin{aligned} V^-(z) &= \left(e^{-2j\beta z_L} \Gamma_L V_0^+ \right) e^{+j\beta z} \\ &= \left(e^{-2j\beta z_L} (0) V_0^+ \right) e^{+j\beta z} \\ &= 0 \end{aligned}$$

Thus, the **total** voltage and current along the transmission line is simply voltage and current of the **incident** wave:

$$V(z) = V^+(z) = V_0^+ e^{-j\beta z}$$

$$I(z) = I^+(z) = \frac{V_0^+}{Z_0} e^{-j\beta z}$$

Meaning that the **line** impedance is likewise **numerically** equal to the **characteristic** impedance of the transmission line for **all** line position z .

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \frac{V_0^+ e^{-j\beta z}}{V_0^+ e^{-j\beta z}} = Z_0$$

And likewise, the reflection coefficient is **zero** at **all** points along the line:

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} = \frac{0}{V^+(z)} = 0$$

We call this condition (when $Z_L = Z_0$) the **matched** condition, and the load $Z_L = Z_0$ a **matched load**.

2. $Z_L = 0$

A device with **no** impedance is called a **short** circuit! I.E.:

$$R_L = 0 \quad \text{and} \quad X_L = 0$$

In this case, the **voltage** across the load—and thus the voltage at the end of the transmission line—is **zero**:

$$V_L = Z_L I_L = 0 \quad \text{and} \quad V(z = z_L) = 0$$

Note that this does **not** mean that the **current** is zero!

$$I_L = I(z = z_L) \neq 0$$

For a **short**, the resulting load reflection coefficient is therefore:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{0 - Z_0}{0 + Z_0} = -1$$

Meaning (assuming $z_L = 0$):

$$V_0^- = -V_0^+$$

As a result, the total **voltage** and **current** along the transmission line is simply:

$$V(z) = V_0^+ (e^{-j\beta z} - e^{+j\beta z}) = -j2V_0^+ \sin(\beta z)$$

$$I(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} + e^{+j\beta z}) = \frac{2V_0^+}{Z_0} \cos(\beta z)$$

Meaning that the **line impedance** can likewise be written in terms of a **trigonometric** function:

$$Z(z) = \frac{V(z)}{I(z)} = -jZ_0 \tan(\beta z)$$

Note that this impedance is **purely reactive**. This means that the current and voltage on the transmission line will be everywhere 90° **out of phase**.

Hopefully, this was likewise apparent to **you** when you **observed** the expressions for $V(z)$ and $I(z)$!

Note at the **end** of the line (i.e., $z = z_L = 0$), we find that:

$$V(z=0) = -j2V_0^+ \sin(0) = 0$$

$$I(z=0) = \frac{2V_0^+}{Z_0} \cos(0) = \frac{2V_0^+}{Z_0}$$

As expected, the voltage is **zero** at the end of the transmission line (i.e. the voltage across the **short**). Likewise, the **current** at the end of the line (i.e., the current through the short) is at a **maximum**!

Finally, we note that the **line impedance** at the **end** of the transmission line is:

$$Z(z=0) = -jZ_0 \tan(0) = 0$$

Just as we expected—a **short** circuit!

Finally, the reflection coefficient **function** is (assuming $z_L = 0$):

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} = \frac{-V_0^+ e^{j\beta z}}{V_0^+ e^{-j\beta z}} = -e^{j\beta z}$$

Note that for **this** case $|\Gamma(z)| = 1$, meaning that:

$$|V^-(z)| = |V^+(z)|$$

In other words, the **magnitude** of each **wave** on the transmission line is the **same**—the reflected wave is **just** as big as the incident wave!

3. $Z_L = \infty$

A device with **infinite** impedance is called an **open** circuit!
I.E.:

$$R_L = \infty \quad \text{and/or} \quad X_L = \pm\infty$$

In this case, the **current** through the load—and thus the current at the end of the transmission line—is **zero**:

$$I_L = \frac{V_L}{Z_L} = 0 \quad \text{and} \quad I(z = z_L) = 0$$

Note that this does **not** mean that the **voltage** is zero!

$$V_L = V(z = z_L) \neq 0$$

For an **open**, the resulting load reflection coefficient is:

$$\Gamma_L = \lim_{Z_L \rightarrow \infty} \frac{Z_L - Z_0}{Z_L + Z_0} = \lim_{Z_L \rightarrow \infty} \frac{Z_L}{Z_L} = 1$$

Meaning (assuming $z_L = 0$):

$$V_0^- = V_0^+$$

As a result, the **total** voltage and current along the transmission line is simply (assuming $z_L = 0$):

$$V(z) = V_0^+ (e^{-j\beta z} + e^{+j\beta z}) = 2V_0^+ \cos(\beta z)$$

$$I(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - e^{+j\beta z}) = -j \frac{2V_0^+}{Z_0} \sin(\beta z)$$

Meaning that the **line impedance** can likewise be written in terms of trigonometric function:

$$Z(z) = \frac{V(z)}{I(z)} = jZ_0 \cot(\beta z)$$

Again note that this impedance is **purely reactive**— $V(z)$ and $I(z)$ are again 90° **out of phase!**

Note at the **end** of the line (i.e., $z = z_L = 0$), we find that

$$V(z = 0) = 2V_0^+ \cos(0) = \frac{2V_0^+}{Z_0}$$

$$I(z = 0) = -j \frac{2V_0^+}{Z_0} \sin(0) = 0$$

As expected, the **current is zero** at the end of the transmission line (i.e. the current through the **open**). Likewise, the **voltage** at the end of the line (i.e., the voltage across the open) is at a **maximum!**

Finally, we note that the **line impedance** at the **end** of the transmission line is:

$$Z(z = 0) = jZ_0 \cot(0) = \infty$$

Just as we expected—an **open** circuit!

Finally, the reflection coefficient is (assuming $z_L = 0$):

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} = \frac{V_0^+ e^{+j\beta z}}{V_0^+ e^{-j\beta z}} = e^{+j2\beta z}$$

Note that likewise for **this case** $|\Gamma(z)| = 1$, meaning **again** that:

$$|V^-(z)| = |V^+(z)|$$

In other words, the **magnitude** of each wave on the transmission line is the **same**—the reflected wave is **just** as big as the incident wave!

$$4. Z_L = jX_L$$

For this case, the load impedance is **purely reactive** (e.g. a capacitor or inductor), and thus the resistive portion is zero:

$$R_L = 0$$

Thus, **both** the current through the load, and voltage across the load, are **non-zero**:

$$I_L = I(z = z_L) \neq 0 \qquad V_L = V(z = z_L) \neq 0$$

The resulting load reflection coefficient is:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{jX_L - Z_0}{jX_L + Z_0}$$

Given that Z_0 is real (i.e., the line is **lossless**), we find that this load reflection coefficient is generally some **complex** number.

We can rewrite this value explicitly in terms of its **real** and **imaginary** part as:

$$\Gamma_L = \frac{jX_L - Z_0}{jX_L + Z_0} = \left(\frac{X_L^2 - Z_0^2}{X_L^2 + Z_0^2} \right) + j \left(\frac{2Z_0 X_L}{X_L^2 + Z_0^2} \right)$$

Yuck! This isn't much help!

Let's instead write this complex value Γ_L in terms of its **magnitude** and **phase**. For **magnitude** we find a much more straightforward result!

$$|\Gamma_L|^2 = \frac{|jX_L - Z_0|^2}{|jX_L + Z_0|^2} = \frac{X_L^2 + Z_0^2}{X_L^2 + Z_0^2} = 1$$

Its magnitude is **one**! Thus, we find that for reactive loads, the reflection coefficient can be simply expressed as:

$$\Gamma_L = e^{j\theta_\Gamma}$$

where

$$\theta_\Gamma = \tan^{-1} \left[\frac{2Z_0 X_L}{X_L^2 - Z_0^2} \right]$$

We can therefore conclude that for a **reactive load**:

$$V_0^- = e^{j\theta_\Gamma} V_0^+$$

As a result, the **total** voltage and current along the transmission line is simply (assuming $z_L = 0$):

$$\begin{aligned} V(z) &= V_0^+ (e^{-j\beta z} + e^{+j\theta_L} e^{+j\beta z}) \\ &= V_0^+ e^{+j\theta_\Gamma/2} (e^{-j(\beta z + \theta_\Gamma/2)} + e^{+j(\beta z + \theta_\Gamma/2)}) \\ &= 2V_0^+ e^{+j\theta_\Gamma/2} \cos(\beta z + \theta_\Gamma/2) \end{aligned}$$

$$\begin{aligned} I(z) &= \frac{V_0^+}{Z_0} (e^{-j\beta z} - e^{+j\beta z}) \\ &= \frac{V_0^+}{Z_0} e^{+j\theta_L/2} (e^{-j(\beta z + \theta_L/2)} - e^{+j(\beta z + \theta_L/2)}) \\ &= -j \frac{2V_0^+}{Z_0} e^{+j\theta_L/2} \sin(\beta z + \theta_L/2) \end{aligned}$$

Meaning that the **line impedance** can again be written in terms of trigonometric function:

$$Z(z) = \frac{V(z)}{I(z)} = jZ_0 \cot(\beta z + \theta_\Gamma/2)$$

Again note that this impedance is **purely reactive**— $V(z)$ and $I(z)$ are once again 90° out of phase!

Note at the **end** of the line (i.e., $z = z_L = 0$), we find that

$$V(z=0) = 2V_0^+ \cos(\theta_\Gamma/2)$$

$$I(z=0) = -j \frac{2V_0^+}{Z_0} \sin(\theta_\Gamma/2)$$

As expected, **neither** the current **nor** voltage at the end of the line are zero.

We also note that the line impedance at the **end** of the transmission line is:

$$Z(z=0) = jZ_0 \cot(\theta_\Gamma/2)$$

With a little trigonometry, we can show (trust me!) that:

$$\cot(\theta_\Gamma/2) = \frac{X_L}{Z_0}$$

and therefore:

$$Z(z=0) = jZ_0 \cot(\theta_\Gamma/2) = j X_L = Z_L$$

Just as we **expected!**

Finally, the reflection coefficient **function** is (assuming $z_L = 0$):

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} = \frac{V_0^+ e^{+j\theta_\Gamma} e^{+j\beta z}}{V_0^+ e^{-j\beta z}} = e^{+j2(\beta z + \theta_\Gamma/2)}$$

Note that likewise for **this** case $|\Gamma(z)| = 1$, meaning **once again**:

$$|V^-(z)| = |V^+(z)|$$

In other words, the **magnitude** of each **wave** on the transmission line is the **same**—the reflected wave is **just** as big as the incident wave!

Q: *Gee, a **reactive** load leads to results very **similar** to that of an **open** or **short** circuit. Is this just coincidence?*

A: Hardly! An open and short **are** in fact reactive loads—they **cannot absorb power** (think about this!).

Specifically, for an **open**, we find $\theta_\Gamma = 0$, so that:

$$\Gamma_L = e^{j\theta_\Gamma} = 1$$

Likewise, for a **short**, we find that $\theta_\Gamma = \pi$, so that:

$$\Gamma_L = e^{j\theta_\Gamma} = -1$$

5. $Z_L = R_L$

For this case, the load impedance is **purely real** (e.g. a **resistor**), meaning its reactive portion is zero:

$$X_L = 0$$

Thus, **both** the current through the load, and voltage across the load, are **non-zero**:

$$I_L = I(z = z_L) \neq 0 \qquad V_L = V(z = z_L) \neq 0$$

The resulting **load reflection coefficient** is:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{R - Z_0}{R + Z_0}$$

Given that Z_0 is real (i.e., the line is **lossless**), we find that this load reflection coefficient must be a purely **real** value!
In other words:

$$\operatorname{Re}\{\Gamma_L\} = \frac{R - Z_0}{R + Z_0} \qquad \operatorname{Im}\{\Gamma_L\} = 0$$

The magnitude is thus:

$$|\Gamma_L| = \left| \frac{R - Z_0}{R + Z_0} \right|$$

whereas the phase θ_r can take on one of two values:

$$\theta_r = \begin{cases} 0 & \text{if } \operatorname{Re}\{\Gamma_L\} > 0 \text{ (i.e., if } R_L > Z_0) \\ \pi & \text{if } \operatorname{Re}\{\Gamma_L\} < 0 \text{ (i.e., if } R_L < Z_0) \end{cases}$$

For this case, the impedance at the **end** of the line must be **real** ($Z(z = z_L) = R_L$). Thus, the current and the voltage at this point are precisely **in phase**.

However, even though the **load** impedance is real, the **line** impedance at all other points on the line is generally **complex**!

Moreover, the **general** current and voltage expressions, as well as reflection coefficient function, **cannot** be further simplified for the case where $Z_L = R_L$.

Q: *Why is that? When the load was purely **imaginary** (reactive), we were able to **simply** our general expressions, and likewise deduce all sorts of interesting results!*

A: True! And here's **why**. Remember, a **lossless** transmission line has series inductance and shunt capacitance **only**. In other words, a length of lossless transmission line is a **purely reactive** device (it absorbs **no** energy!).

* If we attach a **purely reactive** load at the end of the transmission line, we still have a **completely** reactive system (load and transmission line). Because this system has **no** resistive (i.e., real) component, the general expressions for line impedance, line voltage, etc. can be significantly **simplified**.

* However, if we attach a **purely real** load to our reactive transmission line, we now have a **complex** system, with **both** real and imaginary (i.e., resistive and reactive) components.

This **complex** case is exactly what our general expressions **already** describes—no further simplification is possible!

$$5. Z_L = R_L + jX_L$$

Now, let's look at the **general** case, where the **load** has both a **real** (resistive) and **imaginary** (reactive) component.

Q: *Haven't we **already** determined all the **general** expressions (e.g., $\Gamma_L, V(z), I(z), Z(z), \Gamma(z)$) for this general case? Is there **anything** else left to be determined?*

A: There is **one** last thing we need to discuss. It seems trivial, but its ramifications are **very** important!

For you see, the "general" case is **not**, in reality, quite so general. Although the reactive component of the load can be **either** positive or negative ($-\infty < X_L < \infty$), the resistive component of a passive load **must** be positive ($R_L > 0$)—there's **no** such thing as a (passive) **negative** resistor!

This leads to one **very** important and useful result. Consider the **load reflection coefficient**:

$$\begin{aligned}
 \Gamma_L &= \frac{Z_L - Z_0}{Z_L + Z_0} \\
 &= \frac{(R_L + jX_L) - Z_0}{(R_L + jX_L) + Z_0} \\
 &= \frac{(R_L - Z_0) + jX_L}{(R_L + Z_0) + jX_L}
 \end{aligned}$$

Now let's look at the **magnitude** of this value:

$$\begin{aligned}
 |\Gamma_L|^2 &= \left| \frac{(R_L - Z_0) + jX_L}{(R_L + Z_0) + jX_L} \right|^2 \\
 &= \frac{(R_L - Z_0)^2 + X_L^2}{(R_L + Z_0)^2 + X_L^2} \\
 &= \frac{(R_L^2 - 2R_L Z_0 + Z_0^2) + X_L^2}{(R_L^2 + 2R_L Z_0 + Z_0^2) + X_L^2} \\
 &= \frac{(R_L^2 + Z_0^2 + X_L^2) - 2R_L Z_0}{(R_L^2 + Z_0^2 + X_L^2) + 2R_L Z_0}
 \end{aligned}$$

It is apparent that since both R_L and Z_0 are **positive**, the **numerator** of the above expression must be **less** than (or equal to) the **denominator** of the above expression.

→ In other words, the magnitude of the load reflection coefficient is always **less** than or equal to one!

$$|\Gamma_L| \leq 1 \quad (\text{for } R_L \geq 0)$$

Moreover, we find that this means the reflection coefficient **function** likewise always has a magnitude **less** than or equal to one, for **all** values of position z .

$$|\Gamma(z)| \leq 1 \quad (\text{for all } z)$$


Which means, of course, that the **reflected** wave will always have a magnitude **less** than that of the **incident** wave magnitude:

$$|V^-(z)| \leq |V^+(z)| \quad (\text{for all } z)$$

We will find out later that this result is consistent with **conservation of energy**—the reflected wave from a passive load **cannot** be larger than the wave incident on it.

Transmission Line Input Impedance

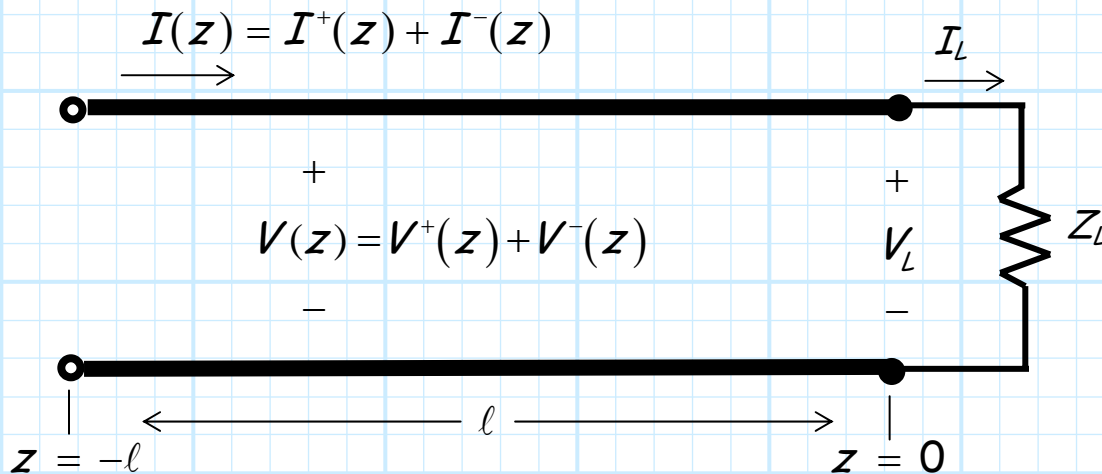Consider a lossless line, length ℓ , terminated with a load Z_L .



Let's determine the **input impedance** of this line!

Q: *Just what do you mean by **input impedance**?*

A: The input impedance is simply the line impedance seen at the **beginning** ($z = -l$) of the transmission line, i.e.:

$$Z_{in} = Z(z = -l) = \frac{V(z = -l)}{I(z = -l)}$$

Note Z_{in} equal to **neither** the load impedance Z_L nor the characteristic impedance Z_0 !

$$Z_{in} \neq Z_L \quad \text{and} \quad Z_{in} \neq Z_0$$

To determine exactly what Z_{in} is, we first must determine the voltage and current at the **beginning** of the transmission line ($z = -\ell$).

$$V(z = -\ell) = V_0^+ [e^{+j\beta\ell} + \Gamma_0 e^{-j\beta\ell}]$$

$$I(z = -\ell) = \frac{V_0^+}{Z_0} [e^{+j\beta\ell} - \Gamma_0 e^{-j\beta\ell}]$$

Therefore:

$$Z_{in} = \frac{V(z = -\ell)}{I(z = -\ell)} = Z_0 \left(\frac{e^{+j\beta\ell} + \Gamma_0 e^{-j\beta\ell}}{e^{+j\beta\ell} - \Gamma_0 e^{-j\beta\ell}} \right)$$

We can explicitly write Z_{in} in terms of load Z_L using the previously determined relationship:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \Gamma_0$$

Combining these two expressions, we get:

$$\begin{aligned} Z_{in} &= Z_0 \frac{(Z_L + Z_0)e^{+j\beta\ell} + (Z_L - Z_0)e^{-j\beta\ell}}{(Z_L + Z_0)e^{+j\beta\ell} - (Z_L - Z_0)e^{-j\beta\ell}} \\ &= Z_0 \left(\frac{Z_L(e^{+j\beta\ell} + e^{-j\beta\ell}) + Z_0(e^{+j\beta\ell} - e^{-j\beta\ell})}{Z_L(e^{+j\beta\ell} + e^{-j\beta\ell}) - Z_0(e^{+j\beta\ell} - e^{-j\beta\ell})} \right) \end{aligned}$$

Now, recall **Euler's equations**:

$$e^{+j\beta\ell} = \cos \beta\ell + j \sin \beta\ell$$

$$e^{-j\beta\ell} = \cos \beta\ell - j \sin \beta\ell$$

Using Euler's relationships, we can likewise write the input impedance without the **complex** exponentials:

$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left(\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right) \end{aligned}$$


Note that depending on the values of β , Z_0 and l , the input impedance can be **radically** different from the load impedance Z_L !

Special Cases

Now let's look at the Z_{in} for some important load impedances and line lengths.

→ You should commit these results to **memory!**

1. $l = \lambda/2$

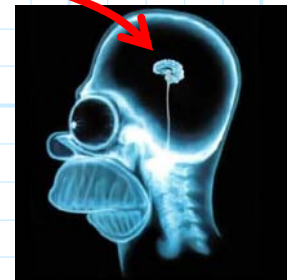

If the length of the transmission line is exactly **one-half** wavelength ($l = \lambda/2$), we find that:

$$\beta l = \frac{2\pi}{\lambda} \frac{\lambda}{2} = \pi$$


meaning that:

$$\cos \beta l = \cos \pi = -1 \quad \text{and} \quad \sin \beta l = \sin \pi = 0$$

and therefore:

$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left(\frac{Z_L (-1) + j Z_L (0)}{Z_0 (-1) + j Z_L (0)} \right) \\ &= Z_L \end{aligned}$$

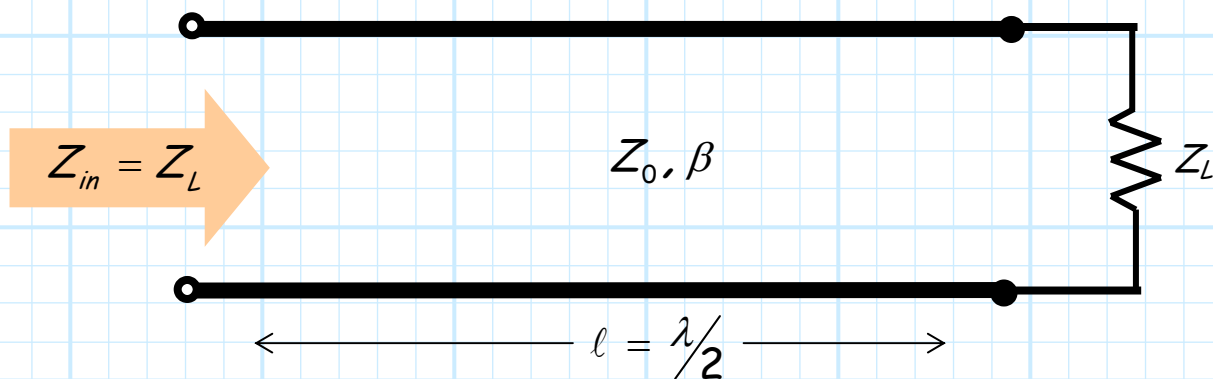In other words, if the transmission line is precisely **one-half wavelength** long, the **input impedance** is equal to the **load impedance**, regardless of Z_0 or β .



2. $l = \lambda/4$

If the length of the transmission line is exactly **one-quarter wavelength** ($l = \lambda/4$), we find that:

$$\beta l = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2}$$

meaning that:

$$\cos \beta l = \cos \pi/2 = 0 \quad \text{and} \quad \sin \beta l = \sin \pi/2 = 1$$

and therefore:


$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left(\frac{Z_L (0) + j Z_0 (1)}{Z_0 (0) + j Z_L (1)} \right) \\ &= \frac{(Z_0)^2}{Z_L} \end{aligned}$$

In other words, if the transmission line is precisely **one-quarter wavelength** long, the **input impedance** is **inversely** proportional to the **load impedance**.

Think about what this means! Say the load impedance is a **short circuit**, such that $Z_L = 0$. The **input impedance** at beginning of the $\lambda/4$ transmission line is therefore:

$$Z_{in} = \frac{(Z_0)^2}{Z_L} = \frac{(Z_0)^2}{0} = \infty$$

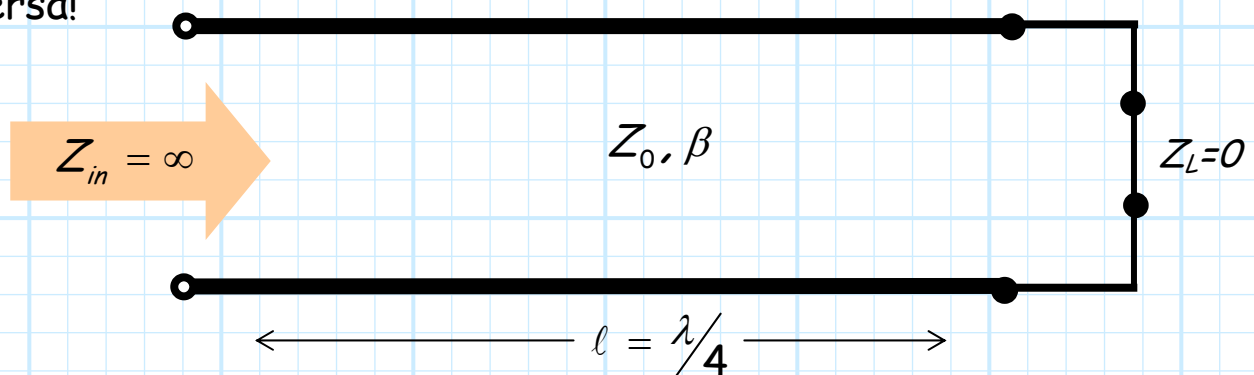$Z_{in} = \infty$! This is an **open circuit**! The quarter-wave transmission line **transforms** a short-circuit into an open-circuit—and vice versa!




$$3. \quad Z_L = Z_0$$

If the load is **numerically equal** to the characteristic impedance of the transmission line (a real value), we find that the input impedance becomes:

$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left(\frac{Z_0 \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_0 \sin \beta l} \right) \\ &= Z_0 \end{aligned}$$

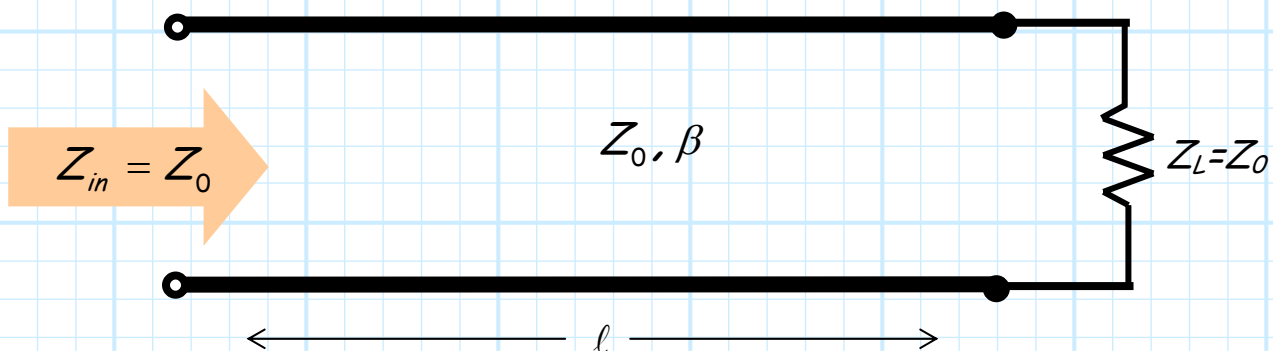In other words, if the **load** impedance is equal to the transmission line **characteristic** impedance, the **input** impedance will be likewise be equal to Z_0 regardless of the transmission line length l .




$$4. \quad Z_L = j X_L$$

If the load is **purely reactive** (i.e., the resistive component is zero), the input impedance is:

$$\begin{aligned}
 Z_{in} &= Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\
 &= Z_0 \left(\frac{j X_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j^2 X_L \sin \beta l} \right) \\
 &= j Z_0 \left(\frac{X_L \cos \beta l + Z_0 \sin \beta l}{Z_0 \cos \beta l - X_L \sin \beta l} \right)
 \end{aligned}$$

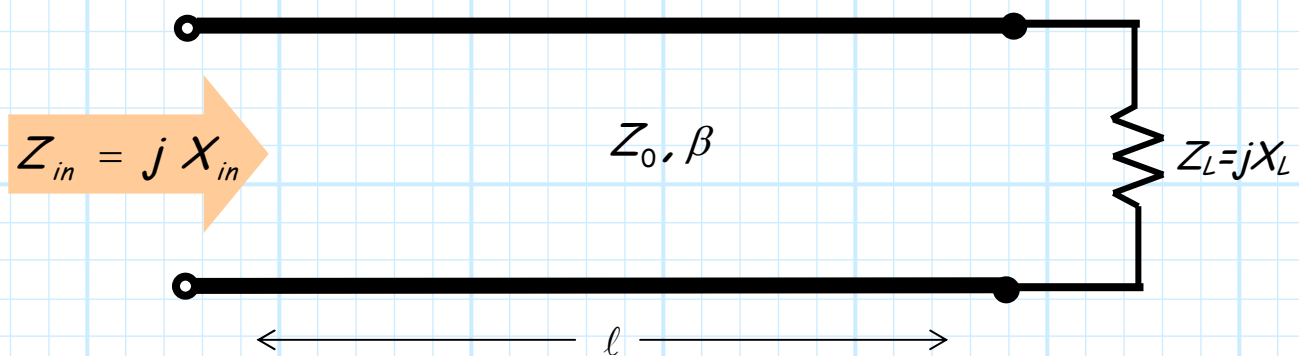In other words, if the load is purely reactive, then the input impedance will **likewise** be purely reactive, **regardless** of the line length l .



Note that the **opposite** is **not** true: even if the load is **purely resistive** ($Z_L = R$), the input impedance will be **complex** (both resistive and reactive components).

Q: *Why is this?*

A:

5. $l \ll \lambda$

If the transmission line is **electrically small**—its length l is small with respect to signal wavelength λ --we find that:

$$\beta l = \frac{2\pi}{\lambda} l = 2\pi \frac{l}{\lambda} \approx 0$$

and thus:

$$\cos \beta l = \cos 0 = 1 \quad \text{and} \quad \sin \beta l = \sin 0 = 0$$

so that the input impedance is:

$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left(\frac{Z_L (1) + j Z_L (0)}{Z_0 (1) + j Z_L (0)} \right) \\ &= Z_L \end{aligned}$$

In other words, if the transmission line length is much smaller than a wavelength, the **input** impedance Z_{in} will **always** be equal to the **load** impedance Z_L .

This is the assumption we used in all previous circuits courses (e.g., EECS 211, 212, 312, 412)! In those courses, we assumed that the signal frequency ω is relatively **low**, such that the signal wavelength λ is **very large** ($\lambda \gg l$).


Note also for this case (the electrically short transmission line), the voltage and current at each end of the transmission line are approximately the **same!**

$$V(z = -\ell) \approx V(z = 0) \quad \text{and} \quad I(z = -\ell) \approx I(z = 0) \quad \text{if} \quad \ell \ll \lambda$$


If $\ell \ll \lambda$, our "wire" behaves **exactly** as it did in EECS 211 !

Example: Input Impedance

Consider the following circuit:

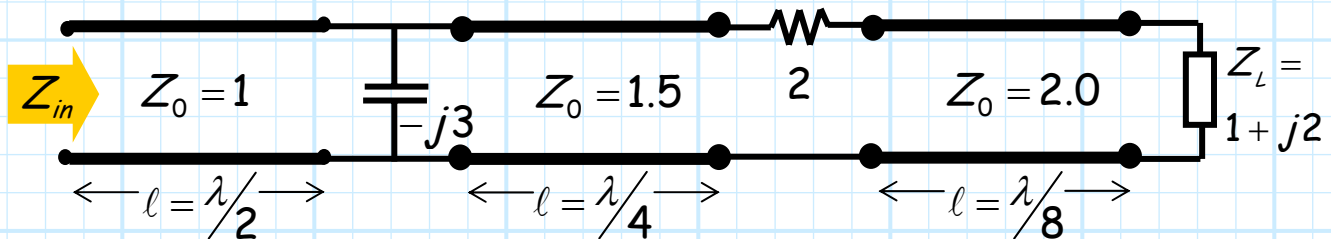

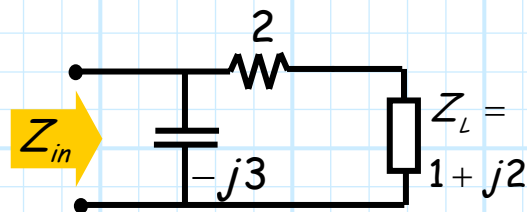If we **ignored** our new μ -wave knowledge, we might **erroneously** conclude that the input impedance of this circuit is:




Therefore:

$$Z_{in} = \frac{-j3(2+1+j2)}{-j3+2+1+j2} = \frac{6-j9}{3-j} = 2.7 - j2.1$$

Of course, this is **not** the correct answer!

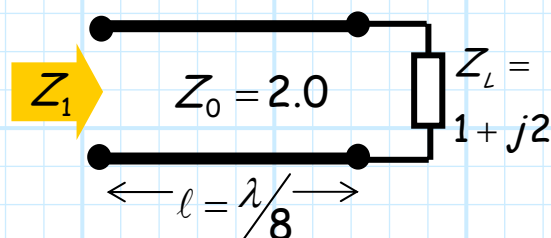
We must use our **transmission line theory** to determine an accurate value. Define Z_1 as the input impedance of the last section:



we find that Z_1 is :


$$\begin{aligned} Z_1 &= Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= 2 \left(\frac{(1 + j2) \cos(\pi/4) + j 2 \sin(\pi/4)}{2 \cos(\pi/4) + j(1 + j2) \sin(\pi/4)} \right) \\ &= 2 \left(\frac{1 + j4}{j} \right) \\ &= 8 - j2 \end{aligned}$$

Therefore, our circuit now becomes:

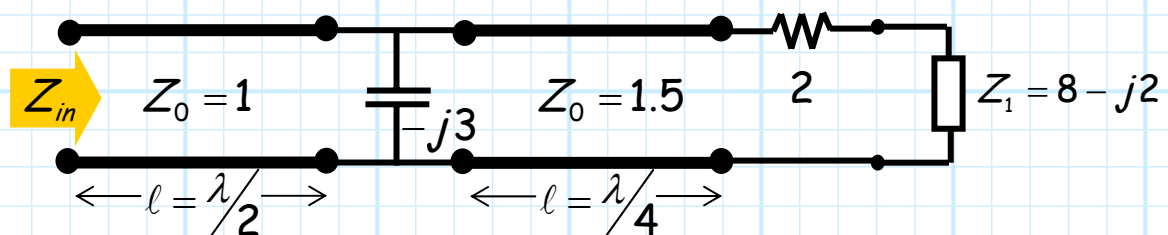


Note the resistor is in **series** with impedance Z_1 . We can **combine** these two into one impedance defined as Z_2 :
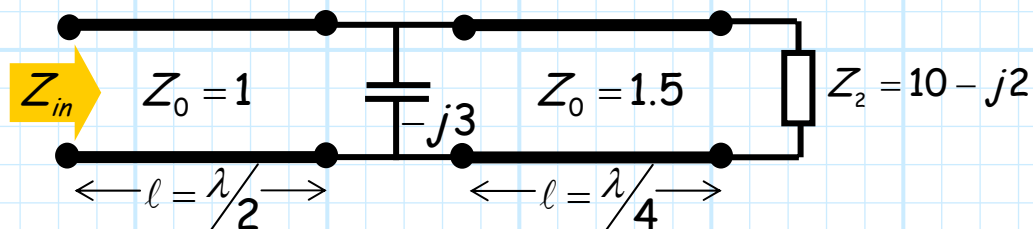
$$Z_2 = 2 + Z_1 = 2 + (8 - j2) = 10 - j2$$



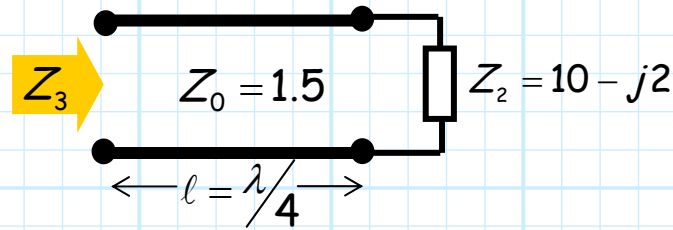Now let's define the input impedance of the **middle** transmission line section as Z_3 :




Note that this transmission line is a **quarter wavelength** ($l = \lambda/4$). This is one of the **special** cases we considered earlier!

The input impedance Z_3 is:

$$\begin{aligned} Z_3 &= \frac{Z_0^2}{Z_L} \\ &= \frac{Z_0^2}{Z_2} \\ &= \frac{1.5^2}{10 - j2} \\ &= 0.21 + j0.043 \end{aligned}$$

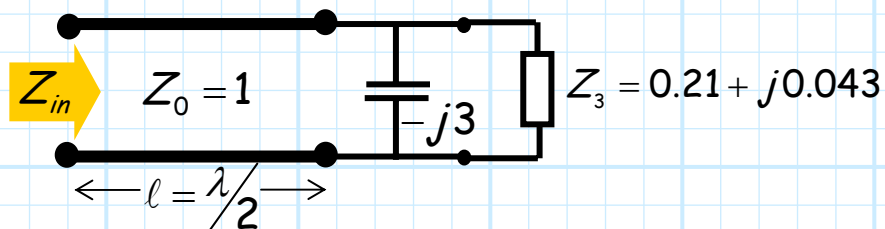
Thus, we can further **simplify** the original circuit as:



Now we find that the impedance Z_3 is **parallel** to the capacitor. We can **combine** the two impedances and define the result as impedance Z_4 :

$$\begin{aligned}
 Z_4 &= -j3 \parallel (0.21 + j0.043) \\
 &= \frac{-j3(0.21 + j0.043)}{-j3 + 0.21 + j0.043} \\
 &= 0.22 + j0.028
 \end{aligned}$$

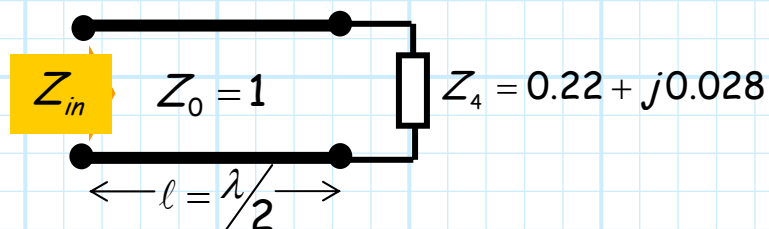
Now we are left with **this** equivalent circuit:




Note that the remaining transmission line section is a **half wavelength!** This is one of the **special** situations we discussed in a previous handout. Recall that the **input** impedance in this case is simply equal to the **load** impedance:

$$Z_{in} = Z_L = Z_4 = 0.22 + j0.028$$

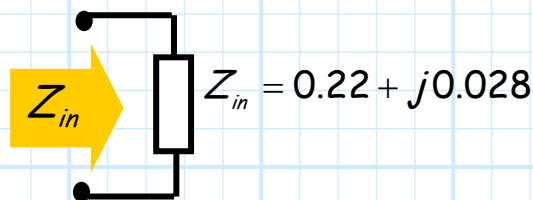
Whew! We are **finally** done. The **input impedance** of the original circuit is:



Note this means that **this** circuit:

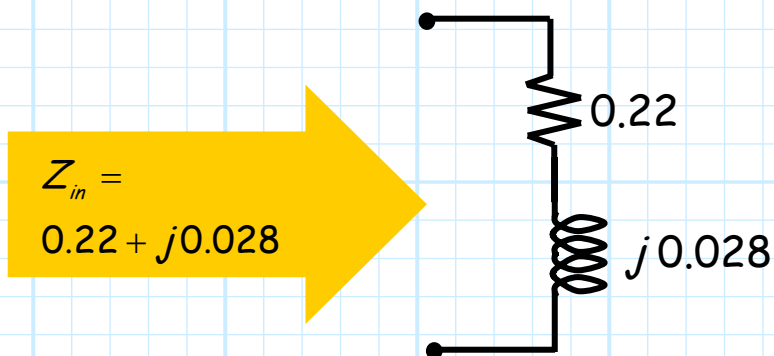

and **this** circuit:

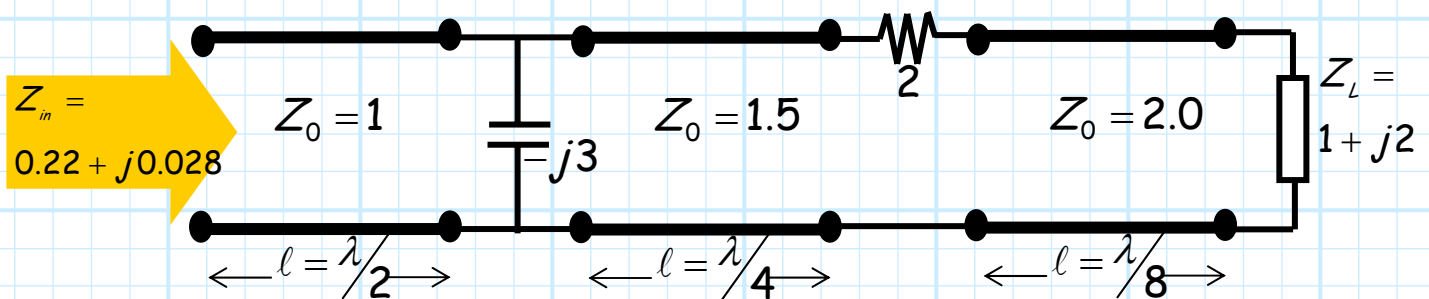

are precisely the **same**! They have **exactly** the same impedance, and thus they "behave" precisely the **same** way in any circuit (but **only** at frequency ω_0 !).


The Reflection Coefficient Transformation

The **load** at the end of some length of a transmission line (with characteristic impedance Z_0) can be specified in terms of its impedance Z_L **or** its reflection coefficient Γ_L .

Note **both** values are complex, and **either one** completely specifies the load—if you know **one**, you know the **other**!

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{and} \quad Z_L = Z_0 \left(\frac{1 + \Gamma_L}{1 - \Gamma_L} \right)$$

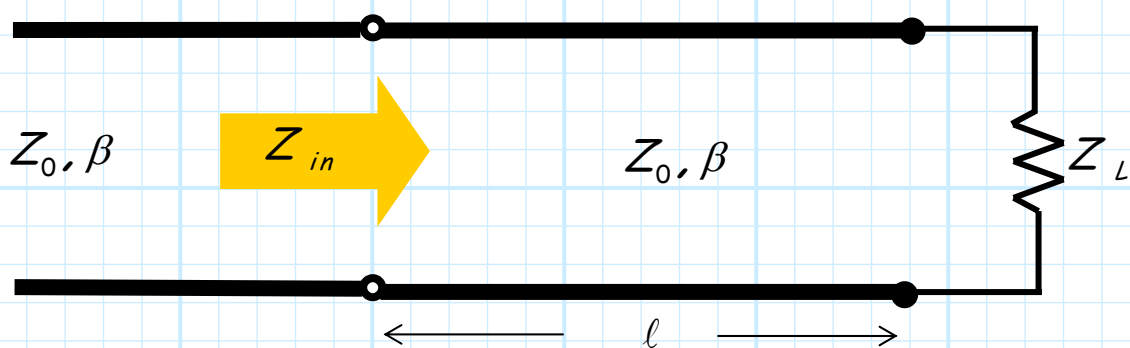Recall that we determined how a length of transmission line **transformed** the load **impedance** into an input **impedance** of a (generally) different value:




where:

$$Z_{in} = Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right)$$

$$= Z_0 \left(\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right)$$

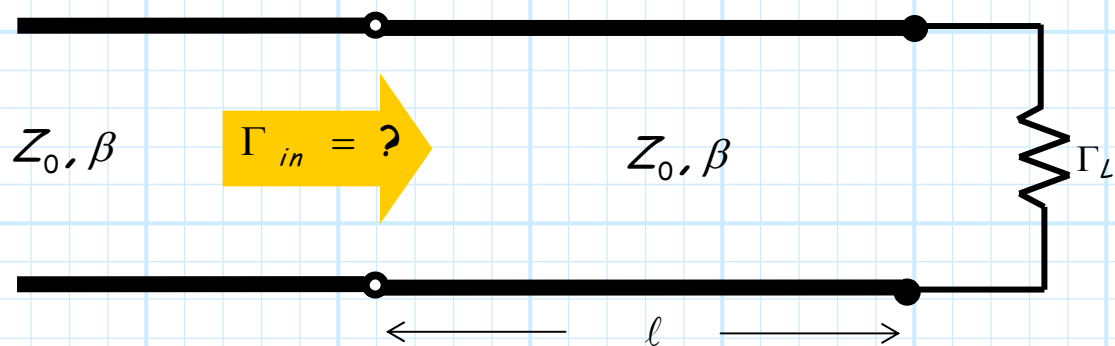Q: Say we know the load in terms of its **reflection coefficient**. How can we express the **input impedance** in terms its **reflection coefficient** (call this Γ_{in})?



A: Well, we could execute these **three** steps:

1. Convert Γ_L to Z_L :

$$Z_L = Z_0 \left(\frac{1 + \Gamma_L}{1 - \Gamma_L} \right)$$

2. Transform Z_L down the line to Z_{in} :

$$Z_{in} = Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right)$$

3. Convert Z_{in} to Γ_{in} :

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

Q: *Yikes! This is a ton of complex arithmetic— isn't there an easier way?*

A: Actually, there is!

Recall in an **earlier handout** that the input impedance of a transmission line length ℓ , terminated with a load Γ_L , is:

$$Z_{in} = \frac{V(z = -\ell)}{I(z = -\ell)} = Z_0 \left(\frac{e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}}{e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell}} \right)$$

Note this **directly** relates Γ_L to Z_{in} (steps 1 and 2 combined!).

If we directly **insert** this equation into:

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

we get an equation **directly** relating Γ_L to Γ_{in} :

$$\begin{aligned}
 \Gamma_{in} &= \frac{Z_0 (e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}) - (e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell})}{Z_0 (e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}) + (e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell})} \\
 &= \frac{2\Gamma_L e^{-j\beta\ell}}{2e^{+j\beta\ell}} \\
 &= \Gamma_L e^{-j\beta\ell} e^{-j\beta\ell} \\
 &= \Gamma_L e^{-j2\beta\ell}
 \end{aligned}$$

Q: Hey! This result looks familiar. Haven't we seen something like this before?

A: Absolutely! Recall that we found that the reflection coefficient function $\Gamma(z)$ can be expressed as:

$$\Gamma(z) = \Gamma_0 e^{j2\beta z}$$

Evaluating this function at the **beginning** of the line (i.e., at $z = z_L - \ell$):

$$\begin{aligned}
 \Gamma(z = z_L - \ell) &= \Gamma_0 e^{j2\beta(z_L - \ell)} \\
 &= \Gamma_0 e^{j2\beta z_L} e^{-j2\beta\ell}
 \end{aligned}$$

But, we recognize that:

$$\Gamma_0 e^{j2\beta z_L} = \Gamma(z = z_L) = \Gamma_L$$

And so:

$$\begin{aligned}
 \Gamma(z = z_L - \ell) &= \Gamma_0 e^{j2\beta z_L} e^{-j2\beta\ell} \\
 &= \Gamma_L e^{-j2\beta\ell}
 \end{aligned}$$

Thus, we find that Γ_{in} is simply the value of function $\Gamma(z)$ **evaluated** at the line input of $z = z_L - \ell$!

$$\Gamma_{in} = \Gamma(z = z_L - \ell) = \Gamma_L e^{-j2\beta\ell}$$

Makes sense! After all, the input impedance is **likewise** simply the line impedance evaluated at the line input of $z = z_L - \ell$:

$$Z_{in} = Z(z = z_L - \ell)$$

It is apparent that from the above expression that the reflection coefficient at the input is simply related to Γ_L by a **phase shift** of $2\beta\ell$.

In other words, the **magnitude** of Γ_{in} is the **same** as the magnitude of Γ_L !

$$\begin{aligned} |\Gamma_{in}| &= |\Gamma_L| \left| e^{j(\theta_\Gamma - 2\beta\ell)} \right| \\ &= |\Gamma_L| (1) \\ &= |\Gamma_L| \end{aligned}$$


If we think about this, it makes **perfect sense!**

Recall that the power **absorbed** by the load Γ_{in} would be:

$$P_{abs}^{in} = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_{in}|^2)$$

while that absorbed by the **load** Γ_L is:

$$P_{abs}^L = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_L|^2)$$

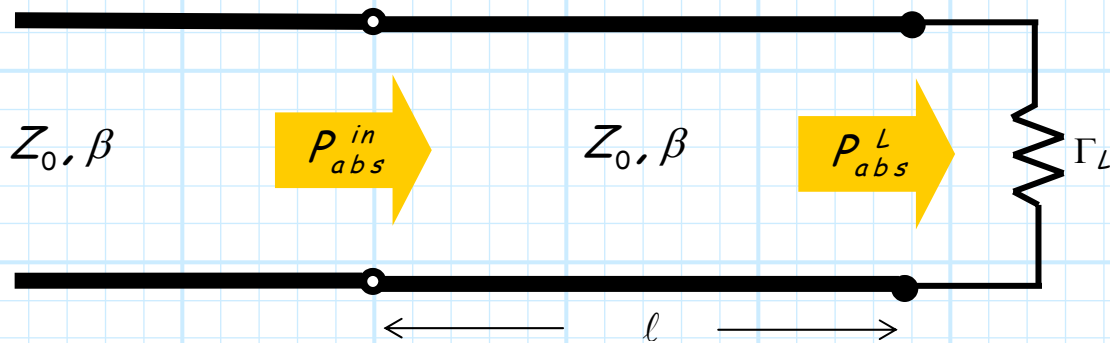

Recall, however, that a lossless transmission line can absorb **no** power! By adding a length of transmission line to load Γ_L , we have added only **reactance**. Therefore, the power absorbed by load Γ_{in} is **equal** to the power absorbed by Γ_L :

$$P_{abs}^{in} = P_{abs}^L$$

$$\frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_{in}|^2) = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_L|^2)$$


$$1 - |\Gamma_{in}|^2 = 1 - |\Gamma_L|^2$$

Thus, we can conclude from **conservation of energy** that:

$$|\Gamma_{in}| = |\Gamma_L|$$

Which of course is **exactly** the result we just found!

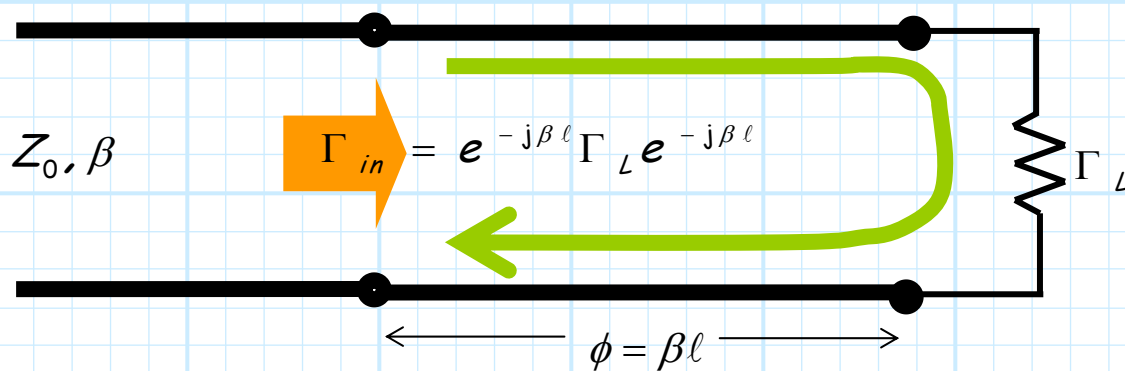Finally, the **phase shift** associated with transforming the load Γ_L down a transmission line can be attributed to the phase shift associated with the wave propagating a length ℓ down the line, reflecting from load Γ_L , and then propagating a length ℓ back up the line:



To **emphasize** this wave interpretation, we recall that by definition, we can write Γ_{in} as:

$$\Gamma_{in} = \Gamma(z = z_L - \ell) = \frac{V^-(z = z_L - \ell)}{V^+(z = z_L - \ell)}$$

Therefore:

$$\begin{aligned} V^-(z = z_L - \ell) &= \Gamma_{in} V^+(z = z_L - \ell) \\ &= e^{-j\beta\ell} \Gamma_L e^{-j\beta\ell} V^+(z = z_L - \ell) \end{aligned}$$

Return Loss and VSWR

The **ratio** of the reflected power from a load, to the incident power on that load, is known as **return loss**. Typically, return loss is expressed in **dB**:

$$R.L. = -10 \log_{10} \left[\frac{P_{ref}}{P_{inc}} \right] = -10 \log_{10} |\Gamma_L|^2$$

The return loss thus tells us the percentage of the incident power reflected by load (expressed in decibels!).

For **example**, if the return loss is **10dB**, then **10%** of the incident power is **reflected** at the load, with the remaining **90%** being **absorbed** by the load—we “lose” 10% of the incident power

Likewise, if the return loss is **30dB**, then **0.1 %** of the incident power is **reflected** at the load, with the remaining **99.9%** being **absorbed** by the load—we “lose” 0.1% of the incident power.

Thus, a **larger** numeric value for return loss **actually** indicates **less** lost power! An **ideal** return loss would be ∞ dB, whereas a return loss of 0 dB indicates that $|\Gamma_L| = 1$ --the load is **reactive!**

Return loss is helpful, as it provides a **real-valued** measure of load match (as opposed to the complex values Z_L and Γ_L).

Another traditional real-valued measure of load match is **Voltage Standing Wave Ratio (VSWR)**. Consider again the **voltage** along a terminated transmission line, as a function of **position z** :

$$V(z) = V_0^+ \left[e^{-j\beta z} + \Gamma_L e^{+j\beta z} \right]$$

Recall this is a **complex** function, the magnitude of which expresses the **magnitude** of the **sinusoidal signal** at position z , while the phase of the complex value represents the relative **phase** of the sinusoidal signal.

Let's look at the **magnitude** only:

$$\begin{aligned} |V(z)| &= |V_0^+| |e^{-j\beta z} + \Gamma_L e^{+j\beta z}| \\ &= |V_0^+| |e^{-j\beta z}| |1 + \Gamma_L e^{+j2\beta z}| \\ &= |V_0^+| |1 + \Gamma_L e^{+j2\beta z}| \end{aligned}$$

It can be shown that the **largest** value of $|V(z)|$ occurs at the location z where:

$$\Gamma_L e^{+j2\beta z} = |\Gamma_L| + j0$$

while the **smallest** value of $|V(z)|$ occurs at the location z where:

$$\Gamma_L e^{+j2\beta z} = -|\Gamma_L| + j0$$

As a result we can conclude that:

$$|V(z)|_{max} = |V_0^+|(1 + |\Gamma_L|)$$

$$|V(z)|_{min} = |V_0^+|(1 - |\Gamma_L|)$$

The ratio of $|V(z)|_{max}$ to $|V(z)|_{min}$ is known as the **Voltage Standing Wave Ratio (VSWR)**:

$$VSWR \doteq \frac{|V(z)|_{max}}{|V(z)|_{min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad \therefore \quad 1 \leq VSWR \leq \infty$$

Note if $|\Gamma_L| = 0$ (i.e., $Z_L = Z_0$), then $VSWR = 1$. We find for this case:

$$|V(z)|_{max} = |V(z)|_{min} = |V_0^+|$$


In other words, the voltage magnitude is a **constant** with respect to position z .

Conversely, if $|\Gamma_L| = 1$ (i.e., $Z_L = jX$), then $VSWR = \infty$. We find for **this** case:

$$|V(z)|_{min} = 0 \quad \text{and} \quad |V(z)|_{max} = 2|V_0^+|$$


In other words, the voltage magnitude varies **greatly** with respect to position z .

As with **return loss**, VSWR is dependent on the **magnitude** of Γ_L (i.e., $|\Gamma_L|$) **only** !

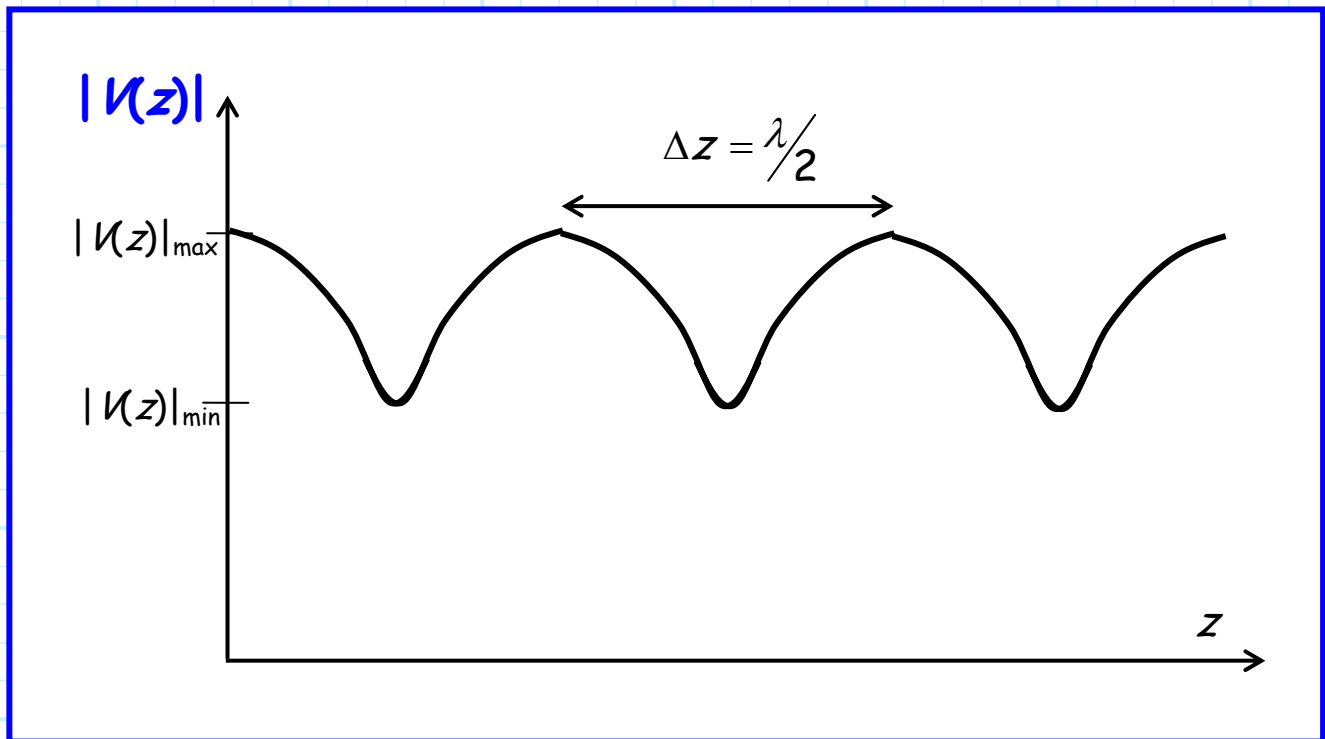

Example: The Transmission Coefficient T

Consider this circuit:

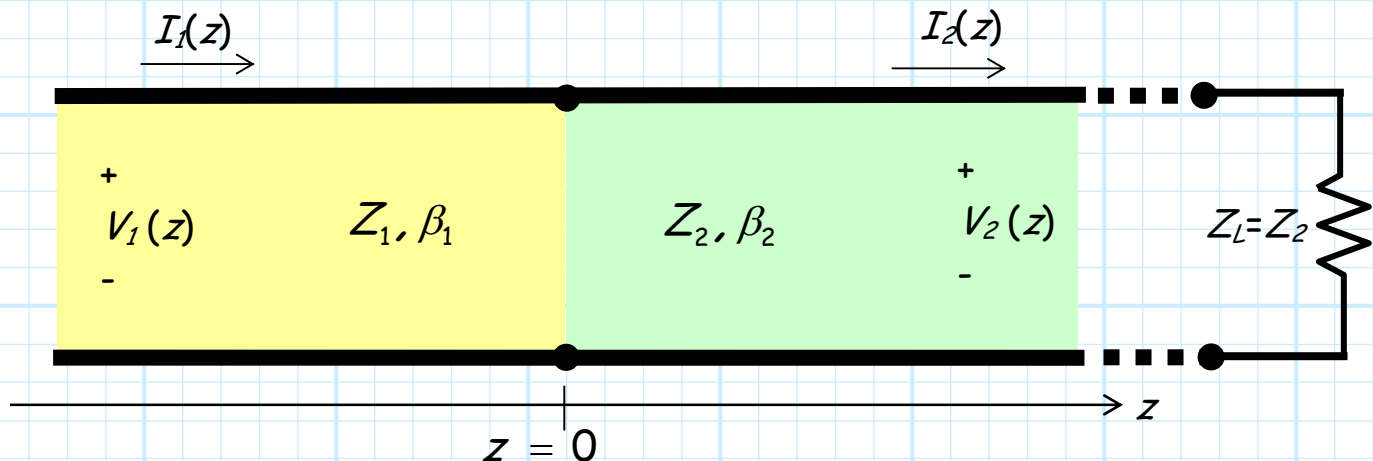

I.E., a transmission line with characteristic impedance Z_1 **transitions** to a **different** transmission line at location $z=0$. This second transmission line has different **characteristic impedance** Z_2 ($Z_1 \neq Z_2$). This second line is **terminated** with a load $Z_L = Z_2$ (i.e., the second line is **matched**).

Q: *What is the voltage and current along each of these two transmission lines? More specifically, what are V_{01}^+ , V_{01}^- , V_{02}^+ and V_{02}^- ??*

A: Since a source has not been specified, we can only determine V_{01}^- , V_{02}^+ and V_{02}^- in terms of complex constant V_{01}^+ . To accomplish this, we must apply a **boundary condition** at $z=0$!

$$z < 0$$

We know that the voltage along the **first** transmission line is:

$$V_1(z) = V_{01}^+ e^{-j\beta_1 z} + V_{01}^- e^{+j\beta_1 z} \quad [\text{for } z < 0]$$

while the **current** along that same line is described as:

$$I_1(z) = \frac{V_{01}^+}{Z_1} e^{-j\beta_1 z} - \frac{V_{01}^-}{Z_1} e^{+j\beta_1 z} \quad [\text{for } z < 0]$$

$$z > 0$$

We likewise know that the voltage along the **second** transmission line is:

$$V_2(z) = V_{02}^+ e^{-j\beta_2 z} + V_{02}^- e^{+j\beta_2 z} \quad [\text{for } z > 0]$$

while the **current** along that same line is described as:

$$I_2(z) = \frac{V_{02}^+}{Z_2} e^{-j\beta_2 z} - \frac{V_{02}^-}{Z_2} e^{+j\beta_2 z} \quad [\text{for } z > 0]$$

Moreover, since the second line is terminated in a **matched load**, we know that the **reflected** wave from this load must be zero:

$$V_2^-(z) = V_{02}^- e^{-j\beta_2 z} = 0$$


The voltage and current along the **second** transmission line is thus simply:

$$V_2(z) = V_2^+(z) = V_{02}^+ e^{-j\beta_2 z} \quad [\text{for } z > 0]$$

$$I_2(z) = I_2^+(z) = \frac{V_{02}^+}{Z_2} e^{-j\beta_2 z} \quad [\text{for } z > 0]$$

$z=0$

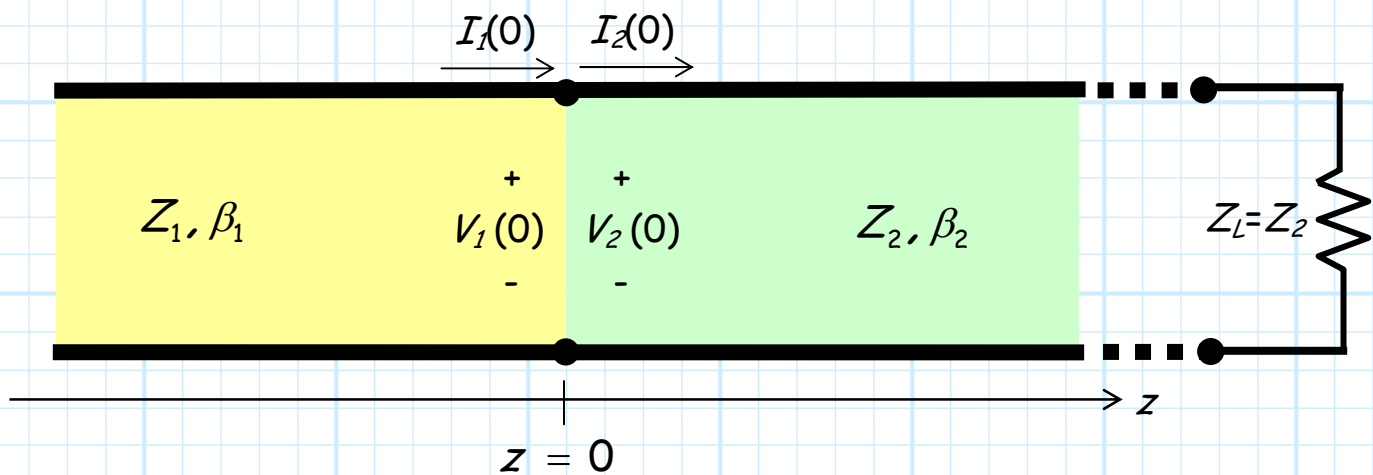At the location where these two transmission lines meet, the current and voltage expressions each **must** satisfy some specific **boundary conditions**:



The **first** boundary condition comes from **KVL**, and states that:

$$V_1(z=0) = V_2(z=0)$$

$$V_{01}^+ e^{-j\beta_1(0)} + V_{01}^- e^{+j\beta_1(0)} = V_{02}^+ e^{-j\beta_2(0)}$$

$$V_{01}^+ + V_{01}^- = V_{02}^+$$

while the **second** boundary condition comes from **KCL**, and states that:

$$I_1(z=0) = I_2(z=0)$$

$$\frac{V_{01}^+}{Z_1} e^{-j\beta_1(0)} - \frac{V_{01}^-}{Z_1} e^{+j\beta_1(0)} = \frac{V_{02}^+}{Z_2} e^{-j\beta_2(0)}$$

$$\frac{V_{01}^+}{Z_1} - \frac{V_{01}^-}{Z_1} = \frac{V_{02}^+}{Z_2}$$

We now have **two** equations and **two** unknowns (V_{01}^- and V_{02}^+)! We can **solve** for each in terms of V_{01}^+ (i.e., the **incident** wave).

From the **first** boundary condition we can state:

$$V_{01}^- = V_{02}^+ - V_{01}^+$$

Inserting this into the **second** boundary condition, we find an expression involving **only** V_{02}^+ and V_{01}^+ :

$$\frac{V_{01}^+}{Z_1} - \frac{V_{01}^-}{Z_1} = \frac{V_{02}^+}{Z_2}$$

$$\frac{V_{01}^+}{Z_1} - \frac{V_{02}^+ - V_{01}^+}{Z_1} = \frac{V_{02}^+}{Z_2}$$

$$\frac{2V_{01}^+}{Z_1} = \frac{V_{02}^+}{Z_2} + \frac{V_{02}^+}{Z_1}$$

Solving this expression, we find:

$$V_{02}^+ = \left(\frac{2Z_2}{Z_1 + Z_2} \right) V_{01}^+$$

We can therefore define a **transmission coefficient**, which relates V_{02}^+ to V_{01}^+ :

$$T_0 \doteq \frac{V_{02}^+}{V_{01}^+} = \frac{2Z_2}{Z_1 + Z_2}$$

Meaning that $V_{02}^+ = T V_{01}^+$, and thus:

$$V_2(z) = V_2^+(z) = T V_{01}^+ e^{-j\beta_2 z} \quad [\text{for } z > 0]$$

We can **likewise** determine the constant V_{01}^- in terms of V_{01}^+ . We again start with the **first** boundary condition, from which we concluded:

$$V_{02}^+ = V_{01}^+ + V_{01}^-$$

We can insert this into the **second** boundary condition, and determine an expression involving V_{01}^- and V_{01}^+ **only**:

$$\begin{aligned} \frac{V_{01}^+}{Z_1} - \frac{V_{01}^-}{Z_1} &= \frac{V_{02}^+}{Z_2} \\ \frac{V_{01}^+}{Z_1} - \frac{V_{01}^-}{Z_1} &= \frac{V_{01}^+ + V_{01}^-}{Z_2} \\ \left(\frac{1}{Z_1} - \frac{1}{Z_2} \right) V_{01}^+ &= \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) V_{01}^- \end{aligned}$$

Solving this expression, we find:


$$V_{01}^- = \left(\frac{Z_2 - Z_1}{Z_2 + Z_1} \right) V_{01}^+$$

We can therefore define a **reflection coefficient**, which relates V_{01}^- to V_{01}^+ :


$$\Gamma_0 \doteq \frac{V_{01}^-}{V_{01}^+} = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$

This result should **not** surprise us!

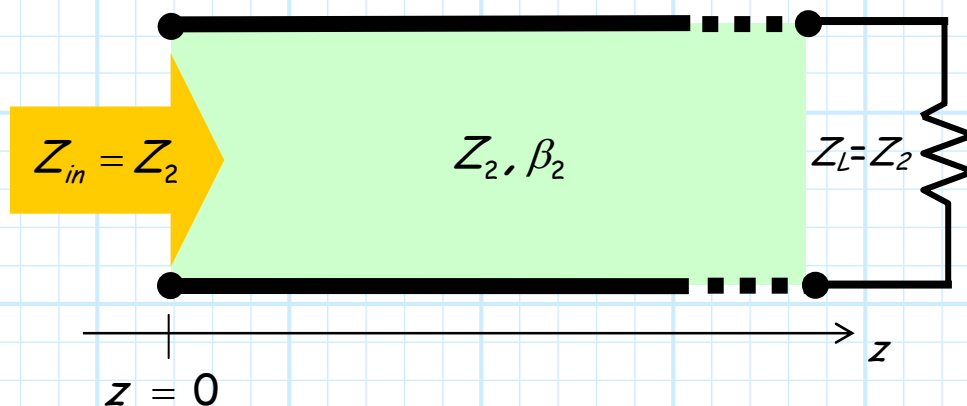Note that because the **second** transmission line is **matched**, its **input impedance** is equal to Z_1 :



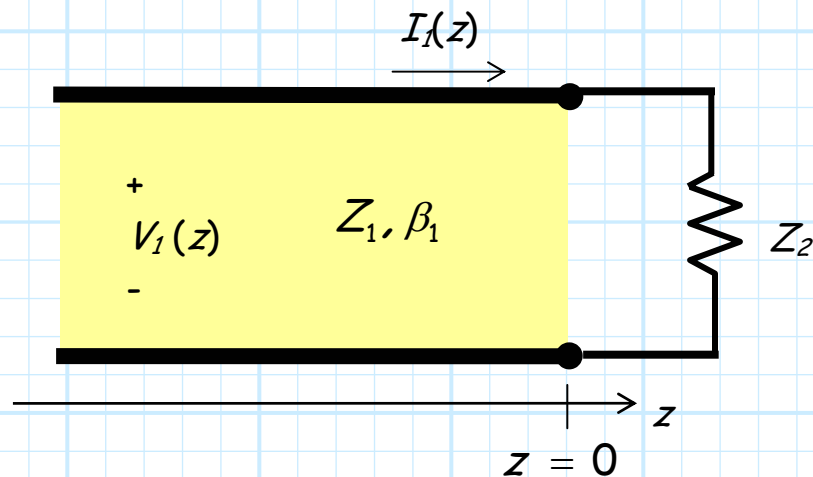and thus we can **equivalently** write the entire circuit as:



We have already analyzed **this** circuit! We know that:

$$\begin{aligned} V_{01}^- &= \Gamma_L V_{01}^+ \\ &= \left(\frac{Z_2 - Z_1}{Z_2 + Z_1} \right) V_{01}^+ \end{aligned}$$

Which is **exactly** the same result as we determined earlier!

The values of the reflection coefficient Γ_0 and the transmission coefficient T_0 are **not** independent, but in fact are directly **related**. Recall the **first** boundary expressed was:

$$V_{01}^+ + V_{01}^- = V_{02}^+$$

Dividing this by V_{01}^+ :

$$1 + \frac{V_{01}^-}{V_{01}^+} = \frac{V_{02}^+}{V_{01}^+}$$


Since $\Gamma_0 = V_{01}^- / V_{01}^+$ and $\mathcal{T}_0 = V_{02}^+ / V_{01}^+$:

$$1 + \Gamma_0 = \mathcal{T}_0$$

Note the result $\mathcal{T}_0 = 1 + \Gamma_0$ is true for **this** particular circuit, and therefore is **not** a universally valid expression for two-port networks!

Example: Applying Boundary Conditions

Consider this circuit:

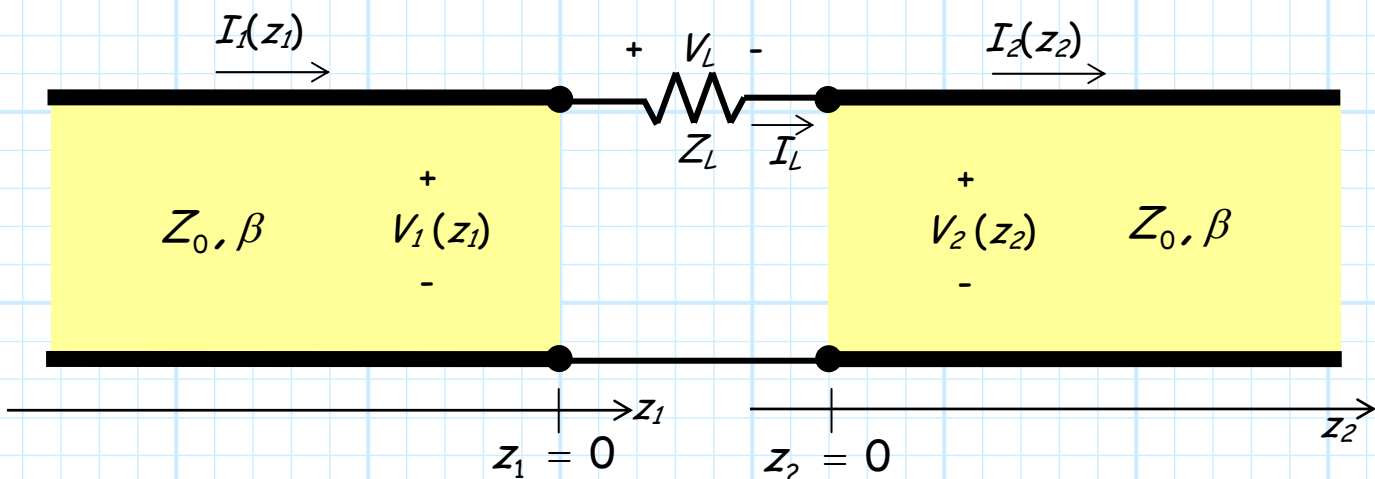

I.E., Two transmissions of **identical** characteristic impedance are connect by a **series** impedance Z_L . This second line is eventually **terminated** with a load $Z_L = Z_0$ (i.e., the second line is **matched**).

Q: *What is the voltage and current along each of these two transmission lines? More specifically, what are V_{01}^+ , V_{01}^- , V_{02}^+ and V_{02}^- ??*

A: Since a source has not been specified, we can only determine V_{01}^- , V_{02}^+ and V_{02}^- in terms of complex constant V_{01}^+ . To accomplish this, we must apply a **boundary conditions** at the end of each line!

$$z_1 < 0$$

We know that the voltage along the **first** transmission line is:

$$V_1(z_1) = V_{01}^+ e^{-j\beta z_1} + V_{01}^- e^{+j\beta z_1} \quad [\text{for } z_1 < 0]$$

while the **current** along that same line is described as:

$$I_1(z_1) = \frac{V_{01}^+}{Z_0} e^{-j\beta z_1} - \frac{V_{01}^-}{Z_0} e^{+j\beta z_1} \quad [\text{for } z_1 < 0]$$

$$z_2 > 0$$

We likewise know that the voltage along the **second** transmission line is:

$$V_2(z_2) = V_{02}^+ e^{-j\beta z_2} + V_{02}^- e^{+j\beta z_2} \quad [\text{for } z_2 > 0]$$

while the **current** along that same line is described as:

$$I_2(z_2) = \frac{V_{02}^+}{Z_0} e^{-j\beta z_2} - \frac{V_{02}^-}{Z_0} e^{+j\beta z_2} \quad [\text{for } z_2 > 0]$$

Moreover, since the second line is terminated in a **matched load**, we know that the **reflected** wave from this load must be zero:

$$V_2^-(z_2) = V_{02}^- e^{-j\beta z_2} = 0$$


The voltage and current along the **second** transmission line is thus simply:

$$V_2(z_2) = V_2^+(z_2) = V_{02}^+ e^{-j\beta z_2} \quad [\text{for } z_2 > 0]$$

$$I_2(z_2) = I_2^+(z_2) = \frac{V_{02}^+}{Z_2} e^{-j\beta z_2} \quad [\text{for } z_2 > 0]$$

$z=0$

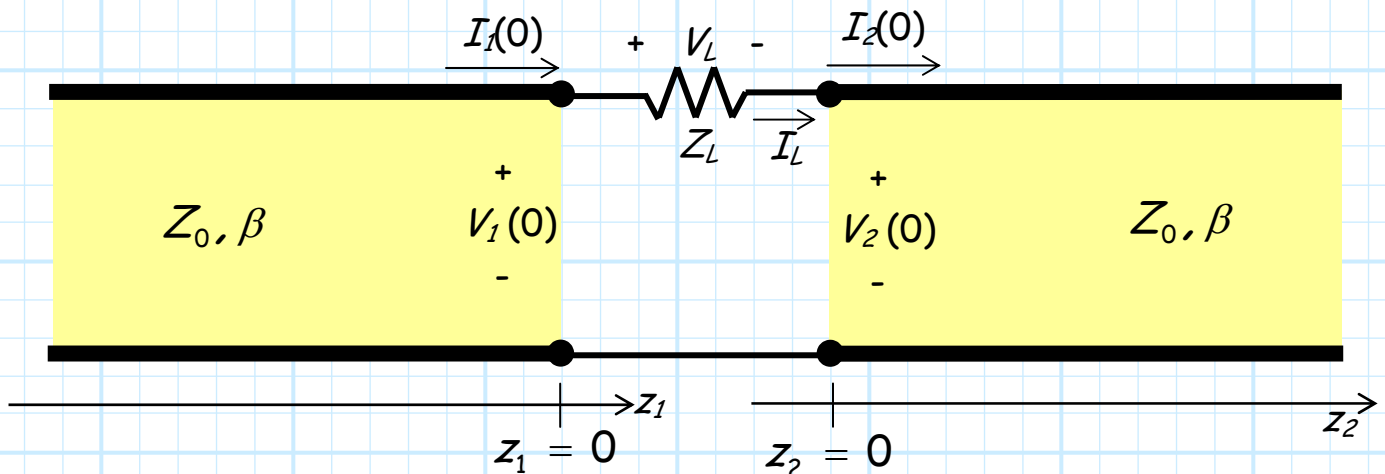At the location where these two transmission lines meet, the current and voltage expressions each **must** satisfy some specific **boundary conditions**:



The **first** boundary condition comes from **KVL**, and states that:

$$V_1(z=0) - I_L Z_L = V_2(z=0)$$

$$V_{01}^+ e^{-j\beta(0)} + V_{01}^- e^{+j\beta(0)} - I_L Z_L = V_{02}^+ e^{-j\beta(0)}$$

$$V_{01}^+ + V_{01}^- - I_L Z_L = V_{02}^+$$

the **second** boundary condition comes from **KCL**, and states that:

$$I_1(z=0) = I_L$$

$$\frac{V_{01}^+}{Z_0} e^{-j\beta(0)} - \frac{V_{01}^-}{Z_0} e^{+j\beta(0)} = I_L$$

$$V_{01}^+ - V_{01}^- = Z_0 I_L$$

while the **third** boundary condition likewise comes from **KCL**, and states that:

$$I_L = I_2(z=0)$$

$$I_L = \frac{V_{02}^+}{Z_0} e^{-j\beta(0)}$$

$$Z_0 I_L = V_{02}^+$$

Finally, we have Ohm's Law:

$$V_L = Z_L I_L$$

Note that we now have **four** equations and **four** unknowns (V_{01}^- , V_{02}^+ , V_L , I_L)! We can **solve** for each in terms of V_{01}^+ (i.e., the **incident** wave).

For **example**, let's determine V_{02}^+ (in terms of V_{01}^+). We combine the **first** and **second** boundary conditions to determine:

$$V_{01}^+ + V_{01}^- - I_L Z_L = V_{02}^+$$

$$V_{01}^+ + (V_{01}^+ - Z_0 I_L) - I_L Z_L = V_{02}^+$$

$$2V_{01}^+ - I_L (Z_0 + Z_L) = V_{02}^+$$

And then adding in the **third** boundary condition:

$$2V_{01}^+ - I_L (Z_0 + Z_L) = V_{02}^+$$


$$2V_{01}^+ - \frac{V_{02}^+}{Z_0} (Z_0 + Z_L) = V_{02}^+$$

$$2V_{01}^+ = V_{02}^+ \left(\frac{2Z_0 + Z_L}{Z_0} \right)$$

Thus, we find that $V_{02}^+ = T_0 V_{01}^+$:

$$T_0 \doteq \frac{V_{02}^+}{V_{01}^+} = \frac{2Z_0}{2Z_0 + Z_L}$$

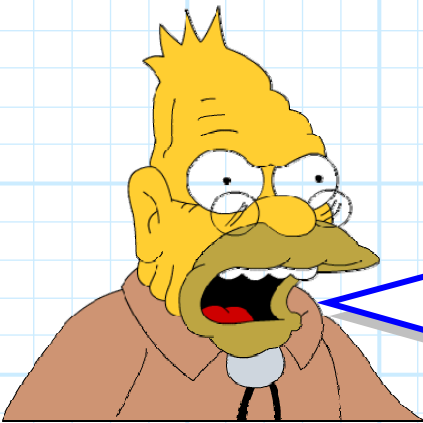Now let's determine V_{01}^- (in terms of V_{01}^+).



Q: *Why are you wasting our time? Don't we already know that $V_{01}^- = \Gamma_0 V_{01}^+$, where:*

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0}$$

A: Perhaps. Humor me while I **continue** with our **boundary condition** analysis.

We combine the **first** and **third** boundary conditions to determine:

$$V_{01}^+ + V_{01}^- - I_L Z_L = V_{02}^+$$

$$V_{01}^+ + V_{01}^- - I_L Z_L = Z_0 I_L$$

$$V_{01}^+ + V_{01}^- = I_L (Z_0 + Z_L)$$

And then adding the **second** boundary condition:

$$V_{01}^+ + V_{01}^- = I_L (Z_0 + Z_L)$$

$$V_{01}^+ + V_{01}^- = \frac{(V_{01}^+ - V_{01}^-)}{Z_0} (Z_0 + Z_L)$$

$$V_{01}^+ \left(\frac{Z_L}{Z_0} \right) = V_{01}^- \left(\frac{2Z_0 + Z_L}{Z_0} \right)$$

Thus, we find that $V_{01}^- = \Gamma_0 V_{01}^+$, where:

$$\Gamma_0 \doteq \frac{V_{01}^-}{V_{01}^+} = \frac{Z_L}{Z_L + 2Z_0}$$


Note this is **not** the expression:

$$\Gamma_0 \neq \frac{Z_L - Z_0}{Z_L + Z_0}$$



This is a completely **different** problem than the transmission line simply terminated by load Z_L . Thus, the **results** are likewise different. This shows that you must always **carefully** consider the problem you are attempting to solve, and guard against using "shortcuts" with previously derived expressions that may be **inapplicable**.

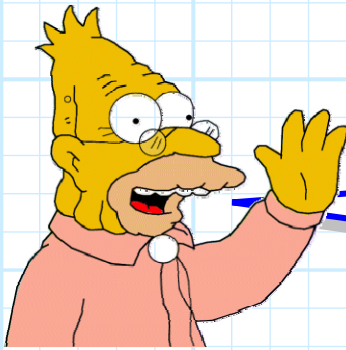
→ This is why you must know **why** a correct answer is correct!




Q: *But, isn't there **some** way to solve this using our previous work?*

A: Actually, there is!

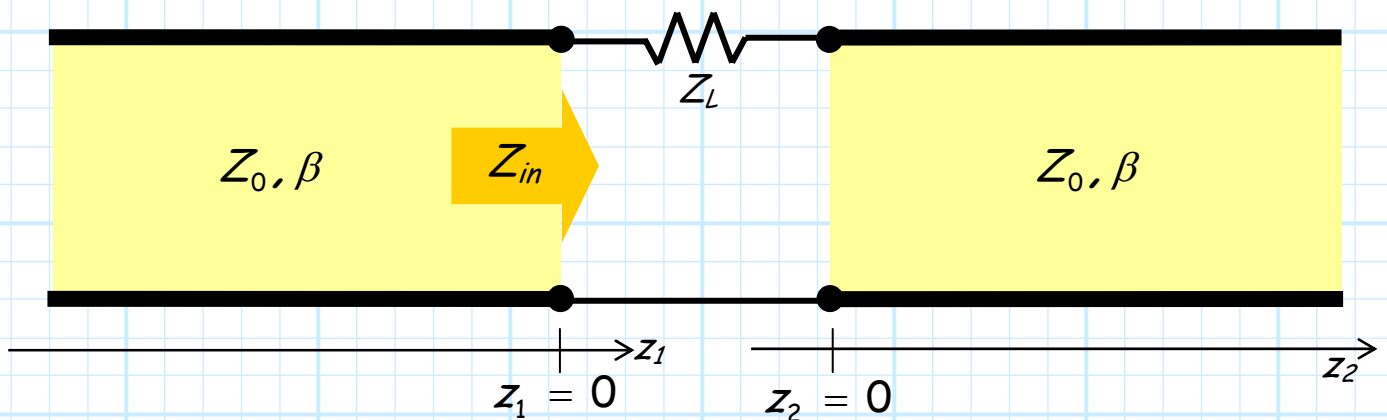
An **alternative** way for finding $\Gamma_0 = V_{01}^- / V_{01}^+$ is to determine the **input impedance at the end of the first transmission line:**



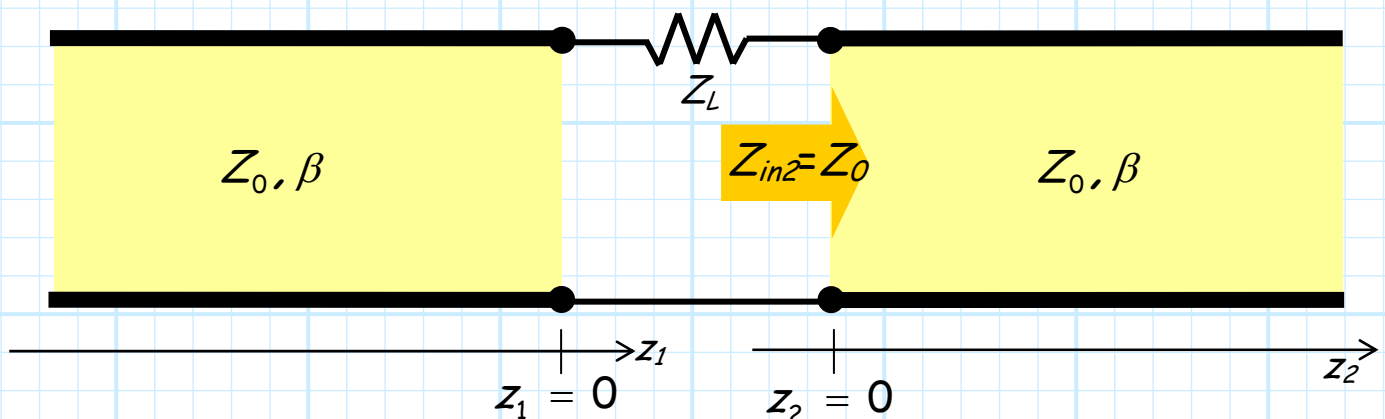Note that since the second line is (eventually) terminated in a matched load, the input impedance at the **beginning** of the **second** line is simply equal to Z_0 .



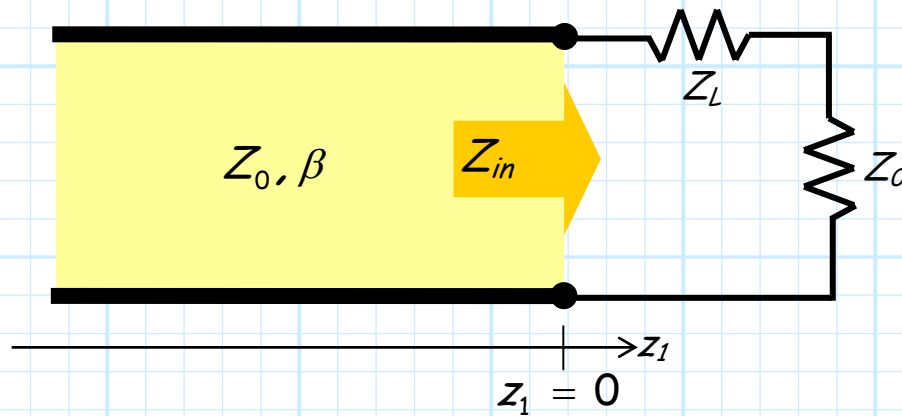
Thus, the **equivalent** circuit becomes:



And it is apparent that:

$$Z_{in} = Z_L + Z_0$$

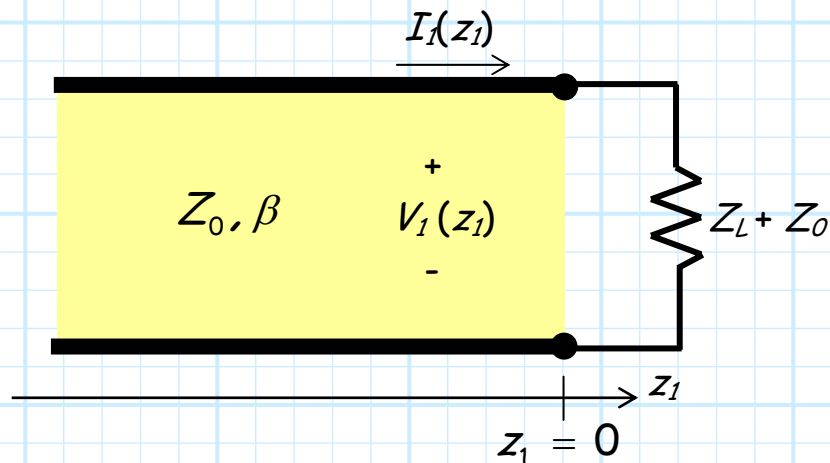As far as the first section of transmission line is concerned, it is **terminated** in a load with impedance $Z_L + Z_0$. The current and voltage along this first transmission line is **precisely** the same as if it **actually** were!



Thus, we find that $\Gamma_0 = V_{01}^- / V_{01}^+$, where:

$$\begin{aligned}\Gamma_0 &= \frac{Z(z_1=0) - Z_0}{Z(z_1=0) + Z_0} \\ &= \frac{(Z_L + Z_0) - Z_0}{(Z_L + Z_0) + Z_0} \\ &= \frac{Z_L}{Z_L + 2Z_0}\end{aligned}$$


Precisely the same result as before!

Now, one **more** point. Recall we found in an **earlier** handout that $T_0 = 1 + \Gamma_0$. But for this example we find that this statement is **not valid**:

$$1 + \Gamma_0 = \frac{2(Z_L + Z_0)}{Z_L + 2Z_0} \neq T_0$$

Again, be **careful** when analyzing microwave circuits!

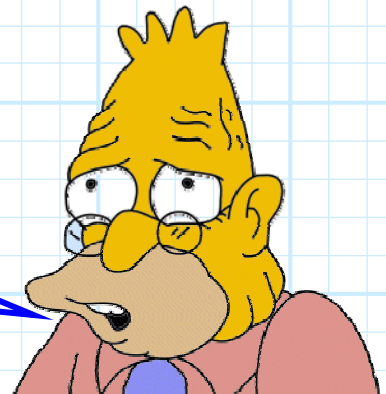Q: *But this seems so difficult. How will I know if I have made a mistake?*



A: An important engineering tool that **you** must master is commonly referred to as the "**sanity check**".

Simply put, a sanity check is simply **thinking** about your result, and determining whether or not it **makes sense**. A great **strategy** is to set one of the variables to a value so that the **physical** problem becomes **trivial**—so trivial that the correct answer is **obvious** to you. Then make sure your results **likewise** provide this obvious answer!


For example, consider the problem we just finished analyzing. Say that the impedance Z_L is actually a **short circuit** ($Z_L=0$). We find that:

$$\Gamma_0 = \frac{Z_L}{Z_L + 2Z_0} \Big|_{Z_L=0} = 0 \qquad \mathcal{T}_0 = \frac{2Z_0}{2Z_0 + Z_L} \Big|_{Z_L=0} = 1$$


Likewise, consider the case where Z_L is actually an **open circuit** ($Z_L=\infty$). We find that:

$$\Gamma_0 = \frac{Z_L}{Z_L + 2Z_0} \Big|_{Z_L=\infty} = 1 \qquad \mathcal{T}_0 = \frac{2Z_0}{2Z_0 + Z_L} \Big|_{Z_L=\infty} = 0$$

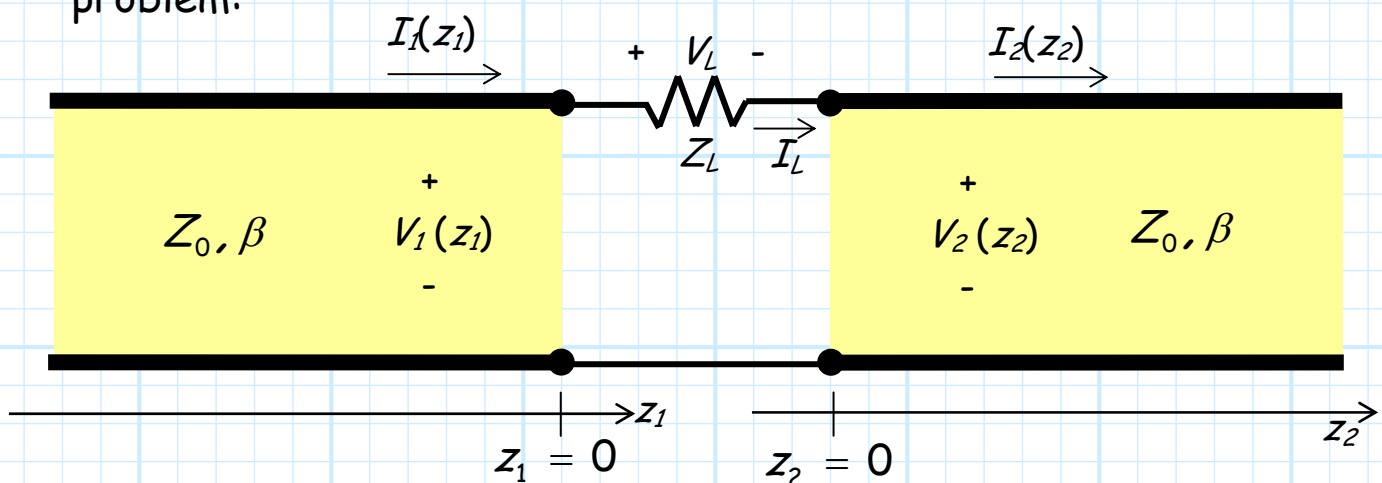Think about what these results mean in terms of the **physical** problem:




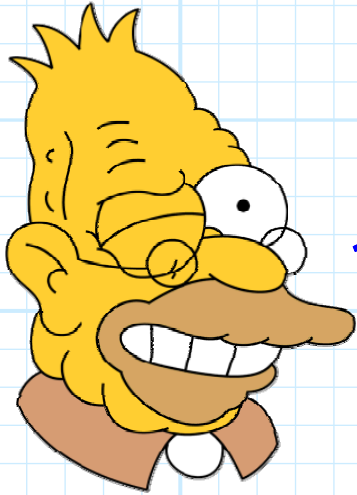Q: Do these results **make sense?** Have we **passed** the sanity check?



A: *I'll let you decide!*
What do you think?

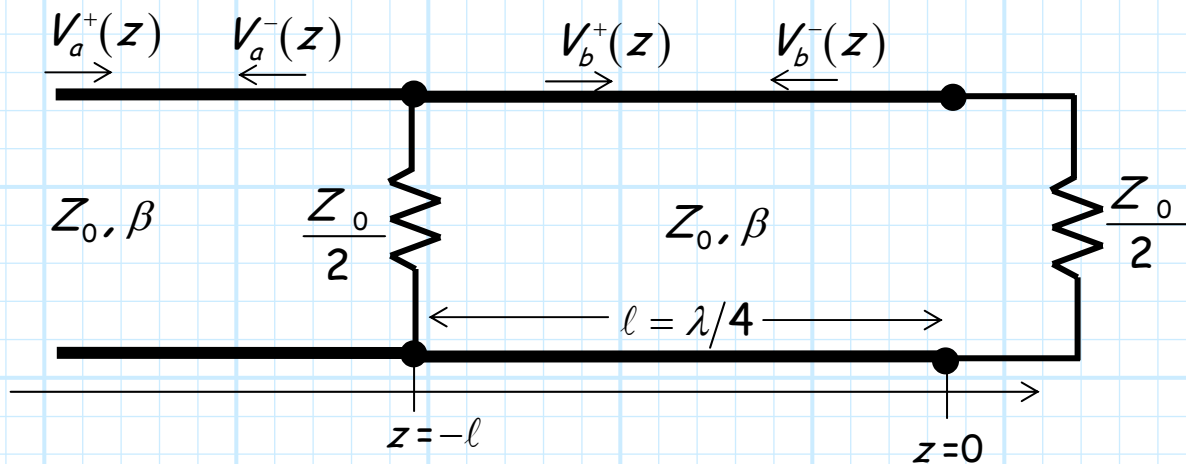Example: Another Boundary Condition Problem



The **total** voltage along the transmission line shown above is expressed as:

$$V(z) = \begin{cases} V_a^+ e^{-j\beta z} + V_a^- e^{+j\beta z} & z < -\ell \\ V_b^+ e^{-j\beta z} + V_b^- e^{+j\beta z} & -\ell < z < 0 \end{cases}$$

Carefully determine and apply boundary conditions at both $z = 0$ and $z = -\ell$ to find the three values:

$$\frac{V_a^-}{V_a^+}, \quad \frac{V_b^+}{V_a^+}, \quad \frac{V_b^-}{V_a^+}$$

Solution

From the telegrapher's equation, we likewise know that the current along the transmission lines is:


$$I(z) = \begin{cases} \frac{V_a^+}{Z_0} e^{-j\beta z} - \frac{V_a^-}{Z_0} e^{+j\beta z} & z < -\ell \\ \frac{V_b^+}{Z_0} e^{-j\beta z} - \frac{V_b^-}{Z_0} e^{+j\beta z} & -\ell < z < 0 \end{cases}$$

To find the values:

$$\frac{V_a^-}{V_a^+}, \quad \frac{V_b^+}{V_a^+}, \quad \frac{V_b^-}{V_a^+}$$

We need only to evaluate boundary conditions!

Boundary Conditions at $z = -\ell$

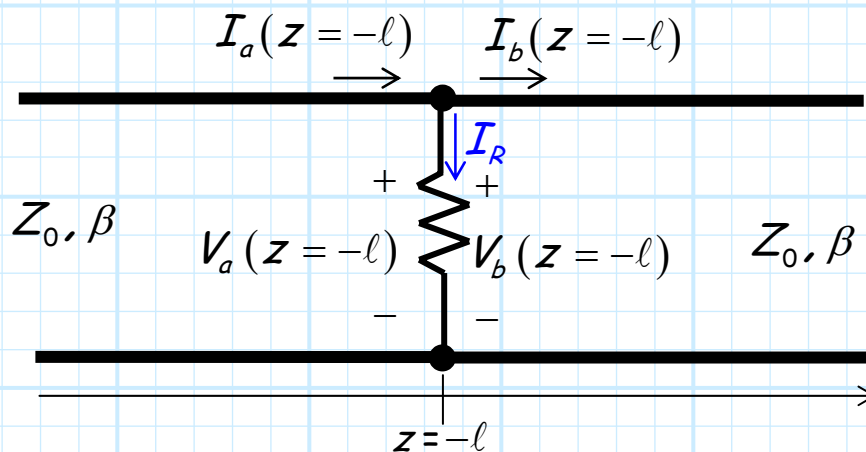

From KVL, we conclude:

$$V_a(z = -\ell) = V_b(z = -\ell)$$

From KCL:

$$I_a(z = -\ell) = I_b(z = -\ell) + I_R$$

And from Ohm's Law:

$$I_R = \frac{V_a(z = -\ell)}{Z_0/2} = \frac{2V_a(z = -\ell)}{Z_0} = \frac{2V_b(z = -\ell)}{Z_0}$$

We likewise know from the telegrapher's equation that:

$$\begin{aligned} V_a(z = -\ell) &= V_a^+ e^{-j\beta(-\ell)} + V_a^- e^{+j\beta(-\ell)} \\ &= V_a^+ e^{+j\beta\ell} + V_a^- e^{-j\beta\ell} \end{aligned}$$

And since $\ell = \lambda/4$, we find:

$$\beta\ell = \left(\frac{2\pi}{\lambda}\right)\left(\frac{\lambda}{4}\right) = \frac{\pi}{2}$$

And so:

$$\begin{aligned} V_a(z = -\ell) &= V_a^+ e^{+j\beta\ell} + V_a^- e^{-j\beta\ell} \\ &= V_a^+ e^{+j(\pi/2)} + V_a^- e^{-j(\pi/2)} \\ &= V_a^+ (j) + V_a^- (-j) \\ &= j(V_a^+ - V_a^-) \end{aligned}$$

We similarly find that:

$$V_b(z = -\ell) = j(V_b^+ - V_b^-)$$

and for currents:

$$I_a(z = -l) = j \frac{V_a^+ + V_a^-}{Z_0}$$

$$I_b(z = -l) = j \frac{V_b^+ + V_b^-}{Z_0}$$

Inserting these results into our KVL boundary condition statement:

$$\begin{aligned} V_a(z = -l) &= V_b(z = -l) \\ j(V_a^+ - V_a^-) &= j(V_b^+ - V_b^-) \\ V_a^+ - V_a^- &= V_b^+ - V_b^- \end{aligned}$$

Normalizing to (i.e., dividing by) V_a^+ , we conclude:

$$1 - \frac{V_a^-}{V_a^+} = \frac{V_b^+}{V_a^+} - \frac{V_b^-}{V_a^+}$$

From Ohm's Law:

$$I_R = \frac{2V_a(z = -l)}{Z_0} = \frac{2j(V_a^+ - V_a^-)}{Z_0}$$

$$I_R = \frac{2V_b(z = -l)}{Z_0} = \frac{2j(V_b^+ - V_b^-)}{Z_0}$$

And finally from our KCL boundary condition:

$$\begin{aligned} I_a(z = -l) &= I_b(z = -l) + I_R \\ j \frac{V_a^+ + V_a^-}{Z_0} &= j \frac{V_b^+ + V_b^-}{Z_0} + I_R \end{aligned}$$

After an **enjoyable** little bit of algebra, we can thus conclude:

$$V_a^+ + V_a^- = V_b^+ + V_b^- - jI_R Z_0$$

And inserting the result from Ohm's Law:

$$\begin{aligned} V_a^+ + V_a^- &= V_b^+ + V_b^- - jI_R Z_0 \\ &= V_b^+ + V_b^- - j \left(\frac{2j(V_b^+ - V_b^-)}{Z_0} \right) Z_0 \\ &= V_b^+ + V_b^- - 2j^2 (V_b^+ - V_b^-) \left(\frac{Z_0}{Z_0} \right) \\ &= V_b^+ + V_b^- - 2(-1)(V_b^+ - V_b^-) \\ &= V_b^+ + V_b^- + 2V_b^+ - 2V_b^- \\ &= 3V_b^+ - V_b^- \end{aligned}$$

Again normalizing to V_a^+ , we get a second relationship:

$$1 + \frac{V_a^-}{V_a^+} = 3 \frac{V_b^+}{V_a^+} - \frac{V_b^-}{V_a^+}$$

Q: *But wait! We now have **two** equations:*

$$1 - \frac{V_a^-}{V_a^+} = \frac{V_b^+}{V_a^+} - \frac{V_b^-}{V_a^+} \qquad 1 + \frac{V_a^-}{V_a^+} = 3 \frac{V_b^+}{V_a^+} - \frac{V_b^-}{V_a^+}$$


but **three** unknowns:

$$\frac{V_a^-}{V_a^+}, \frac{V_b^+}{V_a^+}, \frac{V_b^-}{V_a^+}$$

Did we make a **mistake** somewhere?

A: Nope! We just have more work to do. After all, there is a yet **another boundary** to be analyzed!

Boundary Conditions at $z = 0$

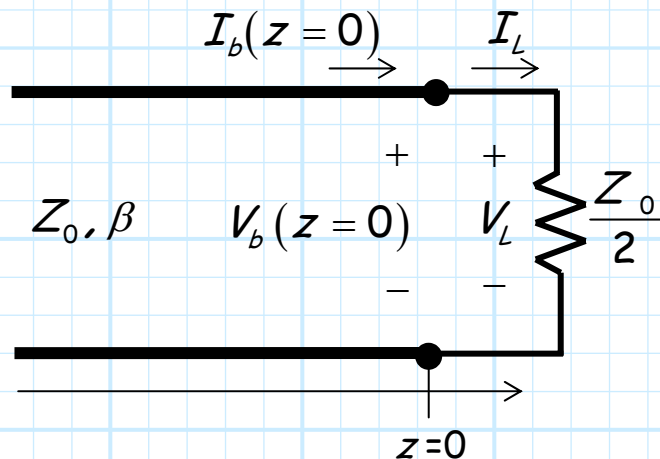

From KVL, we conclude:

$$V_b(z=0) = V_L$$

From KCL:

$$I_b(z=0) = I_L$$

And from Ohm's Law:

$$I_L = \frac{V_L}{Z_0/2} = \frac{2V_L}{Z_0}$$

We likewise know from the telegrapher's equation that:

$$\begin{aligned} V_b(z=0) &= V_b^+ e^{-j\beta(0)} + V_b^- e^{+j\beta(0)} \\ &= V_b^+ (1) + V_b^- (1) \\ &= V_b^+ + V_b^- \end{aligned}$$

We similarly find that:

$$I_b(z=0) = \frac{V_b^+ - V_b^-}{Z_0}$$

Combing this with the above results:

$$I_L = \frac{2V_L}{Z_0}$$

$$I_b(z=0) = \frac{2V_b(z=0)}{Z_0}$$

$$\frac{V_b^+ - V_b^-}{Z_0} = \frac{2(V_b^+ + V_b^-)}{Z_0}$$

From which we conclude:

$$V_b^+ - V_b^- = 2(V_b^+ + V_b^-) \Rightarrow -3V_b^- = V_b^+$$

And so:

$$V_b^- = -\frac{1}{3}V_b^+$$

Note that we could have also determined this using the load reflection coefficient:

$$\frac{V_b^-(z=0)}{V_b^+(z=0)} = \Gamma(z=0) = \Gamma_0$$

Where:

$$V_b^-(z=0) = V_b^- e^{+j\beta(0)} = V_b^-$$

$$V_b^+(z=0) = V_b^+ e^{-j\beta(0)} = V_b^+$$

And we use the boundary condition:

$$\Gamma_0 = \Gamma_{Lb} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{0.5Z_0 - Z_0}{0.5Z_0 + Z_0} = \frac{-0.5}{1.5} = -\frac{1}{3}$$

Therefore, we arrive at the **same result** as before:

$$\frac{V_b^-(z=0)}{V_b^+(z=0)} = \Gamma_0$$

$$\frac{V_b^-}{V_b^+} = -\frac{1}{3}$$

Either way, we can use this result to simplify our first set of boundary conditions:

$$1 - \frac{V_a^-}{V_a^+} = \frac{V_b^+}{V_a^+} - \frac{V_b^-}{V_a^+}$$

$$= \frac{V_b^+}{V_a^+} - \frac{-V_b^+/3}{V_a^+}$$

$$= \frac{V_b^+}{V_a^+} + \frac{1}{3} \frac{V_b^+}{V_a^+}$$

$$= \frac{4}{3} \frac{V_b^+}{V_a^+}$$

And:

$$\begin{aligned}
 1 + \frac{V_a^-}{V_a^+} &= 3 \frac{V_b^+}{V_a^+} - \frac{V_b^-}{V_a^+} \\
 &= 3 \frac{V_b^+}{V_a^+} - \frac{-V_b^+}{3} \\
 &= 3 \frac{V_b^+}{V_a^+} + \frac{1}{3} \frac{V_b^+}{V_a^+} \\
 &= \frac{10}{3} \frac{V_b^+}{V_a^+}
 \end{aligned}$$

NOW we have **two** equations and **two** unknowns:

$$1 - \frac{V_a^-}{V_a^+} = \frac{4}{3} \frac{V_b^+}{V_a^+} \qquad 1 + \frac{V_a^-}{V_a^+} = \frac{10}{3} \frac{V_b^+}{V_a^+}$$

Adding the two equations, we find:


$$\begin{aligned}
 \left(1 - \frac{V_a^-}{V_a^+}\right) + \left(1 + \frac{V_a^-}{V_a^+}\right) &= \left(\frac{4}{3} \frac{V_b^+}{V_a^+}\right) + \left(\frac{10}{3} \frac{V_b^+}{V_a^+}\right) \\
 2 &= \frac{14}{3} \frac{V_b^+}{V_a^+} \\
 \frac{3}{7} &= \frac{V_b^+}{V_a^+}
 \end{aligned}$$

And so using the second equation above:

$$\begin{aligned}
 \frac{V_a^-}{V_a^+} &= \frac{10}{3} \frac{V_b^+}{V_a^+} - 1 \\
 &= \frac{10}{3} \frac{3}{7} - 1 \\
 &= \frac{3}{7}
 \end{aligned}$$

And finally, from one of our original boundary conditions:
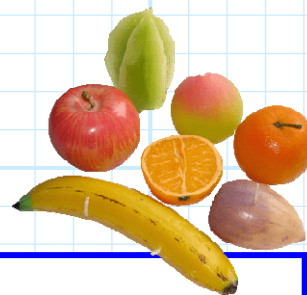
$$\begin{aligned}\frac{V_b^-}{V_a^+} &= \frac{V_b^+}{V_a^+} - 1 + \frac{V_a^-}{V_a^+} \\ &= \frac{3}{7} - 1 + \frac{3}{7} \\ &= -\frac{1}{7}\end{aligned}$$




And so now we **summarize** the fruit of our labor:

$$\frac{V_a^-}{V_a^+} = \frac{3}{7} \quad \frac{V_b^+}{V_a^+} = \frac{3}{7} \quad \frac{V_b^-}{V_a^+} = -\frac{1}{7}$$

Yes it is! It's time for a **sanity check!!!**


The first of our boundary condition equations:
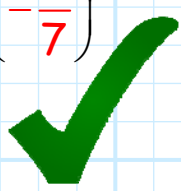
$$\begin{aligned}1 - \frac{V_a^-}{V_a^+} &= \frac{V_b^+}{V_a^+} - \frac{V_b^-}{V_a^+} \\ 1 - \frac{3}{7} &= \frac{3}{7} - \left(-\frac{1}{7}\right) \\ \frac{4}{7} &= \frac{4}{7}\end{aligned}$$


And from the second:

$$1 + \frac{V_a^-}{V_a^+} = 3 \frac{V_b^+}{V_a^+} - \frac{V_b^-}{V_a^+}$$


$$1 + \frac{3}{7} = 3 \frac{3}{7} - \left(-\frac{1}{7} \right)$$

$$\frac{10}{7} = \frac{10}{7}$$

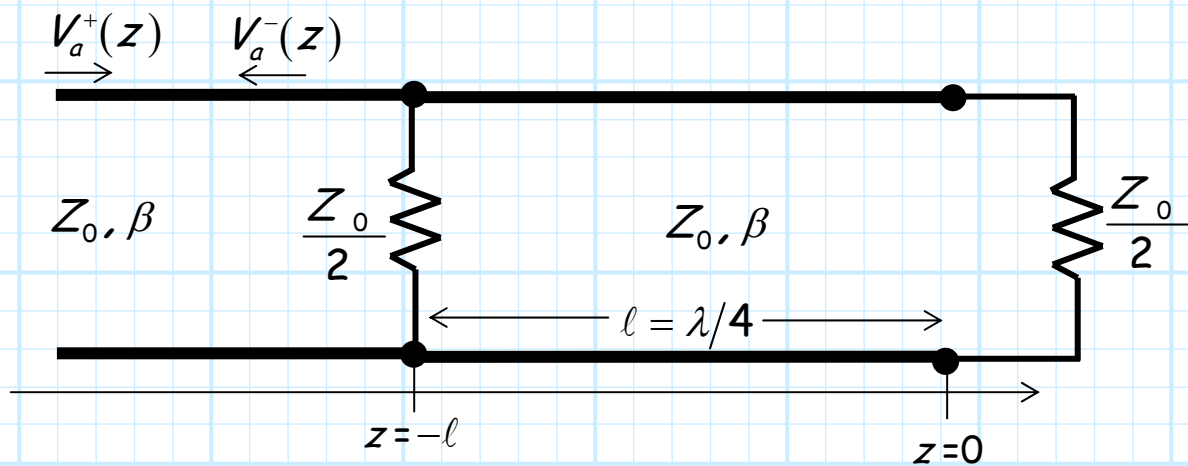
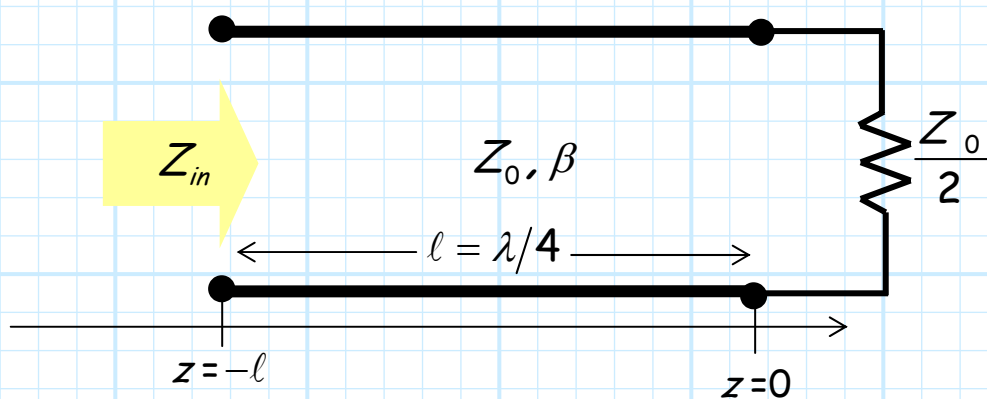
Notice that we can also verify the result:

$$\frac{V_a^-}{V_a^+} = \frac{3}{7}$$

By using the equivalent circuit of:




Specifically, we can determine the input impedance of this circuit:



Since the transmission line is the special case of one quarter wavelength, we know that:

$$Z_{in} = \frac{Z_0^2}{0.5Z_0} = 2.0Z_0$$


And so the equivalent circuit is

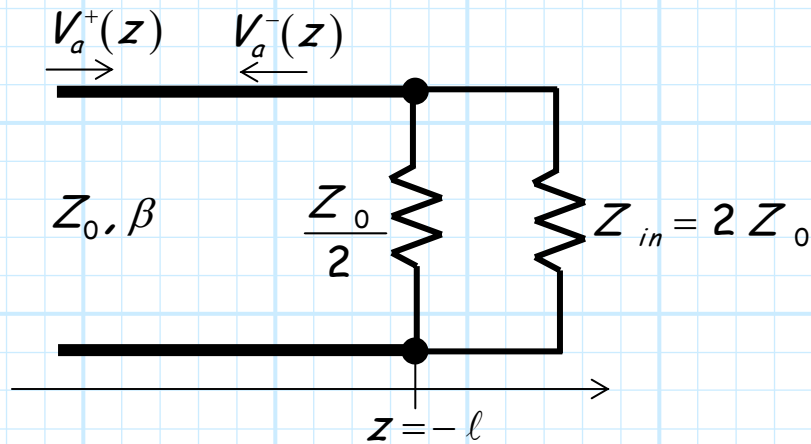

Where the two parallel impedances combine as:

$$0.5Z_0 \parallel 2Z_0 = \frac{Z_0}{2.5} = 0.4Z_0$$

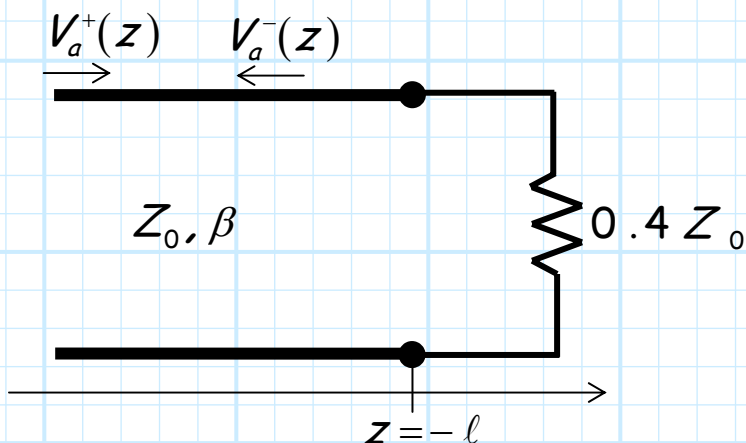And so the equivalent load at $z = -l$ is $0.4Z_0$:



Now, the reflection coefficient of this load is:

$$\Gamma_{La} = \frac{0.4Z_0 - Z_0}{0.4Z_0 + Z_0} = \frac{-0.6}{1.4} = -\frac{3}{7}$$


Q: *Wait a second! Using your fancy "boundary conditions" to solve the problem, you **earlier** arrived at the conclusion:*

$$\frac{V_a^-}{V_a^+} = \frac{3}{7}$$

*But **now** we find that instead:*

$$\frac{V_a^-}{V_a^+} = \Gamma_{La} = -\frac{3}{7}$$

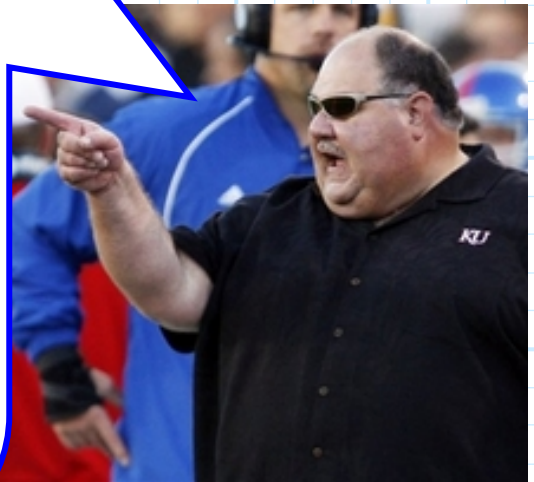*Apparently your annoyingly pretentious boundary condition analysis introduced some sort of **sign error** !*



A: Absolutely not! The boundary condition analysis is perfectly correct, and:

$$\frac{V_a^-}{V_a^+} = \frac{3}{7}$$

is the right answer.

The statement:

~~$$\frac{V_a^-}{V_a^+} = \Gamma_{La} = -\frac{3}{7}$$~~

is **erroneous**!



Q: But how could that possibly be? You earlier determined that:


$$\frac{V_b^-}{V_b^+} = \Gamma_{Lb} = -\frac{1}{3}$$

So why then is:

$$\frac{V_a^-}{V_a^+} \neq \Gamma_{La} \quad \text{????}$$



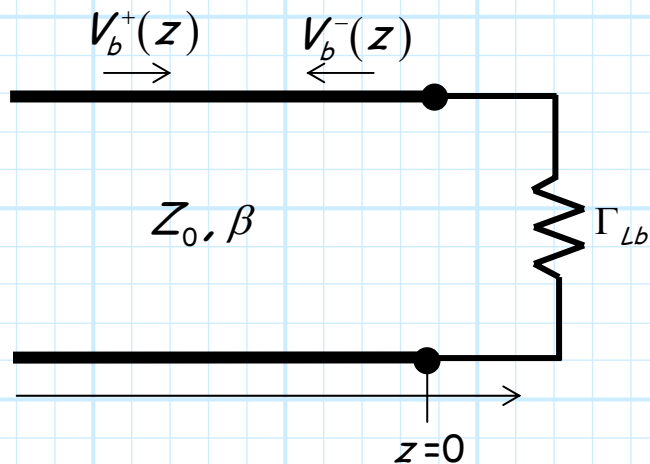A: In the first case, load Γ_{Lb} is located at position $z = 0$, so that:




$$\Gamma_{Lb} = \frac{V_b^-(z=0)}{V_b^+(z=0)} = \frac{V_b^-}{V_b^+}$$

Note this result can be more compactly stated as a boundary condition requirement:

$$\Gamma_{Lb} = \Gamma(z=0) = \frac{V_b^-}{V_b^+} e^{+j\beta(0)} = \frac{V_b^-}{V_b^+}$$

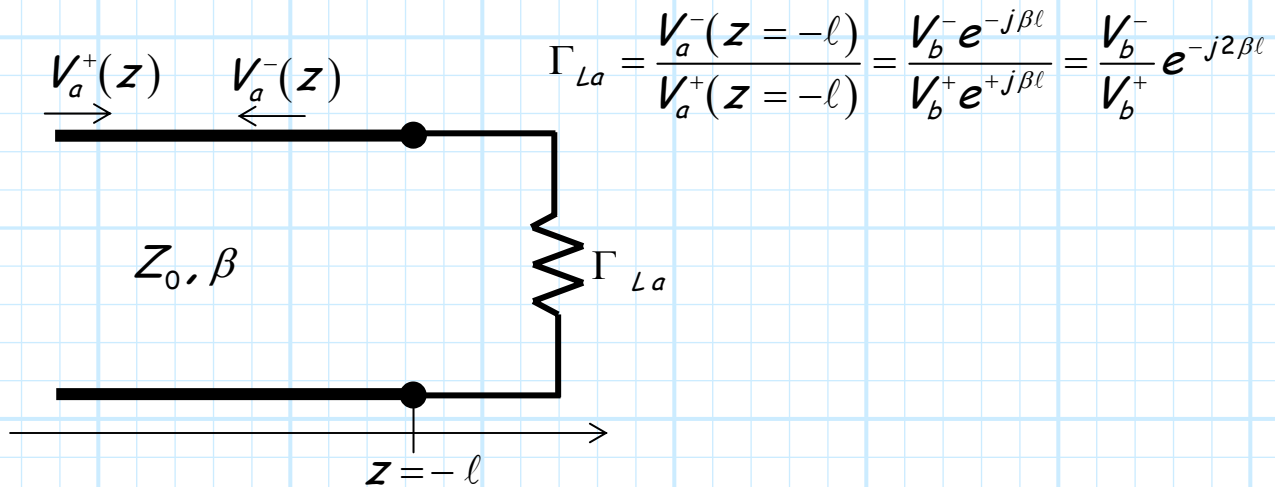For the second case, the load Γ_{La} is located at position $z = 0$, so that:



Note this result can be more compactly stated as a boundary condition requirement:

$$\Gamma_{La} = \Gamma(z = -\ell) = \frac{V_b^-}{V_b^+} e^{-j2\beta\ell}$$

From the equation above we find:

$$\frac{V_b^-}{V_b^+} = \Gamma_{La} e^{+j2\beta\ell} = -\frac{3}{7} e^{+j\pi} = +\frac{3}{7}$$



That's precisely the same result as we determined earlier using our boundary conditions! Our answers are good!