2.6 - Generator and Load Mismatches

Reading Assignment: pp. 76-78

Finally, let's complete our transmission line circuit, by placing at the beginning of the line a source—a device that does not absorb electromagnetic energy, but instead delivers energy to the circuit.

HO: CONNECTING SOURCE AND LOAD

There are a few special cases of source and load impedance that every electrical engineer "knows" to be true—or **do** they?

HO: SPECIAL CASES OF SOURCE AND LOAD

Q: So, can we now **explicitly** determine the **plus**-wave $V^+(z)$ generated on a transmission line?

A: Absolutely! We simply need to evaluate a second boundary condition.

HO: A TRANSMISSION LINE CONNECTING SOURCE AND LOAD

EXAMPLE: BOUNDARY CONDITIONS AND SOURCES

Q: So, how can we determine the **power** delivered by a

source?

A: HO: DELIVERED POWER

Q: So how do we insure that the delivered power is as large as possible?

A: HO: SPECIAL CASES OF SOURCE IMPEDANCE

Make sure you understand how conservation of energy is applied, with respect to delivered, incident, reflected, and absorbed power!

EXAMPLE: CONSERVATION OF ENERGY AND YOU

Connecting a Source and Load

Say we wish to connect the **output** of one microwave network/component to the **input** of another microwave network/component.



The terms "input" and "output" tells us that we wish for signal energy to flow **from** the output network **to** the input network.

Source Delivers; Load Absorbs

We can say that the **output delivers** signal power to the input, or equivalently, that the **input absorbs** power from the output.

In this case, the first network is the **source**, and the second network is the **load**—the **source delivers** power to the load, or equivalently, the **load absorbs** power from the source.



Each of these two networks may be quite complex, but we can always simply this problem by using **equivalent circuits**.

Input Impedance: The Equivalent Load

For example, if we assume time-harmonic signals (i.e., eigen functions!), the load can be modeled as a simple lumped **impedance**, with a **complex** value equal to the **input impedance** of the network.



The Equivalent Source

The source network can likewise be modeled using either a Thevenin's or Norton's equivalent.



Thevenin's and Norton's Equivalent Source

From these two values (V_{out}^{oc} and I_{out}^{sc}) we can determine the **Thevenin's equivalent source**:





Power Absorbed by the Load...

Please note that we have assumed a time harmonic source, such that all the values in the circuit above (V_g , Z_g , I, V, Z_L) are complex (i.e., they have a magnitude and phase).

The **time-averaged power** absorbed (a **real** value!) by the **complex** load impedance is (remember??):

$$P_{abs} = \frac{1}{2} \operatorname{Re} \{ V I^* \}$$

Where * denotes the complex conjugate operator.

Analyzing the equivalent circuit, we find that the power absorbed by the load is:

$$P_{abs} = \frac{1}{2} \operatorname{Re} \left\{ V I^* \right\} = \frac{\left| V_g \right|^2}{2} \frac{R_L}{\left| Z_g + Z_L \right|^2}$$

where R_L is the real (i.e., resistive) part of the load impedance: $Re\{Z_L\} = Re\{R_L + jX_L\} = R_L$

... Equals Power Delivered by the Source







<u>Special Cases of Source</u> <u>and Load Impedance</u>

Consider again the power **absorbed** by the load (delivered by the source):





It is evident that this power transfer is dependent on **each** and **every** element of the equivalent circuit—the **source parameters** V_g and Z_g , as well as the **load impedance** Z_f .

Q: I assume that we want to **maximize** this power transfer. How can we maximize P_{abs} ??

A: The answer to that question is among the best known in electrical engineering. Unfortunately, it is also frequently misunderstood and misapplied—so pay attention!

Match the Load to the Source

First, let's ask this question:

```
Q1: What load impedance Z_{L} will maximize the power delivered by the source (i.e., maximize P_{del})?
```



The Available Power of the Source

We can likewise determine what the value of this maximum power is. For $Z_L = Z_q^*$, we find:

$$P_{del}|_{Z_{L}=Z_{g}^{*}} = \frac{|V_{g}|^{2}}{2} \frac{R_{g}}{|Z_{g}+Z_{g}^{*}|^{2}} = \frac{|V_{g}|^{2}}{2} \frac{R_{g}}{|2R_{g}|^{2}} = \frac{|V_{g}|^{2}}{8} \frac{R_{g}}{|R_{g}|^{2}} = \frac{|V_{g}|^{2}}{8} \frac{R_{g}}{|R_$$

This maximum delivered power is very important and is dubbed the available power P_{avl} of the source:



Note the available power is dependent just on source parameters (i.e., V_g and R_g), and so P_{avl} is a parameter of the source only.

This available power is the **most** that can be **delivered** by the source(i.e., $P_{del} \le P_{avl}$), and this available source power can **only** be delivered if a load $Z_L = Z_g^*$ is connected:

$$P_{del} = P_{avl} = \frac{|V_g|^2}{8R_g} = \text{iff} \quad Z_L = Z_g^*$$

<u>A Completely Different Question!</u>

Now, let's ask completely different question:





Don't Make This Mistake!

Although it is very common for electrical engineers to incorrectly assume the answer to question Q2 is the answer to Q1 (i.e., $Z_g = Z_L^*$), and this is far from the correct answer!

Using the correct solution $Z_q = -jX_L$, we find:

$$P_{abs}|_{Z_g=-jX_L} = \frac{|V_g|^2}{2} \frac{R_L}{|Z_g+Z_L|^2} = \frac{|V_g|^2}{2R_L}$$

Whereas if we enforce a "conjugate match" $Z_q = Z_L^*$ the load instead absorbs:

$$\frac{P_{abs}|_{Z_{g}=Z_{L}^{*}}}{2} = \frac{|V_{g}|^{2}}{2} \frac{R_{L}}{|Z_{L}^{*}+Z_{L}|^{2}} = \frac{1}{4} \left(\frac{|V_{g}|^{2}}{2R_{L}}\right)$$



Dazed and Confused

Q: But if Z_L is not equal to Z_q^* ($Z_L \neq Z_q^*$) isn't the absorbed power less than the available power ??

A: You bet!

If $Z_q = -jX_L$, the absorbed power is **far less** than the **available power**.

Q: I'm so confused!

I thought you said that setting $Z_q = -jX_L$ maximized the absorbed power??

A: See the next page!

ZL cannot alter available power—

but Zg sure the heck can!

A: Here's the deal; altering the value of **load** impedance Z_{L} changes the delivered power P_{del} but does not alter the available power P_{avl} of the source.

The best we can do is set Z_{L} such that all available power is delivered to the load (i.e., set $Z_{L} = Z_{g}^{*}$).

Contrast this with altering the value of source impedance Z_g . Changing Z_g will alter the available power P_{avl} of the source!

Recall:

$$P_{avl} = \frac{\left|V_{g}\right|^{2}}{8R_{g}}$$

The ideal source impedance $(Z_g = -jX_L)$ is purely reactive, so $R_g = 0$ —the available power is therefore **infinite**!

Of course, achieving infinite available power is **not practical**—available power P_{avl} of any **realizable** source is finite.

Don't ever do this!

Still, engineers attempting to maximize the power absorbed by a load should:

- 1. Attempt to select/design/alter the source such that its available power P_{avl} is maximized.
- 2. Attach a load that is conjugate matched $(Z_{L} = Z_{g}^{*})$ to this source, such that all available power is delivered to the load.

A problem that often arises is a source with a large available power has a very low source impedance, such that it is difficult/impractical to provide a load where $Z_L = Z_g^*$.

Engineers sometimes alter/design/select **another source** that it **easier** to "match", but usually this results in a dramatic **decrease in available power**!

See what I mean?

For **example**, consider two cases:

Source	Available Power	Delivered Power
1	500 mW	200mW
2	100 mW	100 mW

For which source is "power transfer maximized"?

For source 2, **100%** of the **available power** is delivered to the load—clearly the **load is matched** to the source impedance.

For source 1, only 40% of the available power is delivered to the load—the load is most definitely not matched to source impedance.

Yet, the mismatched load absorbs twice the power of the mismatched case.

It does so because the available power of source 1 is **five times** larger than that of source 2.

> It's better to have most of alot than all of very little!!

Be careful!

Hence, we need to be **careful** when considering a conjugate match (e.g., what does "maximum power transfer" **really** mean?).

Selecting/altering the load to match a source is a good idea, but selecting/altering the source to match a load is typically not.

This question has—and continues to—spark many **arguments** among electrical engineers!!



<u>A Transmission Line</u>

Connecting Source and Load

We can think of a transmission line as a conduit that allows **power** to flow **from** an **output** of one device/network **to** an **input** of another.

To simplify our analysis, we modeled the **input** of the device **receiving** the power with it input impedance (e.g., Z_L).



The sources are equivalent circuits

We can similarly model the device **delivering** the power with its Thevenin's or

Norton's equivalent circuit.



Typically, the power source is modeled with its Thevenin's equivalent.

However, we will find that the Norton's equivalent circuit is useful if we express the remainder of the circuit in terms of its admittance values (e.g., Y_0 , Y_L , Y(z)).

We've already satisfied one

boundary condition

Recall that we applied **boundary conditions** at location z = 0 to find that:



<u>We must now satisfy a</u> second boundary condition

To determine its exact value, we must now apply boundary conditions at $z = -\ell$.



We know that at the **beginning** of the transmission line:

$$V(z = -\ell) = V_0^+ \left[e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell} \right] \qquad I(z = -\ell) = \frac{V_0^+}{Z} \left[e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell} \right]$$







The plus wave depends on the source and load

There is one very important point that must be made about the result: $V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1+\Gamma_{in}) + Z_q(1-\Gamma_{in})}$

And that is—the wave $V_0^+(z)$ incident on the load Z_L is actually dependent on the value of load Z_L !!!!!

Remember: $\Gamma_{in} = \Gamma(z = -\ell) = \Gamma_{L} e^{-j\beta - \ell}$

We tend to think of the incident wave $V_0^+(z)$ being "caused" by the source, and it is certainly true that $V_0^+(z)$ depends on the source—after all, $V_0^+(z) = 0$ if $V_q = 0$.

However, we find from the equation above that it **likewise** depends on the value of the **load**!

Thus we **cannot**—in general—consider the incident wave to be the "**cause**" and the reflected wave the "**effect**".

Instead, each wave must obtain the proper **amplitude** (e.g., V_0^+, V_0^-) so that the boundary conditions are satisfied at **both** the beginning and end of the transmission line.

Example: Boundary Conditions and Sources





Since the line current is:

$$I(z) = 0.4 \ e^{-j\beta z} - Be^{+j\beta z} = I_0^+ \ e^{-j\beta z} + I_0^- \ e^{+j\beta z}$$

we conclude from inspection that:

$$I_0^+ = 0.4$$
 and $I_0^- = -B$

and since:

$$V_0^+ = Z_0^- I_0^+$$
 and $V_0^- = -Z_0^- I_0^-$

we conclude:

$$V_0^+ = Z_0 I_0^+ = 50(0.4) = 20.0$$
 and $V_0^- = -Z_0 I_0^- = -50(-B) = 50B$

Therefore, the voltage along this transmission line is:

$$V(z) = V^{+}(z) + V^{-}(z)$$

= $V_{0}^{+} e^{-j\beta z} + V_{0}^{-} e^{+j\beta z}$
= $20 e^{-j\beta z} + 50B e^{+j\beta z}$



 $V(z=0) = 20 e^{-j\beta(0)} + 50B e^{+j\beta(0)}$ = 20 + 50B



Inserting this into the previous equation:

$$(20 + 50B) = 25(e^{j0} - (0.4 - B))$$
$$= 25 - 0.4(25) + 25B$$
$$= 15 + 25B$$

One equation and one unknown! Solving for B:

B = -0.2

22

1/8

Delivered and Absorbed Power

Q: If the purpose of a transmission line is to transfer **energy** from a source to a load, then exactly how at what rate is energy **absorbed** by load Z_L in the circuit shown below



A: Now that we have a complete circuit (with two boundary conditions!), we of course can determine the numeric values of wave amplitudes V_0^+ and V_0^- .

$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0 \left(1 + \Gamma_{in}\right) + Z_g \left(1 - \Gamma_{in}\right)} \quad \text{and} \quad V_0^- = \Gamma_L V_0^+$$

Finally! We can calculate numbers

With knowledge of V_0^+ and V_0^- , we likewise can determine the **total** voltage V(z) (**finally**!) and **total** current I(z) along the transmission line.

Of course, we can evaluate this current and voltage at the load (i.e., at z = 0), and then directly compute the rate at which energy is absorbed by the load.



<u>A truck with 30 cases of bananas...</u>

Alternatively, we could likewise determine the absorbed power via the "wave" viewpoint, where we know that the absorbed power is simply the difference between the plus-wave (incident) and minus-wave (reflected).

$$P_{abs} = \frac{\left|V_{0}^{+}\right|^{2}}{2 Z_{0}} \left(1 - \left|\Gamma_{L}\right|^{2}\right)$$

But remember, this simple equation is useful **only** if we first compute the **plus-wave amplitude**:

$$V_{0}^{+} = V_{g} e^{-j\beta\ell} \frac{Z_{0}}{Z_{0} \left(1 + \Gamma_{in}\right) + Z_{g} \left(1 - \Gamma_{in}\right)}$$



Move to the beginning of the line

Q: What about the source? At what rate does it deliver energy to the circuit?

A: Well, we could of course (since we know V_0^+ and V_0^-) determine the total voltage and current at the source (i.e., at $z = -\ell$), and then directly compute the rate at which energy is delivered by the source.



<u>Conservation of energy</u>—

<u>it just makes thing so easy</u>

However, since the transmission line is **lossless**, conservation of energy allows us to correctly conclude that this power **delivered by the source** is likewise the rate at which energy is **absorbed by the load**:

$$P_{abs} = P_{del}$$

Thus, all of the **three** calculations we just discussed will provide the **same correct value** for delivered/absorbed power!

$$P_{del} = \frac{1}{2} \operatorname{Re} \left\{ \mathcal{V} \left(z = -\ell \right) \mathcal{I}^{*} \left(z = -\ell \right) \right\} = \frac{\left| \mathcal{V}_{0}^{+} \right|^{2}}{2 Z_{0}} \left(1 - \left| \Gamma_{L} \right|^{2} \right) = P_{abs} = \frac{1}{2} \operatorname{Re} \left\{ \mathcal{V} \left(z = 0 \right) \mathcal{I}^{*} \left(z = 0 \right) \right\} = P_{abs}$$

Again, for all three results, we must determine
$$V_0^+$$
 and V_0^- .

$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0 (1 + \Gamma_{in}) + Z_g (1 - \Gamma_{in})} \quad \text{and} \quad V_0^- = \Gamma_L V_0^+$$

<u>A 4th way—a way that is even easier</u>

However, there is one method for determining the delivered/absorbed power that does **not** require the calculation of V_0^+ !

Say we replace the transmission line and load with its equivalent circuit—its **input impedance**:

 Z_{g}

Recall that we do **not** need to know V_0^+ to determine input impedance—line impedance Z(z) is independent of either V_0^+ or V_0^- . The **equivalent circuit** is thus:



 $Z_{in} = Z(z = -\ell)$

 Z_{L}

Dust off you introductory circuits text

Now we can easily find the power **delivered** by the source—it's simply **equal** to the rate at which energy is **absorbed** by the input impedance!

We simply have to apply beginning circuit theory.

Note by voltage division we can determine:

$$V(z = -\ell) = V_g \frac{Z_{in}}{Z_g + Z_{in}}$$

And from Ohm's Law we conclude:

$$I(z = -\ell) = \frac{V_g}{Z_g + Z_{in}}$$

 Z_{in}

A power equation without V_0^+

And thus, the **power** P_{in} absorbed by Z_{in} (and thus the **power** P_{del} delivered by the source) is:



By conservation of energy, we know that this is likewise the rate at which the load Z_L absorbs energy:

$$P_{del} = \frac{1}{2} \frac{\left|V_{g}\right|^{2}}{\left|Z_{g} + Z_{in}\right|^{2}} \operatorname{Re}\left\{Z_{in}\right\} = P_{abs}$$



and Load Impedance





The absorbed power is just

the incident power

Likewise, the absorbed/delivered power is simply that of the incident wave:

$$P_{abs} = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_L|^2) = \frac{|V_0^+|^2}{2Z_0}$$

as the **matched** condition causes the reflected power to be **zero** $(P^- = 0)!$

Now, recognizing that the **input impedance** of the transmission line for this case will likewise be $Z_{in} = Z_0$, we can **alternatively** express the **absorbed power** (without determining V_0^+ !):



The 2nd special case: the conjugate match

$$Z_{in} = Z_g^*$$
For this case, we find the load Z_L takes on whatever value
required to make $Z_{in} = Z_g^*$.

Va

 Z_{g}

The input impedance is a conjugate match to the source impedance.

This is of course is a **very** important case!

First, using the fact that:

$$\sum_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z_g^* - Z_0}{Z_g^* + Z_0}$$

We can show that (trust me!) that the plus-wave amplitude simplifies to:



 $Z_{in} = Z_a^*$

Yawn: the load absorbs the available power

Not a particularly interesting result, but now let's look at the absorbed power.



The absorbed power is of course the available power of the source.

Since the input impedance is a **conjugate match** to the source, the source is delivering energy at the **highest rate** it possibly **can**!

5/22

But, the load still reflects power!

Q: But if the power **delivered** is at a maximum, so too is the power **absorbed** by the load. I.E.:

 $P_{abs} = P_{del} = P_{avl}$

If the power absorbed from the load is at a **maximum**, then the power **reflected** from the load must be at a **minimum**.

The load must be absorbing **all** the incident power; **right**?

A: You might think so—and many engineers in fact do think so.

> But those engineers are incorrect!

To see why, consider the load Z_{L} that **minimizes** the reflected power.

We know this load must have one specific value—the matched load $Z_L = Z_0$.

0

O

 \leftarrow

 $Z_{in} = Z_0$



But, if the load is matched to the transmission line (i.e., $Z_L = Z_0$, then the input impedance will likewise be equal to Z_0 :

 $Z_{in} = Z_0$

 Z_0, β



$$Z_{0} \neq Z_{g}^{*} \parallel \parallel$$

$$V_{g} + Z_{g}$$

$$Z_{g} + Z_{g}$$

$$Z_{in} = Z_{0} \neq Z_{g}^{*}$$

$$Z_{in} = Z_{0} \neq Z_{g}^{*}$$

 $Z_L=Z_0$

Look closer at this result

Recall that we just determined that for $Z_L = Z_0$, the absorbed power is:

 $P_{abs} = \frac{|V_g|^2}{2} \frac{Z_0}{|Z_0 + Z_g|^2}$

It can be shown that this value is less than the available power of the source:

$$\frac{\left|V_{g}\right|^{2}}{2}\frac{Z_{0}}{\left|Z_{0}+Z_{g}\right|^{2}} \leq \frac{\left|V_{g}\right|^{2}}{8R_{g}}=P_{av}$$

Q: Huh!? This makes no sense!

After all, just look at the expression for absorbed power:

$$P_{abs} = \frac{\left|V_{0}^{+}\right|^{2}}{2 Z_{0}} \left(1 - \left|\Gamma_{L}\right|^{2}\right)$$

Clearly, this value is maximized when $\Gamma_L = 0$ (i.e., when $Z_L = Z_0$)!!!

Remember, the load affects V^{*}

A: Let's look closer at this result:

$$P_{abs} = \frac{\left|V_{0}^{+}\right|^{2}}{2 Z_{0}} \left(1 - \left|\Gamma_{L}\right|^{2}\right)$$



Remember, we can rewrite this to show that the **absorbed** power is simply the **difference** between the power of the **incident** and **reflected** waves:



<u>Absorbed power is maximized if</u> <u>the *difference* between incident</u> <u>and reflected is maximized!</u>

Of course, it is true that the load impedance Z_{L} affects the minus-wave amplitude V_{0}^{-} , and thus affects likewise the **reflected** wave power P^{-} .

Remember however, that the value of Z_{L} likewise affects the plus-wave amplitude V_{0}^{+} , and thus affects likewise the incident wave power P^{-} !

* Thus, the value of Z_{L} that minimizes P^{-} will **not** generally maximize P^{+} !

* Likewise the value of Z_{L} that maximizes P^{+} will not generally minimize P^{-} .

* Instead, the value of Z_{L} that maximizes the **absorbed** power P_{abs} is, by definition, the value that **maximizes** the **difference** $P^+ - P^-$.

We find that this ideal impedance Z_L is the value that results in the ideal case of $Z_{in} = Z_g^*!$



This is the answer—regardless of the load!

It says that the incident wave in this case is **independent** of the load attached at the other end (the value Γ_{in} is nowhere to be found)!

Thus, for the one case $Z_g = Z_0$, we in fact can consider $V^+(z)$ as being the source wave.

And then the reflected wave $V^{-}(z)$ is the **causal result** of this stimulus.

Specifically, for this case we can write **directly** the plus-wave—without knowing **anything** about the load Z_i :

$$V^{+}(z) = V_{0}^{+}e^{-j\beta z} = \left(\frac{1}{2}V_{g}e^{-j\beta \ell}\right)e^{-j\beta z} = \frac{V_{g}}{2}e^{-j\beta(z+\ell)}$$

This blue box equation will come in guite handy!

Therefore, the value at the load (i.e., z = 0) is:

$$V^{+}(z=0) = \frac{V_{g}}{2} e^{-j\beta}$$

And the value of the **plus**-wave at the source (i.e., $z = -\ell$) is:

$$V^+(z=-\ell)=\frac{V_g}{2}$$

This last result is **very** important.

Remember this result, it will come in quite handy later in the course!



Now consider another **really** important result.

Recall the power associated with the plus-wave is:

$$P^{+} = \frac{\left|V_{0}^{+}\right|^{2}}{2 Z_{0}}$$

Inserting the simplified expression for V_0^+ (i.e., when $Z_g = Z_0$):

$$P^{+} = \frac{|V_{0}^{+}|^{2}}{2Z_{0}} = \frac{|V_{g}e^{-j\beta\ell}|^{2}}{8Z_{0}} = \frac{|V_{g}|^{2}}{8Z_{0}} \quad \leftarrow \text{Wow!}$$

Q: I don't see why this is "wow". Am I missing something?

A: Apparently you are. Look closer at the above result.

Do I have to explain everything?

Remember, this result is for the **special case** where the source impedance is a **real** value, numerically equal to Z_0 :

$$Z_g = Z_0 + j0$$

Therefore:

$$R_{g} = \operatorname{Re}\left\{Z_{g}\right\} = Z_{0}$$

The source resistance is numerically equal to transmission line characteristic impedance Z_0 .

Thus, the **power** of the plus-wave can be alternatively written as:

$$P^{+} = \frac{\left|V_{g}\right|^{2}}{8 Z_{0}} = \frac{\left|V_{g}\right|^{2}}{8 R_{g}} \quad \leftarrow \text{Wow!}$$

Q: This result looks vaguely familiar; haven't we seen this before?

A: Sigh. This result is the available power of the source!!!!!!!



available power (wow)!

 $P^{+} = \frac{\left|V_{g}\right|^{2}}{8 Z_{0}} = \frac{\left|V_{g}\right|^{2}}{8 R_{a}} = P_{avl} \qquad \leftarrow \text{Wow!}$

Therefore:

For the special case $Z_g = Z_0 + j0$, the power P^+ associated with the pluswave (i.e., the **incident** wave) is **equal** to the **available** power P_{avl} of the **source**.

Q: Wow! Does this mean that the power **absorbed** by the load is **equal** to the **available** power P_{avl} of the source?

A: Absolutely not!

But some of this incident power is reflected (Doh!)

Remember, only if $Z_{in} = Z_g^*$ does the power absorbed by the load equal the

available power.



$$P_{abs} = P_{avl}$$

 z_{L}

* Making $Z_g = Z_0 + j0$ causes the power of the **incident** wave to be equal to the **available** power.

[•] But, the value Z_{L} of the **load impedance** determines how much of that incident power is absorbed—and how much gets **reflected**.

The *really* special case!

Q: Hey, that's right!

If the load is matched (i.e., $Z_L = Z_0 + j0$), then wouldn't **none** of the incident power be **reflected** (i.e., $P^- = 0$).

And so wouldn't **all** the incident (i.e., available!) power be **absorbed** by the load?

 $P_{abs} = P_{avl}$

 Z_0



A: That's exactly correct!

Q: But you said earlier that **minimizing** the **reflected** power would **not** result in **maximizing** the **absorbed** power. Aren't you **contradicting** yourself?

A: Not at all.

A conjugate match!

Generally speaking, minimizing the **reflected** power (i.e., $Z_L = Z_0$) will **not** result in maximizing the **absorbed** power.

However, we are considering the special case where also $Z_a = Z_0!$

 $\boldsymbol{z} = -\ell$

 Z_{0}



Thus, maximum power transfer will occur if there is a conjugate match $Z_{in} = Z_a^*$.

Note for this special case $Z_g^* = Z_0$, meaning that input impedance Z_{in} must be equal to Z_0 for maximum power delivery.

Of course, the input impedance Z_{in} will be equal to Z_0 when the load impedance is matched (i.e., $Z_L = Z_0$)!



<u>It's just *so* simple; you hardly</u> deserve credit for this class

The incident (plus) wave is independent of the load impedance:

$$V^{+}(z) = \frac{V_{g}}{2} e^{-j\beta(z+\ell)} \qquad V^{+}(z=0) = \frac{V_{g}}{2} e^{-j\beta\ell} \qquad V^{+}(z=-\ell) = \frac{V_{g}}{2}$$

And the **power** associated with this **incident** wave is **equal** to the **available power** of the source:

$$P^{+} = \frac{\left|V_{g}\right|^{2}}{8 Z_{0}} = P_{av}$$

The **reflected** (minus) wave is **zero**:

$$V^{-}(z) = 0$$



Load AND source is matched—

it's a very good thing

* This again allows us to verify that all available power is absorbed by the load:

$$P_{abs} = P^+ - P^- = P_{avl} - 0 = P_{avl}$$

* Finally, the **total** current and voltage simplifies **nicely**:

Example: Conservation of Energy and You

Consider this circuit, where the transmission line is lossless and has length $\ell = \lambda/4$:



Determine the **magnitude** of source voltage V_g (i.e., determine $|V_g|$).

Hint: This is **not** a boundary condition problem. Do **not** attempt to find V(z) and/or I(z)!

Solution

O

From **conservation of energy**, we find the load absorbes energy at a rate of:

 $P_{abs} = P_{inc} - P_{ref}$ = 0.49 - 0.09= 0.4 W

Since the transmission line is **lossless**, this absorbed power **must** likewise be the power **delivered** by the source to the input of the transmission line (i.e., the power absorbed by input impedance Z_{in}).

$$P_{in} = P_{abs} = 0.40 \ J/s$$

 $Z_{0} = 50 \Omega$

*_____ℓ = ۸/*4 ^{__}

Note the transmission line length has the **special case** $\ell = \lambda/4$, therefore the input impedance is easily computed:

 \rightarrow

$$Z_{in} = \frac{Z_0^2}{Z_i} = \frac{50^2}{125} = 20\Omega = Z_g$$

A conjugate match
$$(Z_{in} = Z_a^*)!$$

 \leftarrow

 $Z_{L} = 125 \Omega$



