

4.2 - Impedance and Admittance Matrices

Reading Assignment: pp. 170-174

A passive load is an example of a **1-port** device—only one transmission line is connected to it.

However, we often use devices with 2, 3, 4, or even more ports—**multiple** transmission lines can be attached to them!

Q: *But, we use impedance Z , admittance Y , or reflection coefficient Γ to characterize a load. How do we characterize a multi-port device?*

A: The analogy to Z , Y , and Γ for a multi-port device is the **impedance matrix**, the **admittance matrix** and the **scattering matrix**.

HO: THE IMPEDANCE MATRIX

HO: THE ADMITTANCE MATRIX

We can determine many things about a device by simply looking at the **elements** of the impedance and scattering matrix.

HO: RECIPROCAL AND LOSSLESS DEVICES

Q: But how can we determine/measure the impedance and admittance matrix?

A: EXAMPLE: EVALUATING THE ADMITTANCE MATRIX

Q: OK, but what are the impedance and admittance matrix good for? How can we use it to solve circuit problems?


A: EXAMPLE: USING THE IMPEDANCE MATRIX

The Impedance Matrix

Consider the **4-port microwave device** shown below:

Note in this example, there are four **identical** transmission lines connected to the same "box". Inside this box there may be a very **simple** linear device/circuit, or it might contain a very large and **complex** linear microwave system.

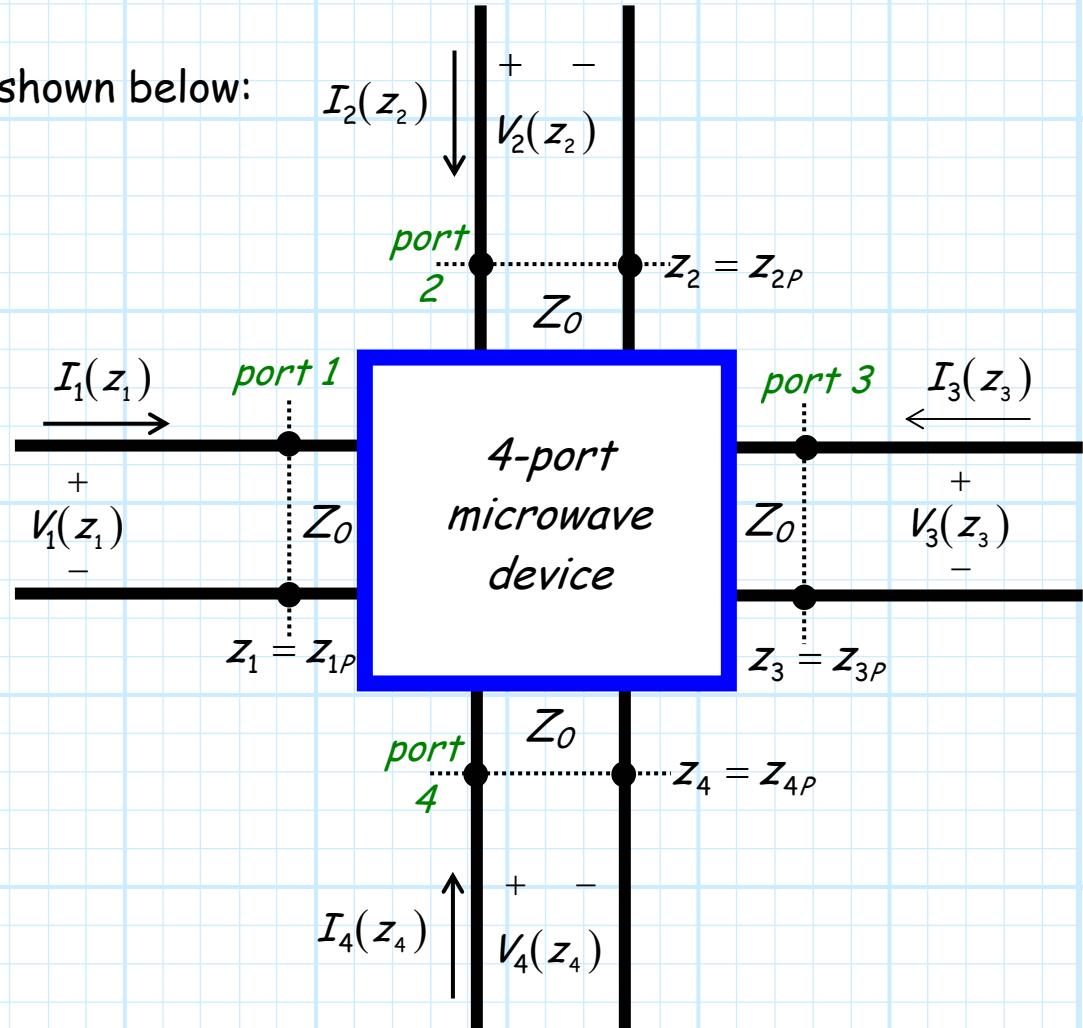→ Either way, the "box" can be fully characterized by its **impedance matrix**!



First, note that each transmission line has a specific **location** that effectively defines the **input** to the device (i.e., z_{1P} , z_{2P} , z_{3P} , z_{4P}). These often arbitrary positions are known as the **port locations**, or **port planes** of the device.

Thus, the **voltage** and **current** at port n is:

$$V_n(z_n = z_{nP})$$

$$I_n(z_n = z_{nP})$$

We can **simplify** this cumbersome notation by simply **defining** port n current and voltage as I_n and V_n :

$$V_n = V_n(z_n = z_{nP})$$

$$I_n = I_n(z_n = z_{nP})$$

For **example**, the current at port 3 would be $I_3 = I_3(z_3 = z_{3P})$.

Now, say there exists a non-zero current at **port 1** (i.e., $I_1 \neq 0$), while the current at all other ports are known to be **zero** (i.e., $I_2 = I_3 = I_4 = 0$).

Say we measure/determine the **current** at port 1 (i.e., determine I_1), and we then measure/determine the **voltage** at the port 2 plane (i.e., determine V_2).

The complex ratio between V_2 and I_1 is known as the **trans-impedance parameter** Z_{21} :

$$Z_{21} = \frac{V_2}{I_1}$$

Likewise, the trans-impedance parameters Z_{31} and Z_{41} are:

$$Z_{31} = \frac{V_3}{I_1} \quad \text{and} \quad Z_{41} = \frac{V_4}{I_1}$$

We of course could **also** define, say, trans-impedance parameter Z_{34} as the ratio between the complex values I_4 (the current into port 4) and V_3 (the voltage at port 3), given that the current at all other ports (1, 2, and 3) are zero.


Thus, more generally, the ratio of the current into port n and the voltage at port m is:

$$Z_{mn} = \frac{V_m}{I_n} \quad (\text{given that } I_k = 0 \text{ for all } k \neq n)$$



Q: But how do we ensure that all but one port current is zero?


A: Place an open circuit at those ports!

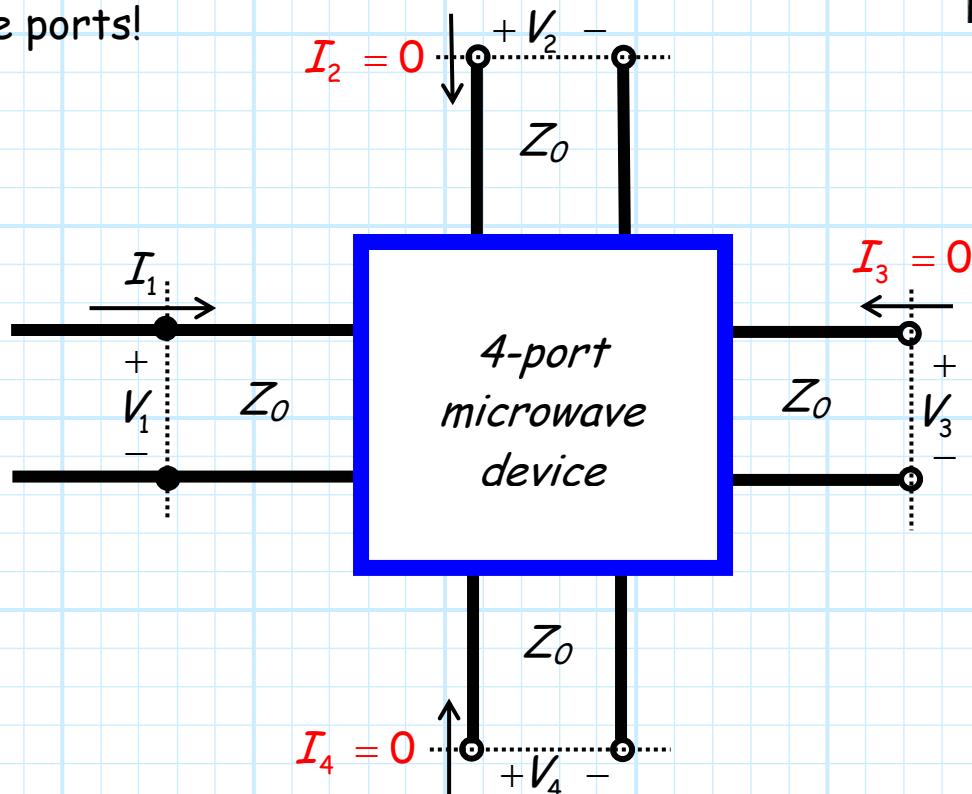

Placing an **open** at a port (and it must be **at the port!**) **enforces** the condition that $I = 0$.

Now, we can thus **equivalently** state the definition of trans-impedance as:
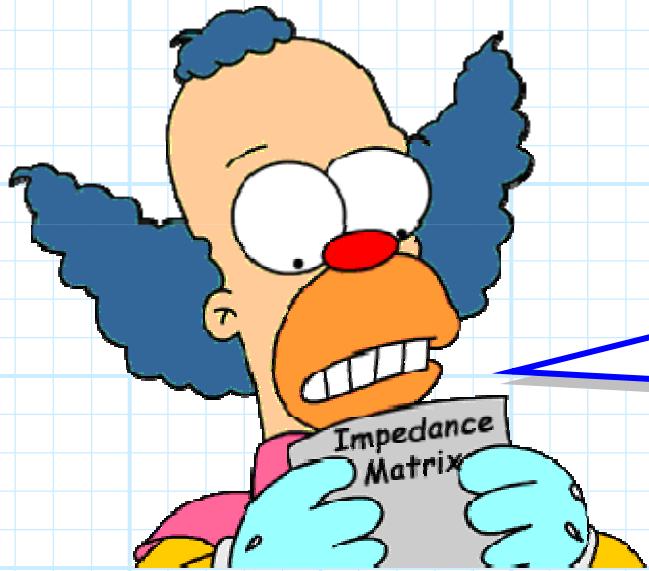
$$Z_{mn} = \frac{V_m}{I_n} \quad (\text{given that all ports } k \neq n \text{ are open})$$



Q: As impossible as it sounds, this handout is even more **boring** and **pointless** than any of your previous efforts. Why are we studying this? After all, what is the likelihood that a device will have an **open** circuit on **all** but one of its ports?!

A: OK, say that **none** of our ports are **open-circuited**, such that we have currents simultaneously on **each** of the four ports of our device.

Since the device is **linear**, the voltage at any **one** port due to **all** the port currents is simply the coherent sum of the voltage at that port due to **each** of the currents!

For example, the voltage at port 3 can be determined by:

$$V_3 = Z_{34} I_4 + Z_{33} I_3 + Z_{32} I_2 + Z_{31} I_1$$

More generally, the voltage at port m of an N -port device is:

$$V_m = \sum_{n=1}^N Z_{mn} I_n$$

This expression can be written in **matrix** form as:

$$\mathbf{V} = \mathbf{Z} \mathbf{I}$$

Where **I** is the **vector**:

$$\mathbf{I} = [I_1, I_2, I_3, \dots, I_N]^T$$

and **V** is the **vector**:

$$\mathbf{V} = [V_1, V_2, V_3, \dots, V_N]^T$$

And the matrix \mathcal{Z} is called the **impedance matrix**:

$$\mathcal{Z} = \begin{bmatrix} Z_{11} & \dots & Z_{1n} \\ \vdots & \ddots & \vdots \\ Z_{m1} & \dots & Z_{mn} \end{bmatrix}$$

The impedance matrix is a N by N matrix that **completely characterizes** a linear, N -port device. Effectively, the impedance matrix describes a multi-port device the way that Z_L describes a single-port device (e.g., a load)!




But **beware!** The values of the impedance matrix for a particular device or network, just like Z_L , are **frequency dependent**! Thus, it may be more instructive to **explicitly write**:

$$\mathcal{Z}(\omega) = \begin{bmatrix} Z_{11}(\omega) & \dots & Z_{1n}(\omega) \\ \vdots & \ddots & \vdots \\ Z_{m1}(\omega) & \dots & Z_{mn}(\omega) \end{bmatrix}$$

The Admittance Matrix

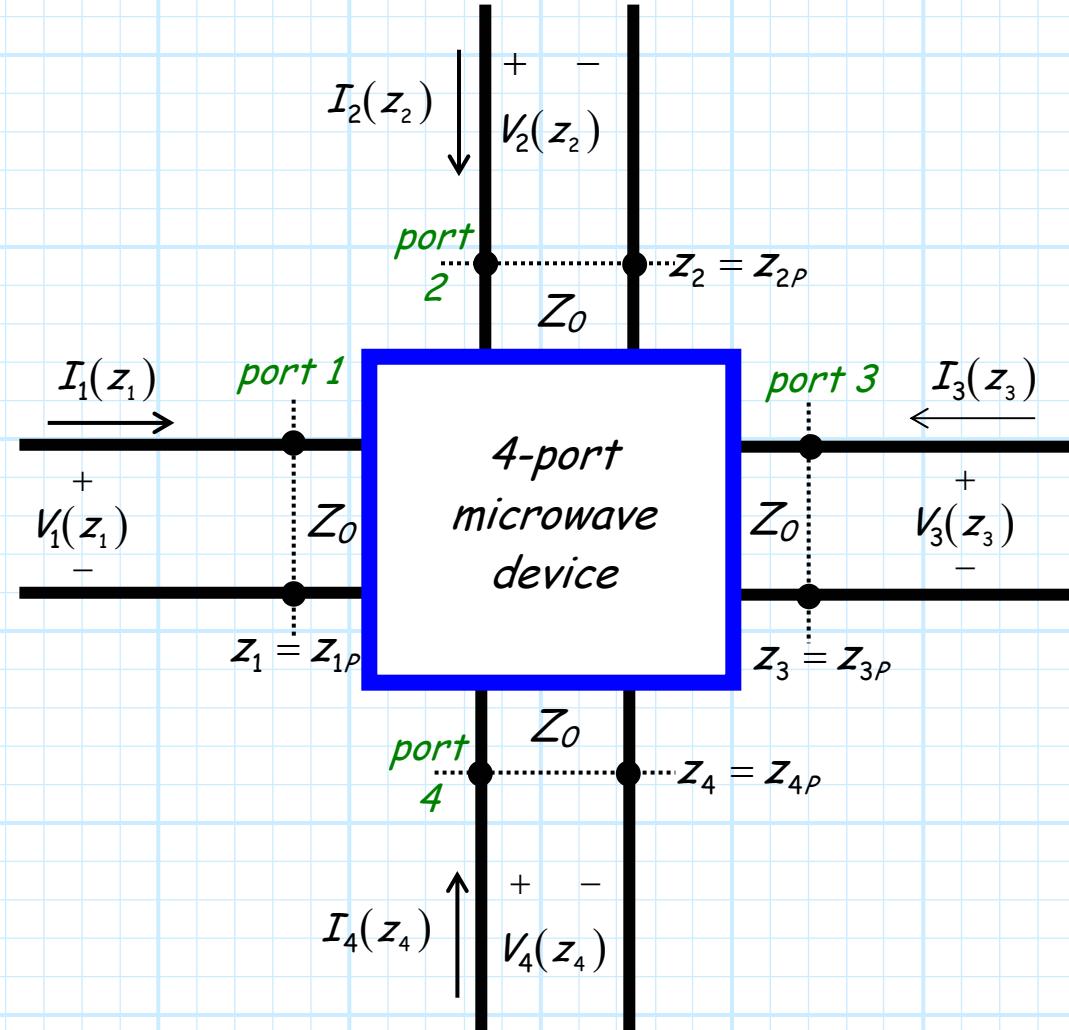Consider again the 4-port microwave device shown below:




In addition to the Impedance Matrix, we can fully characterize this linear device using the **Admittance Matrix**.

The elements of the Admittance Matrix are the **trans-admittance** parameters Y_{mn} , defined as:

$$Y_{mn} = \frac{I_m}{V_n} \quad (\text{given that } V_k = 0 \text{ for all } k \neq n)$$

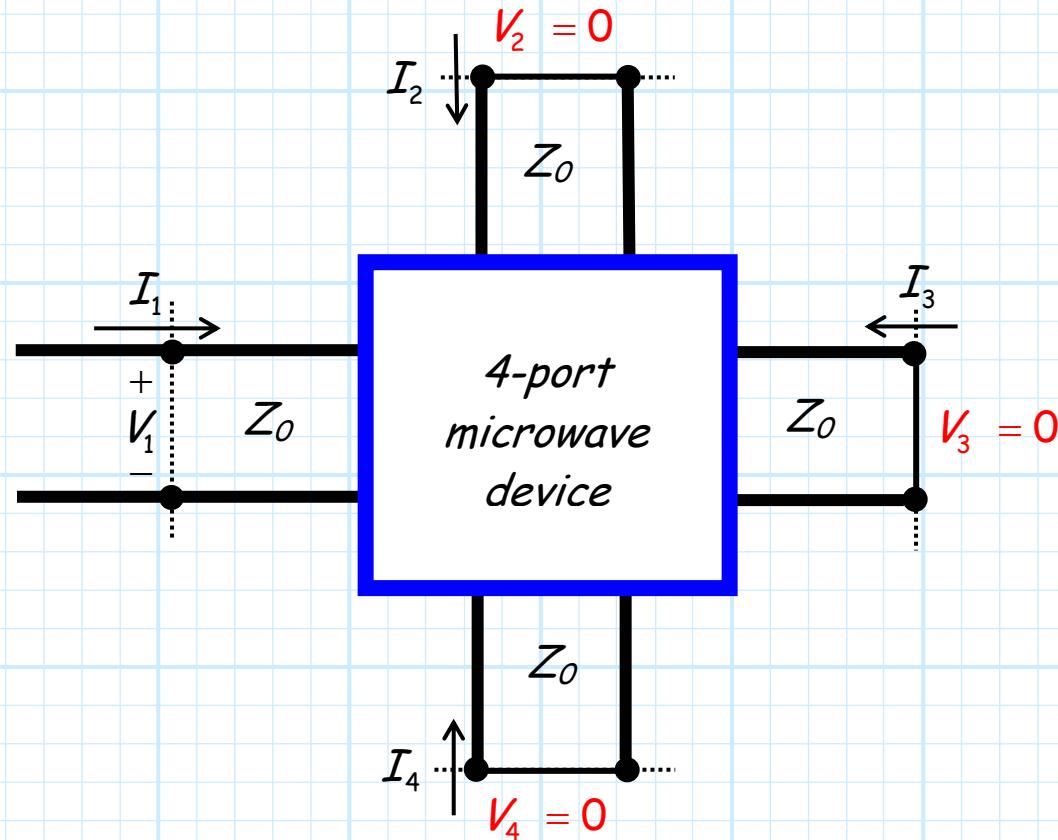Note here that the **voltage** at all but one port **must** be equal to **zero**. We can ensure that by simply placing a **short circuit** at these zero voltage ports!





Note that $Y_{mn} \neq 1/Z_{mn}$!

Now, we can thus **equivalently** state the definition of trans-admittance as:

$$Y_{mn} = \frac{V_m}{I_n} \quad (\text{given that all ports } k \neq n \text{ are short-circuited})$$

Just as with the trans-impedance values, we can use the trans-admittance values to evaluate general circuit problems, where **none** of the ports have zero voltage.

Since the device is **linear**, the current at any **one** port due to **all** the port currents is simply the coherent **sum** of the currents at that port due to **each** of the port voltages!

For example, the current at port 3 can be determined by:

$$I_3 = Y_{34} V_4 + Y_{33} V_3 + Y_{32} V_2 + Y_{31} V_1$$

More generally, the current at port m of an N -port device is:

$$I_m = \sum_{n=1}^N Y_{mn} V_n$$

This expression can be written in **matrix form** as:

$$\mathbf{I} = \mathbf{Y} \mathbf{V}$$

Where **I** is the **vector**:

$$\mathbf{I} = [I_1, I_2, I_3, \dots, I_N]^T$$

and **V** is the **vector**:

$$\mathbf{V} = [V_1, V_2, V_3, \dots, V_N]^T$$

And the matrix \mathcal{Y} is called the **admittance matrix**:

$$\mathcal{Y} = \begin{bmatrix} Y_{11} & \dots & Y_{1n} \\ \vdots & \ddots & \vdots \\ Y_{m1} & \dots & Y_{mn} \end{bmatrix}$$

The admittance matrix is a N by N matrix that **completely characterizes** a linear, N -port device. Effectively, the admittance matrix describes a multi-port device the way that Y_L describes a single-port device (e.g., a load)!



But **beware!** The values of the admittance matrix for a particular device or network, just like Y_L , are **frequency dependent!** Thus, it may be more instructive to **explicitly write**:

$$\mathcal{Y}(\omega) = \begin{bmatrix} Y_{11}(\omega) & \dots & Y_{1n}(\omega) \\ \vdots & \ddots & \vdots \\ Y_{m1}(\omega) & \dots & Y_{mn}(\omega) \end{bmatrix}$$

Q: You said earlier that $Y_{mn} \neq 1/Z_{mn}$. Is there any relationship between the admittance and impedance matrix of a given device?

A: I don't know! Let's see if we can figure it out.

Recall that we can determine the inverse of a matrix. Denoting the matrix inverse of the admittance matrix as \mathcal{Y}^{-1} , we find:

$$\mathbf{I} = \mathcal{Y} \mathbf{V}$$

$$\mathcal{Y}^{-1} \mathbf{I} = \mathcal{Y}^{-1} (\mathcal{Y} \mathbf{V})$$

$$\mathcal{Y}^{-1} \mathbf{I} = (\mathcal{Y}^{-1} \mathcal{Y}) \mathbf{V}$$

$$\mathcal{Y}^{-1} \mathbf{I} = \mathbf{V}$$

Meaning that:

$$\mathbf{V} = \mathcal{Y}^{-1} \mathbf{I}$$

But, we likewise know that:

$$\mathbf{V} = \mathcal{Z} \mathbf{I}$$

By comparing the two previous expressions, we can conclude:

$$\mathcal{Z} = \mathcal{Y}^{-1} \quad \text{and} \quad \mathcal{Z}^{-1} = \mathcal{Y}$$

Reciprocal and Lossless Networks

We can classify multi-port devices or networks as either **lossless** or **lossy**; **reciprocal** or **non-reciprocal**. Let's look at each classification individually:

Lossless

A **lossless** network or device is simply one that **cannot** absorb power. This does **not** mean that the delivered power at **every port** is zero; rather, it means the total power flowing into the **device** must equal the total power exiting the **device**.

A lossless device exhibits an impedance matrix with an interesting **property**. Perhaps not surprisingly, we find for a lossless device that the **elements** of its impedance matrix will be **purely reactive**:

$$\text{Re}\{Z_{mn}\} = 0 \quad \text{for a lossless device.}$$

If the device is lossy, then the elements of the impedance matrix must have at least one element with a real (i.e., resistive) component.

Moreover, we similarly find that if the elements of an admittance matrix are all purely imaginary (i.e., $\text{Re}\{Y_{mn}\} = 0$), then the device is lossless.

Reciprocal

Generally speaking, most **passive**, **linear** microwave components will turn out to be **reciprocal**—regardless of whether the designer intended it to be or not!

Reciprocity is basically a “natural” effect of using simple linear materials such as **dielectrics** and **conductors**. It results from a characteristic in **electromagnetics** called “reciprocity”—a characteristic that is difficult to prevent!

But reciprocity is a tremendously important characteristic, as it greatly **simplifies** an impedance or admittance matrix!

Specifically, we find that a reciprocal device will result in a **symmetric** impedance and admittance matrix, meaning that:

$$Z_{mn} = Z_{nm} \quad Y_{mn} = Y_{nm} \quad \text{for reciprocal devices}$$

For example, we find for a reciprocal device that $Z_{23} = Z_{32}$, and $Y_{21} = Y_{12}$.

Let's illustrate these concepts with four examples:

$$\mathcal{Z} = \begin{bmatrix} j2 & 0.1 & j3 \\ -j & -1 & 1 \\ 4 & -2 & 0.5 \end{bmatrix}$$

Neither lossless nor reciprocal.

$$\mathcal{Z} = \begin{bmatrix} j2 & j0.1 & j3 \\ -j & -j1 & j1 \\ j4 & -j2 & j0.5 \end{bmatrix}$$

Lossless, but not reciprocal.

$$\mathcal{Z} = \begin{bmatrix} j2 & -j & 4 \\ -j & -1 & -j2 \\ 4 & -j2 & j0.5 \end{bmatrix}$$


Reciprocal, but not lossless.

$$\mathcal{Z} = \begin{bmatrix} j2 & -j & j4 \\ -j & -j & -j2 \\ j4 & -j2 & j0.5 \end{bmatrix}$$

Both reciprocal and lossless.


Example: Evaluating the Admittance Matrix

Consider the following two-port device:

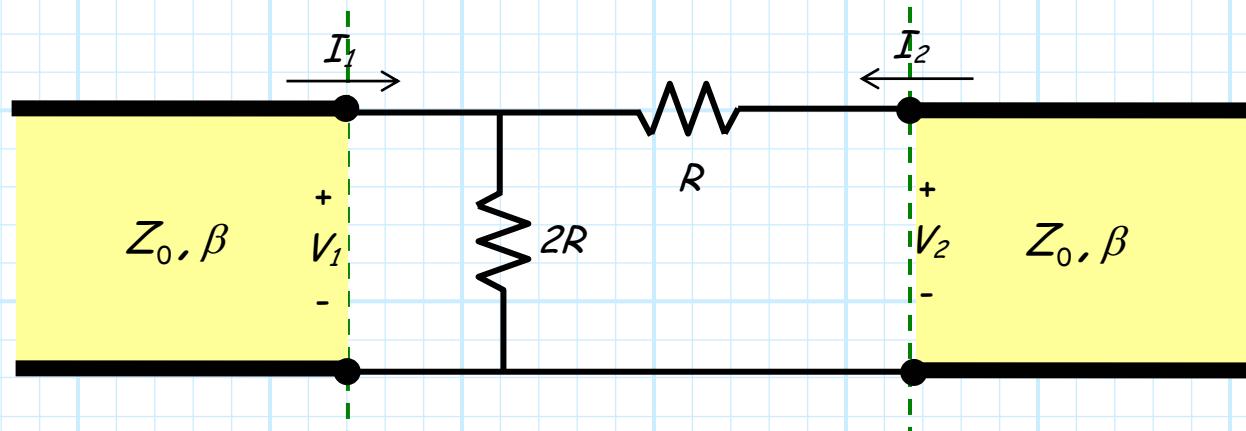

Let's determine the **admittance matrix** of this device!

Step 1: Place a short at port 2.

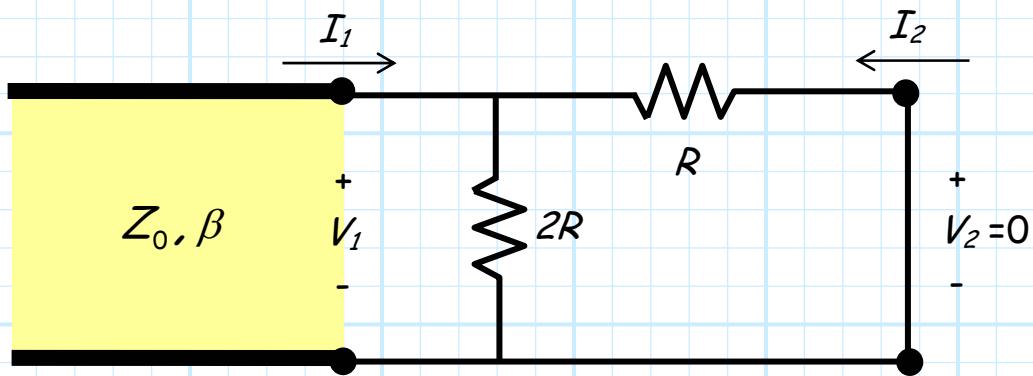

Step 2: Determine currents I_1 and I_2 .

Note that after the short was placed at port 2, both resistors are in parallel, with a potential V_2 across each.

The current I_1 is thus simply the sum of the two currents through each resistor:

$$I_1 = \frac{V_1}{2R} + \frac{V_1}{R} = \frac{3V_1}{2R}$$

The current I_2 is simply the opposite of the current through R :

$$I_2 = -\frac{V_1}{R}$$

Step 3: Determine trans-admittance Y_{11} and Y_{21} .

$$Y_{11} = \frac{I_1}{V_1} = \frac{3}{2R}$$

$$Y_{21} = \frac{I_2}{V_1} = -\frac{1}{R}$$


Note that Y_{21} is real—but negative!



This is still a valid physical result, although you will find that the diagonal terms of an impedance or admittance matrix (e.g., Y_{22} , Z_{11} , Y_{44}) will always have a real component that is positive.

To find the other two trans-admittance parameters, we must move the short and then repeat each of our previous steps!

Step 1: Place a short at port 1.

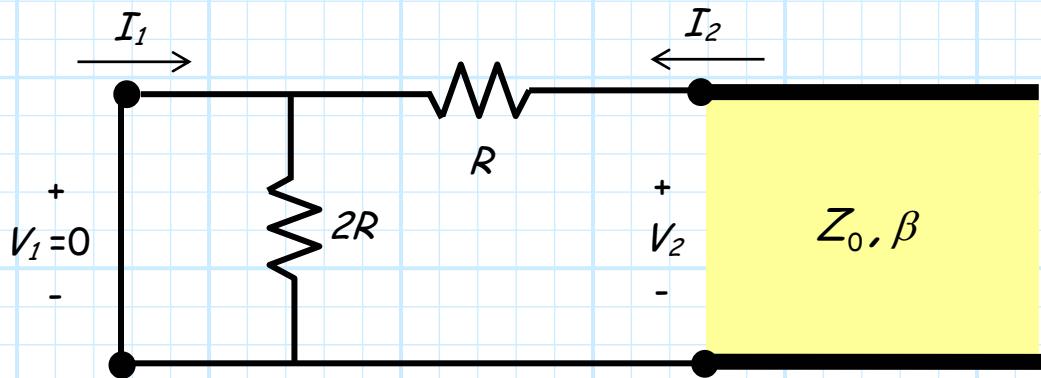

Step 2: Determine currents I_1 and I_2 .

Note that after a short was placed at port 1, resistor $2R$ has zero voltage across it—and thus zero current through it!

Likewise, from KVL we find that the voltage across resistor R is equal to V_2 .

Finally, we see from KCL that $I_1 = I_2$.

The current I_2 thus:

$$I_2 = \frac{V_2}{R}$$

and thus:

$$I_1 = -\frac{V_2}{R}$$

Step 3: Determine trans-admittance Y_{12} and Y_{22} .

$$Y_{12} = \frac{I_1}{V_2} = -\frac{1}{R}$$

$$Y_{22} = \frac{I_2}{V_2} = \frac{1}{R}$$

The **admittance** matrix of this two-port device is therefore:

$$\mathcal{Y} = \frac{1}{R} \begin{bmatrix} 1.5 & -1 \\ -1 & 1 \end{bmatrix}$$

Note this device (as you may have suspected) is **lossy** and **reciprocal**.

Q: What about the **impedance** matrix? How can we determine that?

A: One way is simply determine the **inverse** of the admittance matrix above.

$$\begin{aligned} \mathcal{Z} &= \mathcal{Y}^{-1} \\ &= R \begin{bmatrix} 1.5 & -1 \\ -1 & 1 \end{bmatrix}^{-1} \\ &= R \begin{bmatrix} 2 & 2 \\ 2 & 3 \end{bmatrix} \end{aligned}$$



Q: But I don't know how to invert a matrix! How can I possibly pass one of your long, scary, evil exams?

A: Another way to determine the impedance matrix is simply to apply the **definition** of trans-impedance to directly determine the elements of the impedance matrix—similar to how we just determined the admittance matrix!

Specifically, follow these **steps**:

Step 1: Place an **open** at port 2 (or 1)


Step 2: Determine **voltages** V_1 and V_2 .

Step 3: Determine **trans-impedance** Z_{11} and Z_{21} (or Z_{12} and Z_{22}).

You try this procedure on the circuit of this example, and make sure you get the **same** result for \mathcal{Z} as we determined on the previous page (from matrix inversion)—after all, you want to do **well** on my long, scary, evil exam!

Example: Using the Impedance Matrix

Consider the following circuit:

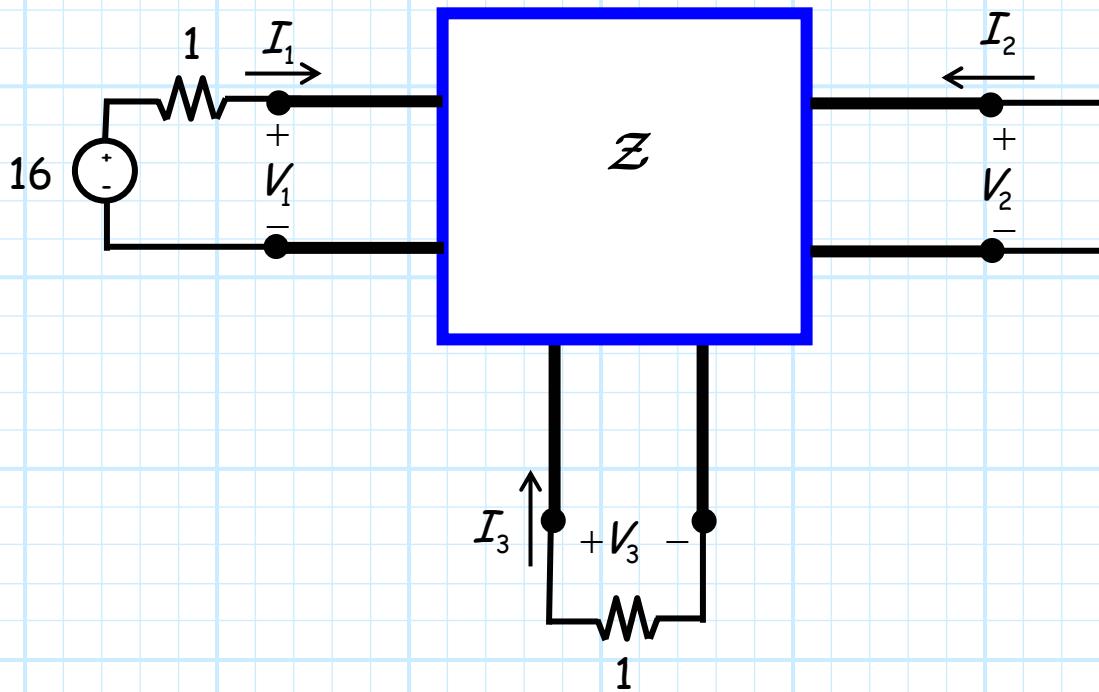

Where the 3-port device is characterized by the **impedance matrix**:

$$\mathcal{Z} = \begin{bmatrix} 2 & 1 & 2 \\ 1 & 1 & 4 \\ 2 & 4 & 1 \end{bmatrix}$$

Let's now determine all port voltages V_1, V_2, V_3 and all currents I_1, I_2, I_3 .



Q: How can we do that—we don't know what the device is made of! What's inside that box?

A: We don't need to know what's inside that box! We know its impedance matrix, and that **completely** characterizes the device (or, at least, characterizes it at **one** frequency).

Thus, we have enough information to solve this problem. From the impedance matrix we know:

$$V_1 = 2I_1 + I_2 + 2I_3$$

$$V_2 = I_1 + I_2 + 4I_3$$

$$V_3 = 2I_1 + 4I_2 + I_3$$

Q: Wait! There are only **3** equations here, yet there are **6** unknowns!?



A: True! The impedance matrix describes the device in the box, but it does **not** describe the devices **attached** to it. We require **more** equations to describe them.

1. The source at port 1 is described by the equation:

$$V_1 = 16.0 - (1) I_1$$

2. The short circuit on port 2 means that:

$$V_2 = 0$$

3. While the load on port 3 leads to:

$$V_3 = -(1) I_3 \quad (\text{note the minus sign!})$$

Now we have 6 equations and 6 unknowns! Combining equations, we find:

$$\begin{aligned} V_1 &= 16 - I_1 = 2I_1 + I_2 + 2I_3 \\ \therefore 16 &= 3I_1 + I_2 + 2I_3 \end{aligned}$$

$$\begin{aligned} V_2 &= 0 = I_1 + I_2 + 4I_3 \\ \therefore 0 &= I_1 + I_2 + 4I_3 \end{aligned}$$

$$\begin{aligned} V_3 &= -I_3 = 2I_1 + 4I_2 + I_3 \\ \therefore 0 &= 2I_1 + 4I_2 + 2I_3 \end{aligned}$$

Solving, we find (I'll let you do the algebraic details!):

$$I_1 = 7.0$$

$$I_2 = -3.0$$

$$I_3 = -1.0$$

$$V_1 = 9.0$$

$$V_2 = 0.0$$

$$V_3 = 1.0$$