

## 5.2 - Single-Stub Tuning

**Reading Assignment:** pp. 228-235

**Q:** *If we cannot use "lumped" elements like inductors or capacitors to build lossless matching networks, what can we use?*

**A:** Recall that a section of **lossless transmission line** is purely reactive, thus we can build lossless matching networks using specific lengths of transmission lines.

We call these lengths of transmission line "**distributed**" elements.

The distributed element analogue of the lumped element L-network is the **single-stub tuner**.


Just like the L-network, there are **two** versions of this design:

**HO: THE SHUNT-STUB TUNER**


**HO: THE SERIES-STUB TUNER**
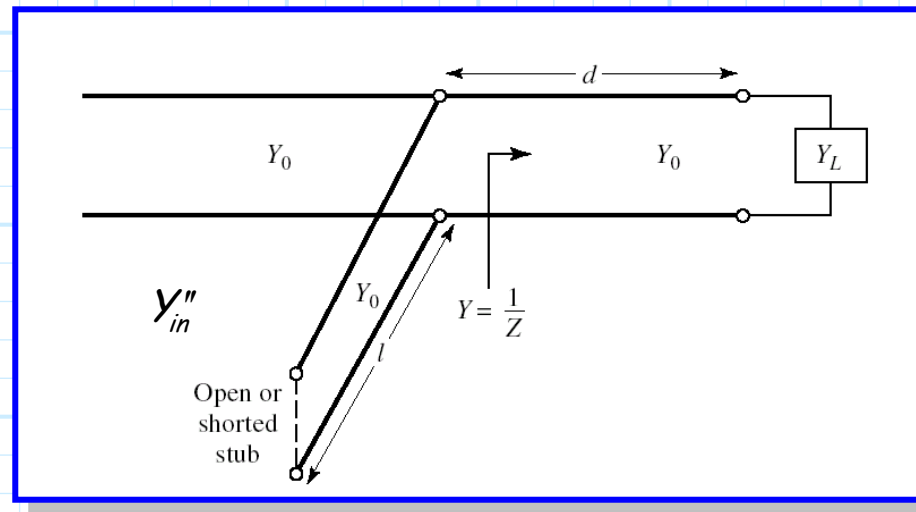
# Shunt Stub Tuning

Consider the follow transmission line structure, with a shunt stub:



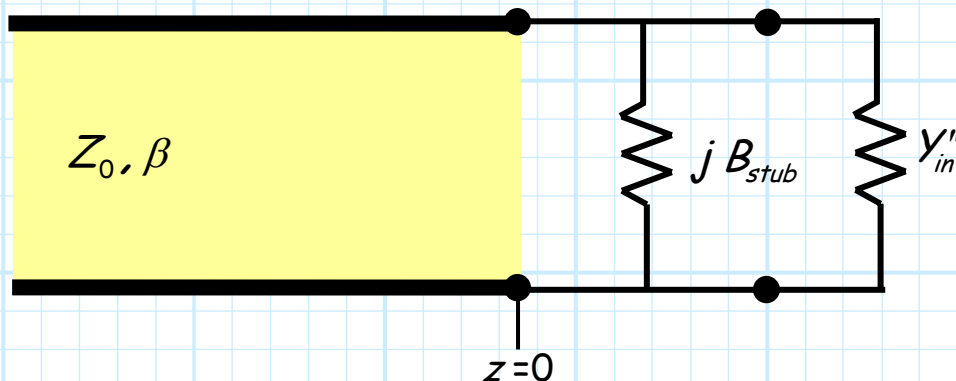The two **design parameters** of this matching network are lengths  $l$  and  $d$ . An equivalent circuit is:



where:

$$y''_{in} = Y_0 \left( \frac{Y_L + j Y_0 \tan \beta d}{Y_0 + j Y_L \tan \beta d} \right)$$

The reactance  $jB_{stub}$  of transmission line **stub** of length  $l$  is either:

$$jB_{stub} = \begin{cases} jY_0 \tan \beta l & \text{for an open-circuit stub} \\ -jY_0 \cot \beta l & \text{for an short-circuit stub} \end{cases}$$

Therefore, for a **matched circuit**, we require:

$$jB_{stub} + Y_{in}'' = Y_0$$

Note this complex equation is actually **two real equations!**

i.e.,

$$\text{Re}\{Y_{in}''\} = Y_0$$

and

$$\text{Im}\{jB_{stub} + Y_{in}''\} = 0 \quad \Rightarrow \quad B_{stub} = -B_{in}''$$

where

$$B_{in}'' \doteq \text{Im}\{Y_{in}''\}$$

Since  $Y_{in}''$  is dependent on  $d$  only, our **design procedure** is:

- 1) Set  $d$  such that  $\text{Re}\{Y_{in}''\} = Y_0$ .
- 2) Then set  $\ell$  such that  $B_{stub} = -B_{in}''$ .

We have **two choices** for determining the lengths  $d$  and  $\ell$ . We can use the design equations (5.9, 5.10, 5.11) on p. 232,


**OR**

we can use the **Smith Chart** to determine the lengths!

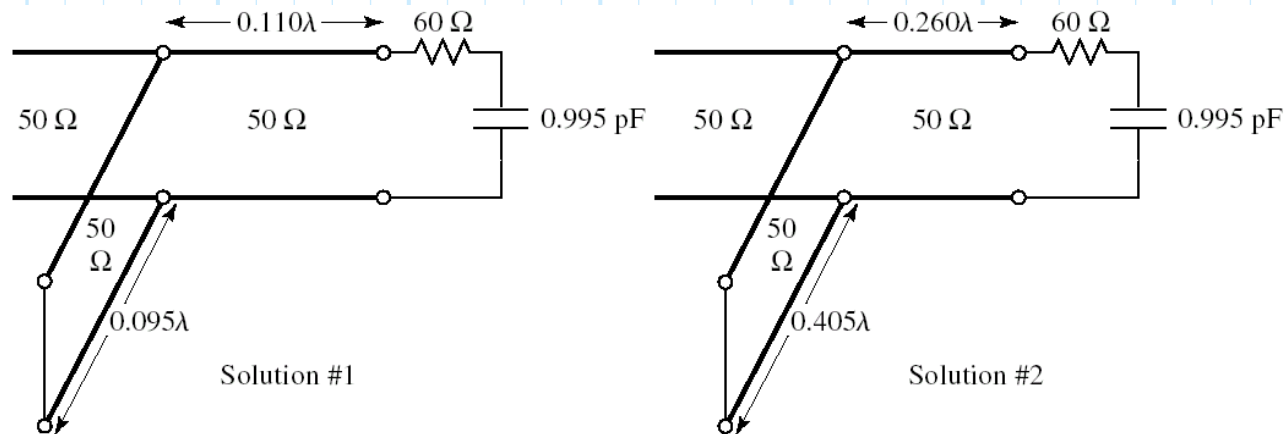
- 1) Rotate **clockwise** around the Smith Chart from  $y_L$  until you intersect the  $g = 1$  circle. The "length" of this rotation determines the value  $d$ . Recall there are **two** possible solutions!
- 2) Rotate **clockwise** from the short/open circuit point around the  $g = 0$  circle, until  $b_{stub}$  equals  $-b_{in}''$ . The "length" of this rotation determines the stub length  $\ell$ .

For example, your **book** describes the case where we want to match a load of  $Z_L = 60 - j80$  (at 2 GHz) to a transmission line of  $Z_0 = 50\Omega$ .

Using **shorted** stubs, we find **two** solutions to this problem:



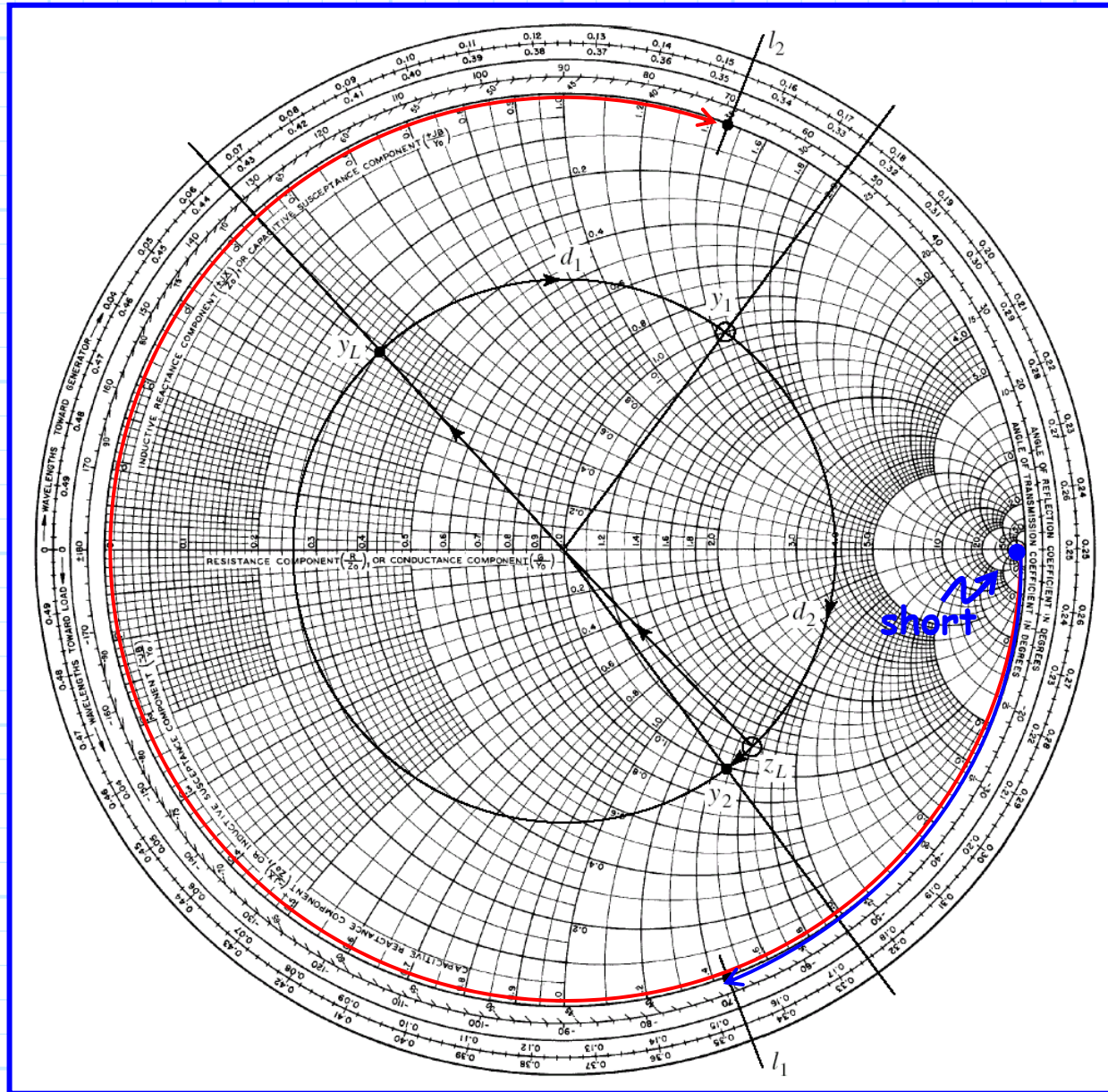Whose length values  $d$  and  $\ell$  were determined from a Smith Chart:




**Q:** *Two solutions! Which one do we use?*

**A:** The one with the **shortest** lengths of transmission line!

**Q:** *Oh, I see! Shorter transmission lines provide **smaller** and (slightly) cheaper matching networks.*

**A:** True! But there is a more **fundamental** reason why we select the solution with the **shortest** lines—the matching **bandwidth** is **larger**!

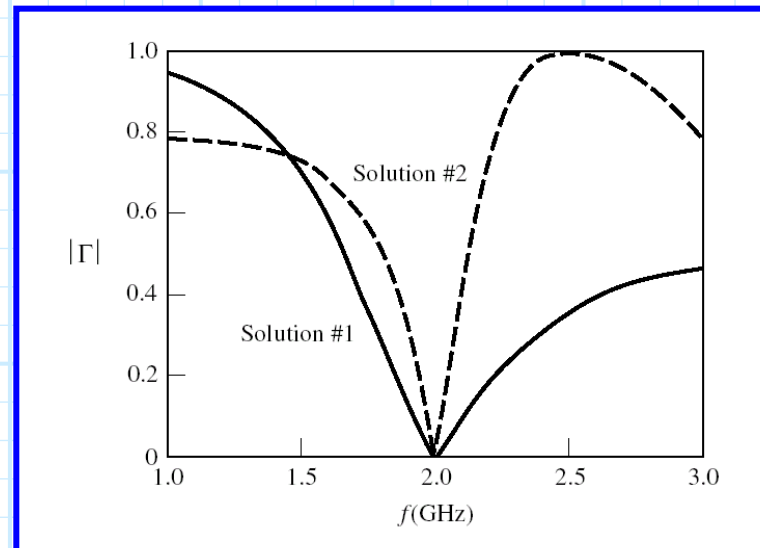
For example, consider the **frequency response** of the two examples:




Clearly, solution 1 provides a **wider** bandwidth!
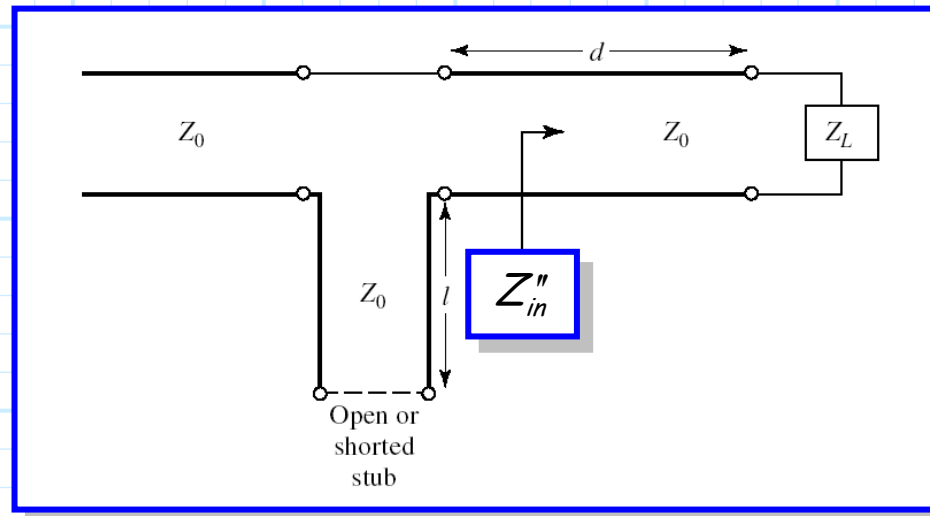
# Series Stub Tuning

Consider the following transmission line structure, with a **series stub**:



Therefore an **equivalent** circuit is:

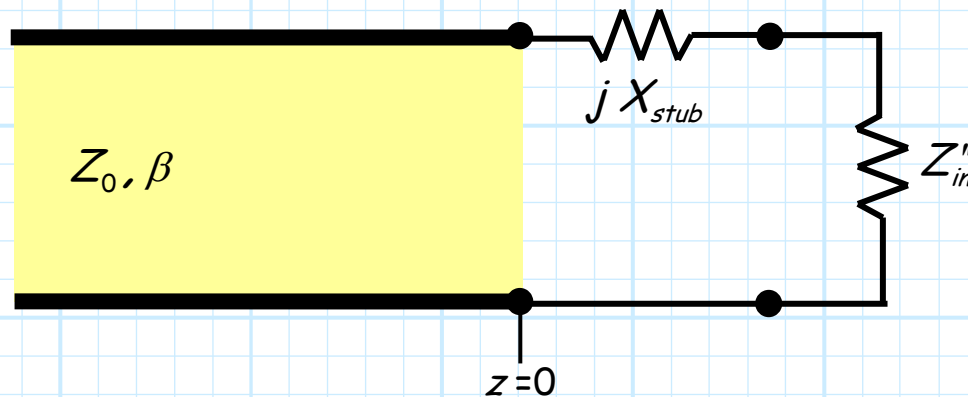

where:

$$Z''_{in} = Z_0 \left( \frac{Z_L + j Z_0 \tan \beta d}{Z_0 + j Z_L \tan \beta d} \right)$$



and the reactance  $jX_{stub}$  is either:

$$jX_{stub} = \begin{cases} -jZ_0 \cot \beta l & \text{for an open-circuit stub} \\ jZ_0 \tan \beta l & \text{for an short-circuit stub} \end{cases}$$

Therefore, for a **matched** circuit, we **require**:

$$jX_{stub} + Z_{in}'' = Z_0$$

i.e.,

$$\text{Re}\{Z_{in}''\} = Z_0$$

and

$$\text{Im}\{jX_{stub} + Z_{in}''\} = 0 \Rightarrow X_{stub} = -X_{in}''$$

where

$$X_{in}'' \doteq \text{Im}\{Z_{in}''\}$$

Note the **design parameters** for this stub tuner are transmission line **lengths**  $d$  and  $\ell$ .

More specifically we:

1) Set  $d$  such that  $\text{Re}\{Z_{in}''\} = Z_0$ .

2) Then set  $\ell$  such that  $X_{stub} = -X_{in}''$ .

We have **two** choices for determining the lengths  $d$  and  $\ell$ . We can use the design equations (5.14, 5.15, 5.16) on pp. 235.

**OR**


we can use the **Smith Chart** to determine the lengths!

1) Rotate clockwise around the Smith Chart from  $z_L$  until you intersect the  $r = 1$  circle. The "length" of this rotation determines the value  $d$ . Recall there are **two** possible solutions!

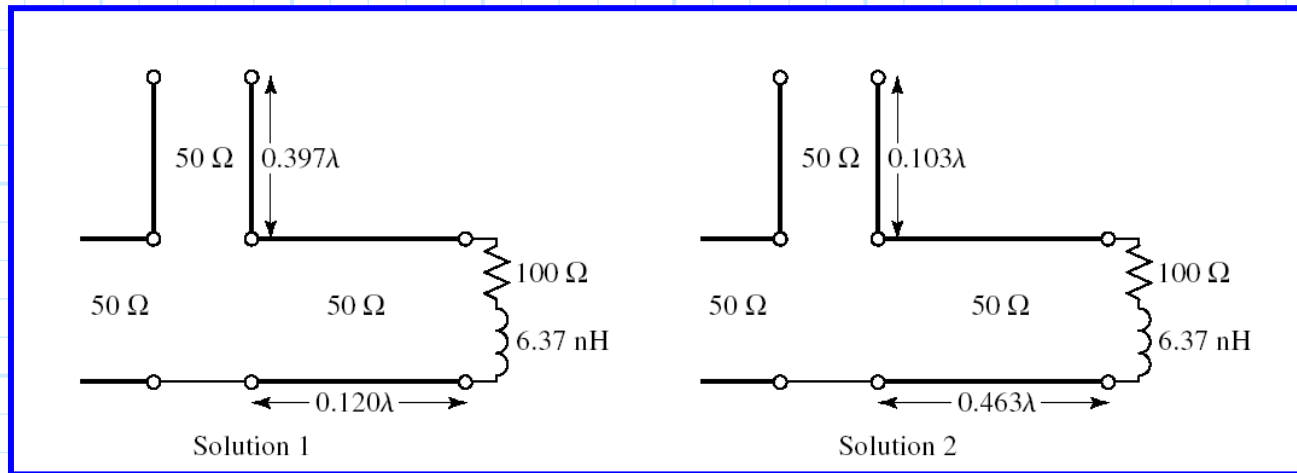
2) Rotate clockwise from the short/open circuit point around the  $r = 0$  circle until  $x_{stub}$  equals  $-x_{in}''$ . The "length" of this rotation determines the stub length  $\ell$ .

For example, your **book** describes the case where we want to match a load of  $Z_L = 100 + j80$  (at 2 GHz) to a transmission line of  $Z_0 = 50\Omega$ .

Using **open stubs**, we find **two** solutions to this problem:



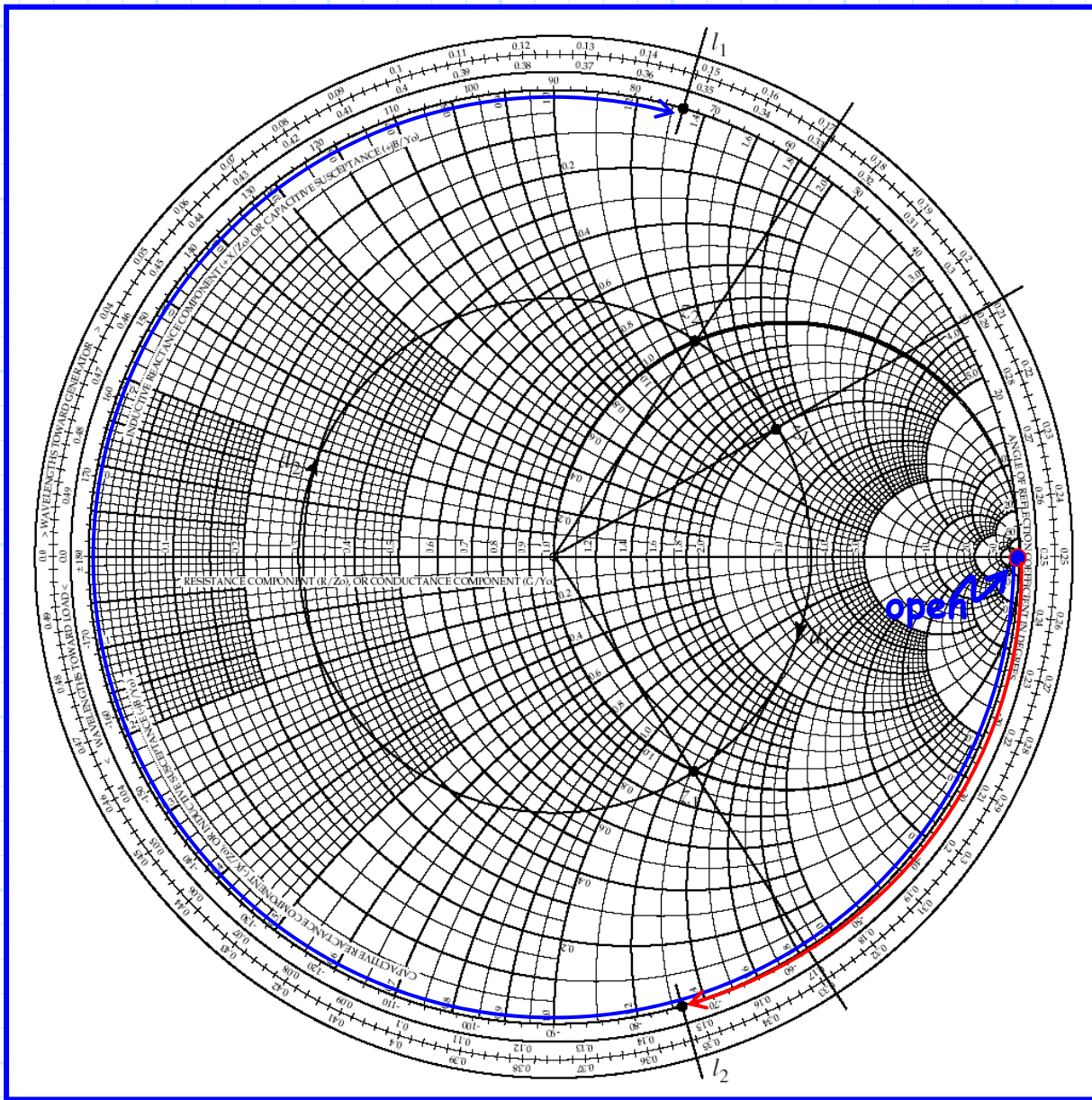Whose values were determined from a **Smith Chart**:



Again, we should use the solution with the **shortest** transmission lines, although in **this** case that distinction is a bit **ambiguous**. As a result, the bandwidth of each design is about the same (depending on how **you** define **bandwidth**!).

