

5.4 - The Quarter-Wave Transformer

Reading Assignment: pp. 73-76, 240-243

By now you've noticed that a **quarter-wave length** of transmission line ($l = \lambda/4$, $2\beta l = \pi$) appears **often** in microwave engineering problems.

Another application of the $l = \lambda/4$ transmission line is as an **impedance matching network**.

HO: THE QUARTER-WAVE TRANSFORMER


HO: THE SIGNAL-FLOW GRAPH OF A QUARTER-WAVE TRANSFORMER

Q: *Why does the quarter-wave matching network work—after all, the quarter-wave line is mismatched at both ends?*

A: **HO: MULTIPLE REFLECTION VIEWPOINT**


The Quarter-Wave Transformer

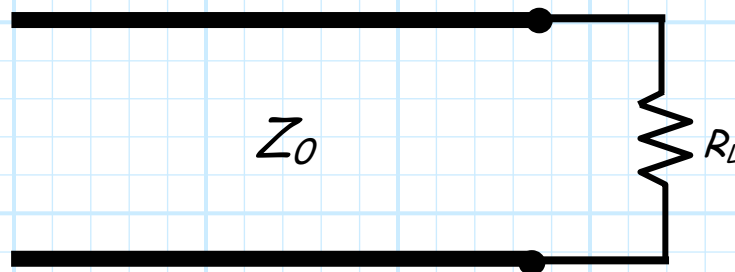Say the end of a transmission line with characteristic impedance Z_0 is terminated with a **resistive** (i.e., real) load.




Unless $R_L = Z_0$, the resistor is **mismatched** to the line, and thus some of the incident power will be **reflected**.

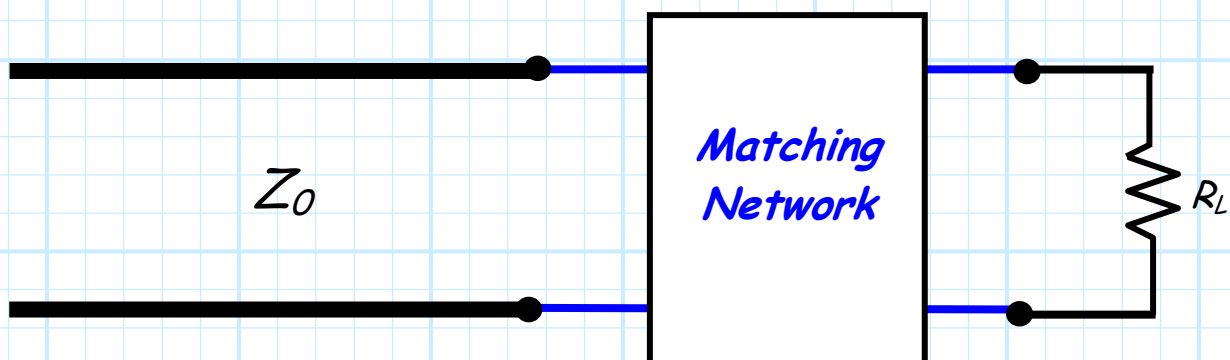We can of course correct this situation by placing a matching network between the line and the load:



In addition to the designs we have just studied (e.g., L-networks, stub tuners), one of the simplest matching network designs is the **quarter-wave transformer**.

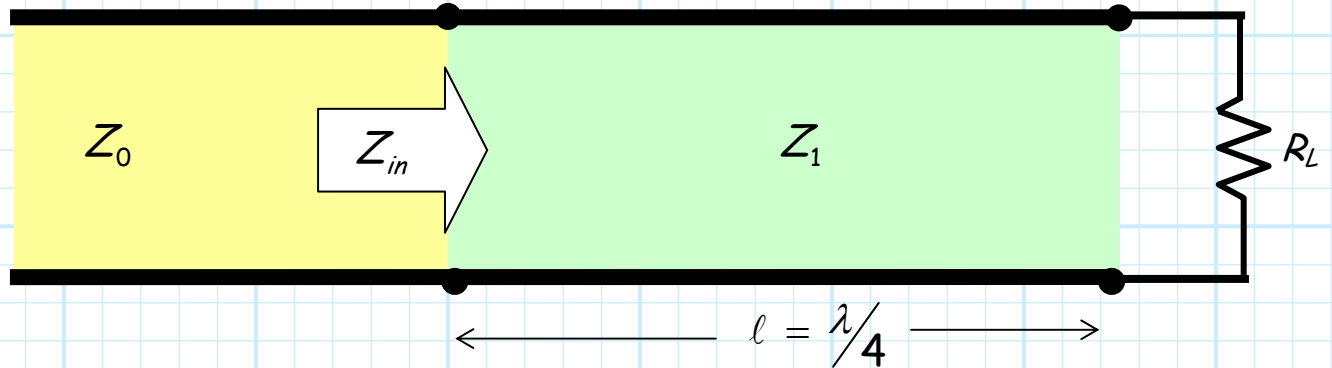The quarter-wave transformer is simply a transmission line with characteristic impedance Z_1 and length $l = \lambda/4$ (i.e., a quarter-wave line).



The $\lambda/4$ line is the **matching network!**

Q: *But what about the characteristic impedance Z_1 ; what should its value be??*

A: Remember, the quarter wavelength case is one of the **special** cases that we studied. We know that the **input** impedance of the quarter wavelength line is:

$$Z_{in} = \frac{(Z_1)^2}{Z_L} = \frac{(Z_1)^2}{R_L}$$

Thus, if we wish for Z_{in} to be numerically equal to Z_0 , we find:

$$Z_{in} = \frac{(Z_1)^2}{R_L} = Z_0$$

Solving for Z_1 , we find its **required** value to be:


$$(Z_1)^2 / R_L = Z_0$$

$$(Z_1)^2 = Z_0 R_L$$

$$Z_1 = \sqrt{Z_0 R_L}$$

In other words, the characteristic impedance of the quarter wave line is the **geometric average** of Z_0 and R_L !

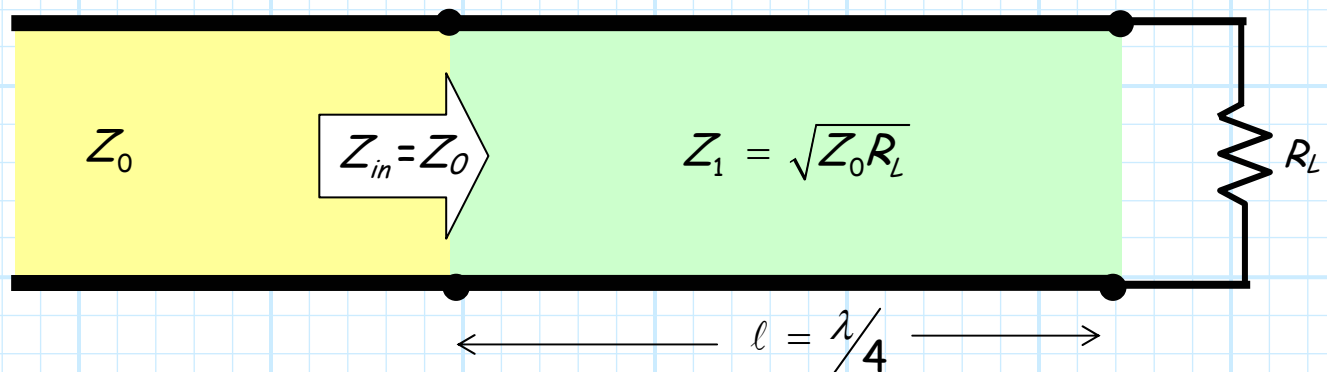Therefore, a $\lambda/4$ line with characteristic impedance $Z_1 = \sqrt{Z_0 R_L}$ will **match** a transmission line with characteristic impedance Z_0 to a resistive load R_L .



Thus, **all power** is delivered to load R_L !

Alas, the quarter-wave transformer (like all our designs) has a few problems!

Problem #1

The matching **bandwidth** is **narrow** !

In other words, we obtain a **perfect** match at precisely the frequency where the length of the matching transmission line is a **quarter-wavelength**.

→ But remember, this length can be a quarter-wavelength at just **one** frequency!

Remember, **wavelength** is related to **frequency** as:

$$\lambda = \frac{v_p}{f} = \frac{1}{f\sqrt{LC}}$$

where v_p is the **propagation velocity** of the wave .

For **example**, assuming that $v_p = c$ (c = the speed of light in a vacuum), one wavelength at 1 GHz is 30 cm ($\lambda = 0.3$ m), while one wavelength at 3 GHz is 10 cm ($\lambda = 0.1$ m). As a result, a transmission line length $\ell = 7.5$ cm is a quarter wavelength for a signal at 1GHz **only**.

Thus, a quarter-wave transformer provides a **perfect** match ($\Gamma_{in} = 0$) at **one and only one** signal frequency!

As the signal frequency (i.e., wavelength) changes, the **electrical** length of the matching transmission line changes. It will **no longer** be a **quarter** wavelength, and thus we **no longer** will have a **perfect** match.

We find that the **closer** R_L (R_{in}) is to characteristic impedance Z_0 , the **wider** the bandwidth of the quarter wavelength transformer.

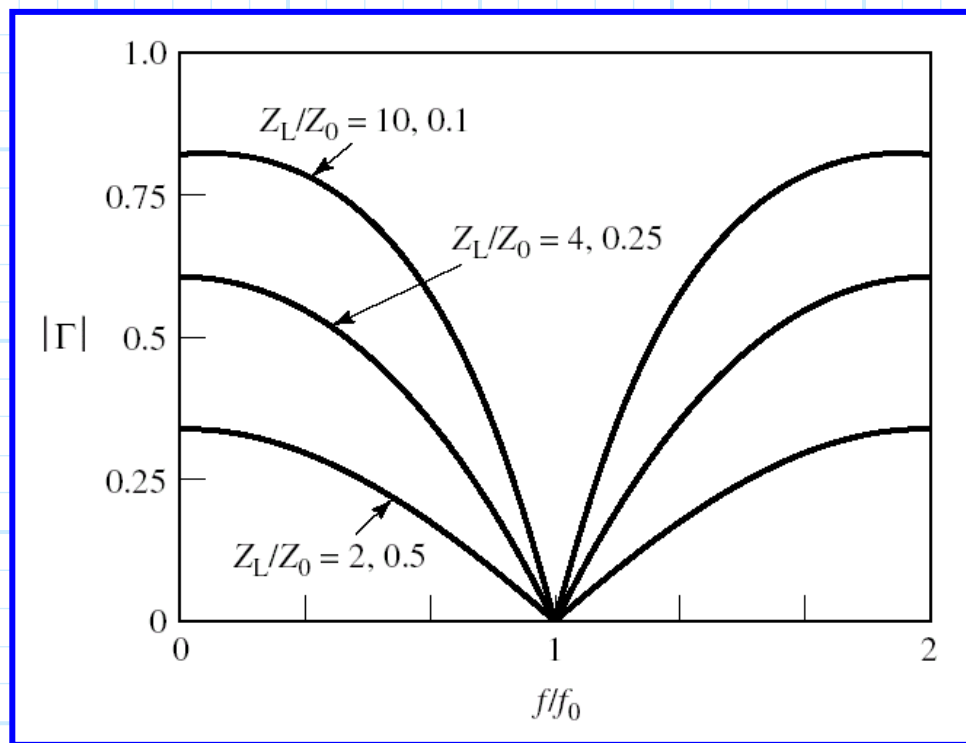


Figure 5.12 (p. 243) Reflection coefficient magnitude versus frequency for a single-section quarter-wave matching transformer with various load mismatches.

We will find that the bandwidth can be **increased** by adding **multiple** $\lambda/4$ sections!


Problem #2

Recall the matching solution was limited to loads that were **purely real!** I.E.:

$$Z_L = R_L + j0$$


Of course, this is a **BIG** problem, as most loads will have a **reactive** component!

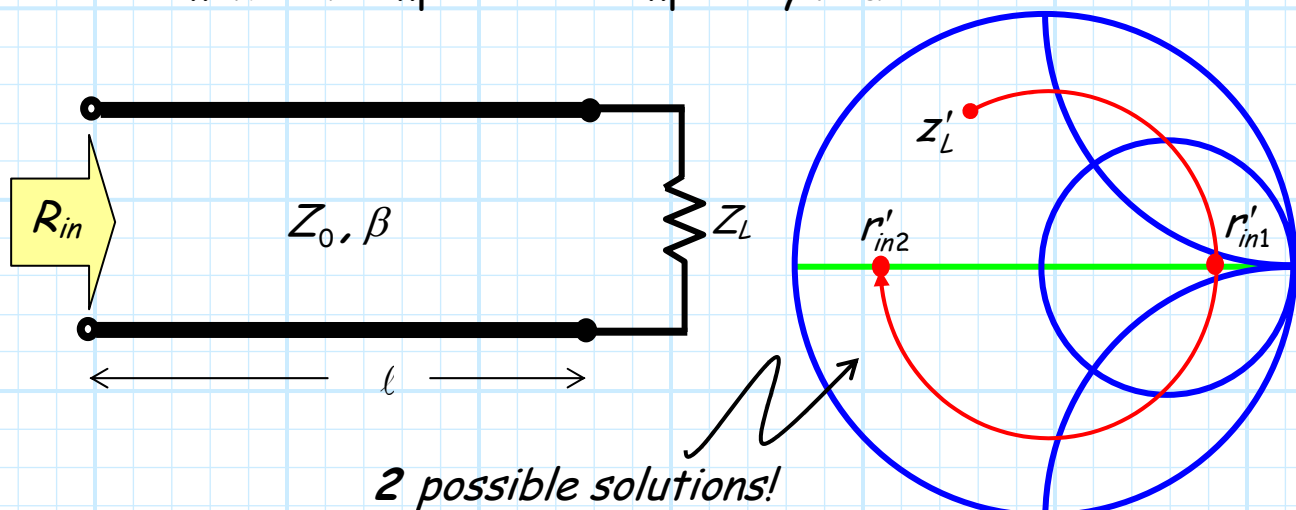Fortunately, we have a relatively easy **solution** to this problem, as we can always add some **length** ℓ of transmission line to the load to make the impedance completely **real**:



However, remember that the input impedance will be purely real at only **one** frequency!

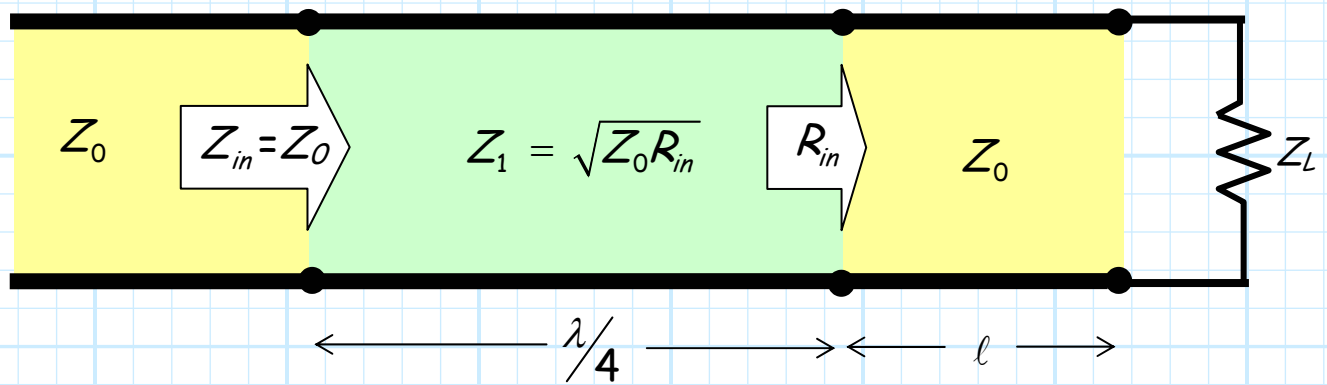
We can then build a quarter-wave transformer to **match** the line Z_0 to resistance R_{in} :



Again, since the transmission lines are lossless, **all** of the incident power is delivered to the load Z_L .

The Signal Flow Graph of a Quarter-Wave Transformer

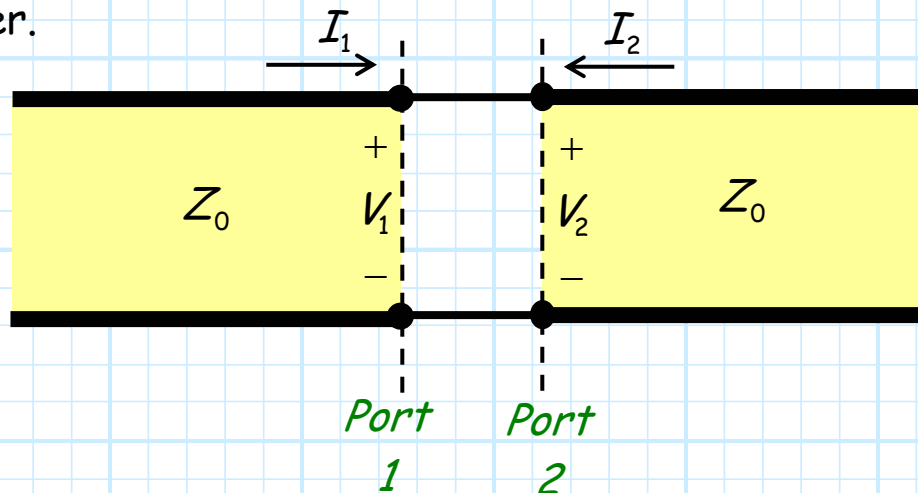First, let's consider the scattering matrix of a **perfect connector**—an electrically very small two-port device that allows us to connect the ends of different transmission lines together.




If the connector is ideal, then it will exhibit **no series inductance nor shunt capacitance**, and thus:


$$V_1 = V_2 \quad I_1 = -I_2$$

The **scattering matrix** for such this ideal connector is therefore:

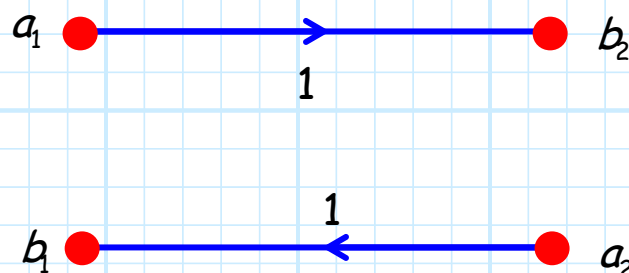
$$S = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$$



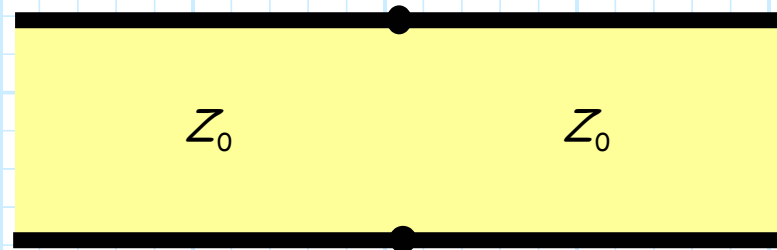As a result, the perfect connector allows two transmission lines of **identical characteristic impedance** to be connected together into one "seamless" transmission line.



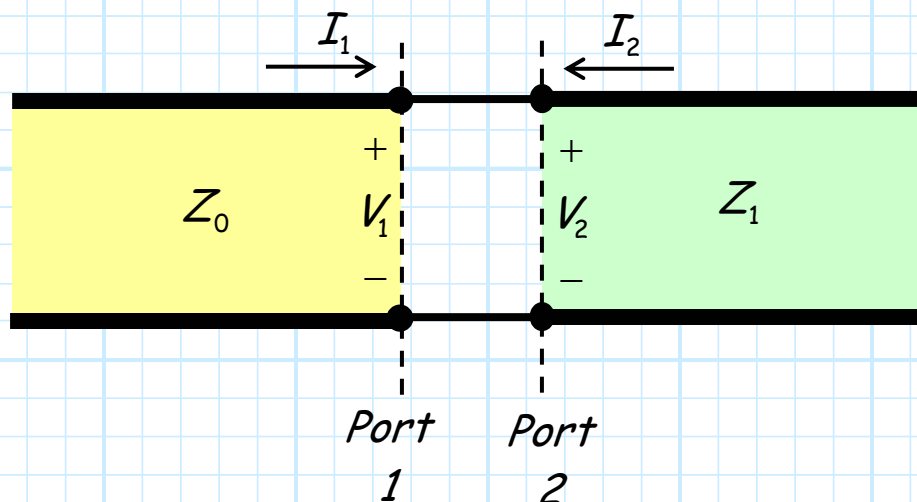Now, however, consider the case where the transmission lines connected together have **dissimilar** characteristic impedances (i.e., $Z_0 \neq Z_1$):




Q: *Won't the scattering matrix of this ideal connector remain the **same**? After all, the **device itself** has not changed!*

A: The impedance, admittance, and transmission matrix **will** remained unchanged—these matrix quantities **do not** depend on the characteristics of the transmission lines connected to the device.


But remember, the **scattering matrix** depends on **both** the device **and** the characteristic impedance of the transmission lines attached to it.

➔ After all, the **incident** and **exiting** waves are traveling on these transmission lines!

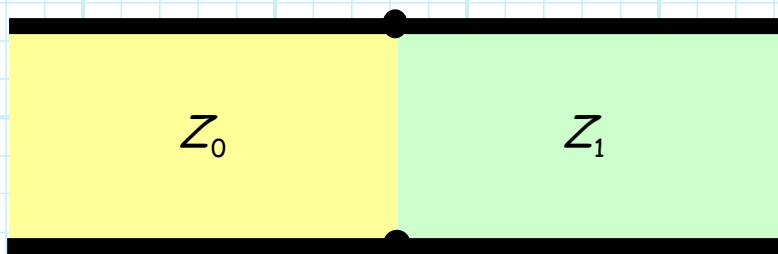The ideal connector in this case establishes a "seamless" interface between two **dissimilar** transmission lines.



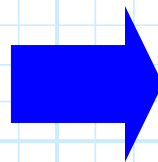Remember, this is the **same** structure that we evaluated in an **earlier** handout!



1/31/2007 The Transmission Coefficient T 1/8

Example: The Transmission Coefficient T

Consider this circuit:

I.E., a transmission line with characteristic impedance Z_1 transitions to a different transmission line at location $z=0$. This second transmission line has different characteristic impedance Z_2 ($Z_1 \neq Z_2$). This second line is terminated with a load $Z_L = Z_2$ (i.e., the second line is matched).

Q: What is the voltage and current along each of these two transmission lines? More specifically, what are V_{01} , V_{01} , V_{02} and V_{02} ??

A: Since a source has not been specified, we can only determine V_{01} , V_{02} and V_{02} in terms of complex constant V_{01} . To accomplish this, we must apply a boundary condition at $z=0$!


Jim Stiles The Univ. of Kansas Dept. of EECS

From the results of that analysis we can conclude that the **scattering matrix** of the ideal connector (when connecting dissimilar transmission lines) is:

$$S = \begin{bmatrix} \frac{Z_1 - Z_0}{Z_1 + Z_0} & \frac{2\sqrt{Z_0 Z_1}}{Z_0 + Z_1} \\ \frac{2\sqrt{Z_0 Z_1}}{Z_0 + Z_1} & \frac{Z_0 - Z_1}{Z_0 + Z_1} \end{bmatrix}$$

Or more **compactly** stated:
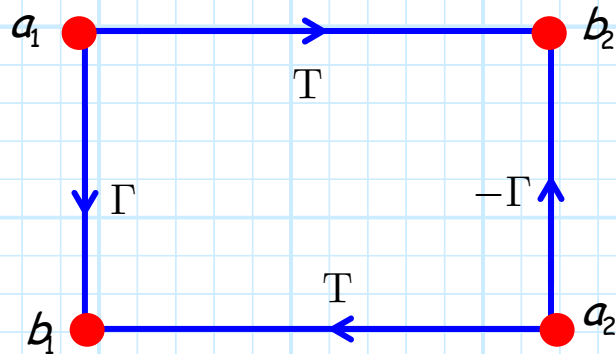
$$\mathcal{S} = \begin{bmatrix} \Gamma & T \\ T & -\Gamma \end{bmatrix}$$



where

$$\Gamma = \frac{Z_1 - Z_0}{Z_1 + Z_0} \quad T = \frac{2\sqrt{Z_0 Z_1}}{Z_0 + Z_1}$$

For a **quarter wave transformer**, we set Z_1 such that:

$$Z_1^2 = Z_0 R_L \quad \Rightarrow \quad Z_0 = Z_1^2 / R_L$$

Inserting this into the expressions above, we find:


$$\Gamma = \frac{R_L - Z_1}{R_L + Z_1} \quad T = \frac{2\sqrt{R_L Z_1}}{R_L + Z_1}$$

Since the device is **lossless**, we can conclude (and likewise show) that:


$$1 = |\Gamma|^2 + |T|^2 = \Gamma^2 + T^2$$

where this last expression is (only) true because Γ and T are **real** valued.

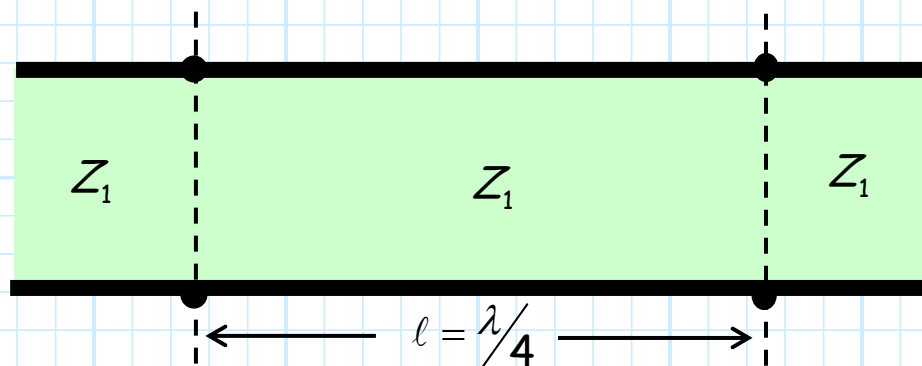
Now, a quarter wavelength of **transmission line** has the scattering matrix:



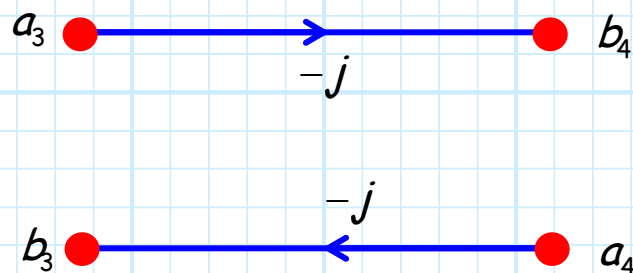
$$S = \begin{bmatrix} 0 & -j \\ -j & 0 \end{bmatrix}$$



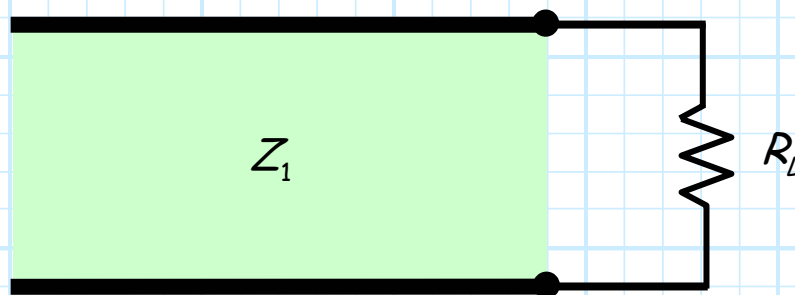While a **load** has a "scattering matrix" of:



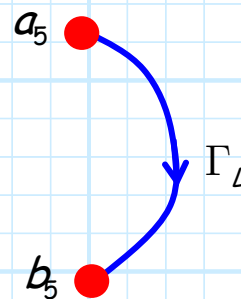
$$S = \begin{bmatrix} R_L - Z_1 \\ R_L + Z_1 \end{bmatrix} = \Gamma_L$$




Note that $\Gamma_L = \Gamma$!!!

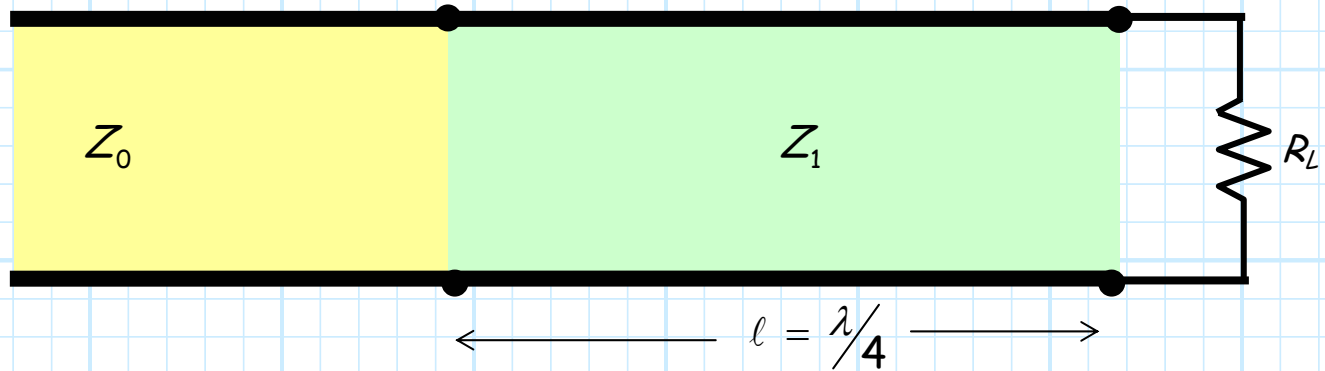
Of course, if we connect the ideal connector to a quarter wavelength of transmission line, and terminate the whole thing with load R_L , we have formed a **quarter wave matching network!**



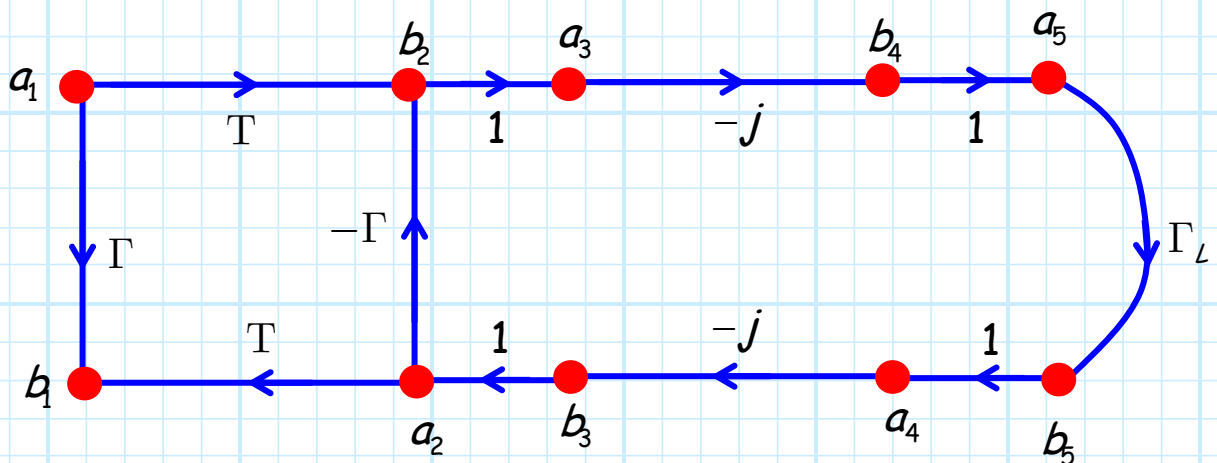We can likewise put the signal-flow graph pieces together to form the **signal-flow graph** of the quarter wave network:




And simplifying:

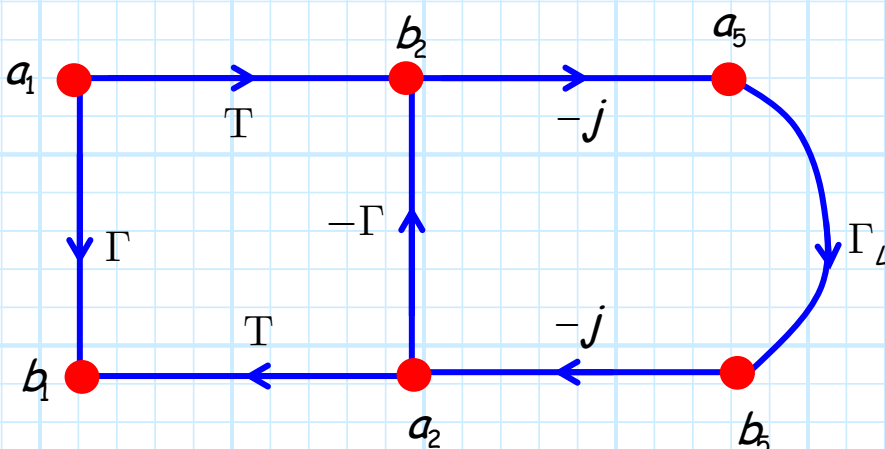


Now, let's see if we can **reduce** this graph to determine:

$$\Gamma_{in} \doteq \frac{b_1}{a_1}$$


From the **series** rule:

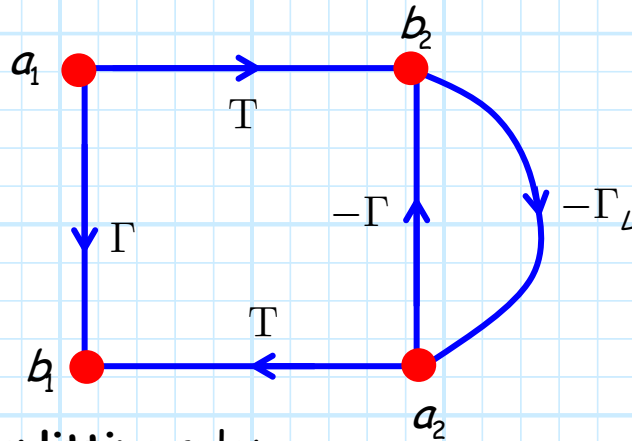


From the **splitting** rule:

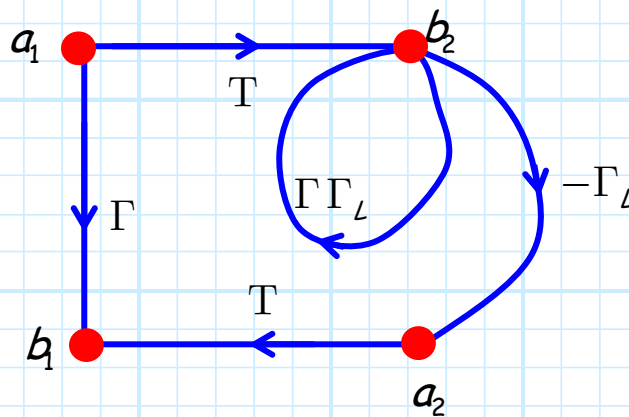


From the **self-loop** rule:

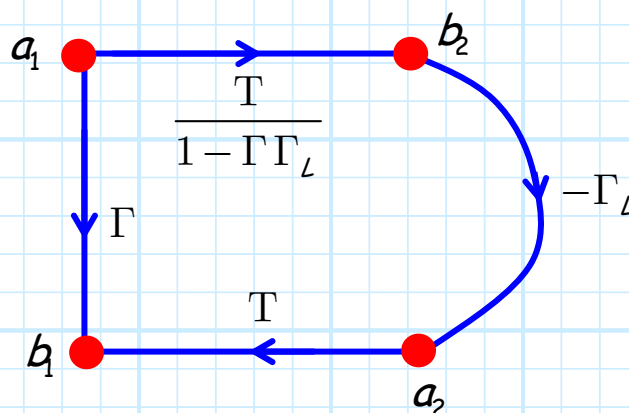

Again with the **series** rule:

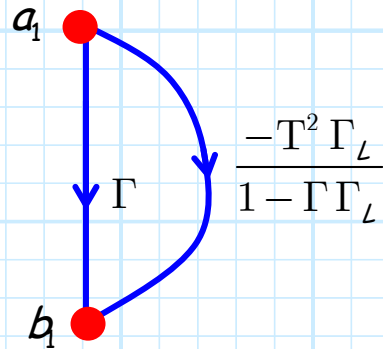

And finally with the **parallel** rule:

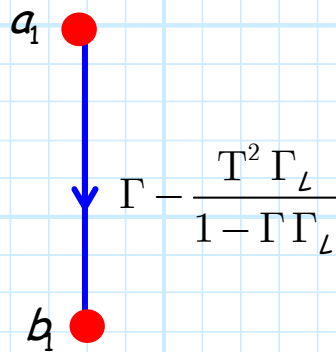

So that:

$$\Gamma_{in} \doteq \frac{b_1}{a_1} = \Gamma - \frac{T^2 \Gamma_L}{1 - \Gamma \Gamma_L}$$

Q: Hey wait! If the quarter-wave transformer is a matching network, shouldn't $\Gamma_{in} = 0$??

A: Who says it doesn't!

Recall that for the quarter-wave transformer, we found that $\Gamma_L = \Gamma$, thus:

$$\begin{aligned}\Gamma_{in} &= \Gamma - \frac{T^2 \Gamma_L}{1 - \Gamma \Gamma_L} \\ &= \Gamma - \frac{T^2 \Gamma}{1 - \Gamma^2}\end{aligned}$$


And likewise since $T^2 = 1 - \Gamma^2$:

$$\begin{aligned}\Gamma_{in} &= \Gamma - \frac{T^2 \Gamma}{1 - \Gamma^2} \\ &= \Gamma - \frac{T^2 \Gamma}{T^2} \\ &= \Gamma - \Gamma \\ &= 0\end{aligned}$$

A perfect match!

Multiple Reflection Viewpoint


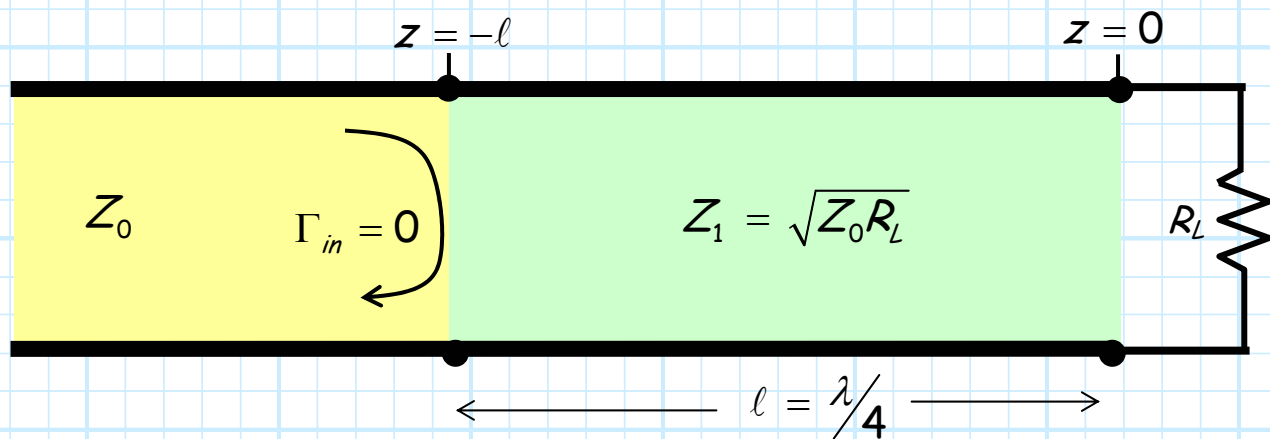
The **quarter-wave** transformer brings up an interesting question in μ -wave engineering.




Q: *Why is there **no** reflection at $z = -l$? It appears that the line is **mismatched** at both $z = 0$ and $z = -l$.*

A: In fact there **are** reflections at these mismatched interfaces—an **infinite** number of them!

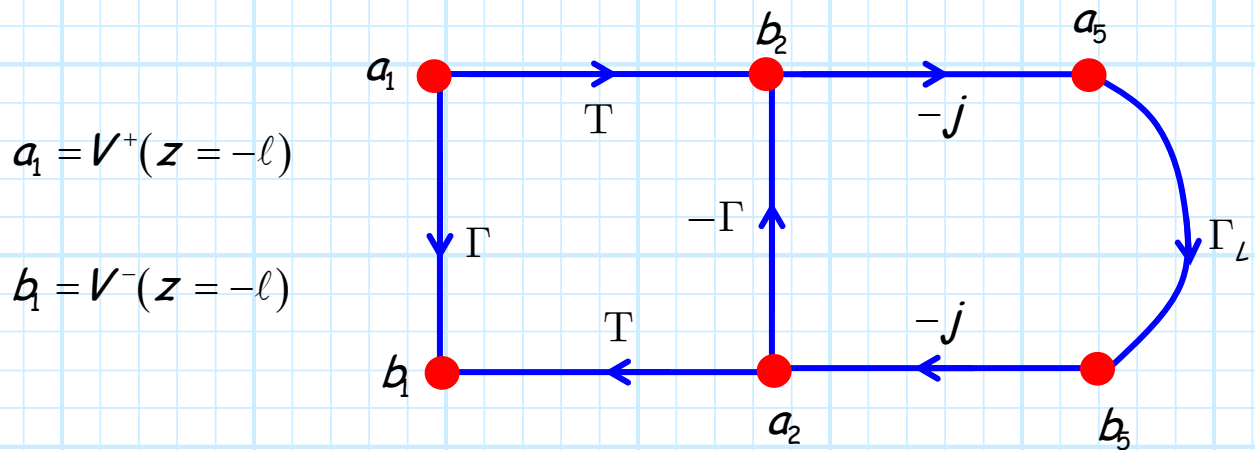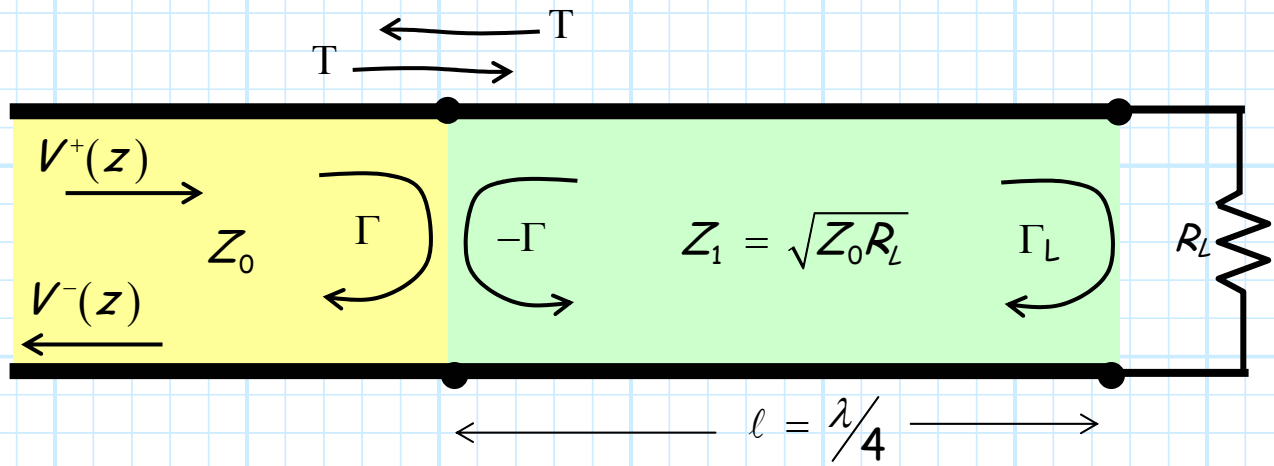We can use our **signal flow graph** to in fact determine all the **propagation paths** through the quarter-wave transformer.




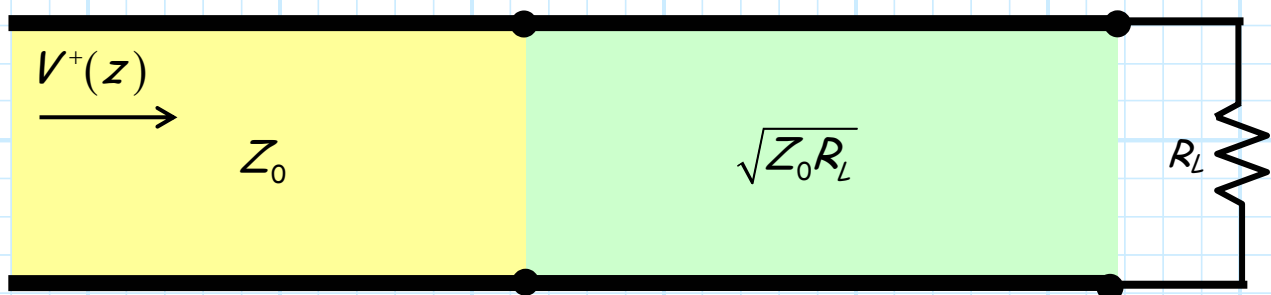Now let's try to interpret what **physically** happens when the **incident** voltage wave:




reaches the interface at $z = -\ell$.

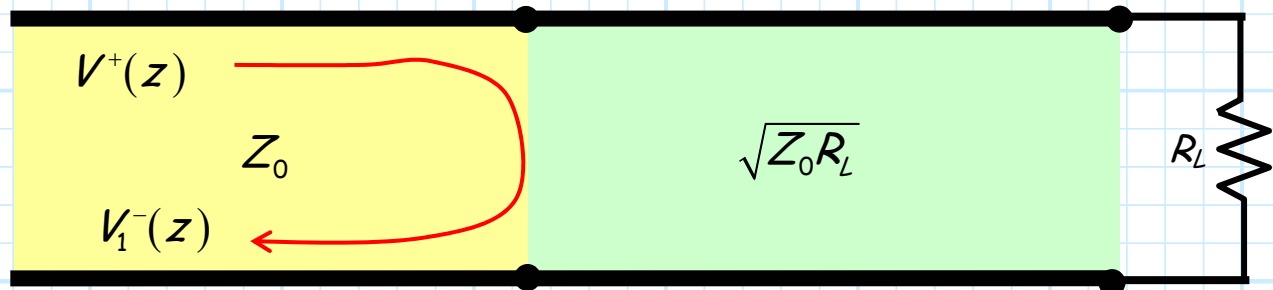
1. At $z = -l$, the characteristic impedance of the transmission line changes from Z_0 to Z_1 . This mismatch creates a **reflected wave**, a wave that we shall call $V_1^-(z)$:



so $V_1^-(z = -l) = \Gamma V^+(z = -l)$.

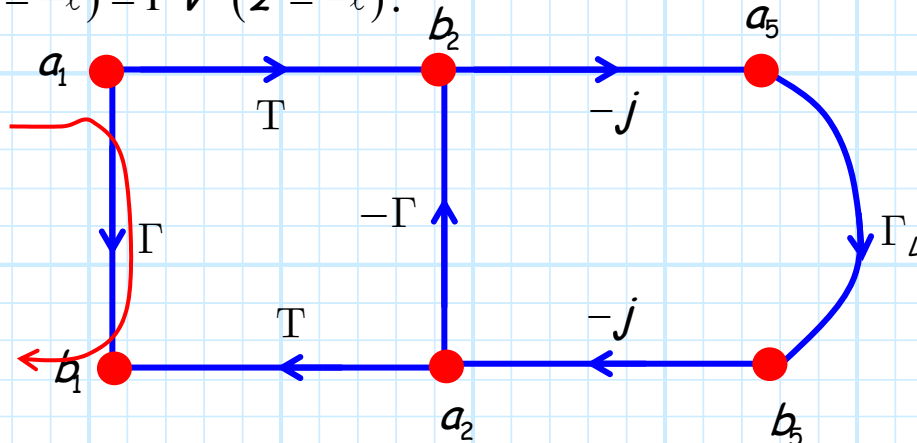


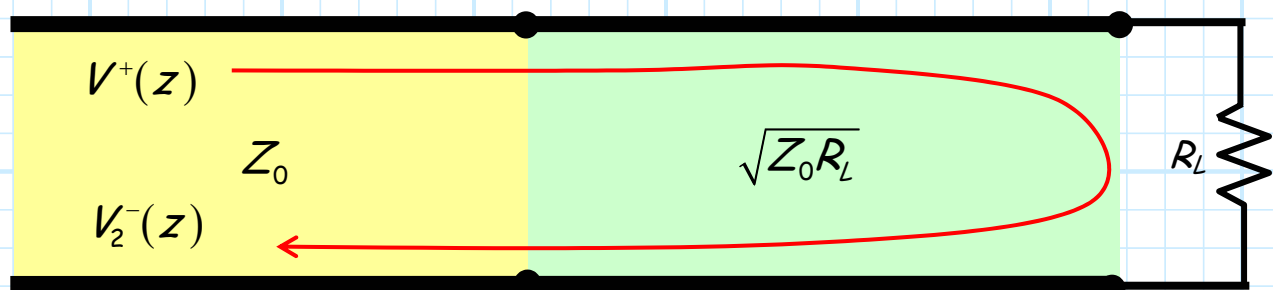2. However, a **portion** of the incident wave is transmitted (T) across the interface at $z = -l$, this wave travels a distance of $\beta l = 90^\circ$ to the load at $z = 0$, where a portion of it is reflected (Γ_L). This wave travels back $\beta l = 90^\circ$ to the interface at $z = -l$, where a portion is again transmitted (T) across into the Z_0 transmission line—**another** reflected wave ($V_2^-(z)$)!




where we have found that traveling $2\beta\ell = 180^\circ$ has produced a **minus** sign in our result:
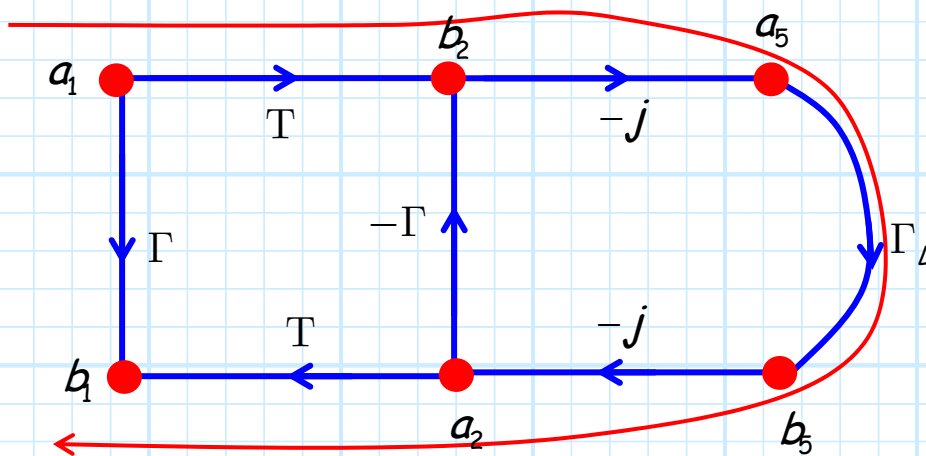
$$\begin{aligned} V_2^-(z = -\ell) &= T e^{-j90^\circ} \Gamma_L e^{-j90^\circ} T V^+(z = -\ell) \\ &= -T^2 \Gamma_L V^+(z = -\ell) \end{aligned}$$




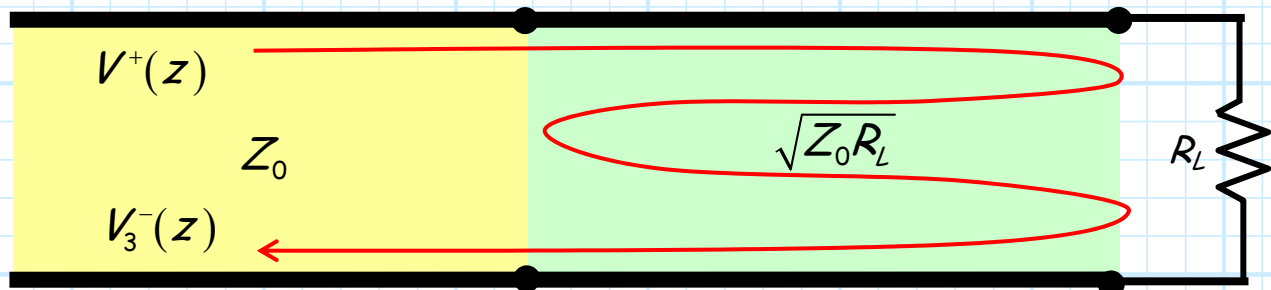3. However, a portion of this **second** wave is also **reflected** (Γ) back into the Z_1 transmission line at $z = -\ell$, where it again travels to $\beta\ell = 90^\circ$ the load, is partially reflected (Γ_L), travels $\beta\ell = 90^\circ$ back to $z = -\ell$, and is partially transmitted into Z_0 (T)—our **third** reflected wave!



where:
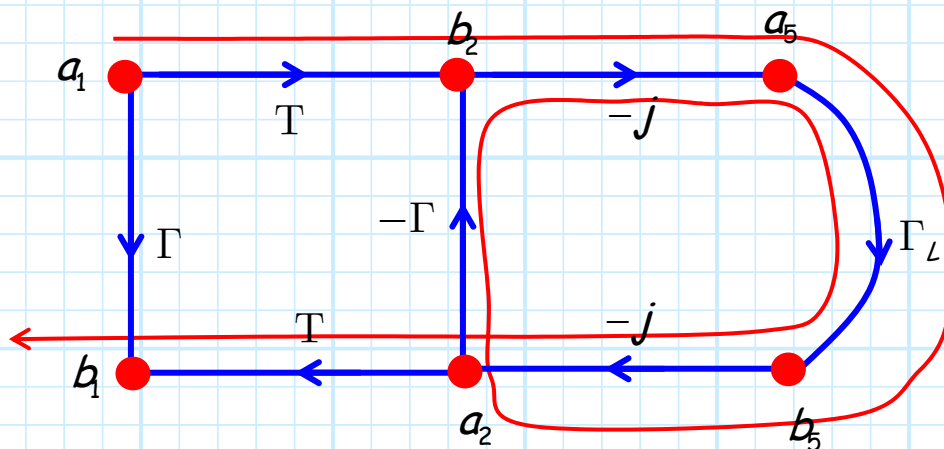
$$\begin{aligned} V_3^-(z = -\ell) &= T e^{-j90^\circ} \Gamma_L e^{-j90^\circ} (-\Gamma) e^{-j90^\circ} \Gamma_L e^{-j90^\circ} T V^+(z = -\ell) \\ &= -T^2 (\Gamma_L)^2 \Gamma V^+(z = -\ell) \end{aligned}$$



n. We can see that this “bouncing” back and forth can go on **forever**, with each trip launching a **new** reflected wave into the Z_0 transmission line.

Note however, that the **power** associated with each successive reflected wave is **smaller** than the previous, and so eventually, the power associated with the reflected waves will **diminish** to insignificance!

Q: *But, why then is $\Gamma = 0$?*

A: Each reflected wave $V_n^-(z)$ is a **coherent** wave. That is, they all oscillate at same frequency ω ; the reflected waves differ only in terms of their **magnitude** and **phase**.

Therefore, to determine the **total** reflected wave, we must perform a **coherent summation** of each reflected wave—a operation easily performed since we have expressed our waves with **complex** notation:

$$V^-(z) = \sum_{n=1}^{\infty} V_n^-(z)$$

It can be shown that this infinite series **converges**, with the result:

$$V^-(z = -\ell) = \left(\frac{\Gamma - \Gamma^2 \Gamma_L - \Gamma^2 \Gamma_L}{1 - \Gamma^2} \right) V^+(z = -\ell)$$

Thus, the **total** reflection coefficient is:

$$\Gamma_{in} = \frac{\Gamma - \Gamma^2 \Gamma_L - \Gamma^2 \Gamma_L}{1 - \Gamma^2}$$

Using our definitions, it can likewise be shown that the **numerator** of the above expression is:

$$\Gamma - \Gamma^2 \Gamma_L - \Gamma^2 \Gamma_L = \frac{2(Z_1^2 - Z_0 R_L)}{(Z_1 + Z_0)(R_L + Z_1)}$$

It is evident that the numerator (and therefore Γ) will be **zero** if:

$$Z_1^2 - Z_0 R_L \Rightarrow Z_1 = \sqrt{Z_0 R_L}$$

Just as we expected!

Physically, this results insures that all the reflected waves add coherently together to produce a **zero value!**

Note **all** of our transmission line analysis has been **steady-state** analysis. We assume our signals are **sinusoidal**, of the form $\exp(j\omega t)$. Note this signal exists for **all time** t —the signal is assumed to have been "on" **forever**, and assumed to continue on forever.

In other words, in steady-state analysis, **all** the multiple reflections have long since occurred, and thus have reached a steady state—the reflected wave is **zero!**