

5.5 - The Theory of Small Reflections

Reading Assignment: *pp. 244-246*

An important and useful **approximation** when considering multi-section matching networks is the **Theory of Small Reflections**.

HO: THE THEORY OF SMALL REFLECTIONS

EXAMPLE: THE THEORY OF SMALL REFLECTIONS

The Theory of Small Reflections provides a simpler mathematical form for analyzing the **frequency response** of many microwave devices.


HO: THE FREQUENCY RESPONSE OF THE QUARTER-WAVE MATCHING NETWORK

We can also use the Theory of Small Reflections to provide an **approximate** analysis of a **multi-section** impedance transformer (i.e., multi-section matching network).

HO: THE MULTI-SECTION TRANSFORMER

The Theory of Small Reflections

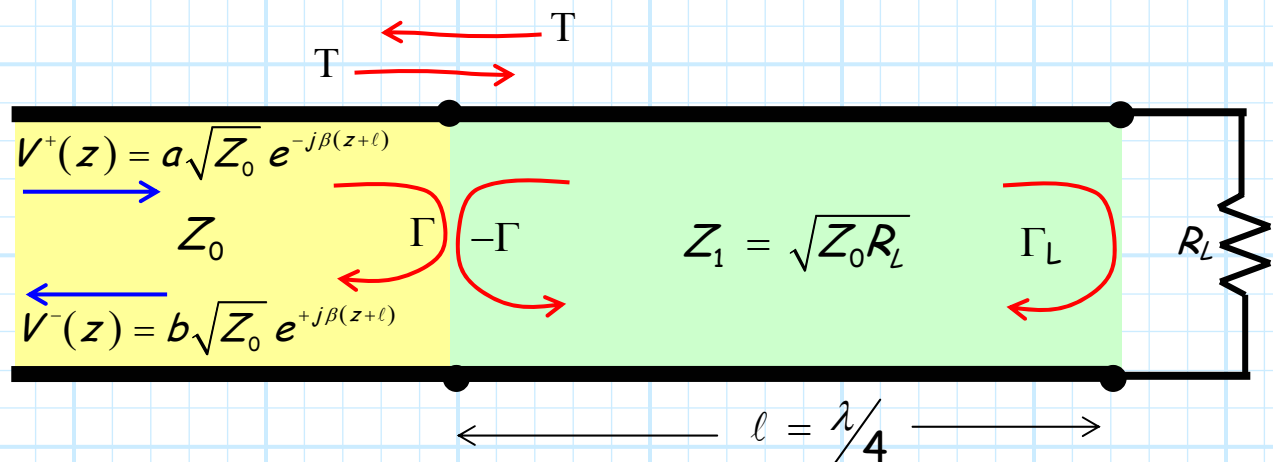Recall that we analyzed a **quarter-wave** transformer using the multiple reflection view point.





We found that the solution could thus be written as an **infinite** summation of terms (the **propagation series**):

$$b = a \sum_{n=1}^{\infty} p_n$$

where each term had a specific **physical** interpretation, in terms of reflections, transmissions, and propagations.

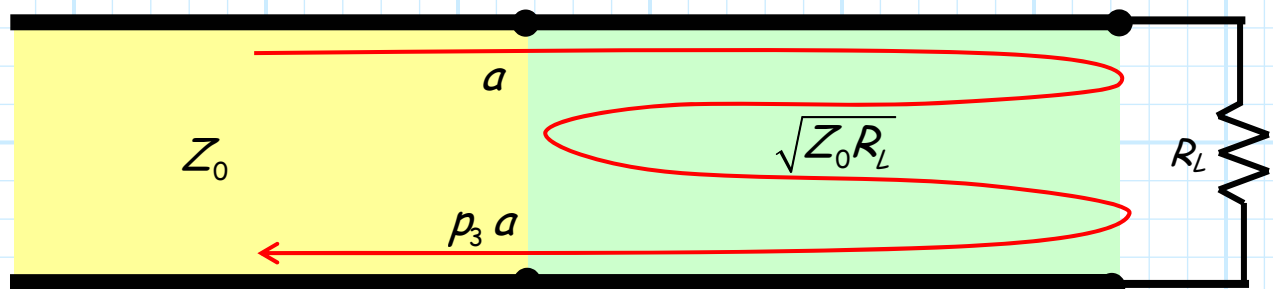For example, the **third** term was path:



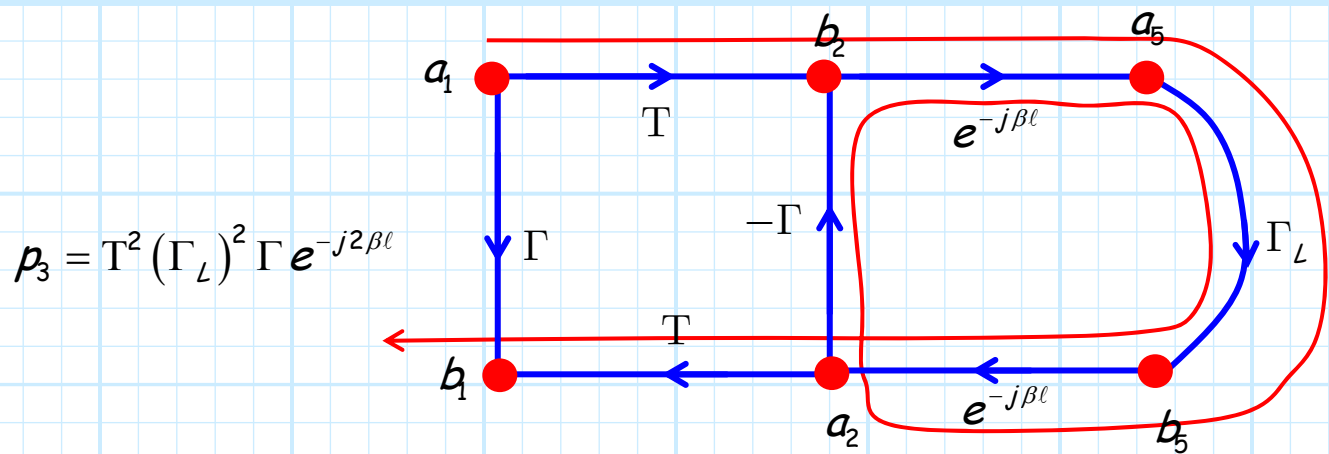

Now let's consider the **magnitude** of this path:

$$\begin{aligned} |\rho_3| &= |T|^2 |\Gamma_L|^2 |\Gamma| |e^{-j2\beta\ell}| \\ &= |T|^2 |\Gamma_L|^2 |\Gamma| \end{aligned}$$

Recall that $\Gamma = \Gamma_L$ for a **properly designed** quarter-wave transformer :

$$\Gamma = \frac{R_L - Z_1}{R_L + Z_1} = \Gamma_L$$

and so:

$$|\rho_3| = |T|^2 |\Gamma_L|^2 |\Gamma| = |T|^2 |\Gamma_L|^3$$

For the case where values R_L and Z_1 are numerically "close" in —i.e., when:

$$|R_L - Z_1| \ll |R_L + Z_1|$$

we find that the magnitude of the reflection coefficient will be **very small**:

$$|\Gamma_L| = \left| \frac{R_L - Z_1}{R_L + Z_1} \right| \ll 1.0$$

As a result, the value $|\Gamma_L|^3$ will be **very, very, very** small.

Moreover, we know (since the connector is **lossless**) that:

$$1 = |\Gamma|^2 + |T|^2 = |\Gamma_L|^2 + |T|^2$$

and so:



$$|T|^2 = 1 - |\Gamma_L|^2 \approx 1$$

We can thus conclude that the **magnitude** of path p_3 is likewise **very, very, very** small:

$$|p_3| = |T|^2 |\Gamma_L|^3 \approx |\Gamma_L|^3 \ll 1$$

This is a **classic case** where we can approximate the propagation series using only the **forward paths!!**

Recall there are **two** forward paths:

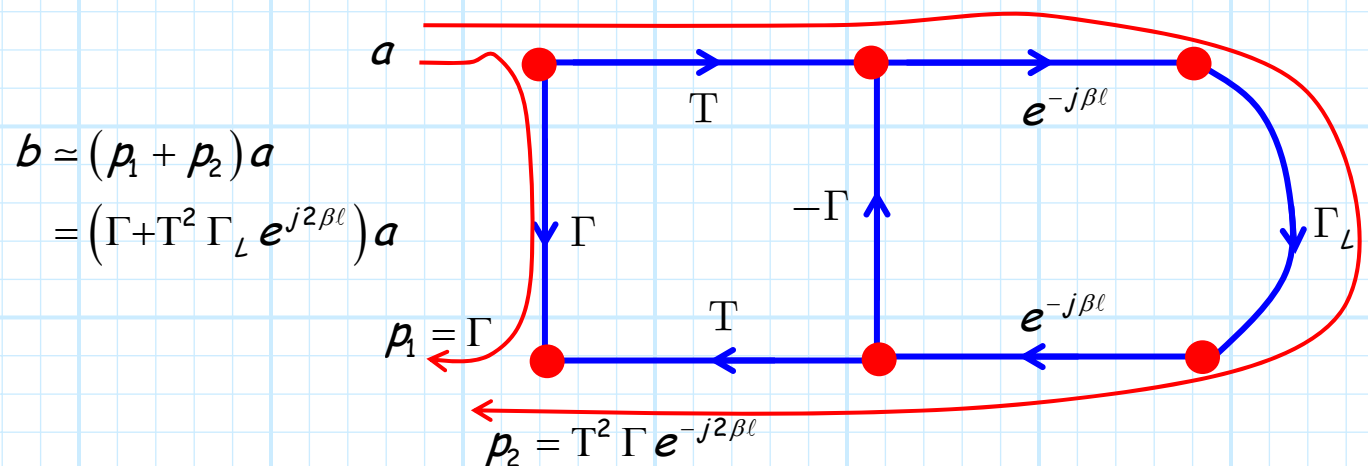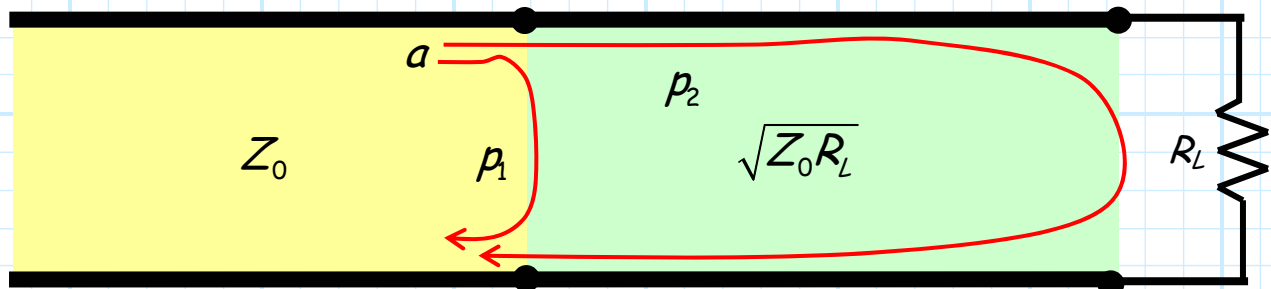

Therefore **IF** Z_0 and R_L are very **close** in value, we find that we can **approximate** the reflected wave using only the **direct paths** of the infinite series:

$$\begin{aligned} b &\approx (\rho_1 + \rho_2) a \\ &= (\Gamma + \Gamma^2 \Gamma_L e^{j2\beta\ell}) a \end{aligned}$$

Therefore:

$$\begin{aligned} V^-(z) &= b \sqrt{Z_0} e^{+j\beta(z+\ell)} \\ &\cong (\Gamma + \Gamma^2 \Gamma_L e^{j2\beta\ell}) a \sqrt{Z_0} e^{+j\beta(z+\ell)} \end{aligned}$$

Now, if we likewise apply the **approximation** that $|\Gamma| \approx 1.0$, we conclude for this quarter wave transformer (at the design frequency):

$$\begin{aligned} b &\approx (\rho_1 + \rho_2) a \\ &= (\Gamma + \Gamma_L e^{j2\beta\ell}) a \end{aligned}$$

Therefore:


$$\begin{aligned} V^-(z) &= b \sqrt{Z_0} e^{+j\beta(z+\ell)} \\ &\cong (\Gamma + \Gamma_L e^{j2\beta\ell}) a \sqrt{Z_0} e^{+j\beta(z+\ell)} \end{aligned}$$

This **approximation**, where we:

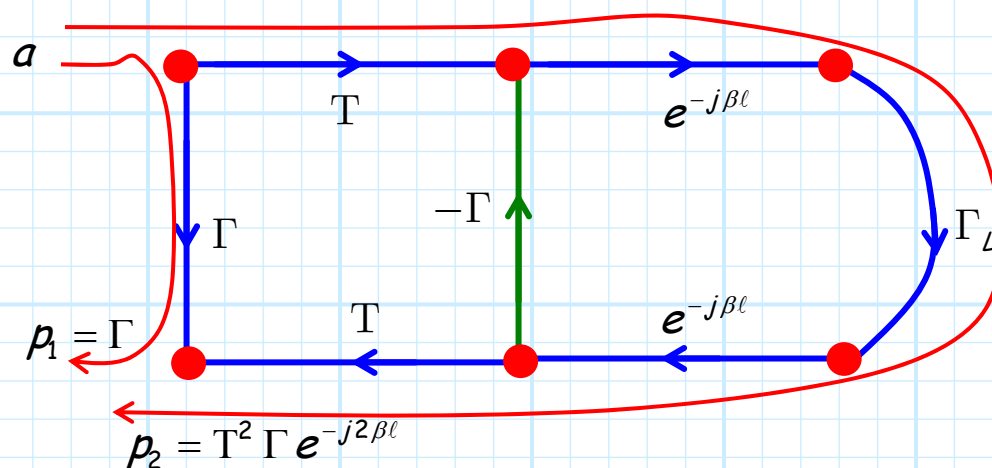
1. use only the **direct paths** to calculate the propagation series,
2. approximate the **transmission coefficients** as **one** (i.e., $T = 1$).

is known as the **Theory of Small Reflections**, and allows us to use the propagation series as an **analysis** tool (we don't have to consider an **infinite** number of terms!).


Consider again the quarter-wave matching network *SFG*. Note there is **one branch** ($-\Gamma = S_{22}$ of the connector), that is **not included** in either **direct path**.



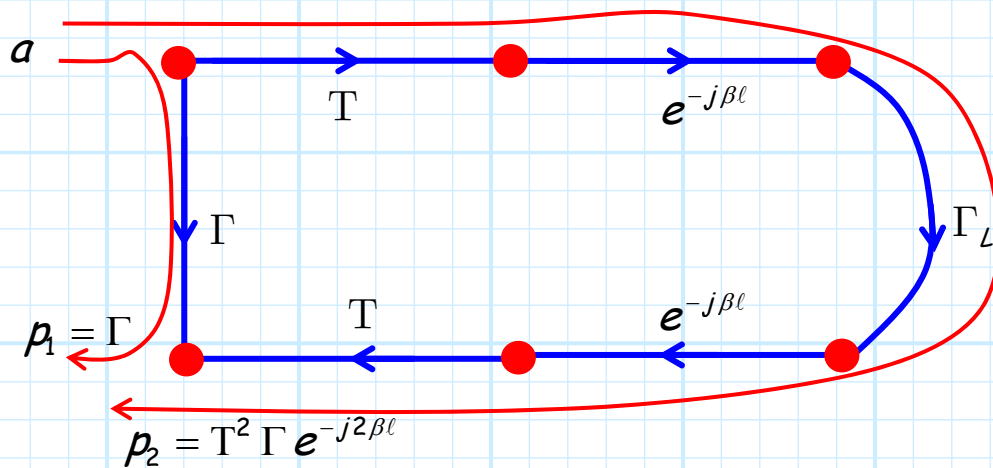With respect to the theory of small reflections (where **only** direct paths are considered), this branch can be **removed** from the *SFG* without affect.



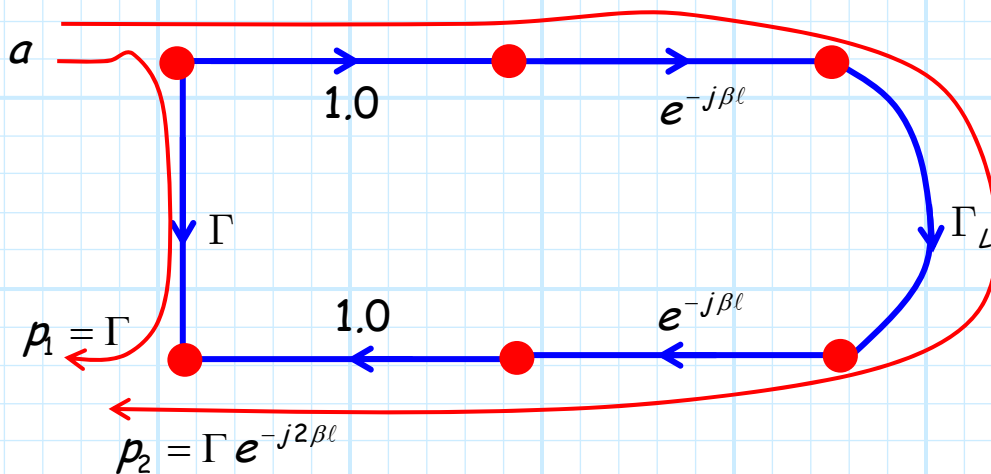Moreover, the theory of small reflections implements the **approximation** $T = 1$, so that the *SFG* becomes:



Reducing this SFG by combining the 1.0 branch and the $e^{-j\beta\ell}$ branch via the **series rule**, we get the following **approximate SFG**:

$$\Gamma_{in} = \frac{b}{a}$$

$$= \Gamma + \Gamma_L e^{j2\beta\ell}$$

A reduced signal flow graph with two nodes, a (top) and b (bottom). A blue arrow points from a to b through a reflection coefficient Γ . A blue arrow points from a to the right, then down through Γ_L , then left through $e^{-j\beta\ell}$, then up through $e^{-j\beta\ell}$, and finally right to a .

The approximate SFG when applying the theory of small reflections!


Note this **approximate SFG** provides **precisely** the results of the theory of small reflections!

Q: *Why is that?*


A: The approximate "theory of small reflections SFG" Contains all of the **significant physical propagation mechanisms** of the two *forward paths*, and **only** the two significant propagation mechanisms of the two forward paths.


Namely:

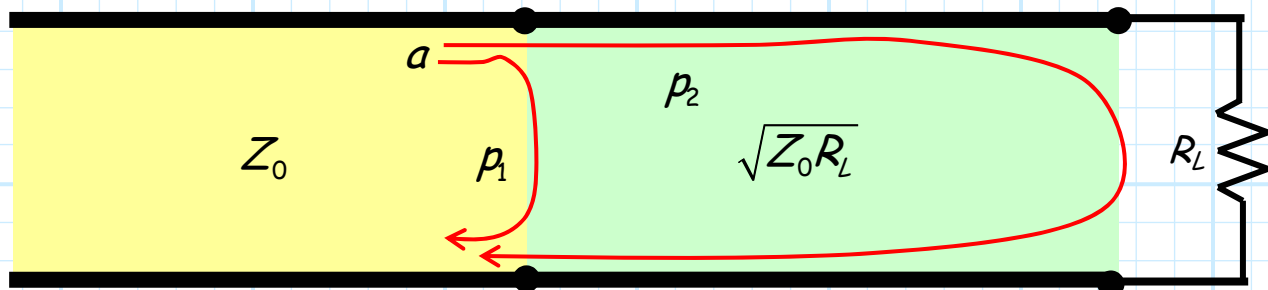1. The **reflection** at the connector (i.e., Γ).
2. The **propagation down** the quarter-wave transmission line ($e^{-j\beta\ell}$), the **reflection** off the load (Γ_L), and the **propagation back up** the quarter-wave transmission line ($e^{-j\beta\ell}$).



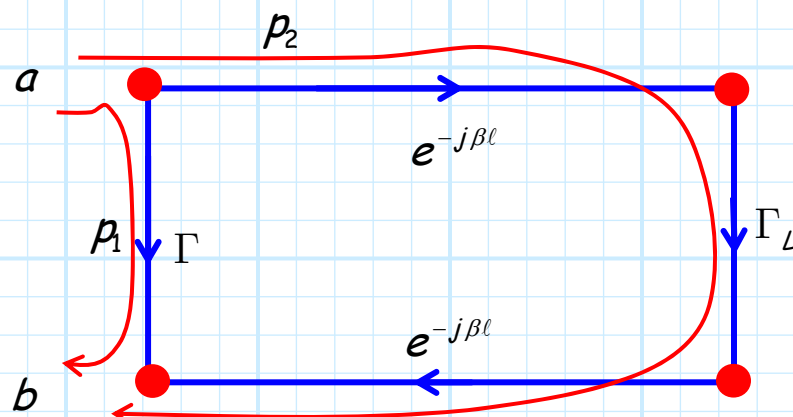The approximate SFG when applying the theory of small reflections!



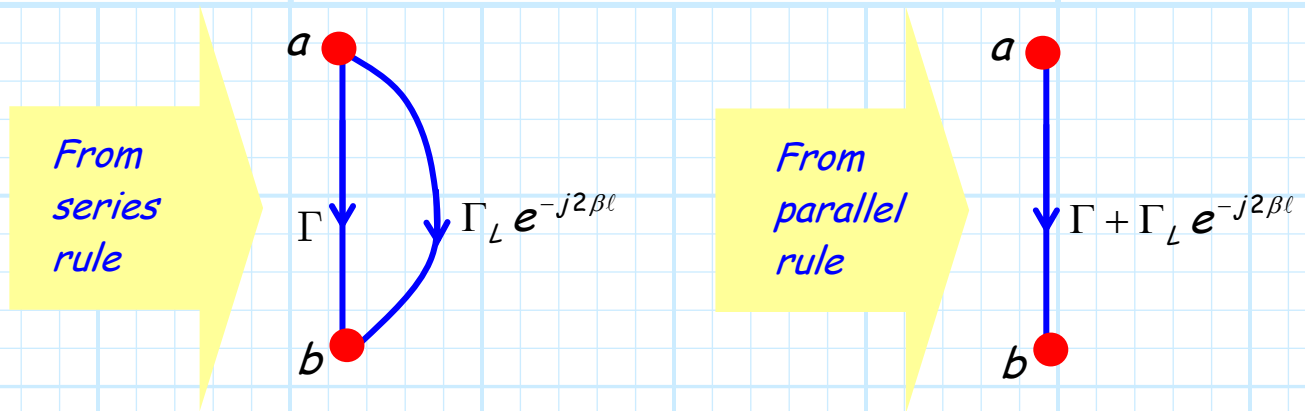

Q: But wait! The quarter-wave transformer is a **matching network**, therefore $\Gamma_{in} = 0$. The **theory of small reflections**, however, provides the **approximate result**:

$$\Gamma_{in} \approx \Gamma + \Gamma_L e^{-j2\beta\ell}$$

Is this **approximation very accurate**? How **close** is this **approximate value** to the correct answer of $\Gamma_{in} = 0$?

A: Let's find out!

Recall that $\Gamma = \Gamma_L$ for a properly designed quarter-wave matching network, and so:

$$\begin{aligned} \Gamma_{in} &\approx \Gamma + \Gamma_L e^{-j2\beta\ell} \\ &= \Gamma_L (1 + e^{-j2\beta\ell}) \end{aligned}$$

Likewise, $\ell = \lambda/4$ (but **only** at the design frequency!) so that:

$$2\beta\ell = 2 \left(\frac{2\pi}{\lambda} \right) \frac{\lambda}{4} = \pi$$

where you of course recall that $\beta = 2\pi/\lambda$!

Thus:

$$\begin{aligned}\Gamma_{in} &\approx \Gamma_L (1 + e^{-j2\beta\ell}) \\ &= \Gamma_L (1 + e^{-j\pi}) \\ &= \Gamma_L (1 - 1) \\ &= 0 \quad !!!\end{aligned}$$

Q: *Wow! The theory of small reflections appears to be a perfect approximation—no error at all!?!*

A: Not so fast.

The **theory of small reflections** most definitely provides an **approximate** solution (e.g., it **ignores** most of the terms of the propagation series, and it **approximates** connector transmission as $T = 1$, when in fact $T \neq 1$).

As a result, the solutions derived using the **theory of small reflections** will—generally speaking—exhibit **some** (hopefully small) **error**.




We just got a bit “**lucky**” for the quarter-wave matching network; the “approximate” result $\Gamma_{in} = 0$ was exact for this one case!

→ The **theory of small reflections** is an **approximate** analysis tool!

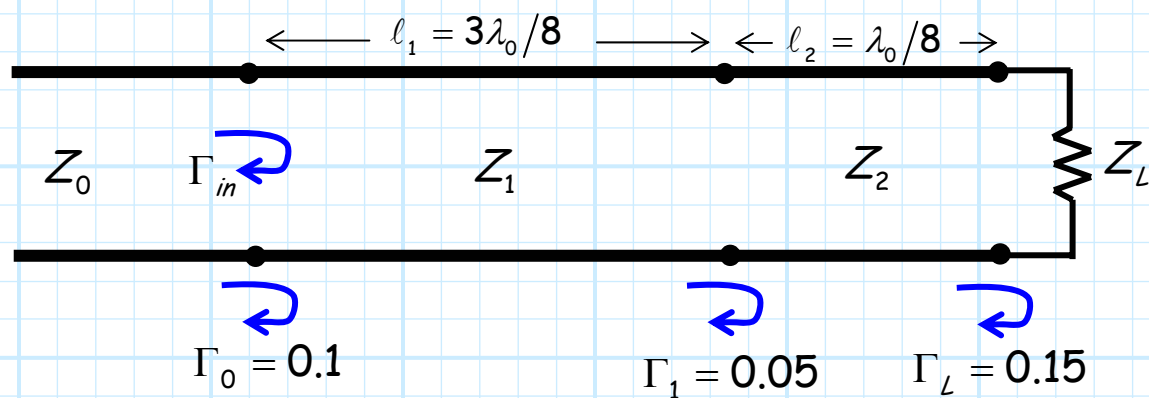Example: The Theory of Small Reflections


Use the **theory of small reflections** to determine a **numeric** value for the **input reflection coefficient** Γ_{in} , at the design frequency ω_0 .



Note that the transmission line sections have **different lengths!**

Solution

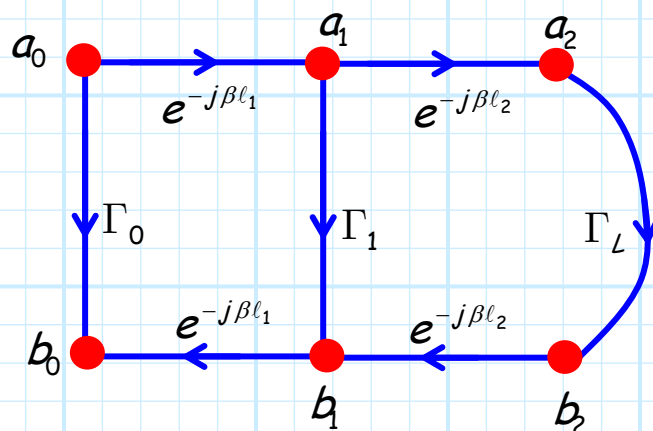Applying the theory of small reflections, the **approximate signal flow graph** of the structure becomes:




$$e^{-j\beta l_1} = e^{-j\left(\frac{2\pi}{\lambda} \frac{3\lambda}{8}\right)} = e^{-j\left(\frac{3\pi}{4}\right)}$$


$$e^{-j\beta l_2} = e^{-j\left(\frac{2\pi}{\lambda} \frac{\lambda}{8}\right)} = e^{-j\left(\frac{\pi}{4}\right)}$$

Note there are three **direct** propagation paths:

Path 1

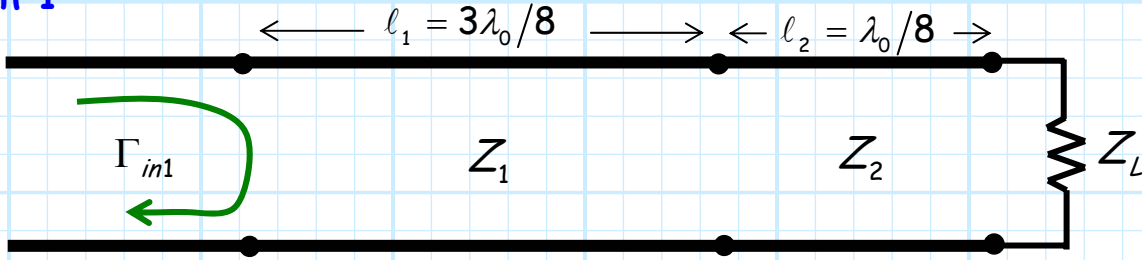


$\therefore \rho_1 = \Gamma_0 = 0.1$

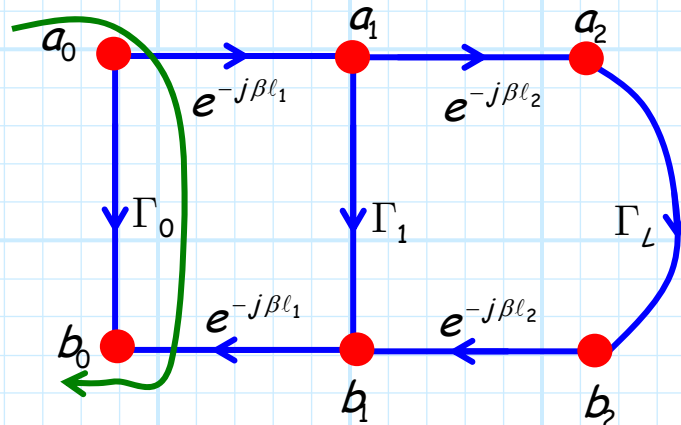


Path 2

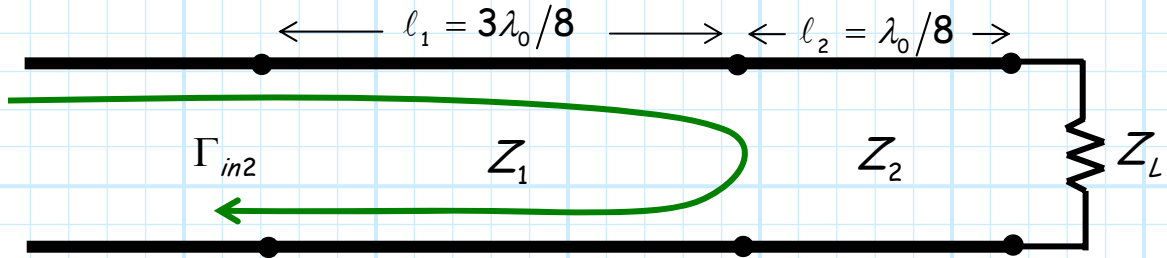This path includes propagation **down** and **back** a transmission line length l_1 !




$$\begin{aligned} \rho_2 &= e^{-j\beta l_1} \Gamma_1 e^{-j\beta l_1} \\ &= e^{-j^{3\pi/4}} 0.05 e^{-j^{3\pi/4}} \\ &= e^{-j^{3\pi/2}} 0.05 \\ &= +j0.05 \end{aligned}$$

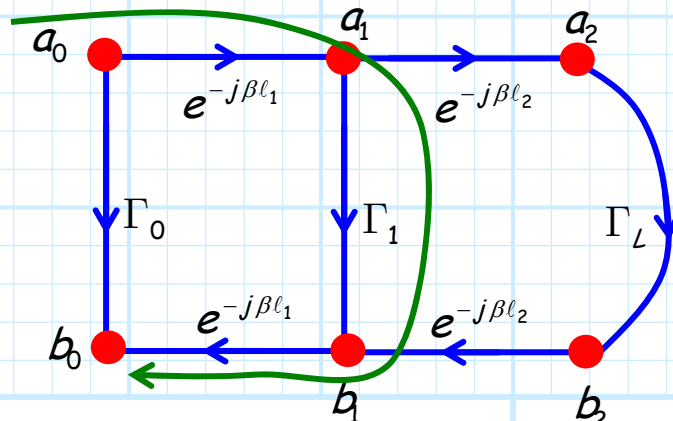


Path 3

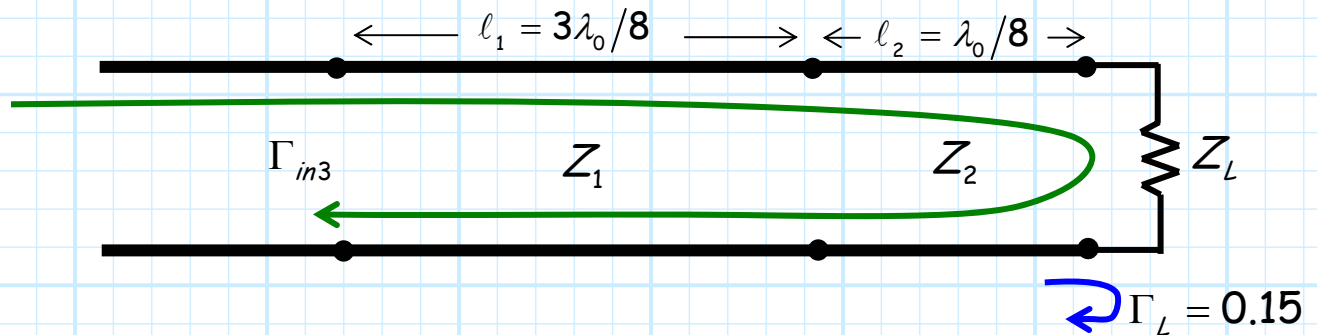This path includes propagation **down** and **back** transmission line lengths of $l_1 + l_2$!


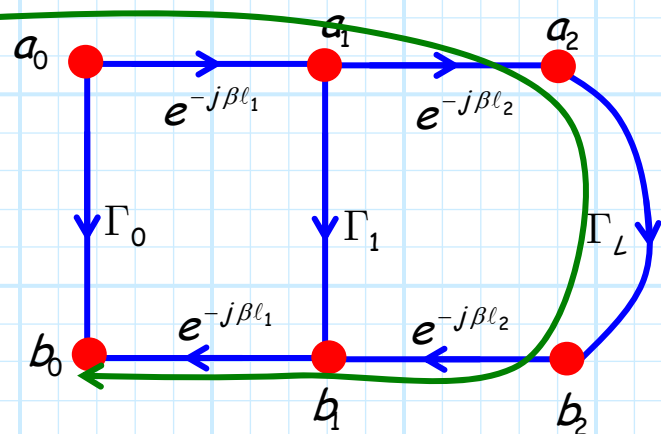
$$\begin{aligned} p_3 &= e^{-j\beta(l_1+l_2)} \Gamma_L e^{-j\beta(l_1+l_2)} \\ &= e^{-j\pi} 0.15 e^{-j\pi} \\ &= e^{-j2\pi} 0.15 \\ &= 0.15 \end{aligned}$$




Thus, using the **theory of small reflections** we can determine approximately the input reflection coefficient:

$$\begin{aligned} \Gamma_{in} &= \frac{b_0}{a_0} \\ &= p_1 + p_2 + p_3 \\ &= 0.1 + j0.05 + 0.15 \\ &= \underline{\underline{0.25 + j0.05}} \end{aligned}$$

The Frequency Response of a Quarter-Wave Matching Network

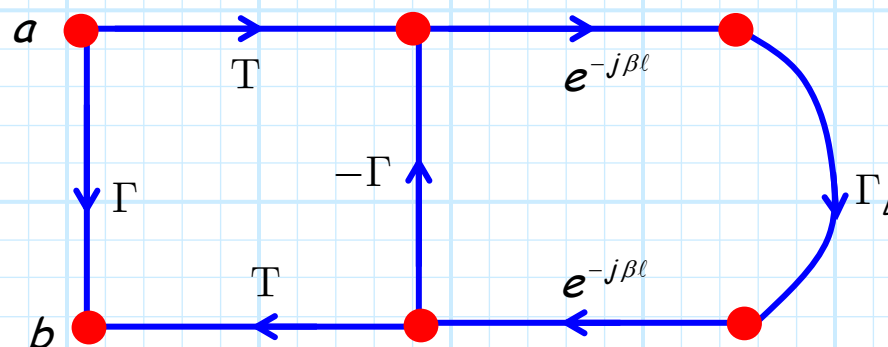Q: *You have once again provided us with **confusing** and perhaps useless information. The quarter-wave matching network has an **exact SFG** of:*




Using our reduction rules, we can quickly conclude that:

$$\Gamma_{in} \doteq \frac{b}{a} = \Gamma + \frac{T^2 \Gamma_L e^{-j2\beta l}}{1 - \Gamma \Gamma_L}$$

*You could have left this **simple** and **precise** analysis **alone**—
BUT NOOO!!*

*You had to foist upon us a long, **rambling** discussion of "the propagation series" and "direct paths" and "the theory of*

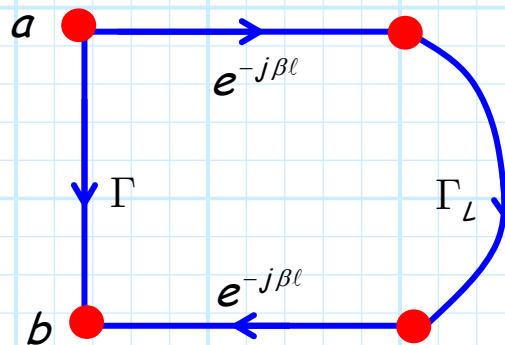small reflections", culminating with the **approximate** (i.e., less accurate!) SFG:



From which we were able to conclude the **approximate** (i.e., less accurate!) result:

$$\Gamma_{in} \doteq \frac{b}{a} = \Gamma + \Gamma_L e^{-j2\beta\ell}$$

The **exact** result was **simple**—and **exact**! Why did you make us determine this **approximate** result?

A: In a word: frequency response*.

Although the exact analysis is **about** as simple to determine as the approximation provided by the theory of small reflections, the **mathematical form** of the result is much simpler to **analyze** and/or **evaluate** (e.g., no fractional terms!).

Q: What exactly would we be analyzing and/or evaluating?

A: The **frequency response** of the matching network, for one thing.

* OK, **two** words.

Remember, all matching networks must be **lossless**, and so must be made of **reactive** elements (e.g., lossless transmission lines). The impedance of every reactive element is a **function of frequency**, and so too then is Γ_{in} .

Say we wish to determine this **function** $\Gamma_{in}(\omega)$.

Q: *Isn't $\Gamma_{in}(\omega) = 0$ for a quarter wave matching network?*

A: Oh my gosh **no!** A properly designed matching network will typically result in a perfect match (i.e., $\Gamma_{in} = 0$) at **one frequency** (i.e., the design frequency). However, if the signal frequency is **different** from this design frequency, then no match will occur (i.e., $\Gamma_{in} \neq 0$).

Recall we discussed this behavior **before**:

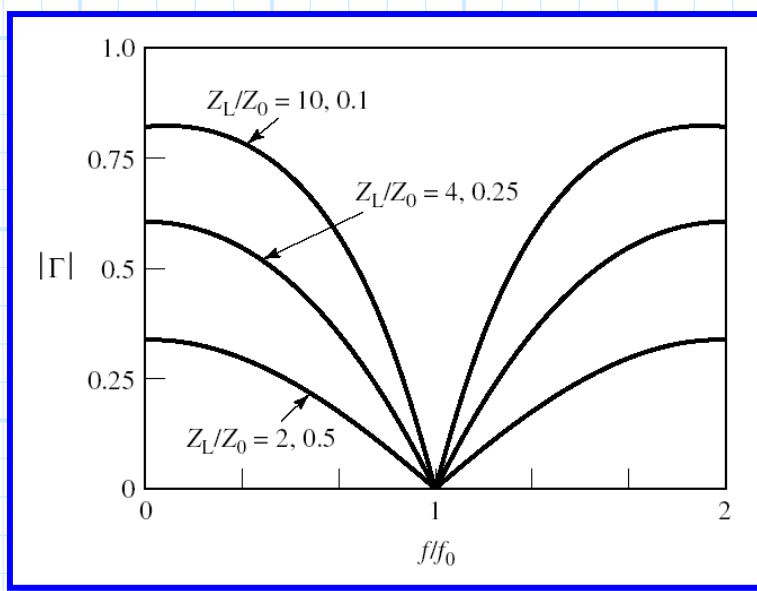


Figure 5.12 (p. 243)

Reflection coefficient magnitude versus frequency for a single-section quarter-wave matching transformer with various load mismatches.

Q: *But why is the result:*

$$\Gamma_{in} = \Gamma + \frac{\Gamma^2 \Gamma_L e^{-j2\beta\ell}}{1 - \Gamma \Gamma_L}$$

or its approximate form:

$$\Gamma_{in} = \Gamma + \Gamma_L e^{-j2\beta\ell}$$

dependent on frequency? I don't see frequency variable ω anywhere in these results!

A: Look closer!

Remember that the value of spatial frequency β (in radians/meter) is dependent on the frequency ω of our eigen function (aka "the signal"):

$$\beta = \left(\frac{1}{v_p} \right) \omega$$

where **you** will recall that v_p is the propagation velocity of a wave moving along a transmission line. This velocity is a constant (i.e., $v_p = 1/\sqrt{LC}$), and so the spatial frequency β is directly proportional to the temporal frequency ω .

Thus, we can rewrite:

$$\beta \ell = \frac{\omega \ell}{v_p} = \omega T$$

Where $T = \ell/v_p$ is the **time** required for the wave to **propagate** a distance ℓ down a transmission line.

As a result, we can write the input reflection coefficient as a function of **spatial frequency** β :

$$\Gamma_{in}(\beta) = \Gamma + \Gamma_L e^{-j2\beta\ell}$$

Or equivalently as a function of **temporal frequency** ω :

$$\Gamma_{in}(\omega) = \Gamma + \Gamma_L e^{-j2\omega T}$$

Frequently, the reflection coefficient is simply written in terms of the **electrical length** θ of the transmission line, which is simply the **difference in relative phase** between the wave at the beginning and end of the length ℓ of the transmission line.

$$\beta \ell = \theta = \omega T$$

So that:

$$\Gamma_{in}(\theta) = \Gamma + \Gamma_L e^{-j2\theta}$$

Note we can simply insert the value $\theta = \beta \ell$ into the expression above to get $\Gamma_{in}(\beta)$, or insert $\theta = \omega T$ into the expression to get $\Gamma_{in}(\omega)$.

Now, we know that $\Gamma = \Gamma_L$ for a properly designed quarter-wave matching network, so the reflection coefficient function can be written as:

$$\Gamma_{in}(\theta) = \Gamma_L (1 + e^{-j2\theta})$$

Note that: $1 = e^{j0} = e^{-j(\theta-\theta)} = e^{-j\theta} e^{+j\theta}$

And that: $e^{-j2\theta} = e^{-j(\theta+\theta)} = e^{-j\theta} e^{-j\theta}$

And so:

$$\begin{aligned} \Gamma_{in}(\theta) &= \Gamma_L (1 + e^{-j2\theta}) \\ &= \Gamma_L (e^{-j\theta} e^{+j\theta} + e^{-j\theta} e^{-j\theta}) \\ &= \Gamma_L e^{-j\theta} (e^{+j\theta} + e^{-j\theta}) \\ &= \Gamma_L e^{-j\theta} (2 \cos\theta) \end{aligned}$$

Where we have used **Euler's equation** to determine that:

$$e^{+j\theta} + e^{-j\theta} = 2 \cos\theta$$

Now, let's determine the **magnitude** of our result:

$$|\Gamma_{in}(\theta)| = |\Gamma_L| |e^{-j\theta}| 2 |\cos\theta| = 2 |\Gamma_L| |\cos\theta|$$

Note that $|\Gamma_{in}(\theta)|$ is **zero-valued** only when $\cos\theta = 0$. This of course occurs when $\theta = \pi/2$:

$$|\Gamma_{in}(\theta)|_{\theta=\pi/2} = 2 |\Gamma_L| |\cos\pi/2| = 0$$

In other words, a **perfect match** occurs when $\theta = \pi/2$!!

Q: *What the heck does this mean?*

A: Remember, $\theta = \beta\ell$. Thus if $\theta = \pi/2$:

$$\ell = \frac{\theta}{\beta} = \frac{\pi/2}{2\pi/\lambda} = \frac{\lambda}{4} \quad !!$$

As we (should have) suspected, the match occurs at the frequency whose wavelength is equal to **four times** the matching (Z_1) transmission line length, i.e. $\lambda = 4\ell$.

In other words, a perfect match occurs at the **frequency** where $\ell = \lambda/4$.

Note the **physical length** ℓ of the transmission line does **not** change with frequency, but the signal **wavelength** does:

$$\lambda = \frac{v_p}{f}$$

Q: *So, at precisely what **frequency** does a quarter-wave transformer with length ℓ provide a **perfect match**?*

A: Recall also that $\theta = \omega T$, where $T = \ell/v_p$. Thus, for $\theta = \pi/2$:

$$\theta = \frac{\pi}{2} = \omega T \quad \Rightarrow \quad \omega = \frac{\pi}{2} \frac{1}{T} = \frac{\pi}{2} \frac{v_p}{\ell}$$

This frequency is called the **design frequency** of the matching network—it's the frequency where a **perfect match** occurs. We denote this as frequency ω_0 , which has wavelength λ_0 , i.e.:

$$\omega_0 = \frac{\pi}{2T} = \pi \frac{v_p}{2\ell} \quad f_0 = \frac{\omega_0}{2\pi} = \frac{1}{4T} = \frac{v_p}{4\ell} \quad \lambda_0 = \frac{v_p}{f_0} = 4v_p T = 4\ell$$

Given this, yet **another way** of expressing $\theta = \beta\ell$ is:

$$\theta = \beta\ell = \frac{\omega}{v_p} \left(\pi \frac{v_p}{2\omega_0} \right) = \pi \frac{\omega}{2\omega_0} = \pi \frac{f}{2f_0}$$

Thus, we conclude:

$$|\Gamma_{in}(f)| = 2 |\Gamma_L| \left| \cos\left(\pi \frac{f}{2f_0}\right) \right|$$

From this result we can determine (approximately) the **bandwidth** of the quarter-wave transformer!

First, we must **define** what we mean by bandwidth. Say the **maximum** acceptable level of the reflection coefficient is value Γ_m . This is an arbitrary value, set by **you** the microwave engineer (typical values of Γ_m range from 0.05 to 0.2).

We will denote the frequencies where this maximum value Γ_m occurs f_m . In other words:

$$|\Gamma_{in}(f = f_m)| = \Gamma_m = 2 |\Gamma_L| \left| \cos\left(\pi \frac{f_m}{2f_0}\right) \right|$$

There are **two solutions** to this equation, the first is:


$$f_{m1} = \frac{2f_0}{\pi} \cos^{-1} \left(\frac{\Gamma_m}{2|\Gamma_L|} \right)$$

And the second:

$$f_{m2} = \frac{2f_0}{\pi} \cos^{-1} \left(-\frac{\Gamma_m}{2|\Gamma_L|} \right)$$

Important note! Make sure $\cos^{-1} x$ is expressed in **radians**!

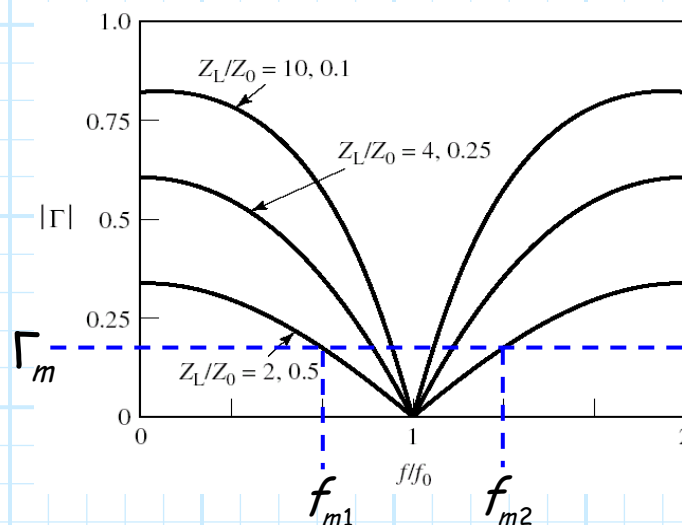
You will find that $f_{m1} < f_0 < f_{m2}$ so, the values f_{m1} and f_{m2} define the **lower** and **upper** limits on matching network **bandwidth**.



All this analysis was brought to you by the “**simple**” **mathematical form** of $\Gamma_{in}(f)$ that resulted from the theory of small reflections!

The Multi-section Transformer

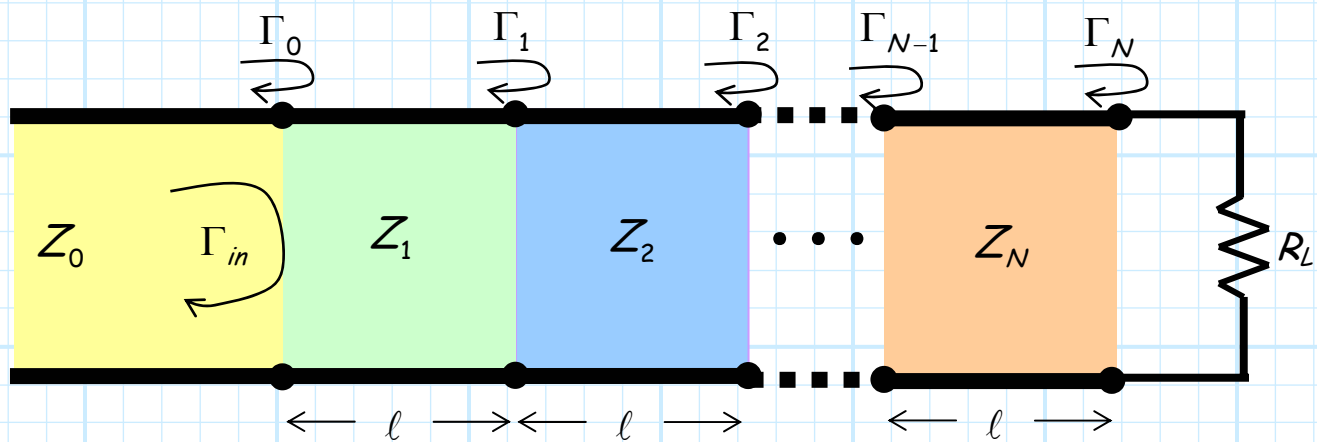Consider a sequence of N transmission line sections; each section has **equal length** ℓ , but **dissimilar** characteristic impedances:



Where the marginal reflection coefficients are:

$$\Gamma_0 \doteq \frac{Z_1 - Z_0}{Z_1 + Z_0} \quad \Gamma_n \doteq \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n} \quad \Gamma_N \doteq \frac{R_L - Z_N}{R_L + Z_N}$$

If the load resistance R_L is **less** than Z_0 , then we should design the transformer such that:

$$Z_0 > Z_1 > Z_2 > Z_3 \cdots > Z_N > R_L$$

Conversely, if R_L is **greater** than Z_0 , then we will design the transformer such that:

$$Z_0 < Z_1 < Z_2 < Z_3 \cdots < Z_N < R_L$$

In other words, we **gradually transition** from Z_0 to R_L !

Note that since R_L is **real**, and since we assume **lossless** transmission lines, all Γ_n will be **real** (this is important!).

Likewise, since we **gradually** transition from one section to another, each value:


$$Z_{n+1} - Z_n$$

will be **small**.


As a result, each marginal reflection coefficient Γ_n will be **real** and have a **small** magnitude.

This is also **important**, as it means that we can apply the "**theory of small reflections**" to analyze this multi-section transformer!

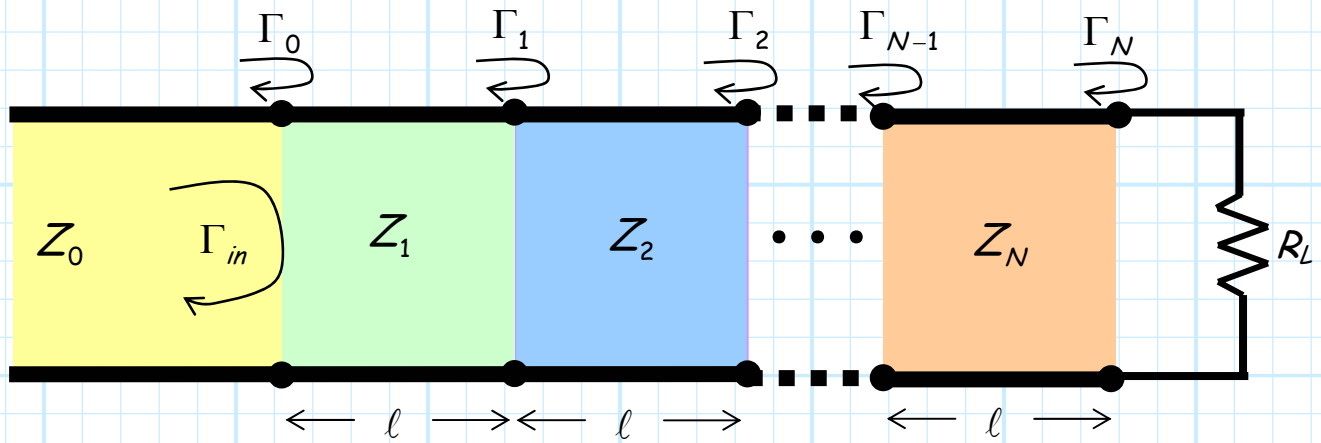The theory of small reflections allows us to **approximate** the input reflection coefficient of the transformer as:



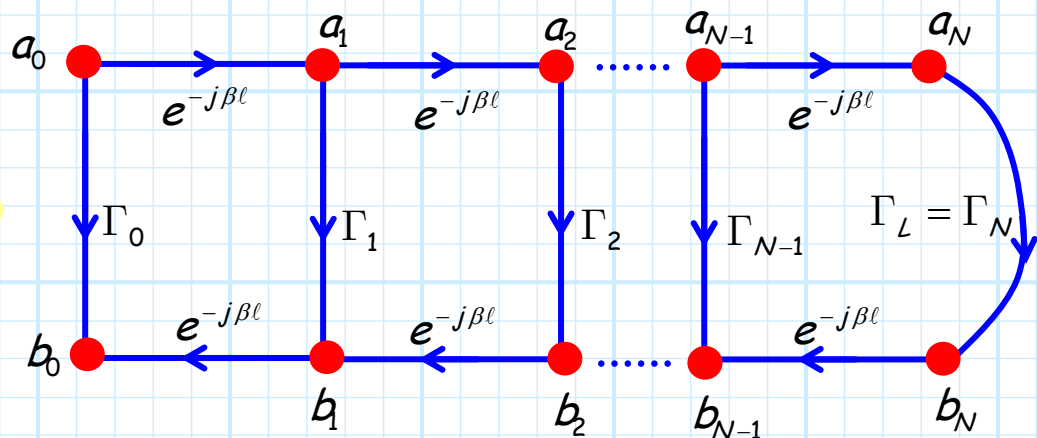The approximate SFG when applying the theory of small reflections!



$$\begin{aligned} \frac{b_0}{a_0} &= \Gamma_{in}(\beta) \\ &\approx \Gamma_0 + \Gamma_1 e^{-j2\beta l} + \Gamma_2 e^{-j4\beta l} + \dots + \Gamma_N e^{-j2N\beta l} \\ &= \sum_{n=0}^N \Gamma_n e^{-j2n\beta l} \end{aligned}$$

We can alternatively express the input reflection coefficient as a function of **frequency** ($\beta l = \omega T$):

$$\begin{aligned} \Gamma_{in}(\omega) &= \Gamma_0 + \Gamma_1 e^{-j2\omega T} + \Gamma_2 e^{-j4\omega T} + \dots + \Gamma_N e^{-j2N\omega T} \\ &= \sum_{n=0}^N \Gamma_n e^{-j(2nT)\omega} \end{aligned}$$

where:

$$T \doteq \frac{\ell}{v_p} = \text{propagation time through 1 section}$$

We see that the function $\Gamma_{in}(\omega)$ is expressed as a **weighted set of N basis functions!** I.E.,

$$\Gamma_{in}(\omega) = \sum_{n=0}^N c_n \Psi(\omega)$$

where:

$$c_n = \Gamma_n \quad \text{and} \quad \Psi(\omega) = e^{-j(2nT)\omega}$$

We find, therefore, that by **selecting** the proper values of basis weights c_n (i.e., the proper values of reflection coefficients Γ_n), we can **synthesize** any function $\Gamma_{in}(\omega)$ of frequency ω , provided that:

1. $\Gamma_{in}(\omega)$ is **periodic** in $\omega = 1/2T$
2. we have sufficient **number** of sections N .

Q: *What function **should** we synthesize?*

A: **Ideally**, we would want to make $\Gamma_{in}(\omega) = 0$ (i.e., the reflection coefficient is zero for all frequencies).

Bad news: this **ideal** function $\Gamma_{in}(\omega) = 0$ would require an **infinite** number of sections (i.e., $N = \infty$)!

Instead, we seek to find an "optimal" function for $\Gamma_{in}(\omega)$, given a finite number of N elements.

Once we determine these optimal functions, we can find the values of coefficients Γ_n (or equivalently, Z_n) that will result in a matching transformer that exhibits this **optimal** frequency response.

To **simplify** this process, we can make the transformer **symmetrical**, such that:

$$\Gamma_0 = \Gamma_N, \quad \Gamma_1 = \Gamma_{N-1}, \quad \Gamma_2 = \Gamma_{N-2}, \quad \dots$$



Note that this **does NOT** mean that:

$$Z_0 = Z_N, \quad Z_1 = Z_{N-1}, \quad Z_2 = Z_{N-2}, \quad \dots$$

We find then that:

$$\Gamma(\omega) = e^{-jN\omega T} \left[\Gamma_0 \left(e^{jN\omega T} + e^{-jN\omega T} \right) + \Gamma_1 \left(e^{j(N-2)\omega T} + e^{-j(N-2)\omega T} \right) + \Gamma_2 \left(e^{j(N-4)\omega T} + e^{-j(N-4)\omega T} \right) + \dots \right]$$

and since:

$$e^{jx} + e^{-jx} = 2 \cos(x)$$

we can write for N even:

$$\Gamma(\omega) = 2 e^{-jN\omega T} \left[\Gamma_0 \cos N\omega T + \Gamma_1 \cos(N-2)\omega T \right. \\ \left. + \dots + \Gamma_n \cos(N-2n)\omega T + \dots + \frac{1}{2} \Gamma_{N/2} \right]$$

whereas for N odd:

$$\Gamma(\omega) = 2 e^{-jN\omega T} \left[\Gamma_0 \cos N\omega T + \Gamma_1 \cos(N-2)\omega T \right. \\ \left. + \dots + \Gamma_n \cos(N-2n)\omega T + \dots + \Gamma_{(N-1)/2} \cos \omega T \right]$$

The remaining **question** then is this: given an optimal and realizable function $\Gamma_{in}(\omega)$, **how** do we determine the necessary number of **sections** N , and **how** do we determine the **values** of all reflection coefficients Γ_n ??