

5.5 - The Theory of Small Reflections

Reading Assignment: *pp. 244-246*

An important and useful **approximation** when considering multi-section matching networks is the **Theory of Small Reflections**.


HO: THE THEORY OF SMALL REFLECTIONS

We can use the Theory of Small Reflections to provide an **approximate** analysis of a multi-section impedance transformer (i.e., multi-section matching network).

HO: THE MULTISECTION TRANSFORMER

The Theory of Small Reflections

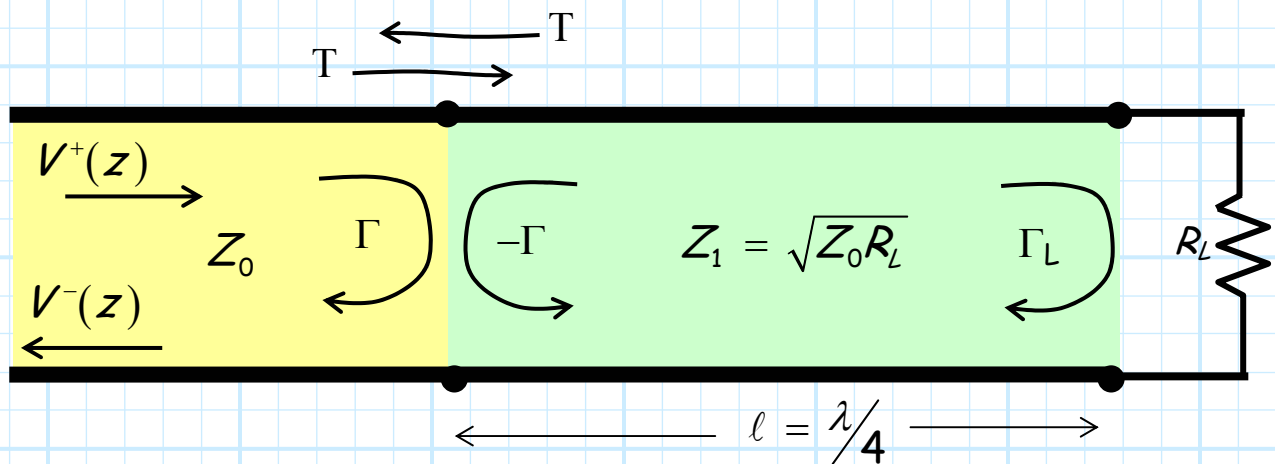Recall that we analyzed a **quarter-wave** transformer using the multiple reflection view point.





We found that the solution could be written as an **infinite** summation of terms:

$$V^-(z) = \sum_{n=1}^{\infty} V_n^-(z)$$



where each term had a specific **physical** interpretation, in terms of reflections, transmissions, and propagations.

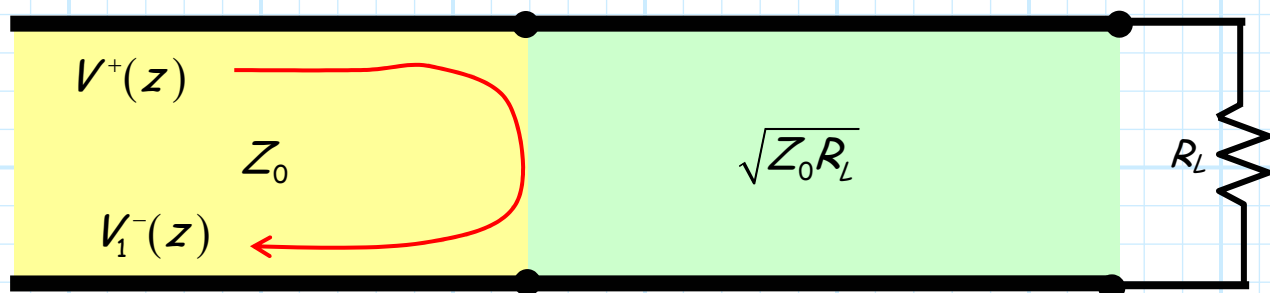For example, the **first** term was $V_1^-(z = -\ell) = \Gamma V^+(z = -\ell)$:




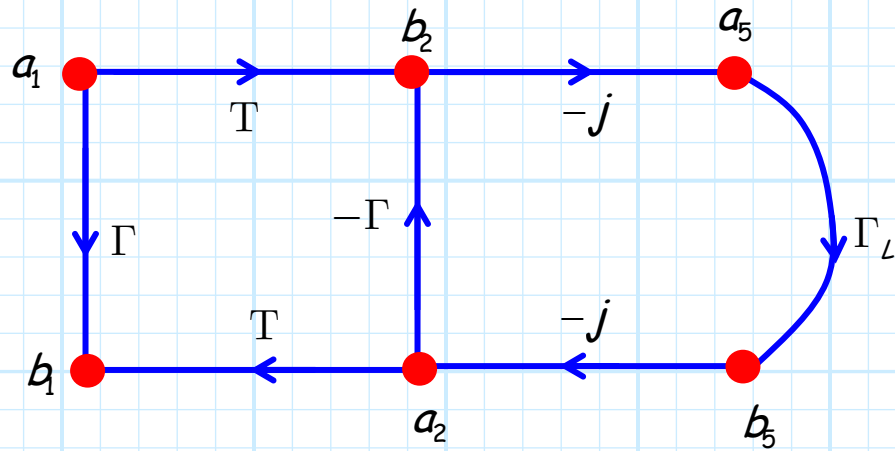


While the second term was:

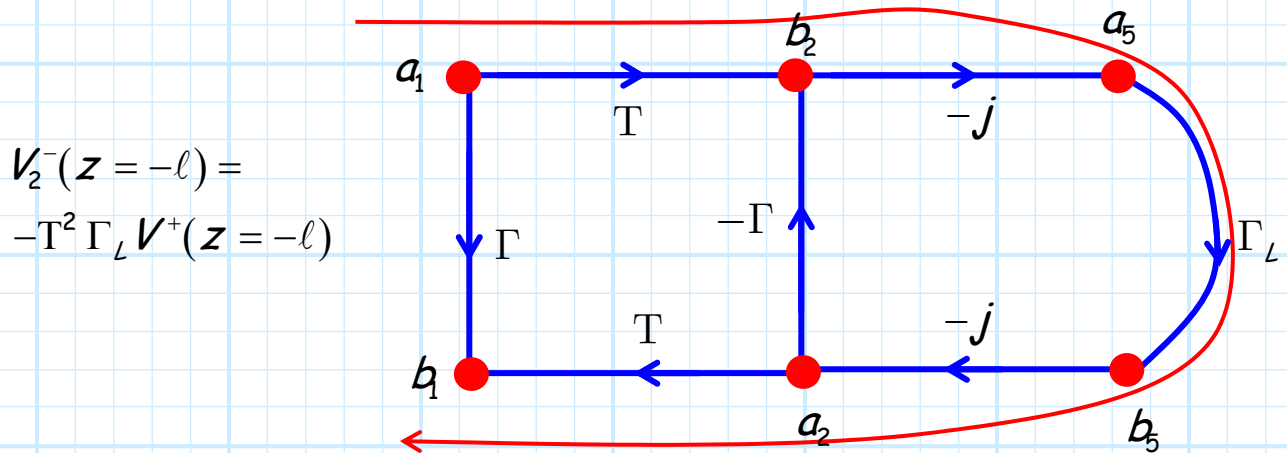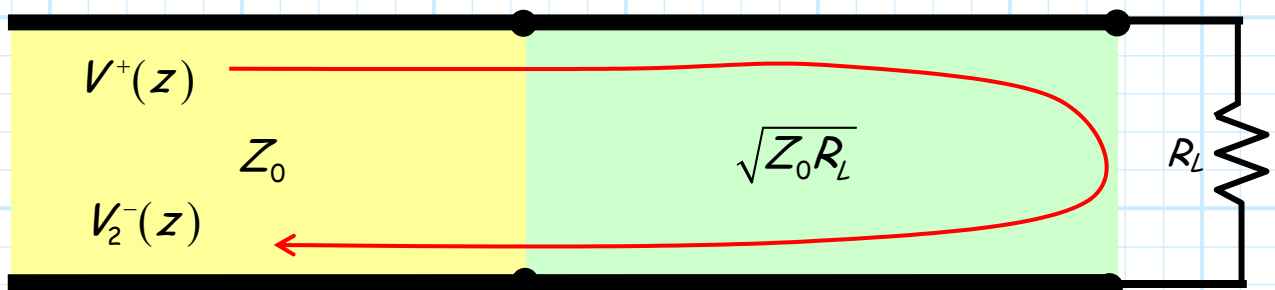

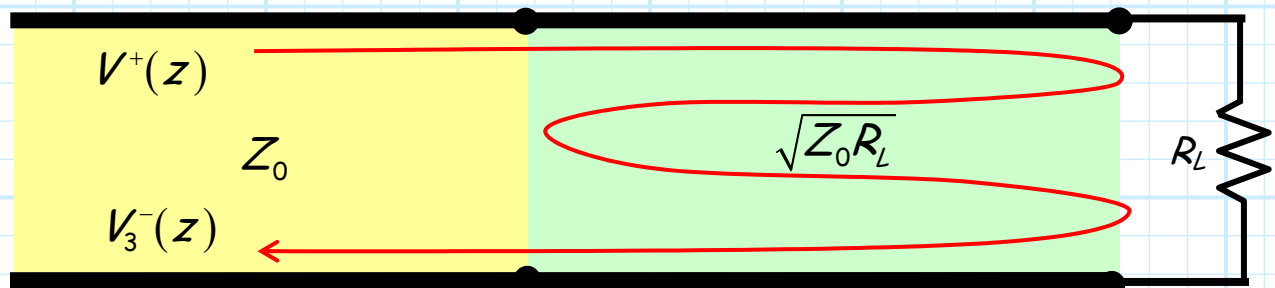Contrast these first two terms with the third term:



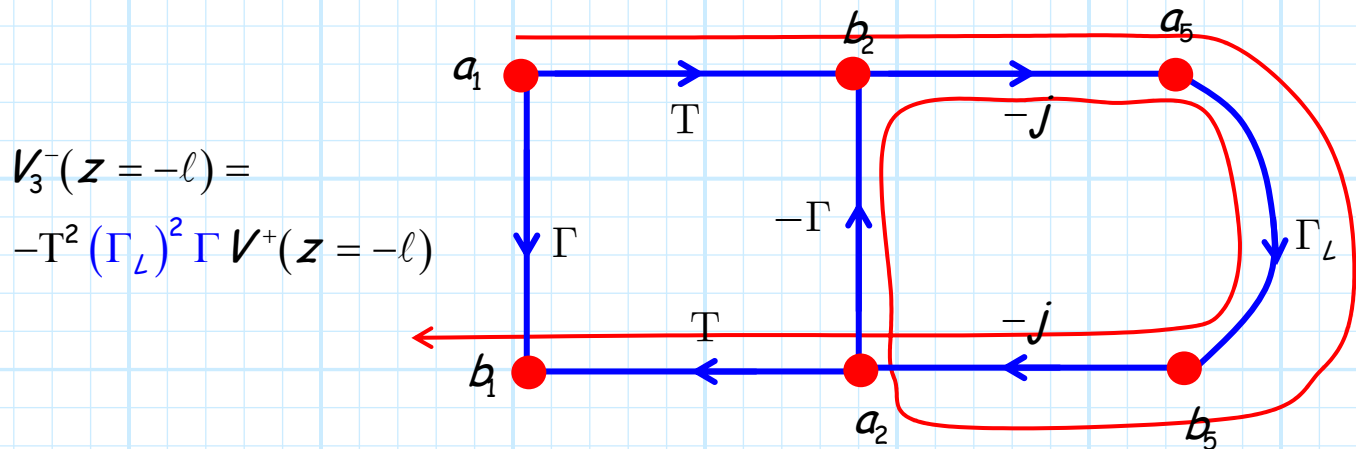

This third term is characterized by **three** reflections, and thus there is a **product** of **three** reflection coefficient values Γ in the term. In fact, **all** other terms in this **infinite** series will likewise describe mechanisms with **multiple** reflections.

This is in **contrast** with the first **two** terms, which exhibit just a **single** reflection coefficient in the product.

Q: *How is this even remotely important?*

A: This is an important observation when we consider the case where Z_0 and R_L are very **close** in value. If this is true, then the value $\sqrt{Z_0 R_L}$ must **likewise** be close in value to both Z_0 and R_L .

As a result, we find that the magnitudes of the marginal **reflection** coefficients Γ and Γ_L will be **very small**:

$$|\Gamma| \ll 1$$

while the magnitudes of the marginal **transmission** coefficient T will be approximately equal to **one**:

$$|T| \approx 1.0$$

This means that all **higher-order** terms (those with multiple reflections and thus with **products** of multiple reflection coefficients) will be **very, very small**:

$$|\Gamma|^n \approx 0 \quad \text{for } n \geq 2$$

The result is that these higher order terms make **little** difference in the final result—the **first two** (single reflection) terms are the **dominant** terms in the infinite series.

Therefore **IF** Z_0 and R_L are very **close** in value, we find that we can approximate the reflected wave using only the first two terms of the infinite series:


$$\begin{aligned} V^-(z = -\ell) &\approx \Gamma V^+(z = -\ell) - T^2 \Gamma_L V^+(z = -\ell) \\ &= (\Gamma - T^2 \Gamma_L) V^+(z = -\ell) \end{aligned}$$

Now, if we likewise apply the approximation that $|T| \approx 1.0$, we conclude for this quarter wave transformer (at the design frequency):


$$\begin{aligned} V^-(z = -\ell) &\approx (\Gamma - T^2 \Gamma_L) V^+(z = -\ell) \\ &\approx (\Gamma - \Gamma_L) V^+(z = -\ell) \end{aligned}$$

This approximation (using only **single reflection** terms) is known as the **Theory of Small Reflections**, and allows us to use the multiple reflection view point as an **analysis** tool (we don't have to consider an infinite number of terms!).

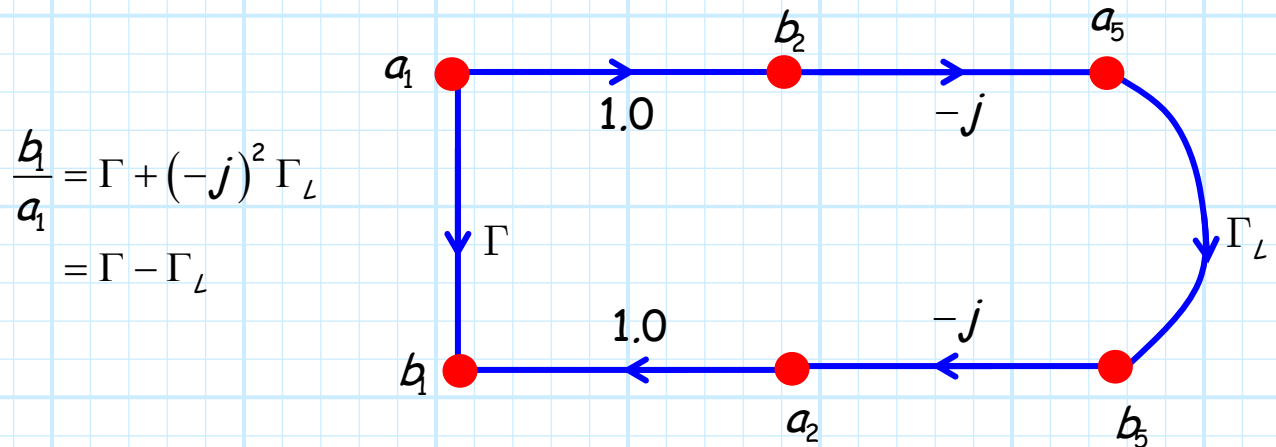Note that this result is provided from the signal flow graph:



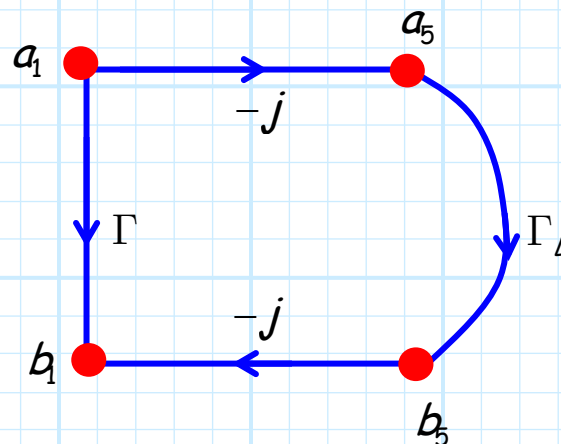
The approximate SFG when applying the theory of small reflections!



However, we can only use this **approximation** when the marginal reflection coefficient at each transition is **very small** (i.e., the change in impedance is **slight**).

The Multi-section Transformer

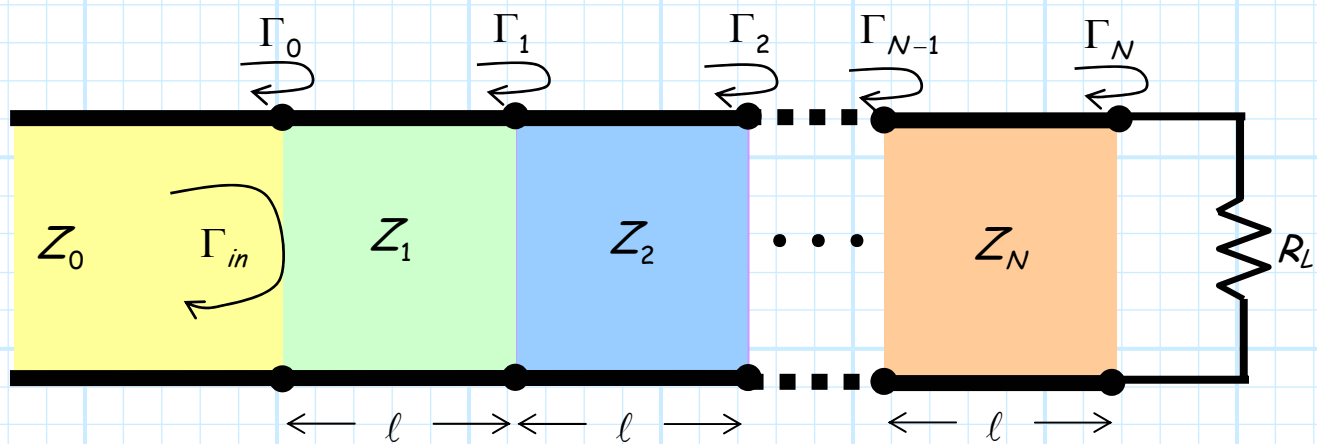Consider a sequence of N transmission line sections; each section has **equal length** ℓ , but **dissimilar** characteristic impedances:



Where the marginal reflection coefficients are:

$$\Gamma_0 \doteq \frac{Z_1 - Z_0}{Z_1 + Z_0} \quad \Gamma_n \doteq \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n} \quad \Gamma_N \doteq \frac{R_L - Z_N}{R_L + Z_N}$$

If the load resistance R_L is **less** than Z_0 , then we should design the transformer such that:

$$Z_0 > Z_1 > Z_2 > Z_3 \cdots > Z_N > R_L$$

Conversely, if R_L is **greater** than Z_0 , then we will design the transformer such that:

$$Z_0 < Z_1 < Z_2 < Z_3 \cdots < Z_N < R_L$$

In other words, we **gradually transition** from Z_0 to R_L !

Note that since R_L is **real**, and since we assume **lossless** transmission lines, all Γ_n will be **real** (this is important!).

Likewise, since we **gradually** transition from one section to another, each value:


$$Z_{n+1} - Z_n$$

will be **small**.


As a result, each marginal reflection coefficient Γ_n will be **real** and have a **small** magnitude.

This is also **important**, as it means that we can apply the "**theory of small reflections**" to analyze this multi-section transformer!

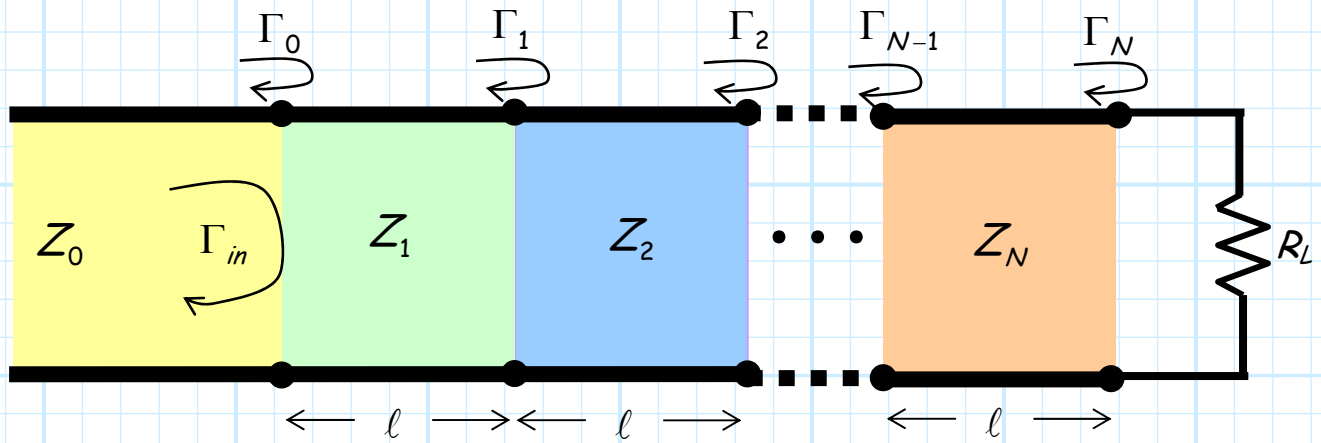The theory of small reflections allows us to **approximate** the input reflection coefficient of the transformer as:



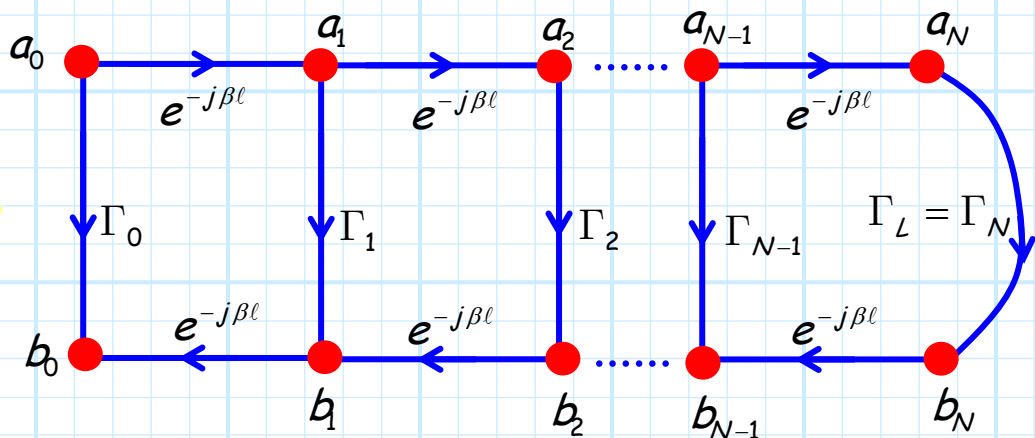The approximate SFG when applying the theory of small reflections!



$$\begin{aligned} \frac{b_0}{a_0} &= \Gamma_{in}(\beta) \\ &\approx \Gamma_0 + \Gamma_1 e^{-j2\beta l} + \Gamma_2 e^{-j4\beta l} + \dots + \Gamma_N e^{-j2N\beta l} \\ &= \sum_{n=0}^N \Gamma_n e^{-j2n\beta l} \end{aligned}$$

Q: So why is the input reflection coefficient a function of β ? Isn't β a constant?

A: Nope. Recall that for a lossless line:

$$\beta = \omega \sqrt{LC}$$

In other words, beta (and thus the electrical length of each transmission line section) is a **function of frequency!** Recall:

$$\beta l = \omega \frac{l}{v_p} = \omega T$$

where:

$$T \doteq \frac{l}{v_p} = \text{propagation time through 1 section}$$

Therefore, we can alternatively express the input reflection coefficient as a function of **frequency**:

$$\begin{aligned} \Gamma_{in}(\omega) &= \Gamma_0 + \Gamma_1 e^{-j2\omega T} + \Gamma_2 e^{-j4\omega T} + \dots + \Gamma_N e^{-j2N\omega T} \\ &= \sum_{n=0}^N \Gamma_n e^{-j(2nT)\omega} \end{aligned}$$

We see that the function $\Gamma_{in}(\omega)$ is expressed as a **weighted set** of N **basis functions**! I.E.,

$$\Gamma_{in}(\omega) = \sum_{n=0}^N c_n \Psi(\omega)$$

where:

$$c_n = \Gamma_n \quad \text{and} \quad \Psi(\omega) = e^{-j(2nT)\omega}$$

We find, therefore, that by **selecting** the proper values of basis weights c_n (i.e., the proper values of reflection coefficients Γ_n), we can **synthesize** any function $\Gamma_{in}(\omega)$ of frequency ω , provided that:

1. $\Gamma_{in}(\omega)$ is **periodic** in $\omega = 1/2T$

2. we have sufficient **number** of sections N .

Q: *What function **should** we synthesize?*

A: **Ideally**, we would want to make $\Gamma_{in}(\omega) = 0$ (i.e., the reflection coefficient is zero for all frequencies).

Bad news: this **ideal** function $\Gamma_{in}(\omega) = 0$ would require an **infinite** number of sections (i.e., $N = \infty$)!

Instead, we seek to find an "**optimal**" function for $\Gamma_{in}(\omega)$, given a **finite** number of N elements.

Once we determine these optimal functions, we can find the values of coefficients Γ_n (or equivalently, Z_n) that will result in a matching transformer that exhibits this **optimal** frequency response.

To **simplify** this process, we can make the transformer **symmetrical**, such that:

$$\Gamma_0 = \Gamma_N, \Gamma_1 = \Gamma_{N-1}, \Gamma_2 = \Gamma_{N-2}, \dots$$



Note that this **does NOT** mean that:

$$Z_0 = Z_N, Z_1 = Z_{N-1}, Z_2 = Z_{N-2}, \dots$$

We find then that:

$$\Gamma(\omega) = e^{-jN\omega T} \left[\Gamma_0 \left(e^{jN\omega T} + e^{-jN\omega T} \right) + \Gamma_1 \left(e^{j(N-2)\omega T} + e^{-j(N-2)\omega T} \right) \right. \\ \left. + \Gamma_2 \left(e^{j(N-4)\omega T} + e^{-j(N-4)\omega T} \right) + \dots \right]$$

and since:

$$e^{jx} + e^{-jx} = 2 \cos(x)$$

we can write for *N* even:

$$\Gamma(\omega) = 2 e^{-jN\omega T} \left[\Gamma_0 \cos N\omega T + \Gamma_1 \cos(N-2)\omega T \right. \\ \left. + \dots + \Gamma_n \cos(N-2n)\omega T + \dots + \frac{1}{2} \Gamma_{N/2} \right]$$

whereas for *N* odd:

$$\Gamma(\omega) = 2 e^{-jN\omega T} \left[\Gamma_0 \cos N\omega T + \Gamma_1 \cos(N-2)\omega T \right. \\ \left. + \dots + \Gamma_n \cos(N-2n)\omega T + \dots + \Gamma_{(N-1)/2} \cos \omega T \right]$$

The remaining **question** then is this: given an optimal and realizable function $\Gamma_{in}(\omega)$, **how** do we determine the necessary number of **sections** *N*, and **how** do we determine the **values** of all reflection coefficients Γ_n ??