Reading Assignment: pp. 246-250

One way to maximize bandwidth is to construct a multisection matching network with a function $\Gamma(f)$ that is maximally flat.

Q: Maximally flat? What kind of function is maximally flat?

This function maximizes bandwidth by providing a solution that is **maximally flat**.

A: HO: Maximally Flat Functions

1. We can build a multisection matching network such that the function $\Gamma(f)$ is a **binomial function**.

2. The binomial function is maximally flat.

Q: Meaning?

A: Meaning the function $\Gamma(f)$ is maximally flat \rightarrow a wideband solution!

HO: The Binomial Multi-section Matching Transformer

1/5

Maximally Flat Functions

Consider some function f(x). Say that we know the value of the function **at** x=1 is 5:

$$f(x=1)=5$$

This of course says something about the function f(x), but it doesn't tell us much!

We can additionally determine the **first derivative** of this function, and likewise evaluate this derivative **at** x = 1. Say that this value turns out to be **zero**:

$$\frac{df(x)}{dx}\bigg|_{x=1} = 0$$

Note that this does not mean that the derivative of f(x) is equal to zero, it merely means that the derivative of f(x) is zero at the value x = 1. Presumably, df(x)/dx is non-zero at other values of x.

So, we now have **two** pieces of information about function f(x). We can add to this list by continuing to take higher-order derivatives and evaluating them at the single point x=1.

Let's say that the values of **all** the derivatives (at x=1) turn out to have a zero value:

$$\frac{df^{n}(x)}{dx^{n}}\Big|_{x=1} = 0 \text{ for } n = 1, 2, 3, \dots, \infty$$

We say that this function is **completely flat** at the point x=1. Because **all** the derivatives are zero at x=1, it means that the function cannot change in value from that at x=1.

In other words, if the function has a value of 5 at x=1, (i.e., f(x=1)=5), then the function **must** have a value of 5 at **all** x!

The function f(x) thus must be the **constant** function:

$$f(x) = 5$$

Now let's consider the following **problem**—say some function f(x) has the following form:

$$f(x) = a x^3 + b x^2 + c x$$

We wish to **determine** the values *a*, *b*, and *c* so that:

$$f(x=1)=5$$

and that the value of the function f(x) is as **close** to a value of 5 as possible in the region where x = 1.

In other words, we want the function to have the value of 5 at x=1, and to change from that value as slowly as possible as we

"move" from x=1.

Q: Don't we simply want the **completely** flat function f(x) = 5?

A: That would be the **ideal** function for this case, but notice that solution is **not** an option. Note there are **no** values of *a*, *b*, and *c* that will make:

$$ax^3+bx^2+cx=5$$

for all values x.

Q: So what do we do?

A: Instead of the completely flat solution, we can find the maximally flat solution!

The **maximally flat** solution comes from determining the values *a*, *b*, and *c* so that as many derivatives **as possible** are **zero** at the point x=1.

For example, we wish to make the **first derivate** equal to zero at x=1:

$$0 = \frac{df(x)}{dx} \bigg|_{x=1}$$
$$= (3ax^{2} + 2bx + c)$$
$$= 3a + 2b + c$$

Likewise, we wish to make the **second derivative** equal to zero at x=1:

$$0 = \frac{d^2 f(x)}{d x^2} \bigg|_{x=1}$$
$$= (6ax + 2b) \bigg|_{x=1}$$
$$= 6a + 2b$$

Here we must **stop** taking derivatives, as our solution only has **three degrees of design freedom** (i.e., 3 unknowns *a*, *b*, *c*).

Q: But we only have taken **two** derivatives, can't we take **one more**?

A: No! We already have a **third** "design" equation: the value of the function **must** be 5 at x=1:

$$5 = f(x = 1)$$

= $a(1)^{3} + b(1)^{2} + c(1)$
= $a + b + c$

So, we have used the **maximally flat** criterion at x=1 to generate **three** equations and **three** unknowns:

$$0 = 3a + 2b + c$$

0 = 6*a* + 2*b*

Solving, we find: *a* = 5 *b* = -15 *c* = 15 Therefore, the maximally flat function (at x=1) is: $f(x) = 5x^3 - 15x^2 + 15x$ 10 7.5 f(x) 5 2.5 0 0.5 1 1.5 2 0 Х

<u>The Binomial Multi-</u> <u>Section Transformer</u>

Recall that a **multi-section matching network** can be described using the theory of small reflections as:

$$\Gamma_{in}(\omega) = \Gamma_0 + \Gamma_1 e^{-j2\omega T} + \Gamma_2 e^{-j4\omega T} + \dots + \Gamma_N e^{-j2N\omega T}$$
$$= \sum_{n=0}^{N} \Gamma_n e^{-j2n\omega T}$$

where:

 $T \doteq \frac{\ell}{\nu_p}$ = propagation time through 1 section

Note that for a multi-section transformer, we have Ndegrees of design freedom, corresponding to the Ncharacteristic impedance values Z_n .

Q: What should the values of Γ_n (i.e., Z_n) be?

A: We need to define Nindependent design equations, which we can then use to solve for the Nvalues of characteristic impedance Z_n .

First, we start with a single **design frequency** ω_0 , where we wish to achieve a **perfect** match:

$$\Gamma_{in}\left(\omega=\omega_{0}\right)=\mathbf{0}$$

That's just one design equation: we need N - 1 more!

These addition equations can be selected using **many** criteria—one such criterion is to make the function $\Gamma_{in}(\omega)$ **maximally flat** at the point $\omega = \omega_0$.

To accomplish this, we first consider the **Binomial Function**:

$$\Gamma(\theta) = \mathcal{A} \left(\mathbf{1} + \boldsymbol{e}^{-j2\theta} \right)^{h}$$

This function has the desirable **properties** that:

$$\Gamma\left(\theta = \pi/2\right) = \mathcal{A}\left(1 + e^{-j\pi}\right)^{N}$$
$$= \mathcal{A}\left(1 - 1\right)^{N}$$
$$= 0$$

and that:

$$\frac{d^n \Gamma(\theta)}{d\theta^n} \bigg|_{\theta = \frac{\pi}{2}} = 0 \text{ for } n = 1, 2, 3, \cdots, N - 2$$

In other words, this Binomial Function is **maximally flat** at the point $\theta = \pi/2$, where it has a value of $\Gamma(\theta = \pi/2) = 0$.

Q: So? What does **this** have to do with our multi-section matching network?

A: Let's expand (multiply out the Nidentical product terms) of the Binomial Function:

$$\Gamma(\theta) = \mathcal{A} \left(\mathbf{1} + e^{-j2\theta} \right)^{N}$$
$$= \mathcal{A} \left(\mathcal{C}_{0}^{N} + \mathcal{C}_{1}^{N} e^{-j2\theta} + \mathcal{C}_{2}^{N} e^{-j4\theta} + \mathcal{C}_{3}^{N} e^{-j6\theta} + \dots + \mathcal{C}_{N}^{N} e^{-j2N\theta} \right)$$

where:

$$C_n^N \doteq \frac{N!}{(N-n)!\,n!}$$

Compare this to an **N-section** transformer function:

$$\Gamma_{in}(\omega) = \Gamma_0 + \Gamma_1 e^{-j2\omega T} + \Gamma_2 e^{-j4\omega T} + \dots + \Gamma_N e^{-j2N\omega T}$$

and it is obvious the two functions have **identical** forms, **provided** that:

$$\Gamma_n = \mathcal{A} \, \mathcal{C}_n^N$$
 and $\omega T = \theta$

Moreover, we find that this function is very **desirable** from the standpoint of the a matching network. Recall that $\Gamma(\theta) = 0$ at $\theta = \pi/2$ --a **perfect** match!

Additionally, the function is maximally flat at $\theta = \pi/2$, therefore $\Gamma(\theta) \approx 0$ over a wide range around $\theta = \pi/2$ --a wide bandwidth!

Q: But how does $\theta = \pi/2$ relate to frequency ω ?

A: Remember that $\omega T = \theta$, so the value $\theta = \pi/2$ corresponds to the frequency:

$$\omega_0 = \frac{1}{T}\frac{\pi}{2} = \frac{\nu_p}{\ell}\frac{\pi}{2}$$

This (ω_0) is our **design** frequency—the frequency where we have a **perfect** match.

Note that the length ℓ has an interesting **relationship** with this frequency:

 $\ell = \frac{\nu_{p}}{\omega_{0}} \frac{\pi}{2} = \frac{1}{\beta_{0}} \frac{\pi}{2} = \frac{\lambda_{0}}{2\pi} \frac{\pi}{2} = \frac{\lambda_{0}}{4}$

In other words, a **Binomial** Multi-section matching network will have a **perfect** match at the frequency where the section lengths ℓ are a **quarter wavelength**!

Thus, we have our first design rule:

Set section lengths ℓ so that they are a quarterwavelength $(\lambda_0/4)$ at the design frequency ω_0 .

Q: I see! And then we select all the values Z_n such that $\Gamma_n = A C_n^N$. But wait! **What** is the value of **A** ??

 $\omega = 0$.

A: We can determine this value by evaluating a **boundary** condition!

Specifically, we can **easily** determine the value of $\Gamma(\omega)$ at

$$Z_{0} \qquad Z_{in} \qquad Z_{1} \qquad Z_{2} \qquad \cdots \qquad Z_{N}$$


$$\leftarrow \qquad \ell \rightarrow \leftarrow \qquad \ell \rightarrow \qquad \leftarrow \qquad \ell \rightarrow$$

Note as ω approaches **zero**, the electrical length $\beta \ell$ of each section will **likewise** approach zero. Thus, the input impedance Z_{in} will simply be equal to R_L as $\omega \to 0$.

As a result, the input reflection coefficient $\Gamma(\omega = 0)$ must be:

$$\Gamma(\omega = 0) = \frac{Z_{in}(\omega = 0) - Z_0}{Z_{in}(\omega = 0) + Z_0}$$
$$= \frac{R_L - Z_0}{R_L + Z_0}$$

However, we likewise know that:

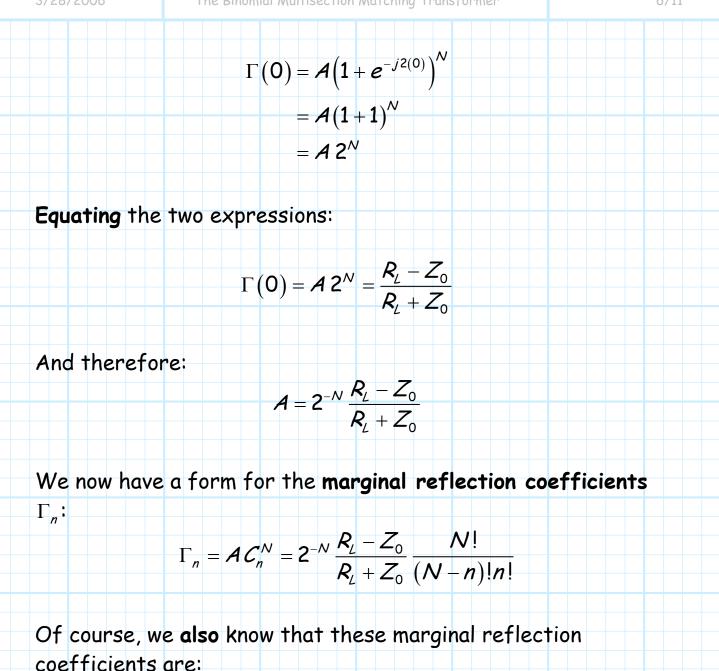

$$\Gamma_n = \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n}$$

Now, we know that the values of Z_{n+1} and Z_n are typically very close, such that $Z_{n+1} - Z_n$ is small. It turns out for this case that we can use a helpful approximation for the marginal reflection coefficient:

$$\Gamma_{n} = \frac{Z_{n+1} - Z_{n}}{Z_{n+1} + Z_{n}} \approx \frac{1}{2} / n \left(\frac{Z_{n-1}}{Z_{n}} \right) \quad (\text{for } |\Gamma_{n}| \text{ small})$$
Therefore we can conclude:

$$\Gamma_{n} = \frac{1}{2} / n \left(\frac{Z_{n+1}}{Z_{n}} \right) = 2 \frac{N}{R_{L}} \frac{R_{L} - Z_{0}}{Z_{0}} C_{n}^{N}$$
Solving for Z_{n+1} , we find:

$$Z_{n+1} = Z_{n} \exp \left[2^{-N+1} \frac{R_{L} - Z_{0}}{R_{L} + Z_{0}} C_{n}^{N} \right]$$
We can further simplify this with yet another approximation:

$$Z_{n,1} \approx Z_{n} \exp \left[2^{-N} / n \left(\frac{R_{L}}{Z_{0}} \right) C_{n}^{N} \right]$$
This is our second design rule. Note it is an iterative rule—we determine Z_{l} from Z_{0} , Z_{2} from Z_{l} , and so forth.
The result is a maximally flat, Binomial reflection coefficient function $\Gamma(\omega)$.



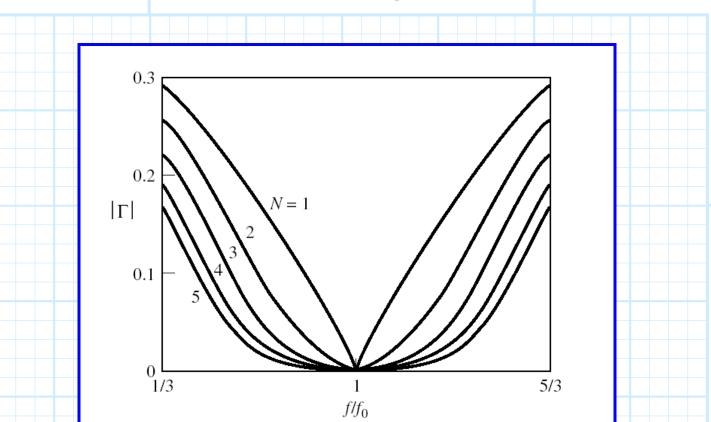


Figure 5.15 (p. 250)

Reflection coefficient magnitude versus frequency for multisection **binomial** matching transformers of Example 5.6 Z_L = 50 Ω and Z_0 = 100 Ω .

Note that as we **increase** the number of **sections**, the matching **bandwidth** increases.

Q: Can we determine the value of this bandwidth?

A: Sure! But we first must **define** what we mean by bandwidth.

As we move from the design (perfect match) frequency f_0 the value $|\Gamma(f)|$ will increase. At some frequency (f_m , say) the magnitude of the reflection coefficient will increase to some

unacceptably high value (Γ_m , say). At that point, we **no longer** consider the device to be matched.

Note there are **two** values of frequency f_m —one value less than design frequency f_0 , and one value greater than design frequency f_0 . These two values define the **bandwidth** of the matching network.

Q: So what is the **numerical** value of Γ_m ?

A: I don't know—it's up to you to decide!

Every engineer must determine what **they** consider to be an acceptable match (i.e., decide Γ_m). This decision depends on the **application** involved, and the **specifications** of the overall microwave system being designed.

However, we **typically** set Γ_m to be 0.2 or less.

Q: OK, after we have selected Γ_m , can we determine the **two** frequencies f_m ?

A: Sure! We just have to do a little algebra.

We start by rewriting the **Binomial function**:

$$\Gamma(\theta) = \mathcal{A} \left(1 + e^{-j2\theta} \right)^{N}$$
$$= \mathcal{A} e^{-jN\theta} \left(e^{+j\theta} + e^{-j\theta} \right)^{N}$$
$$= \mathcal{A} e^{-jN\theta} \left(e^{+j\theta} + e^{-j\theta} \right)^{N}$$
$$= \mathcal{A} e^{-jN\theta} \left(2\cos\theta \right)^{N}$$

Now, we take the **magnitude** of this function:

$$|\Gamma(\theta)| = 2^{N} |A| |e^{-jN\theta} ||\cos\theta|^{N}$$
$$= 2^{N} |A| |\cos\theta|^{N}$$

Now, we define the values θ where $|\Gamma(\theta)| = \Gamma_m$ as θ_m . I.E., :

$$\Gamma_{m} = \left| \Gamma \left(\theta = \theta_{m} \right) \right|$$
$$= 2^{N} \left| \mathcal{A} \right| \left| \cos \theta_{m} \right|^{N}$$

We can now solve for θ_m (in **radians**!) in terms of Γ_m :

$$\theta_m = \cos^{-1} \left| \frac{1}{2} \left(\frac{\Gamma_m}{|\mathcal{A}|} \right)^{1/N} \right|$$

Note that there are two solutions to the above equation (one greater that $\pi/2$ and one less than $\pi/2$)!

Now, we can convert the values of θ_m into specific frequencies.

Jim Stiles

Recall that $\omega T = \theta$, therefore:

$$\omega_m = \frac{1}{T} \theta_m = \frac{v_p}{\ell} \theta_m$$

But recall also that $\ell = \lambda_0/4$, where λ_0 is the wavelength at the **design frequency** f_0 (not f_m !), and where $\lambda_0 = v_p/f_0$.

Thus we can conclude:

$$\omega_m = \frac{\mathbf{v}_p}{\ell} \,\theta_m = \frac{\mathbf{4v}_p}{\lambda_0} \,\theta_m = (\mathbf{4f}_0) \,\theta_m$$

where θ_m is expressed in **radians**. Thus we can conclude that:

