

7.5 - The Quadrature Hybrid

Reading Assignment: pp. 333-336

There are **two** different types of ideal **4-port 3dB** couplers: the **symmetric** solution and the **anti-symmetric** solution. The symmetric solution is called the **Quadrature Hybrid**.

HO: THE QUADRATURE HYBRID

The Quadrature Hybrid possesses **D_4 symmetry**—it has **two** planes of bilateral reflection symmetry.

Q: *So?*

A: This fact leads to circuit analysis procedure that is an extension of odd-even mode analysis. **Instead** of 2 modes (odd-even), the circuit can be expressed as a superposition of **4 modes!**

Q: *Four modes?! That's **twice** as many as 2 modes; that sounds like twice as much work!*

A: Nope! It turns out that analyzing each of the four modes is simple and direct—much easier than analyzing the odd and/or even mode. As a result, this 4-mode analysis is much easier than the odd-even mode analysis.

HO: A QUAD-MODE ANALYSIS OF THE QUADRATURE HYBRID

The 90° Hybrid Coupler

The 90° Hybrid Coupler is a 4-port device, otherwise known as the **quadrature** coupler or **branch-line** coupler. Its scattering matrix (ideally) has the **symmetric** solution for a matched, lossless, reciprocal 4-port device:


$$\mathbf{S} = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$

However, for **this** coupler we find that

$$\alpha = \beta = \frac{1}{\sqrt{2}}$$

Therefore, the **scattering matrix** of a quadrature coupler is:
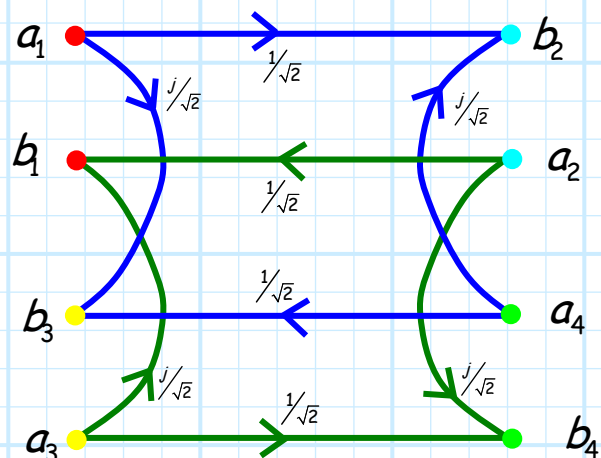
$$\mathbf{S} = \begin{bmatrix} 0 & 1/\sqrt{2} & j/\sqrt{2} & 0 \\ 1/\sqrt{2} & 0 & 0 & j/\sqrt{2} \\ j/\sqrt{2} & 0 & 0 & 1/\sqrt{2} \\ 0 & j/\sqrt{2} & 1/\sqrt{2} & 0 \end{bmatrix}$$



It is evident that, just as with the directional coupler, the ports are **matched** and the device is **lossless**. Note also, that if a signal is incident on one port only, then there will be a port from which **no** power will exit (i.e., an **isolation** port).

Unlike the directional coupler, the power that flows into the input port will be **evenly** divided between the two non-isolated ports.

For example, if 10 mW is incident on port 3 (and all other ports are matched), then 5 mW will flow out of **both** port 1 and port 4, while no power will exit port 2 (the isolated port).

Note however, that although the **magnitudes** of the signals leaving ports 1 and 4 are **equal**, the relative **phase** of the two signals are separated by **90 degrees** ($e^{j\pi/2} = j$).

We find, therefore, that if in **real** terms the voltage out of port 1 is:

$$v_1(z, t) = \frac{|V_{03}|}{\sqrt{2}} \cos(\omega_0 t + \beta z)$$


then the signal from port 4 will be:

$$v_4(z, t) = \frac{|V_{03}|}{\sqrt{2}} \sin(\omega_0 t + \beta z)$$

There are **many** useful applications where we require both the **sine** and **cosine** of a signal!


Q: *But how do we construct this device?*

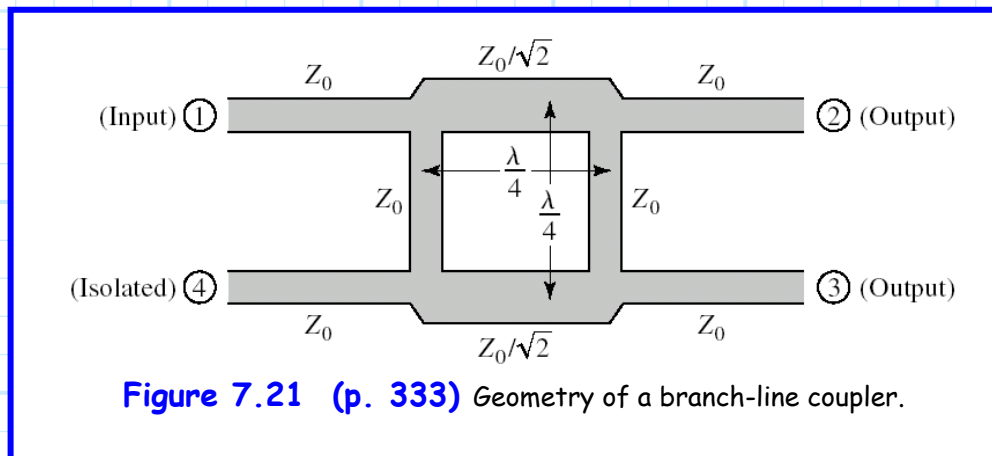A: Similar to the Wilkinson power divider, we construct a quadrature hybrid with **quarter-wavelength** sections of transmission lines.



Q: *Wow! How can we analyze such a complex circuit?*

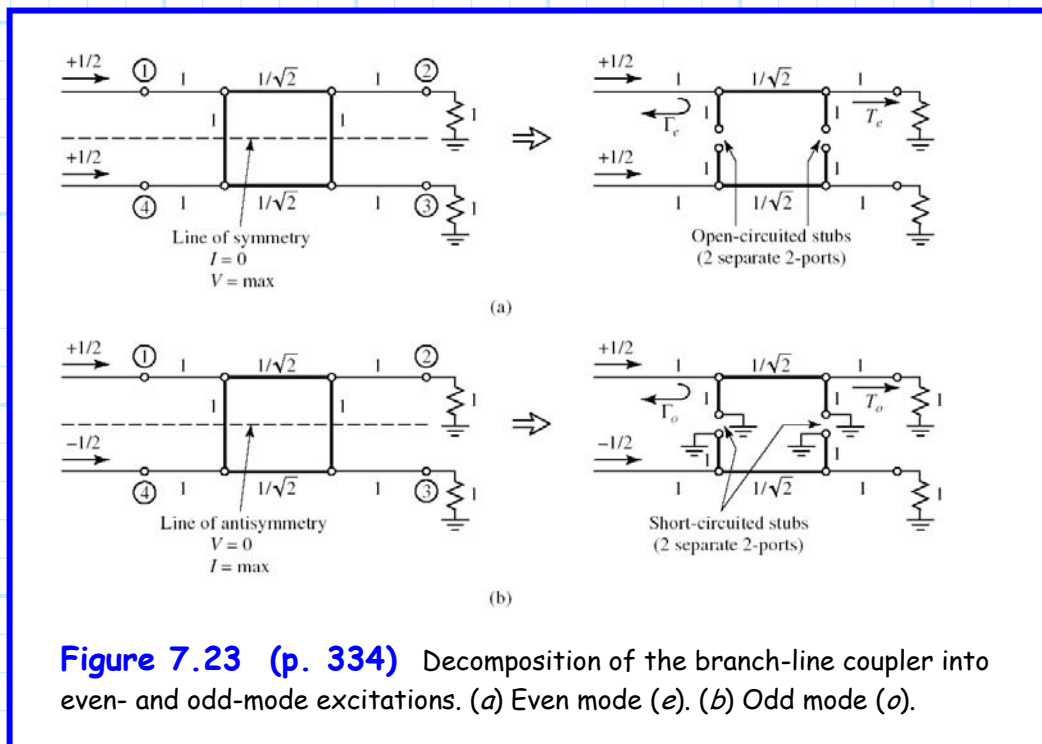A: Note that this circuit is **symmetric**—we can use **odd/even mode analysis**!



The **details** of this odd/even mode analysis are provide on pages 333-335 of **your** textbook.

Note that the $\lambda/4$ structures make the quadrature hybrid an inherently **narrow-band** device.


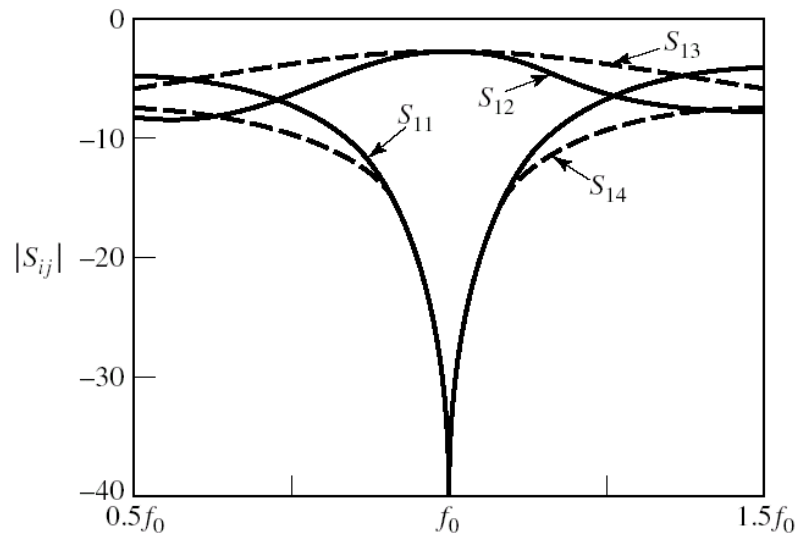



Figure 7.25 (p. 337) S parameter magnitudes versus frequency for the branch-line coupler of Example 7.5

A Quad-Mode Analysis of the Quadrature Hybrid

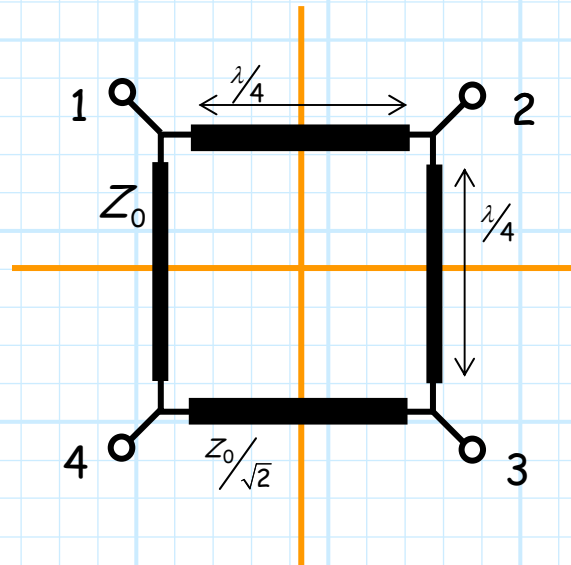
The quadrature hybrid is a matched, lossless, reciprocal four-port network that possesses two planes of **bilateral symmetry** (i.e. D_4 symmetry):



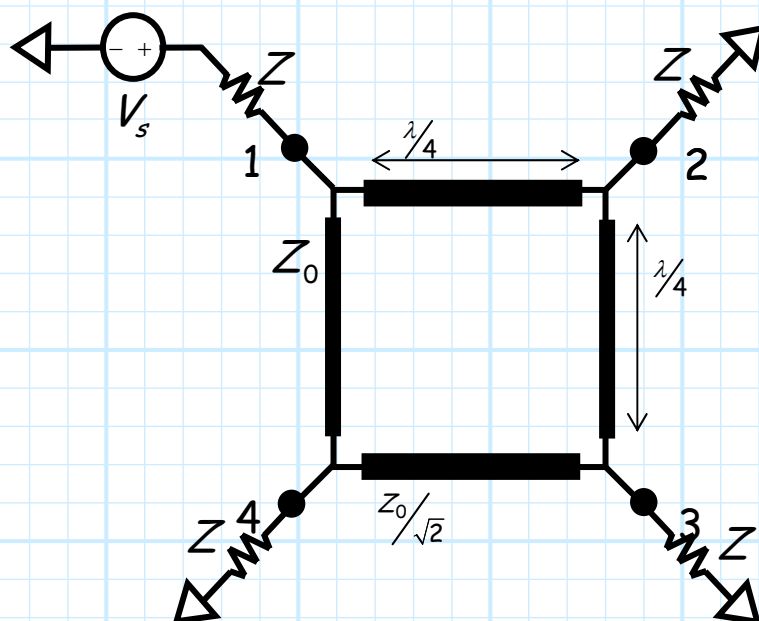To determine the scattering parameters $S_{11}, S_{21}, S_{31}, S_{41}$, of this network, a matched source is placed on port 1, while matched loads terminate the other 3 ports.



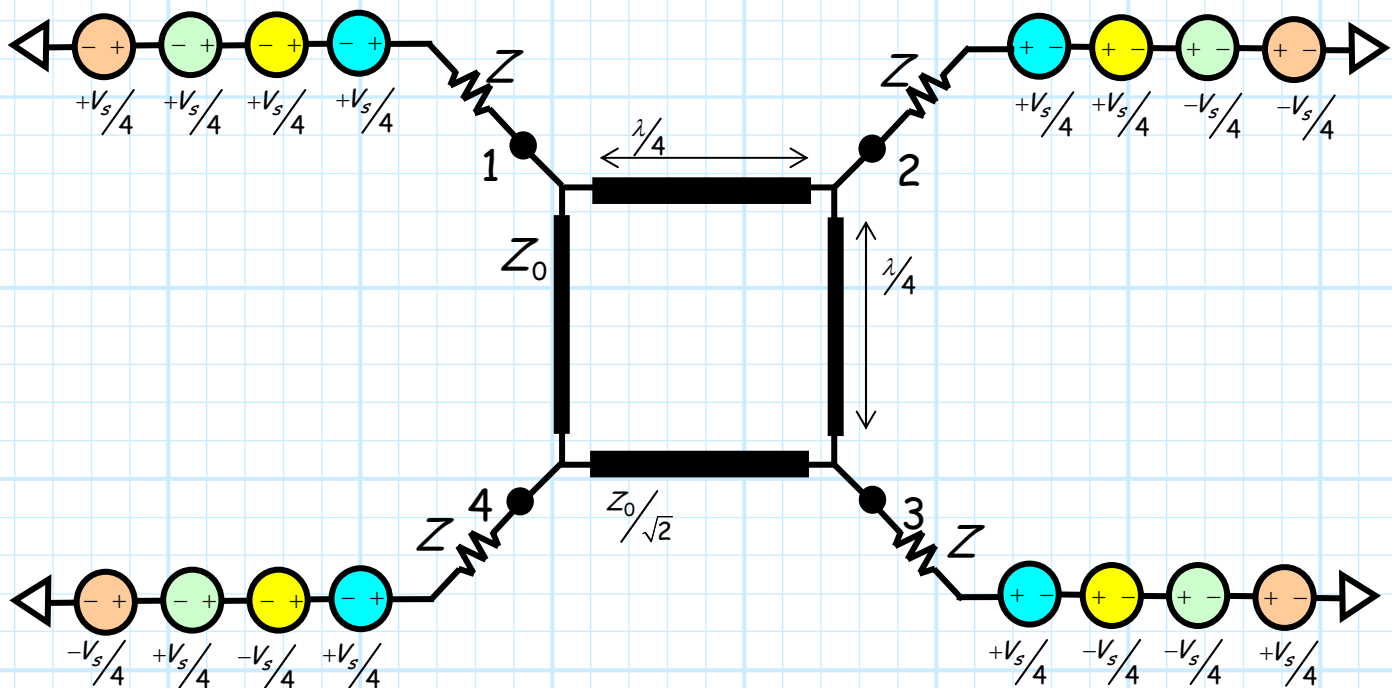This source destroys both planes of bilateral symmetry in the circuit. We can however recast the circuit above with a precisely equivalent circuit:




Note that the four series voltage sources on port 1 add to the original value of V_s , while the series source at the other four ports add to a value of **zero**—thus providing short circuit from the passive load Z_0 to ground.

To analyze this circuit, we can apply **superposition**.

Sequentially turning off all but one source at each of the 4 ports provides us with **four "modes"**. Each of these four modes can be analyzed, and the resulting circuit response is simply a coherent summation of the results of each of the four modes!

The benefit of this procedure is that each of the four modes preserve circuit symmetry. As a result, the planes of bilateral symmetry become virtual shorts and/or virtual opens.


Mode A

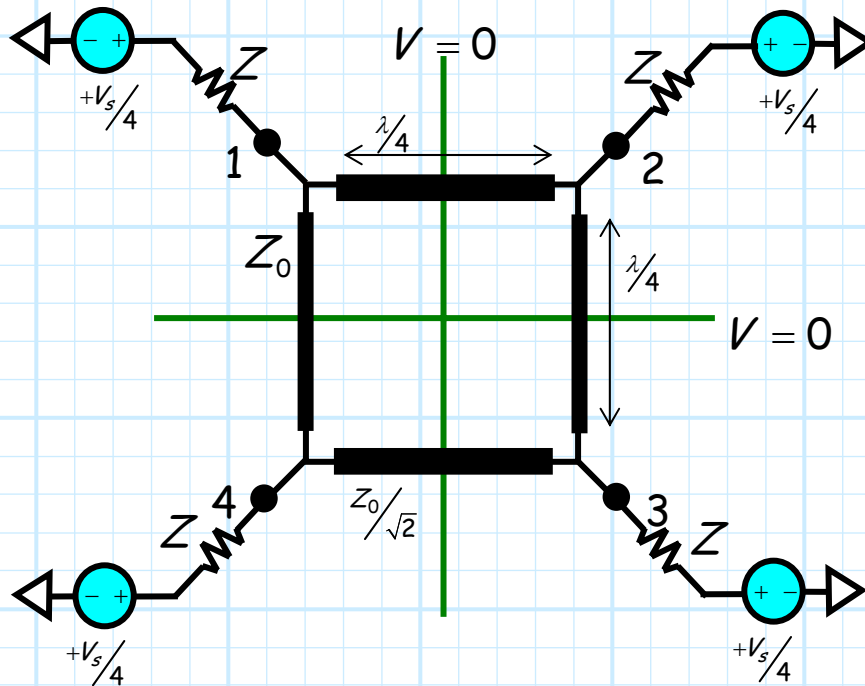

The even symmetry of this circuit is now restored, and so the voltages at each port are identical:

$$V_{1a}^+ = V_{2a}^+ = V_{3a}^+ = V_{4a}^+ = \frac{V_s}{8} \quad \text{and} \quad V_{1a}^- = V_{2a}^- = V_{3a}^- = V_{4a}^-$$

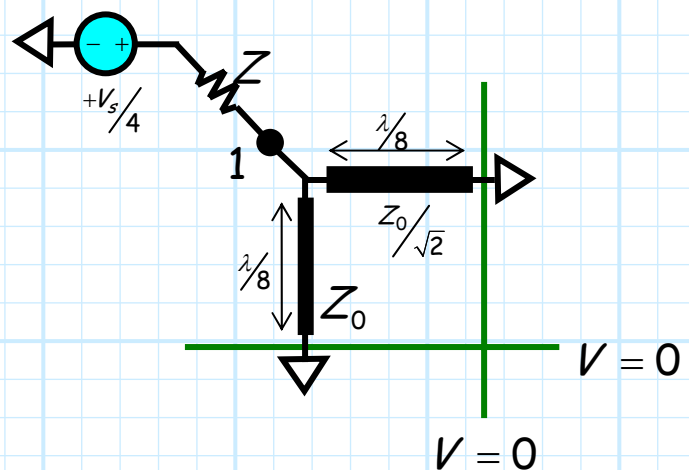The two virtual shorts segment this circuit into 4 identical sections. To determine the amplitude V_{1a}^- , we need only analyze one of these sections:



The circuit has simplified to a 1-port device consisting of the parallel combination of two $\lambda/8$ short-circuited stubs. The admittance of a $\lambda/8$ short-circuit stub is:

$$\begin{aligned} Y_{stub}^{sc} &= -jY_0 \tan \beta \ell \\ &= -jY_0 \tan \lambda/8 \\ &= -jY_0 \end{aligned}$$

As a result, the input admittance is:

$$\begin{aligned} Y_{in}^a &= -j\sqrt{2} Y_0 - j Y_0 \\ &= -jY_0(\sqrt{2} + 1) \end{aligned}$$

The corresponding reflection coefficient is:

$$\begin{aligned} \Gamma_a &= \frac{Y_0 - Y_{in}^a}{Y_0 + Y_{in}^a} \\ &= \frac{Y_0 + jY_0(\sqrt{2} + 1)}{Y_0 - jY_0(\sqrt{2} + 1)} \\ &= \frac{1 + j(\sqrt{2} + 1)}{1 - j(\sqrt{2} + 1)} \end{aligned}$$

Since the input admittance is purely reactive, the magnitude of this reflection coefficient is $|\Gamma_a| = 1.0$. The phase of this complex value can be determined from its real and imaginary part:

$$\begin{aligned}
 \Gamma_a &= \frac{1 + j(\sqrt{2} + 1)}{1 - j(\sqrt{2} + 1)} \left(\frac{1 + j(\sqrt{2} + 1)}{1 + j(\sqrt{2} + 1)} \right) \\
 &= \frac{1 + j2(\sqrt{2} + 1) - (\sqrt{2} + 1)^2}{1 + (\sqrt{2} + 1)^2} \\
 &= \frac{-2(\sqrt{2} + 1) + j2(\sqrt{2} + 1)}{4 + 2\sqrt{2}} \\
 &= \frac{-(\sqrt{2} + 1) + j(\sqrt{2} + 1)}{\sqrt{2}(\sqrt{2} + 1)} \\
 &= \frac{-1 + j}{\sqrt{2}}
 \end{aligned}$$

So that:

$$\operatorname{Re}\{\Gamma_a\} = \frac{-1}{\sqrt{2}} \quad \text{and} \quad \operatorname{Im}\{\Gamma_a\} = \frac{1}{\sqrt{2}}$$

Thus the reflection coefficient for mode A is:

$$\Gamma_a = -\frac{1}{\sqrt{2}} + j\frac{1}{\sqrt{2}} = e^{j3\pi/4}$$


And thus the amplitude of the reflected wave at port 1 is:

$$V_{1a}^- = \Gamma_a V_{1a}^+ = V_s \frac{e^{j3\pi/4}}{8}$$

And so from the even symmetry of mode A we conclude:

$$V_{1a}^- = V_{2a}^- = V_{3a}^- = V_{4a}^- = V_s \frac{e^{j3\pi/4}}{8}$$


Mode B

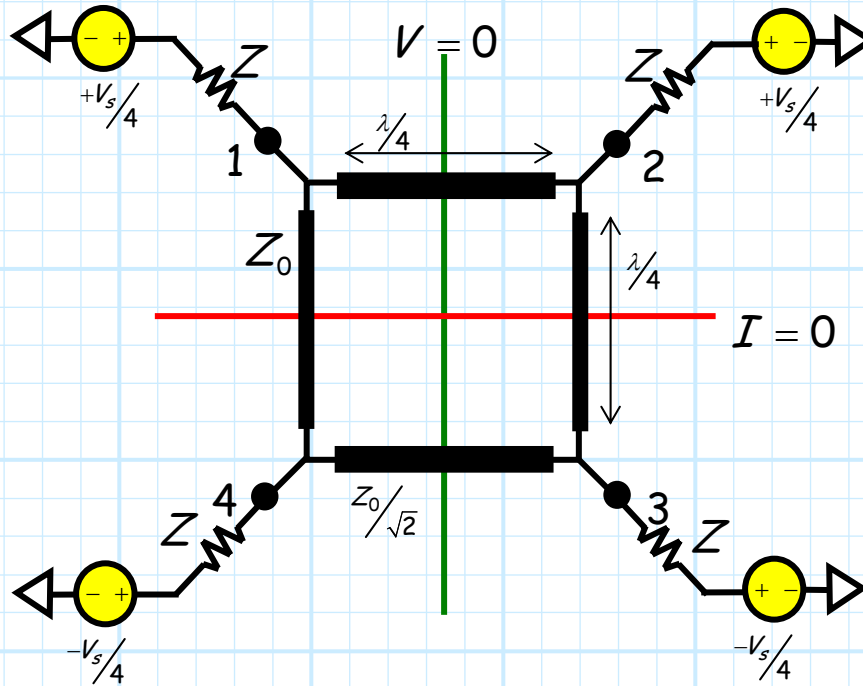

For mode B, the even symmetry exists about the vertical circuit plane, while odd symmetry occurs across the horizontal plane.

$$V_{1b}^+ = V_{2b}^+ = -V_{3b}^+ = -V_{4b}^+ = \frac{V_s}{8} \quad \text{and} \quad V_{1b}^- = V_{2b}^- = -V_{3b}^- = -V_{4b}^-$$

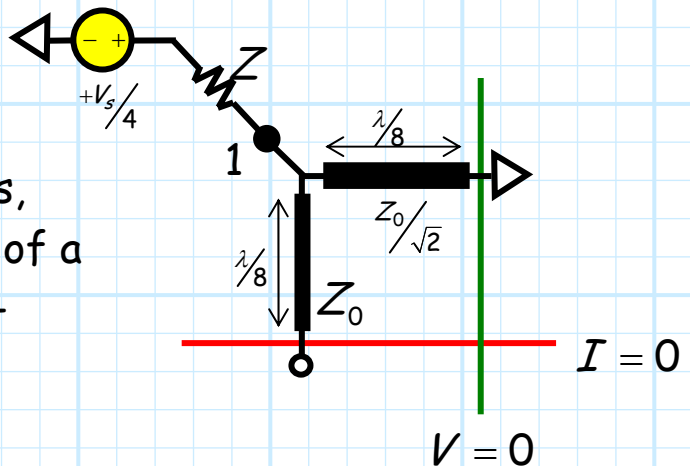The circuit can again be segmented into four sections, with each section consisting of a shorted $\lambda/8$ stub and an open-circuited $\lambda/8$ stub in parallel.



The admittance of a $\lambda/8$ open-circuit stub is:

$$\begin{aligned} Y_{stub}^{oc} &= jY_0 \cot \beta l \\ &= jY_0 \cot \lambda/8 \\ &= jY_0 \end{aligned}$$

As a result, the input admittance is:

$$\begin{aligned} Y_{in}^b &= -j\sqrt{2} Y_0 + j Y_0 \\ &= -jY_0(\sqrt{2} - 1) \end{aligned}$$

The corresponding reflection coefficient is:

$$\begin{aligned} \Gamma_b &= \frac{1 + j(\sqrt{2} - 1)}{1 - j(\sqrt{2} - 1)} \\ &= \frac{1 + j2(\sqrt{2} - 1) - (\sqrt{2} - 1)^2}{1 + (\sqrt{2} - 1)^2} \\ &= \frac{2(\sqrt{2} - 1) + j2(\sqrt{2} - 1)}{2\sqrt{2}(\sqrt{2} - 1)} \\ &= \frac{1}{\sqrt{2}} + j \frac{1}{\sqrt{2}} \\ &= e^{j\pi/4} \end{aligned}$$


And thus the amplitude of the reflected wave at port 1 is:

$$V_{1b}^- = \Gamma_b V_{1b}^+ = V_s \frac{e^{j\pi/4}}{8}$$

And so from the symmetry of mode B we conclude:

$$V_{1b}^- = V_{2b}^- = -V_{3b}^- = -V_{4b}^- = V_s \frac{e^{j\pi/4}}{8}$$


Mode C

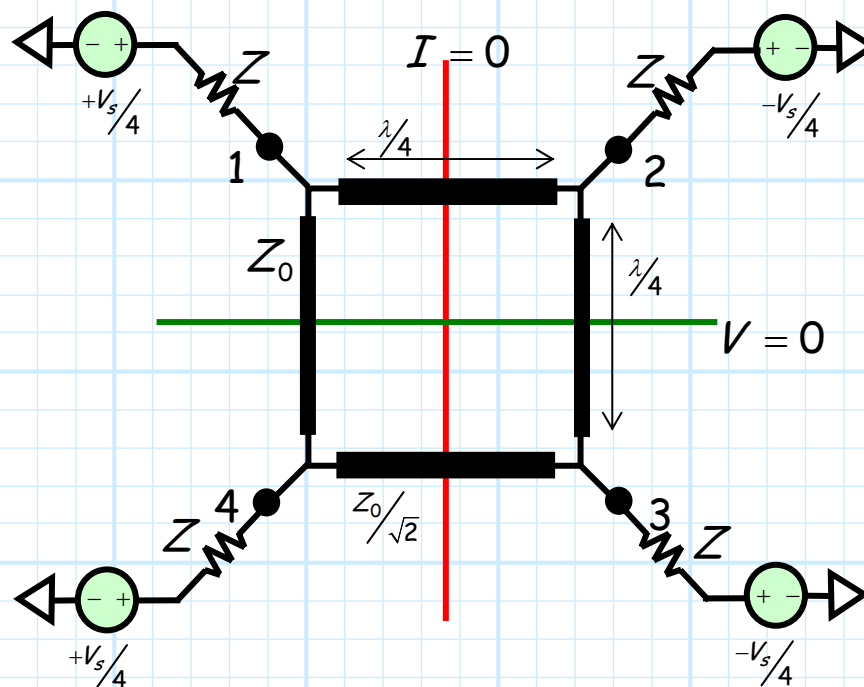

For mode C, odd symmetry exists about the vertical circuit plane, while even symmetry occurs across the horizontal plane.

$$V_{1c}^+ = -V_{2c}^+ = -V_{3c}^+ = V_{4c}^+ = \frac{V_s}{8} \quad \text{and} \quad V_{1c}^- = -V_{2c}^- = -V_{3c}^- = V_{4c}^-$$

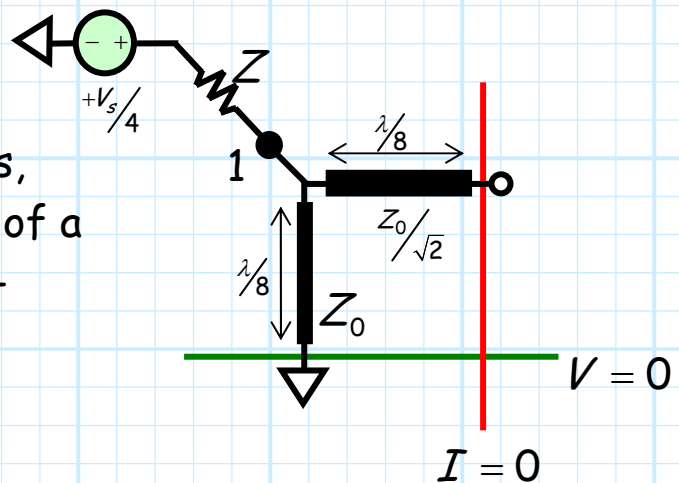The circuit can again be segmented into four sections, with each section consisting of a shorted $\lambda/8$ stub and an open-circuited $\lambda/8$ stub in parallel.



As a result, the input admittance is:

$$\begin{aligned} Y_{in}^c &= j\sqrt{2} Y_0 + j Y_0 \\ &= j Y_0 (\sqrt{2} - 1) \end{aligned}$$

Note that this result is simply the complex conjugate of Y_{in}^b , and so we can immediately conclude:


$$\Gamma_c = \Gamma_b^* = e^{-j\pi/4}$$

And thus the amplitude of the reflected wave at port 1 is:

$$V_{1c}^- = \Gamma_c V_{1c}^+ = V_s \frac{e^{-j\pi/4}}{8}$$

And so from the symmetry of mode C we conclude:


$$V_{1c}^- = -V_{2c}^- = -V_{3c}^- = V_{4c}^- = V_s \frac{e^{-j\pi/4}}{8}$$

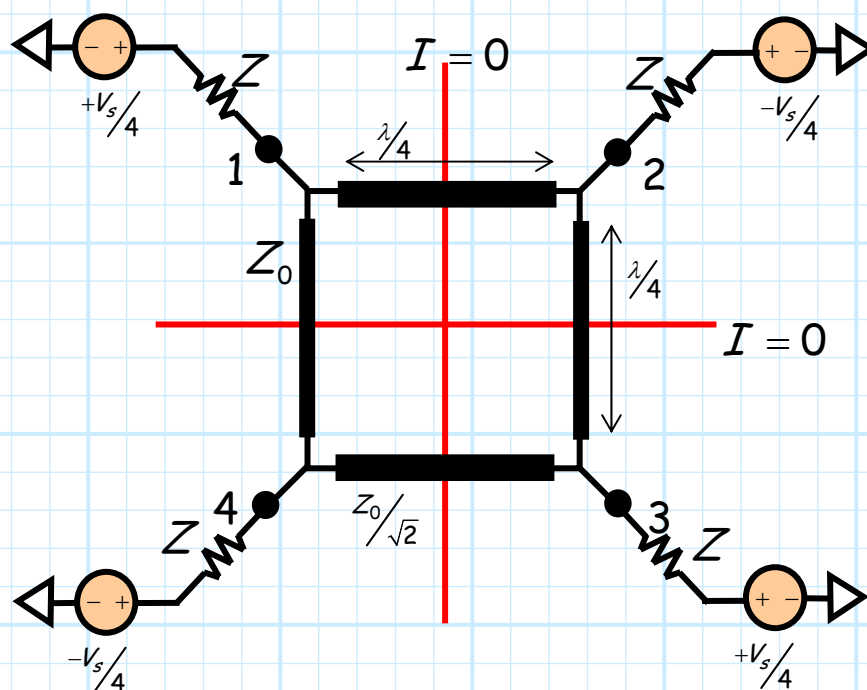Mode D

For mode D, odd symmetry exists about both planes of circuit symmetry.

$$+V_{1c}^+ = -V_{2c}^+ = +V_{3c}^+ = -V_{4c}^+ = \frac{V_s}{8} \quad \text{and} \quad +V_{1c}^- = -V_{2c}^- = +V_{3c}^- = -V_{4c}^-$$

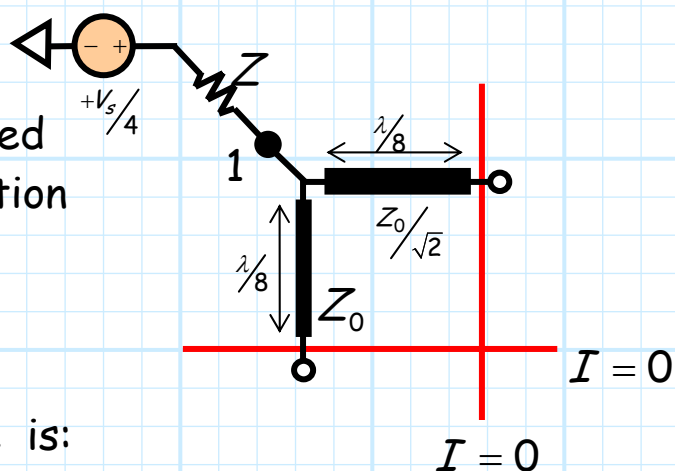The circuit can again be segmented into four sections, with each section consisting two open-circuited $\lambda/8$ stubs in parallel.



As a result, the input admittance is:

$$y_{in}^d = j\sqrt{2} Y_0 + j Y_0 = jY_0(\sqrt{2} + 1)$$

Note that this result is simply the complex conjugate of Γ_{in}^a , and so we can immediately conclude:

$$\Gamma_d = \Gamma_a^* = e^{-j3\pi/4}$$


And thus the amplitude of the reflected wave at port 1 is:

$$V_{1d}^- = \Gamma_d V_{1d}^+ = V_s \frac{e^{-j3\pi/4}}{8}$$


And so from the symmetry of mode D we find:

$$+V_{1c}^- = -V_{2c}^- = +V_{3c}^- = -V_{4c}^- = V_s \frac{e^{-j3\pi/4}}{8}$$

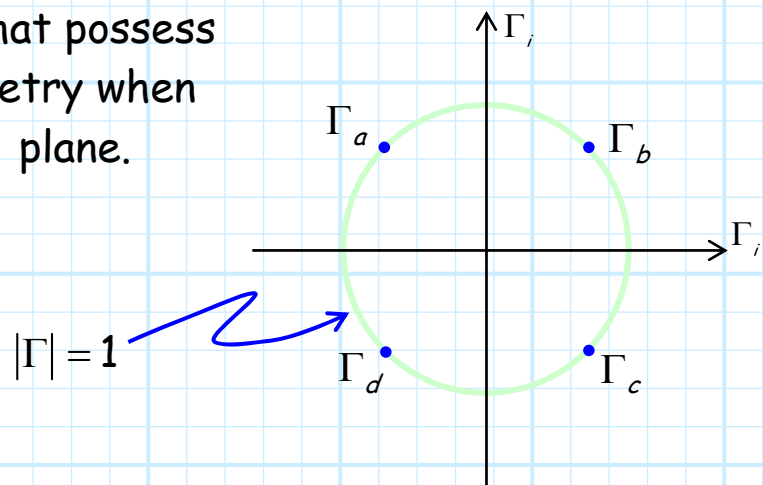Not surprisingly, the symmetry of the quadrature hybrid has resulted in four modal solutions that possess precisely the same symmetry when plotted on the complex Γ plane.



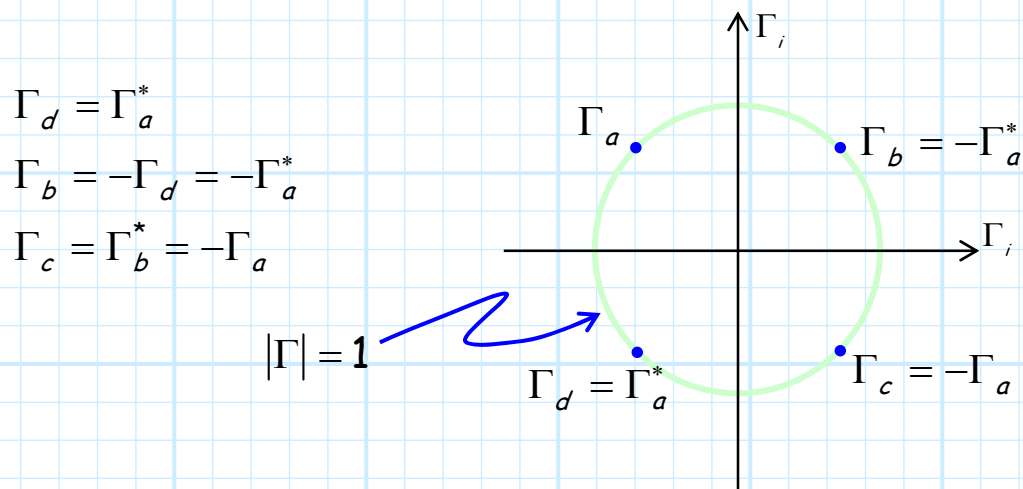The modal solutions associated with the other three ports are simply symmetric permutations of the port 1 solutions:



Since our circuit is linear, we can determine the solution to our original circuit as a superposition of our four modal solutions:

$$\begin{aligned}V_{01}^- &= V_{1a}^- + V_{1b}^- + V_{1c}^- + V_{1d}^- \\ &= \frac{V_s}{8} e^{j3\pi/4} + \frac{V_s}{8} e^{j\pi/4} + \frac{V_s}{8} e^{-j\pi/4} + \frac{V_s}{8} e^{-j3\pi/4} \\ &= \left(e^{j3\pi/4} + e^{j\pi/4} + e^{-j\pi/4} + e^{-j3\pi/4} \right) \frac{V_s}{8} \\ &= (2 \cos 3\pi/4 + 2 \cos \pi/4) \frac{V_s}{8} \\ &= (-2 \cos \pi/4 + 2 \cos \pi/4) \frac{V_s}{8} \\ &= 0\end{aligned}$$

$$\begin{aligned}
 V_{02}^- &= V_{2a}^- + V_{2b}^- + V_{2c}^- + V_{2d}^- \\
 &= \frac{V_s}{8} e^{j3\pi/4} + \frac{V_s}{8} e^{j\pi/4} - \frac{V_s}{8} e^{-j\pi/4} - \frac{V_s}{8} e^{-j3\pi/4} \\
 &= \left(e^{j3\pi/4} + e^{j\pi/4} - e^{-j\pi/4} - e^{-j3\pi/4} \right) \frac{V_s}{8} \\
 &= \left(2 \sin 3\pi/4 + 2 \sin \pi/4 \right) \frac{V_s}{8} \\
 &= \left(2 \cos \pi/4 + 2 \cos \pi/4 \right) \frac{V_s}{8} \\
 &= V_s \frac{1}{2\sqrt{2}}
 \end{aligned}$$

$$\begin{aligned}
 V_{03}^- &= V_{3a}^- + V_{3b}^- + V_{3c}^- + V_{3d}^- \\
 &= \frac{V_s}{8} e^{j3\pi/4} - \frac{V_s}{8} e^{j\pi/4} - \frac{V_s}{8} e^{-j\pi/4} + \frac{V_s}{8} e^{-j3\pi/4} \\
 &= \left(e^{j3\pi/4} - e^{j\pi/4} - e^{-j\pi/4} + e^{-j3\pi/4} \right) \frac{V_s}{8} \\
 &= \left(2 \cos 3\pi/4 - 2 \cos \pi/4 \right) \frac{V_s}{8} \\
 &= \left(-2 \cos \pi/4 - 2 \cos \pi/4 \right) \frac{V_s}{8} \\
 &= V_s \frac{-1}{2\sqrt{2}}
 \end{aligned}$$

$$\begin{aligned}
 V_{04}^- &= V_{4a}^- + V_{4b}^- + V_{4c}^- + V_{4d}^- \\
 &= \frac{V_s}{8} e^{j3\pi/4} - \frac{V_s}{8} e^{j\pi/4} + \frac{V_s}{8} e^{-j\pi/4} - \frac{V_s}{8} e^{-j3\pi/4} \\
 &= \left(e^{j3\pi/4} - e^{j\pi/4} + e^{-j\pi/4} - e^{-j3\pi/4} \right) \frac{V_s}{8} \\
 &= \left(-2 \sin^{3\pi/4} - 2 \sin \pi/4 \right) \frac{V_s}{8} \\
 &= \left(-2 \sin \pi/4 - 2 \sin \pi/4 \right) \frac{V_s}{8} \\
 &= -\frac{V_s}{2\sqrt{2}}
 \end{aligned}$$

From these results we can determine the scattering parameters $S_{11}, S_{21}, S_{31}, S_{41}$:

$$S_{11} = \frac{V_{01}^-}{V_{01}^+} = \frac{2}{V_s} 0 = 0$$

$$S_{21} = \frac{V_{02}^-}{V_{01}^+} = \frac{2}{V_s} \frac{V_s}{2\sqrt{2}} = \frac{1}{\sqrt{2}}$$

$$S_{31} = \frac{V_{03}^-}{V_{01}^+} = \frac{2}{V_s} \frac{-V_s}{2\sqrt{2}} = \frac{-1}{\sqrt{2}}$$

$$S_{41} = \frac{V_{04}^-}{V_{01}^+} = \frac{2}{V_s} 0 = 0$$

Given the symmetry of the device, we can extend these four results to determine the entire scattering matrix:

$$\mathbf{S} = \begin{bmatrix} 0 & 1/\sqrt{2} & j/\sqrt{2} & 0 \\ 1/\sqrt{2} & 0 & 0 & j/\sqrt{2} \\ j/\sqrt{2} & 0 & 0 & 1/\sqrt{2} \\ 0 & j/\sqrt{2} & 1/\sqrt{2} & 0 \end{bmatrix}$$

Precisely the correct result!