

## 8.5 Filter Implementations

Reading Assignment: pp. 405-411

**Q:** *So, we now know how to make any and all filters with lumped elements—but this is a microwave engineering course!*

*You said that lumped elements were difficult to make and implement at microwave frequencies. You said that distributed elements were used to make microwave components. So how do we make a filter with **distributed elements**!?!*

**A:** There are **many, many** ways to make microwave filters with distributed elements. Perhaps the most straightforward is to “**realize**” each individual lumped element with transmission line sections, and then insert these **approximations** in our lumped element solutions.

The first of these realizations is:


### HO: RICHARD'S TRANSFORMATIONS

To easily **implement** Richard's Transforms in a microstrip or stripline circuit, we must apply one of **Kuroda's Identities**.

### HO: KURODA'S IDENTITIES

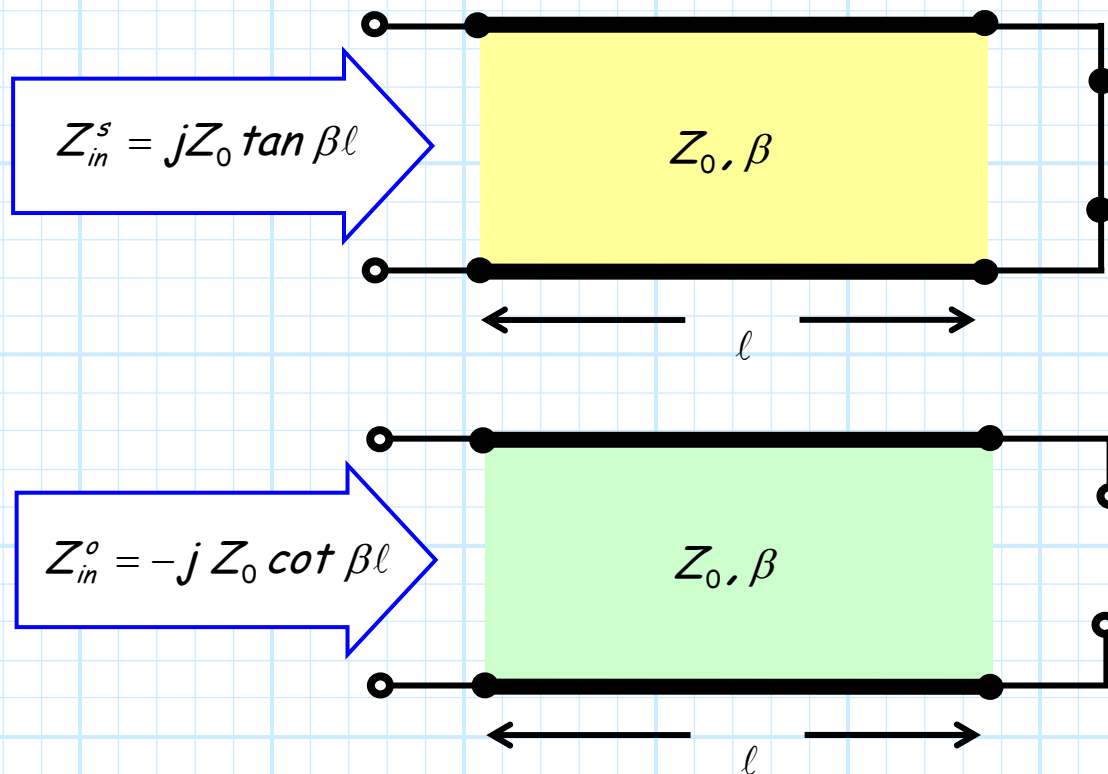
# Richard's Transformations

Recall the input impedances of short-circuited and open-circuited transmission line **stubs**.



Note that the input impedances are purely **reactive**—just like **lumped** elements!

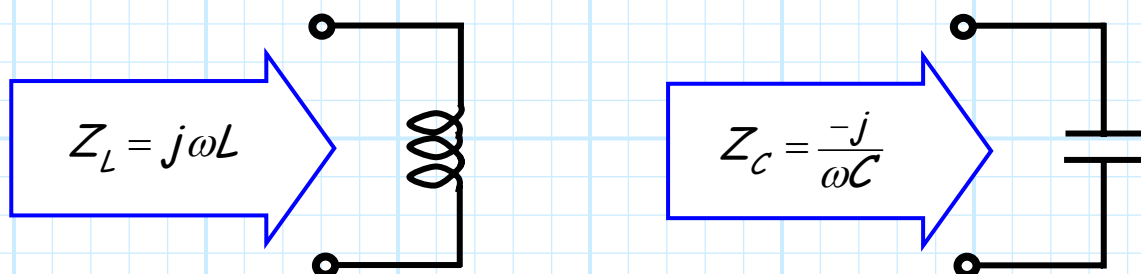However, the reactance of lumped inductors and capacitors have a **much** different mathematical form to that of transmission line stubs:



In other words, the impedance of transmission line stubs and lumped elements (capacitors and inductors) are different functions with respect to **frequency**. Therefore, we can say in general that, for example:

$$Z_{in}^s \neq Z_L \qquad Z_{in}^o \neq Z_C$$

However, for a given lumped element ( $L$  or  $C$ ) and a given stub (with a given  $Z_0$  and length  $\ell$ ) the functions **will** be equal at precisely **one frequency**!

For example, there is one frequency—let's call it  $\omega_c$ —that satisfies **this** equation for a given  $L, Z_0$ , and  $\ell$ :

$$\begin{aligned} j\omega_c L &= j Z_0 \tan \beta_c \ell \\ &= j Z_0 \tan \left[ \frac{\omega_c}{v_p} \ell \right] \end{aligned}$$

or similarly satisfies **this** equation:

$$\begin{aligned} \frac{-j}{\omega_c C} &= -j Z_0 \cot \beta_c \ell \\ &= -j Z_0 \cot \left[ \frac{\omega_c}{v_p} \ell \right] \end{aligned}$$

To make things easier, let's set the **length** of our transmission line stub to  $\lambda_c/8$ , where:

$$\lambda_c = \frac{v_p}{\omega_c} = \frac{2\pi}{\beta_c}$$

**Q:** Why  $l = \lambda_c/8$  ?


**A:** Well, for **one** reason,  $\beta_c l = \pi/4$  and therefore  $\tan(\pi/4) = 1.0!$

This of course greatly **simplifies** our earlier results:


$$j\omega_c L = j Z_0 \tan\left(\frac{\pi}{4}\right) = j Z_0$$

$$\frac{-j}{\omega_c C} = -j Z_0 \cot\left(\frac{\pi}{4}\right) = -j Z_0$$

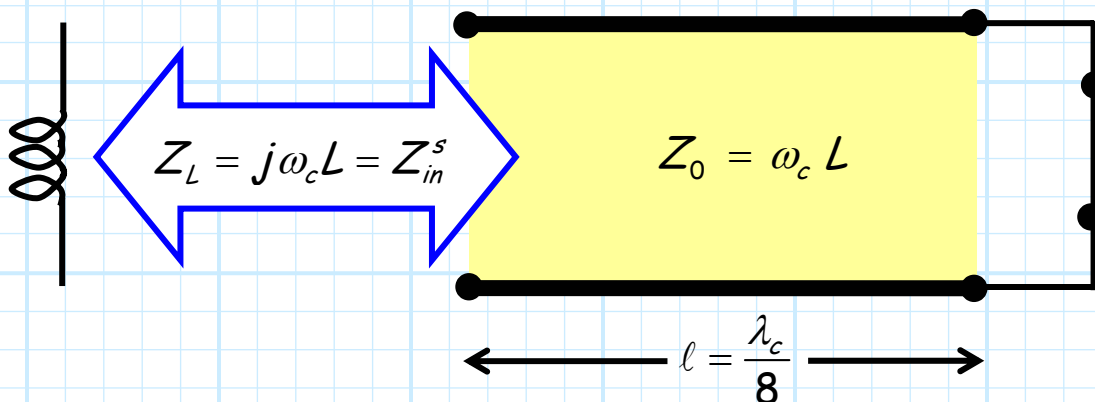Therefore, if we wish to build a **short-circuited** stub with the **same** impedance as an **inductor**  $L$  at frequency  $\omega_c$ , we set the **characteristic impedance** of the stub transmission line to be  $Z_0 = \omega_c L$ :



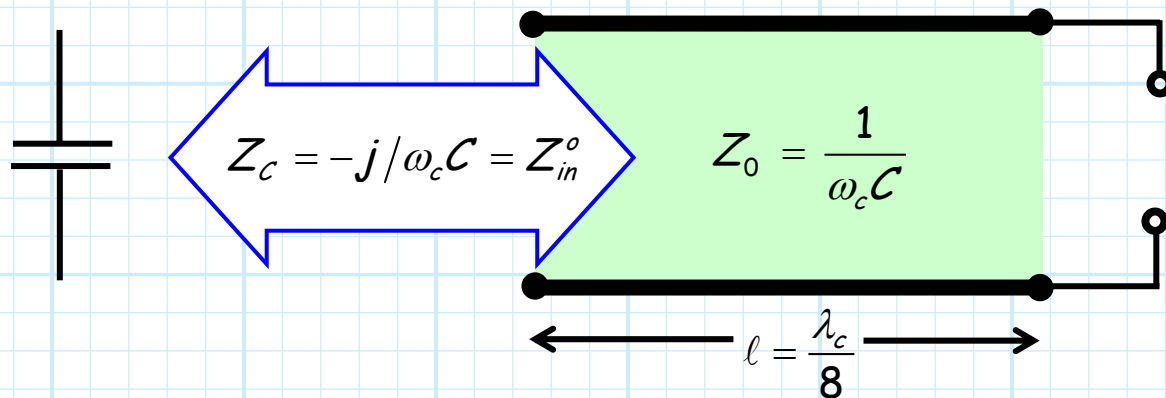Likewise, if we wish to build an **open-circuited** stub with the **same** impedance as an **capacitor**  $C$  at frequency  $\omega_c$ , we set the **characteristic impedance** of the stub transmission line to be  $Z_0 = 1/\omega_c C$ :



We call these two results **Richard's Transformations**.


However, it is important to remember that Richard's Transformations do **not** result in **perfect** replacements for lumped elements—the stubs **do not** behave like capacitors and inductors!

Instead, the transformation is **perfect**—the impedances are **equal**—at **only one frequency** ( $\omega_c$ ).

We can use Richard's transformations to replace the inductors and capacitors of a lumped element filter design. In fact, for **lowpass filter design**, the frequency  $\omega_c$  is the filter's **cutoff frequency**.

Using these stubs to **replace** inductors and capacitors will result in a filter response **similar** to that of the lumped element design—a low pass filter with cutoff frequency  $\omega_c$ .

However, the behavior of the filter in the **stopband** will be **very** different from the lumped element design. For example, at the (high) frequencies where the stub length becomes a **multiple** of  $\lambda/2$ , the filter response will be that of  $\omega = 0$ —near perfect **transmission!**

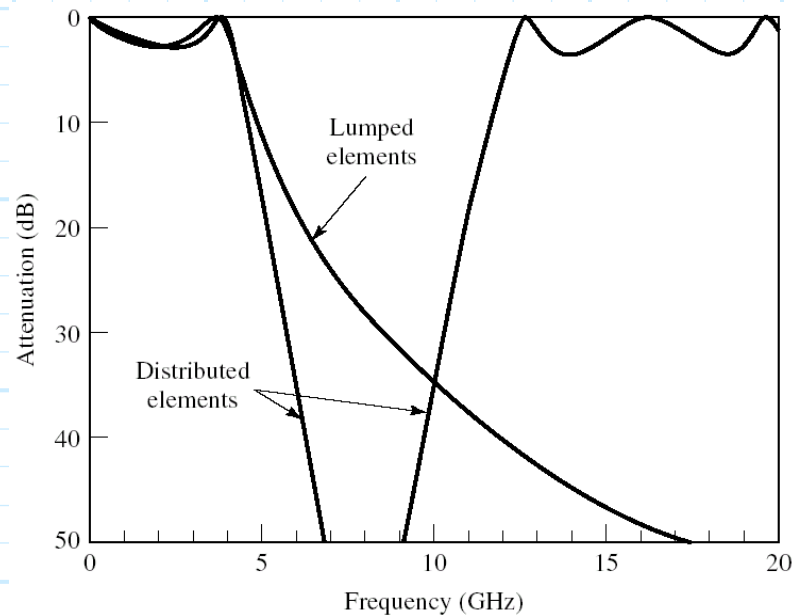

**Figure 8.37 (p. 411)** *Amplitude responses of lumped-element and distributed-element low-pass filter of Example 8.5.*

**Q:** *So why does the filter response match the lumped element response so well in the passband?*

**A:** To see why, we first note that the **Taylor Series approximation** for  $\tan \phi$  and  $\cot \phi$  when  $\phi$  is small (i.e.,  $\phi \ll 1$ ) is:

$$\tan \phi \approx \phi \quad \text{and} \quad \cot \phi \approx \frac{1}{\phi} \quad \text{for} \quad \phi \ll 1$$

and  $\phi$  is expressed in **radians**.

The **impedance** of our Richard's transformation shorted stub at some **arbitrary frequency**  $\omega$  is:

$$\begin{aligned} Z_{in}^s(\omega) &= j Z_0 \tan\left(\beta \frac{\lambda_c}{8}\right) \\ &= j(\omega_c L) \tan\left(\frac{\omega}{v_p} \frac{\lambda_c}{8}\right) \\ &= j(\omega_c L) \tan\left(\frac{\omega}{\omega_c} \frac{\pi}{4}\right) \end{aligned}$$

Therefore, when  $\omega \ll \omega_c$  (i.e., frequencies in the **passband** of a low-pass filter!), we can **approximate** this impedance as:

$$\begin{aligned} Z_{in}^s(\omega) &= j(\omega_c L) \tan\left(\frac{\omega}{\omega_c} \frac{\pi}{4}\right) \\ &\approx j \omega_c L \left(\frac{\omega}{\omega_c} \frac{\pi}{4}\right) \\ &= j \omega L \left(\frac{\pi}{4}\right) \quad \text{when } \omega \ll \omega_c \end{aligned}$$

Compare this to a **lumped inductor** impedance:

$$Z_L = j \omega L$$

Since the value  $\pi/4$  is **relatively** close to one, we find that the Richard's Transformation shorted stub has an input impedance **very** close to the lumped element inductor for **all** frequencies **less than**  $\omega_c$  (i.e., all frequencies of the low-pass filter pass-band)!

Similarly, we find that the Richard's transformation **open-circuit stub** has an input impedance of **approximately**:

$$\begin{aligned} Z_{in}^o(\omega) &= \frac{-j}{\omega_c \mathcal{C}} \cot\left(\frac{\omega}{\omega_c} \frac{\pi}{4}\right) \\ &\approx \frac{-j}{\omega_c \mathcal{C}} \left(\frac{\omega_c}{\omega} \frac{4}{\pi}\right) \\ &= \frac{1}{j\omega \mathcal{C}} \left(\frac{4}{\pi}\right) \quad \text{when } \omega \ll \omega_c \end{aligned}$$

Again, when compared to the **lumped element capacitor** impedance:

$$Z_c = \frac{1}{j\omega \mathcal{C}}$$

we find that results are approximately the **same** for all pass-band frequencies (i.e., when  $\omega \ll \omega_c$ ).



# Kuroda's Identities

We find that **Kuroda's Identities** can be very useful in making the implementation of Richard's transformations more **practicable**.

Kuroda's Identities essentially provide a list of **equivalent** two port networks. By equivalent, we mean that they have **precisely** the same scattering/impedance/admittance/transmission matrices.

In other words, we can **replace** one two-port network with its equivalent in a circuit, and the behavior and characteristics (e.g., its scattering matrix) of the circuit will **not** change!

**Q:** *Why would we want to do this?*


**A:** Because one of the equivalent may be more **practical** to implement!

For example, we can use Kuroda's Identities to:

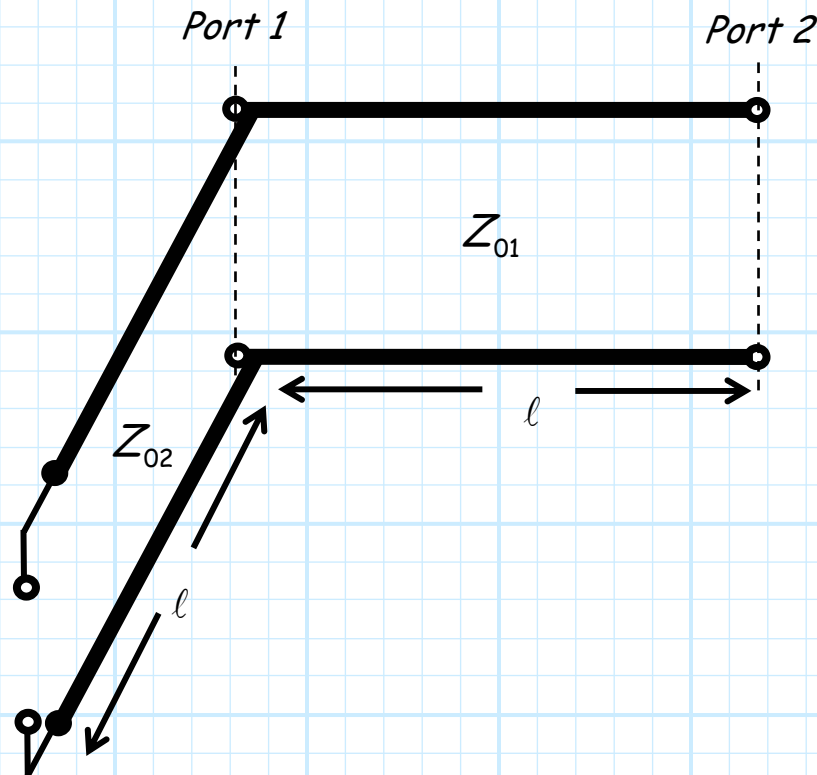- 1) Physically **separate** transmission line stubs.
- 2) Transform series stubs into **shunt** stubs.
- 3) Change impractical **characteristic impedances** into more realizable ones.


**Four** Kuroda's identities are provided in a very **ambiguous** and confusing table (Table 8.7) in your **book**. We will find the **first two** identities to be the most useful.

Consider the following two-port network, constructed with a length of transmission line, and an **open-circuit shunt stub**:



Note that the **length** of the stub and the transmission line are **identical**, but the characteristic **impedance** of each are **different**.

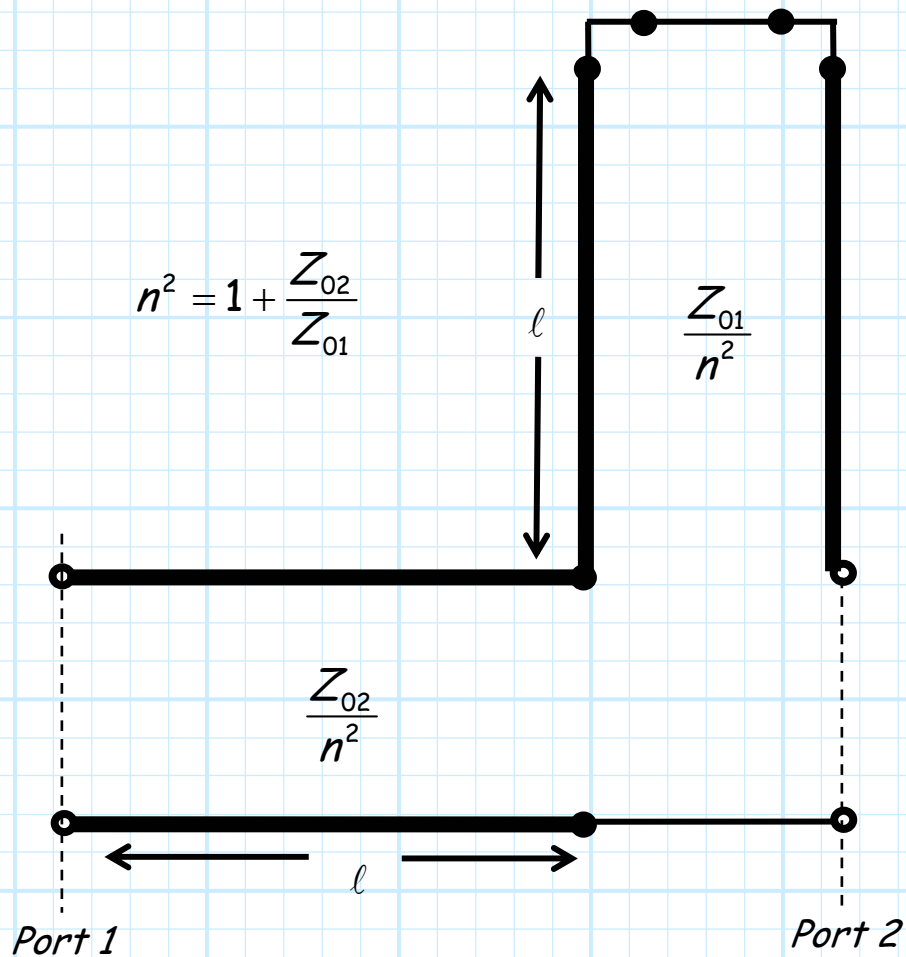
The **first Kuroda identity** states that the two-port network above is **precisely** the same two-port network as **this** one:




Thus, we can **replace** the first structure in some circuit with the one above, and the behavior that circuit will **not change** in the least!

Note this equivalent circuit uses a **short-circuited series stub**.

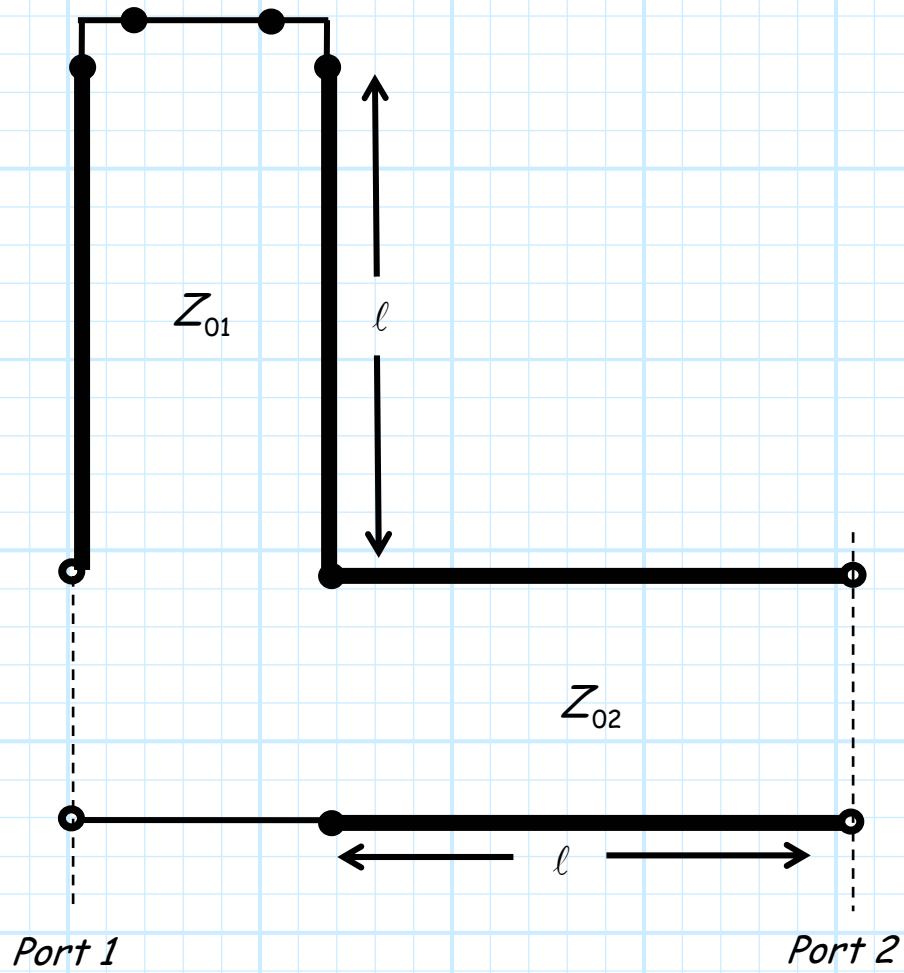The **second** of Kuroda's Identities states that this two port network:




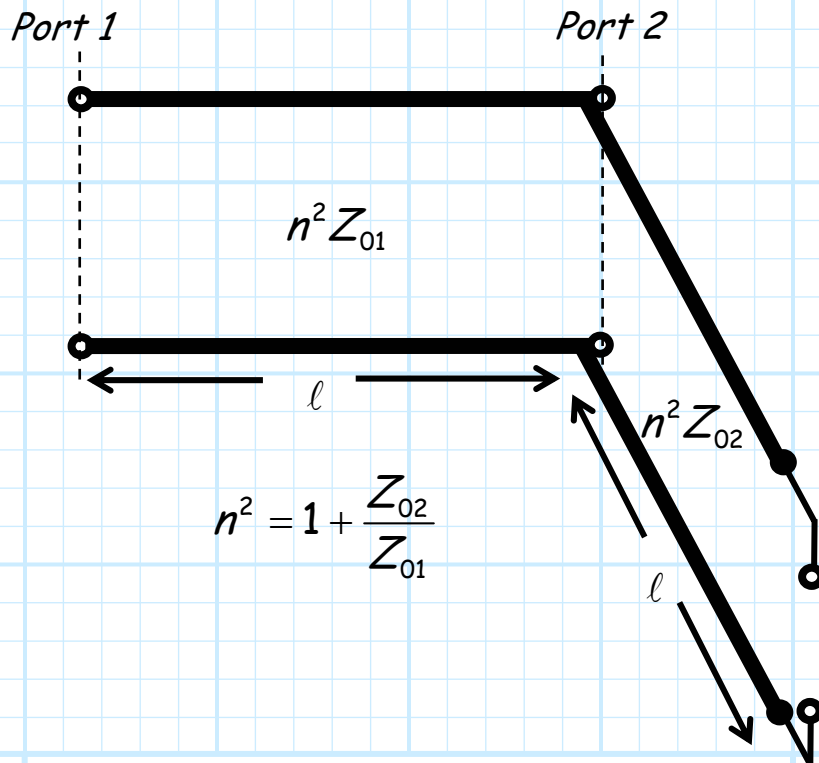Is precisely identical to this two-port network:



With regard to **Richard's Transformation**, these identities are useful when we replace the series inductors with **shorted stubs**.

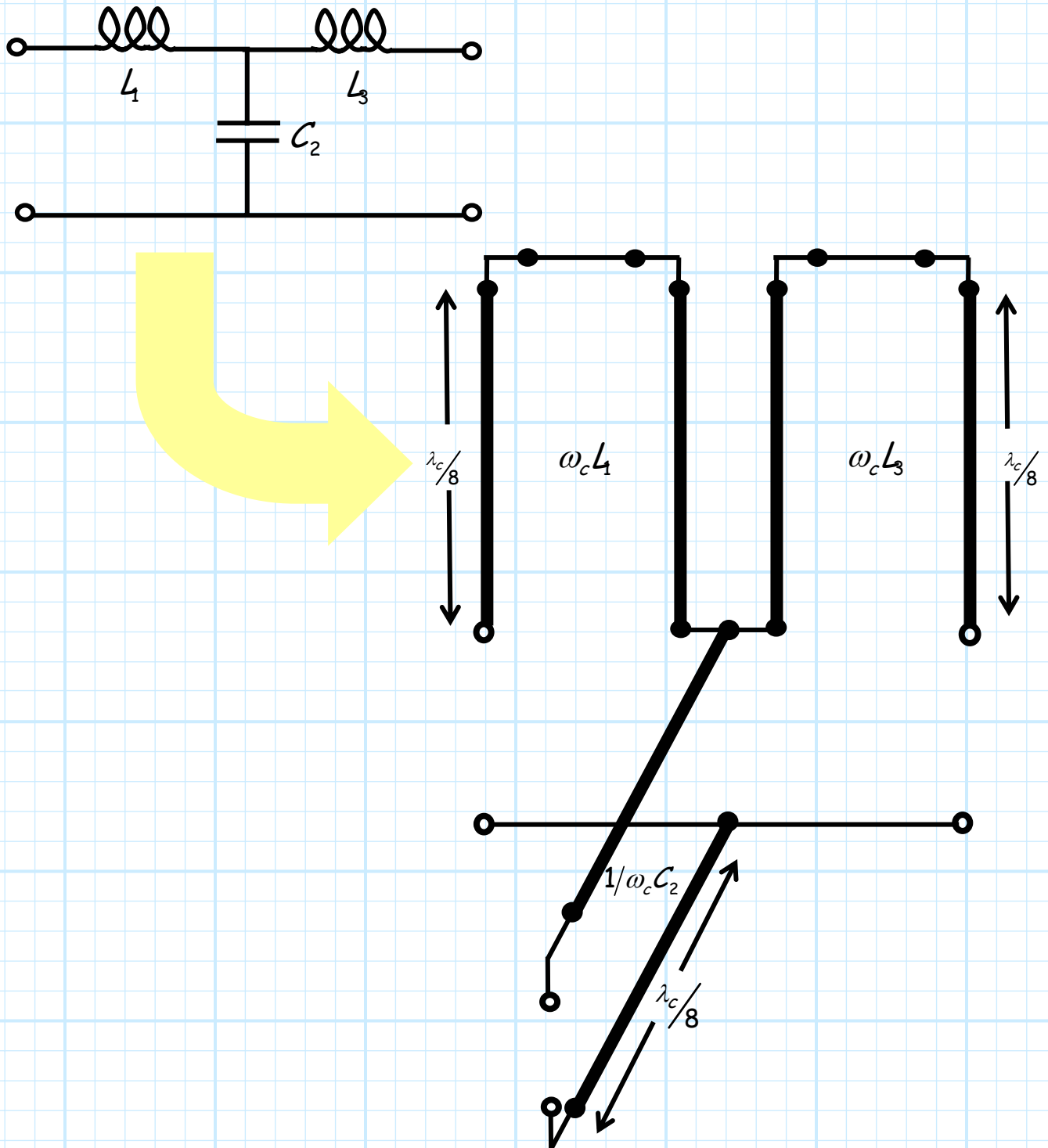To see **why** this is useful when implementing a **lowpass filter** with distributed elements, consider this third order filter example, realized using Richard's Transformations:




Note that we have a few **problems** in terms of implementing this design!

First of all the stubs are ideally **infinitely close** to each other—how do we build that? We could physically **separate** them, but this would introduce some **transmission line length** between them that would **mess up** our filter response!


Secondly, **series** stubs are difficult to construct in microstrip/stripline—we like **shunt** stubs **much better!**

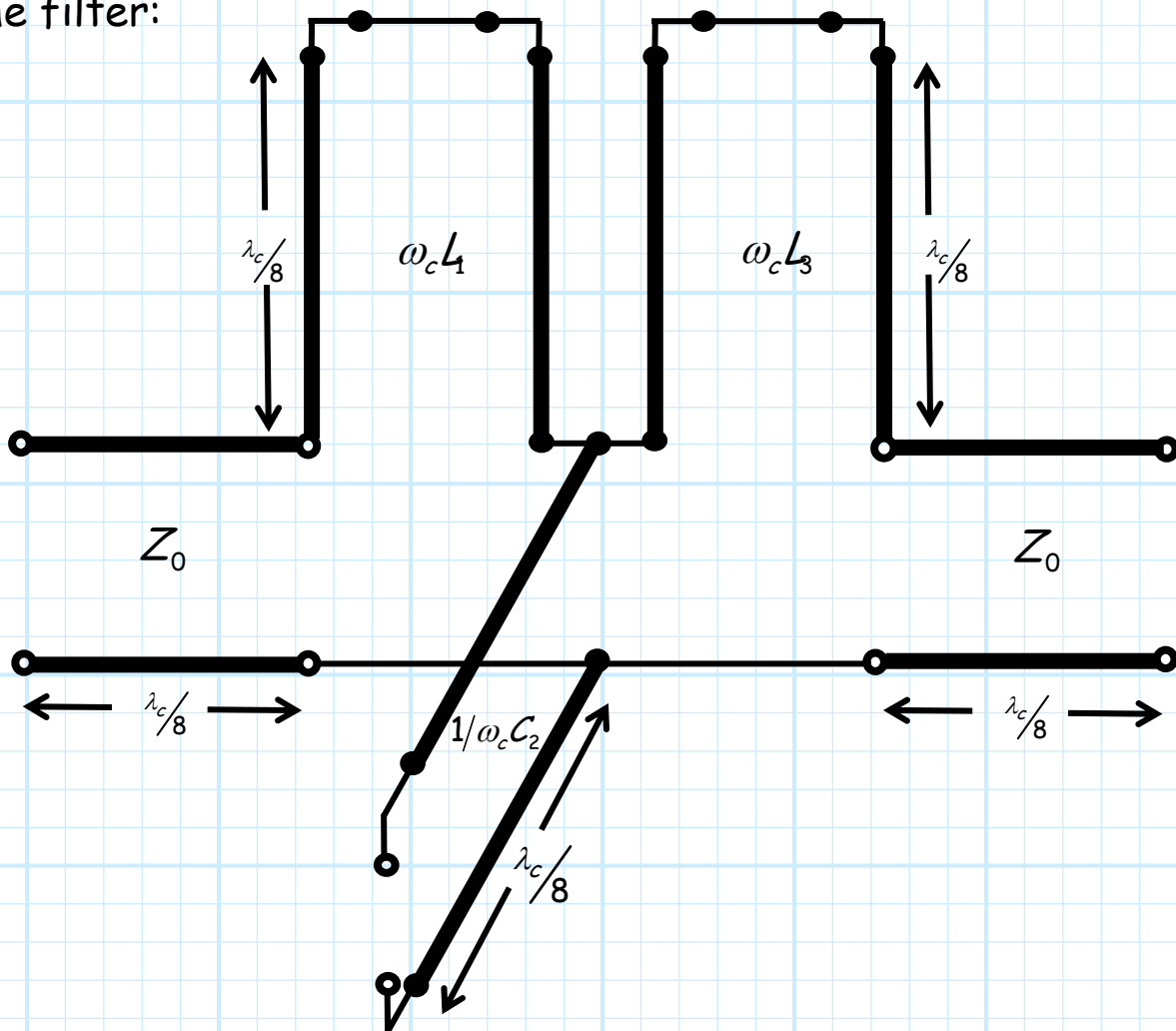To solve these problems, we first **add** a short length of transmission line ( $Z_0$  and  $\ell = \lambda_c/8$ ) to the **beginning** and **end** of the filter:



Note adding these lengths only results in a **phase shift** in the filter response—the transmission and reflection functions will remain **unchanged**.

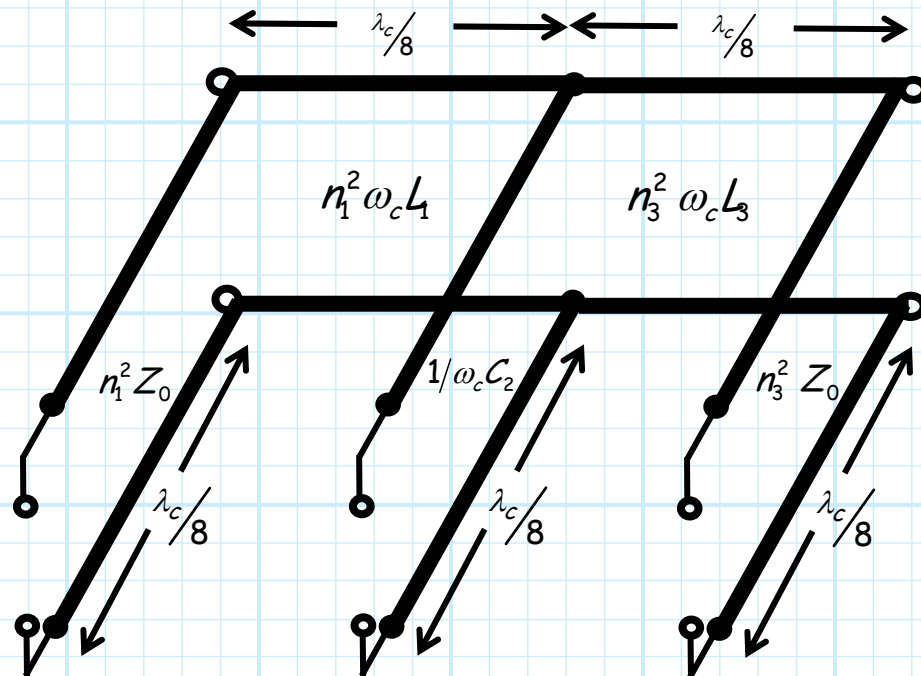Now we can use the second of **Kuroda's Identities** to replace the **series stubs** with **shunts**:



where:

$$n_1^2 = 1 + \frac{Z_0}{\omega_c L_1}$$

$$n_3^2 = 1 + \frac{Z_0}{\omega_c L_3}$$

Now **this** is a realizable filter! Note the **three stubs** are separated, and they are all **shunt stubs**.

Note that a specific **numerical** example (example 8.5) of this procedure is given on pp. 409-411 of **your book**.