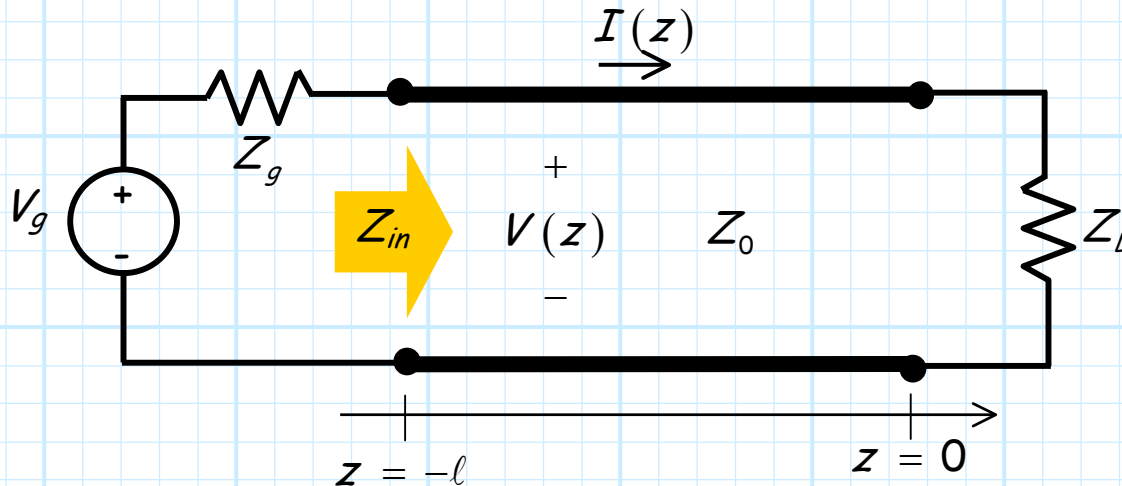


Delivered Power

Q: If the purpose of a transmission line is to transfer **power** from a source to a load, then exactly how much power is **delivered** to Z_L for the circuit shown below ??



A: We of course **could** determine V_0^+ and V_0^- , and then determine the power absorbed by the load (P_{abs}) as:


$$P_{abs} = \frac{1}{2} \operatorname{Re} \{ V(z=0) I^*(z=0) \}$$

However, if the transmission line is **lossless**, then we know that the power delivered to the load must be **equal** to the power "delivered" to the **input** (P_{in}) of the transmission line:

$$P_{abs} = P_{in} = \frac{1}{2} \operatorname{Re} \{ V(z=-l) I^*(z=-l) \}$$

However, we can determine this power **without** having to solve for V_0^+ and V_0^- (i.e., $V(z)$ and $I(z)$). We can simply use our knowledge of **circuit theory!**

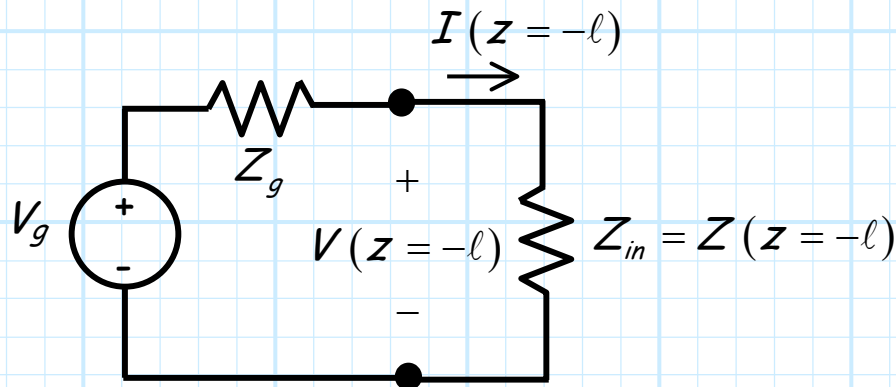We can **transform** load Z_L to the beginning of the transmission line (by direct calculation—or with a Smith Chart!), so that we can replace the transmission line with its **input impedance** Z_{in} :



Note by **voltage division** we can determine:

$$V(z = -l) = V_g \frac{Z_{in}}{Z_g + Z_{in}}$$

And from **Ohm's Law** we conclude:

$$I(z = -l) = \frac{V_g}{Z_g + Z_{in}}$$

And thus, the **power** P_{in} delivered to Z_{in} (and thus the **power** P_{abs} delivered to the load Z_L) is:

$$\begin{aligned}
 P_{abs} &= P_{in} = \frac{1}{2} \operatorname{Re} \{ V(z = -\ell) I^*(z = -\ell) \} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ V_g \frac{Z_{in}}{Z_g + Z_{in}} \frac{V_g^*}{(Z_g + Z_{in})^*} \right\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \operatorname{Re} \{ Z_{in} \} \\
 &= \frac{1}{2} |V_g|^2 \frac{|Z_{in}|^2}{|Z_g + Z_{in}|^2} \operatorname{Re} \{ y_{in} \}
 \end{aligned}$$

Note that we could **also** determine P_{abs} from our **earlier** expression:

$$P_{abs} = \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2)$$

But we would of course have to **first** determine V_0^+ (!):

$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 + \Gamma_{in})}$$