

Special Problem 5.2-1

A **matching network** has been constructed to match a **complex load** to a transmission line with characteristic impedance $Z_0 = 50 \Omega$.

Note that this matching network is **not** specifically one of the standard designs that we studied.

Determine the **complex admittance** Y_L of the load (you can alternatively express the load in terms of its impedance).

