

### Special Problem 2.3-14

Determine the input impedance  $Z_{in}$  of the network below.

Make sure you **explain** how you arrived at this result!

**Hint:** Don't make this hard!

