

Special Problem 2.3-4

Using the results of problem 2.24 in your book, determine the power associated with the waves defined by V^i , V^+ and V^- .

Determine also the power absorbed by resistor R_L .

Show that energy is conserved.