

Special Problem 2.3-5

Determine the **input impedance** of the network below.

Make sure you **explain** how you arrived at this result!

