

Special Problem 2.4-1

Use a Smith Chart to determine the input **admittance** of the following circuit:

