

Special Problem 2-6.1

In the circuit below, the load Z_L and line length ℓ are **unknown!**

However, we **do** know that the voltage on the transmission line has the form:

$$V(z) = Ae^{-j\beta z} - 0.5e^{j\beta z}$$

Apply a **boundary condition (!)** at point $z=0$ (look where this!) and find the value of constant A .

What is the **input impedance** (at $z=0$) of this transmission line?

