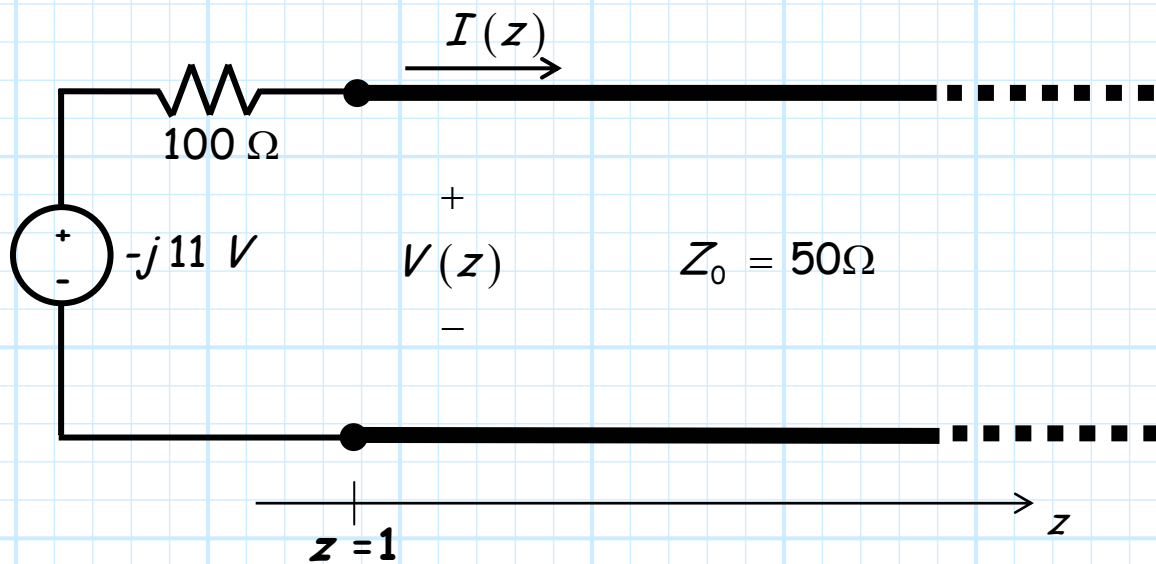


Special Problem 2.6-11

Consider the circuit below:



It is known that the **voltage** along the transmission line is:

$$V(z) = 3e^{-j\beta z} + B e^{+j\beta z} \text{ V}$$

where B is some unknown complex value, and $\beta = \pi/2$.

Determine the value of B .